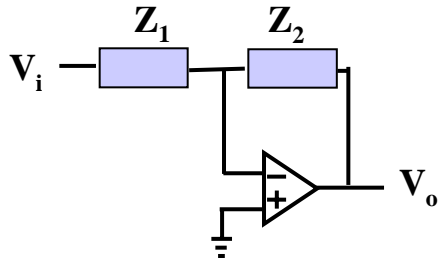


In the ideal op amp circuit below,


- (a) find the complex transfer function  $G = V_o/V_i$  in terms of  $Z_1$  and  $Z_2$ .  
 (b) If the circuit is a high pass filter, find  $Z_1$  and  $Z_2$  in terms of  $R_1$ ,  $R_2$  and  $C$  and sketch the circuit. (8)  
 (c) Find the complex transfer function  $G = V_o/V_i$  in terms of  $R_1$ ,  $R_2$ ,  $C$  and  $j\omega$ . (6)  
 (d) If for the high pass filter, cutoff frequency = 10kHz and  $|G| = 5$  at cutoff. Find  $R_1$  and  $C$ . Given  $R_2 = 1k\Omega$ . (14)  
 (e) Sketch  $|G|$  (in dB) ( $= 20\log |G|$ ) versus angular frequency  $\omega$ . Show clearly all intercepts in your sketch. (6)



(a) **Transfer function  $G$**   $\therefore G = \frac{V_o}{V_i} = -\frac{Z_2}{Z_1}$

**If circuit is a high pass filter**  $\therefore Z_1 = R_1 + \frac{1}{j\omega C}$

$\therefore Z_2 = R_2$

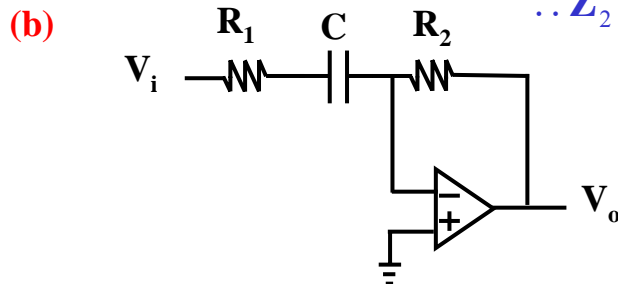

$$\therefore G = \frac{V_o}{V_i} = -\frac{Z_2}{Z_1} = -\frac{R_2}{R_1 + \frac{1}{j\omega C}} = -\frac{R_2}{R_1} \frac{1}{1 + j\frac{-1}{\omega CR_1}}$$

(c) **At cut-off**  $\therefore G = -\frac{R_2}{R_1} \frac{1}{1 - j}$


(d) **If at cut-off, frequency is 10kHz and  $|V_o/V_i| = 5$**

$$\therefore \omega_{\text{cutoff}} = 2\pi(10k) = \frac{1}{CR_1}$$

$$\therefore |G| = 5 = \frac{R_2}{R_1} \frac{1}{\sqrt{2}}$$

**Given  $R_2 = 1k$**   $\therefore R_1 = \frac{R_2}{|G|} \frac{1}{\sqrt{2}} = \frac{1k\Omega}{5} \frac{1}{\sqrt{2}} = 141\Omega$
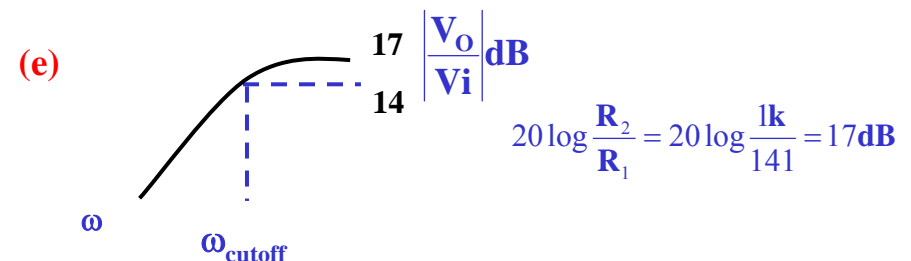
$$\therefore C = \frac{1}{\omega_{\text{cutoff}} R_1} = \frac{1}{2\pi(10k)141} \approx 1.13 \times 10^{-7} \text{ F} = 0.113 \mu\text{F}$$





In the ideal op amp circuit, the diode has the reverse characteristics as shown. The diode equation is  $I = I_0 \exp [(V/25\text{mV}) - 1]$ .

(a) Find the circuit model of the diode at breakdown.


(b) Find  $I_D$  if  $V_{in} = 1\text{V}$ .

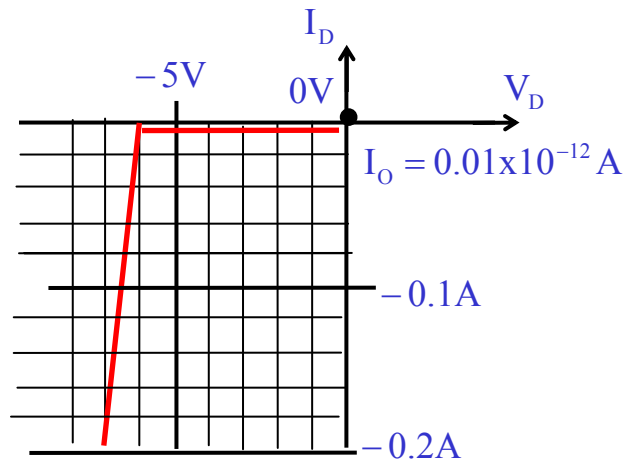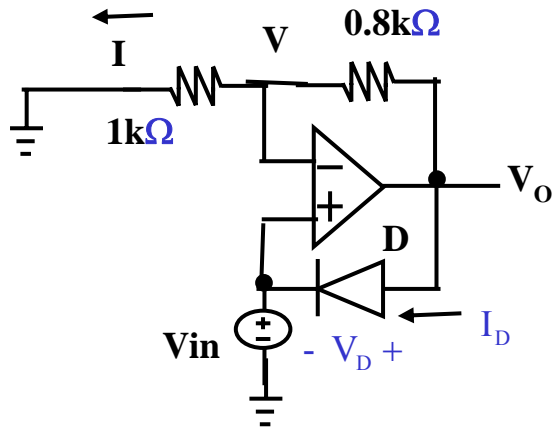(c) Find  $I_D$  if  $I = -10\text{mA}$ . (30)



(a)

**Model of diode at breakdown**

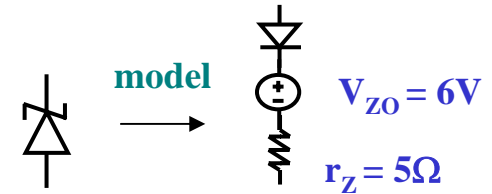

(b)

**When  $V_{in} = 1\text{V}$**

$$V_{in} = 1\text{V}, \therefore V = 1\text{V}$$

$$\therefore I = 1\text{mA}, \therefore V_O = 1.8\text{V}$$

$$\therefore I_D = I_0 (e^{\frac{V_D}{25\text{mV}}} - 1)$$

$$= 0.01 \times 10^{-12} \text{ A} (e^{\frac{1.8-1}{25\text{mV}}} - 1) = 0.79\text{A}$$

(c)

**When  $I = -10\text{mA}$**

$$V_O = -18\text{V}$$

$$V_{in} = -10\text{V}$$

D is breakdown

$$I_D = -\frac{-10 - (-18\text{V} - 6\text{V})}{5\Omega} = -0.4\text{A}$$

1. Given the ideal op amp filter circuit and  $V_s = V_m \cos \omega t$  V

(a) Find  $V_o / V$ .


(b) Show that the complex transfer function  $G (= V_o / V_s) =$ .

(c) Find the cut-off frequency  $\omega_o$  (in rad/s). Find also the DC voltage gain (value of  $G$  when  $V_s$  is a DC voltage).

(d) Find magnitude of  $G (= |G|)$  **in dB** when  $\omega = 0$  and when  $\omega = \omega_o$ . Given  $|G| \text{ in dB} = 20 \log_{10} |G|$ .

(e) Plot  $|G|$  versus  $\omega$ . Show clearly the value of  $|G|$  when  $\omega = 0$  and  $\omega = \omega_o$  in your plot. Is the op amp circuit a low pass filter?

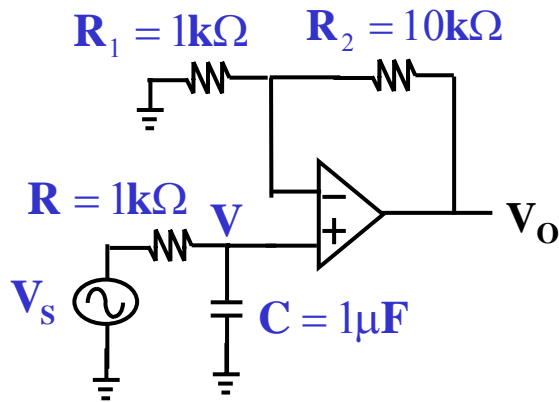(f) If  $V_s = 1 \cos 1kt$  V, find magnitude of  $V_o$  in  $V_{\text{rms}}$ .  
(55)



1

apply KCL

a

$$\Rightarrow \frac{0V - V_-}{R_1} \cong \frac{V_- - V_o}{R_2}$$

$$V_- \cong V_+ = V$$

$$\therefore \frac{V_o}{V} \cong 1 + \frac{R_2}{R_1} = 1 + \frac{10k\Omega}{1k\Omega} = 11$$

b

$$V = V_s * \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = V_s * \frac{1}{1 + j\omega CR}$$

$$V_o = 11V = 11 * V_s \frac{1}{1 + j\omega CR}$$

$$= \frac{11V_s}{1 + j\omega(1\mu F * 1k\Omega)}$$

$$G = \frac{V_o}{V_s} = \frac{11}{1 + j\omega * 1ms}$$

**c**  $\omega_0$  = **cut-off frequency**

$$\omega_0 = \frac{1}{1\text{ms}} = 1\text{krad/s}$$

when  $\omega = 0$


$$|G| = 11$$

**d**  $|G|$  in dB =  $20\log_{10} 11 \cong 20.8$  dB

At cut-off frequency,

$$|G| = \frac{11}{\sqrt{2}}$$
$$|G| \text{ in dB} = 20\log_{10} \frac{11}{\sqrt{2}} \cong 17.8 \text{ dB}$$

**e**

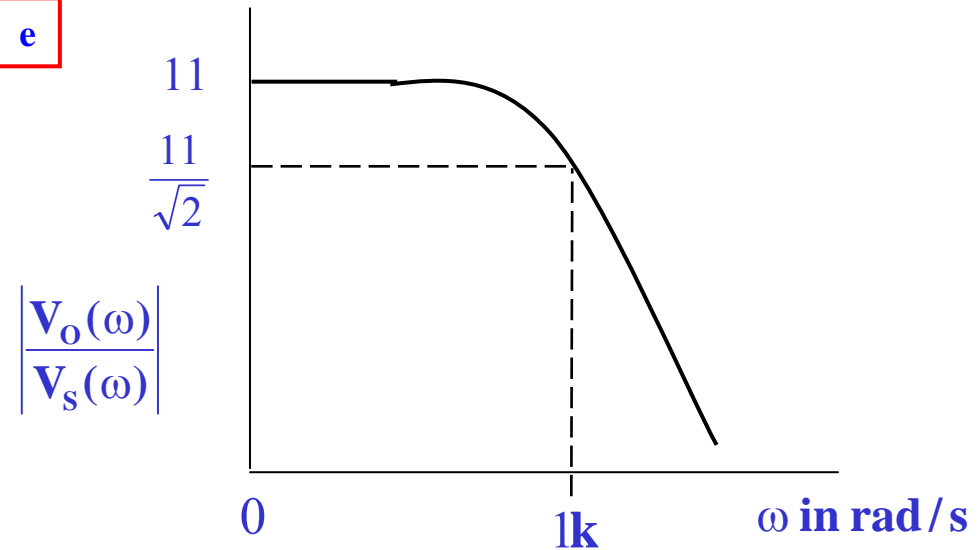

Circuit is a low pass filter



**f**

If  $V_i = 1 \cos(1kt)$  V




$$V_o = \frac{11}{\sqrt{2}} * \frac{1}{\sqrt{2}} V_{\text{rms}} = 5.5 V_{\text{rms}}$$

**7****(30)**

7. (a) In the ideal diode circuit, sketch  $V_o(t)$ . Label clearly the voltages in your sketch. (12)
- (b) In the ideal diode circuit, plot  $V_o$  versus  $V_i$  for  $0V \leq V_i \leq 35V$ . Label clearly all voltages in your sketch. (18)

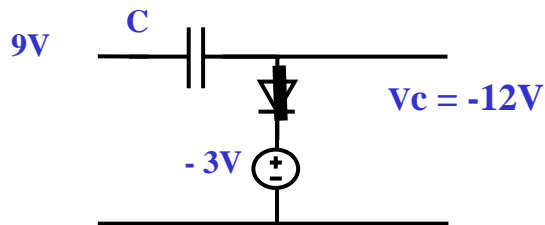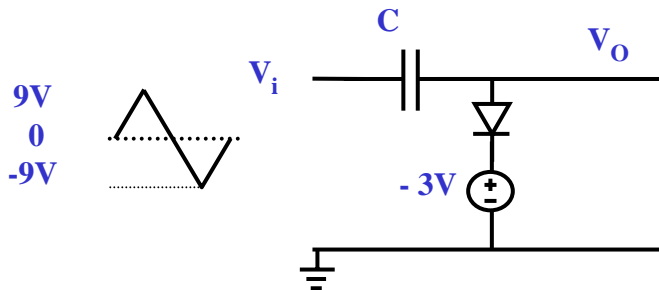**a**

$$V_o = V_i + V_c = V_i - 12$$

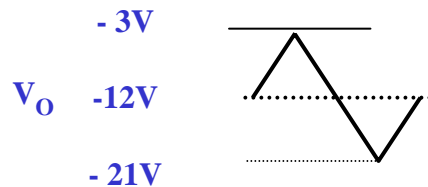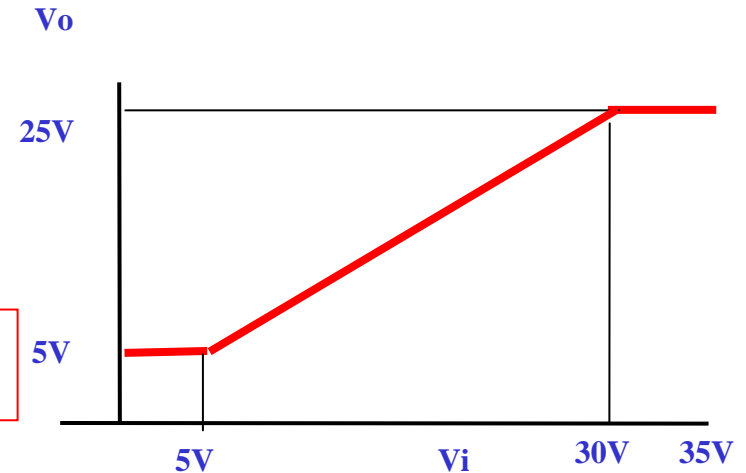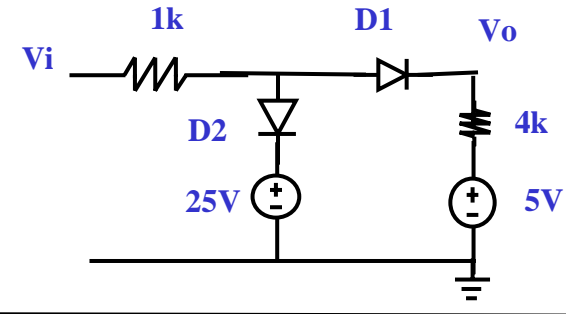**b**




$V_i < 5V$ , D1 and D2 OFF,  $V_o = 5V$

$V_i > 5V$ , D1 ON,  
 $V_o = 5 + I(4k)$   
 $= 5 + (V_i - 5)4k/(4k + 1k)$   
 $= 5 + (V_i - 5)4/5$   
 $V_i = 30, V_o = 5 + 25*4/5 = 25$


$V_i = 30V, V_o = 25$ , D2 ON,  $V_o$  is fixed at 25V

2

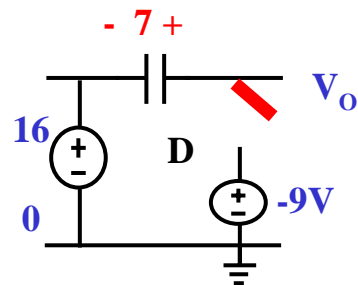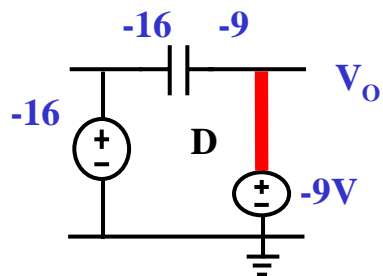
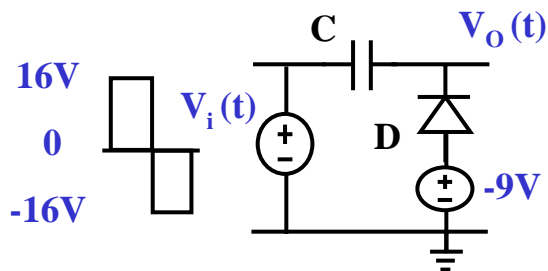
(a) In the ideal diode circuit, sketch  $V_o(t)$ . Explain briefly the reasons for your answers. (12)



$$V_o = V_i + V_c = V_i + 7V$$

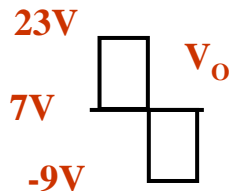

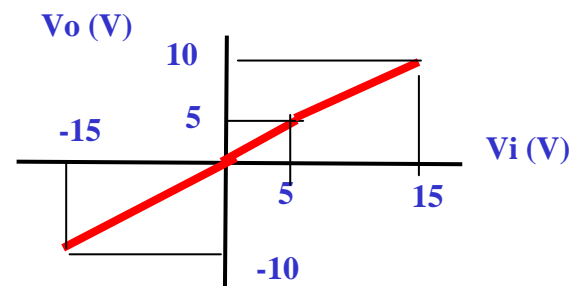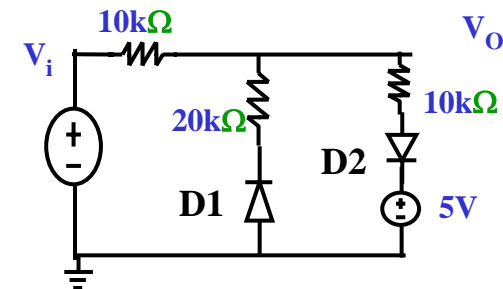(b) In the ideal diode circuit below, plot  $V_o$  versus  $V_i$  for  $-15V \leq V_i \leq 15V$ . Label clearly all voltages in your sketch. Explain briefly the reasons for your answers. (15)



$V_i = -15$  to  $0V$ , D1 ON, D2 OFF  
 $V_o = V_i(2/3)$

$V_i = 0$  to  $5V$ , D1 OFF, D2 OFF  
 $V_o = V_i$

$V_i = 5$  to  $15V$ , D1 OFF, D2 ON  
 $V_o = 5 + (V_i - 5)/2$

6

6. In the diode circuit, the diode has the reverse characteristics as shown. The diode equation is

$$I_D = I_S (e^{V_D / 25 \text{mV}} - 1)$$

(a) Sketch the circuit model of the diode at breakdown.



(b) If  $V_1 = 4\text{V}$ ,  $R_1 = 1\text{k}\Omega$ ,  $R_2 = 1\text{k}\Omega$ , find  $I_O$

(c) If  $V_1 = -5.6\text{V}$ ,  $R_1 = 0.7\Omega$ ,  $R_2 = 0.1\Omega$ , find  $I_O$ .


(d) If  $V_1 = 16\text{V}$ ,  $R_1 = 2\text{k}\Omega$ ,  $R_2 = 2\text{k}\Omega$ , find  $V_O$ .

Show clearly your reasons

(45)

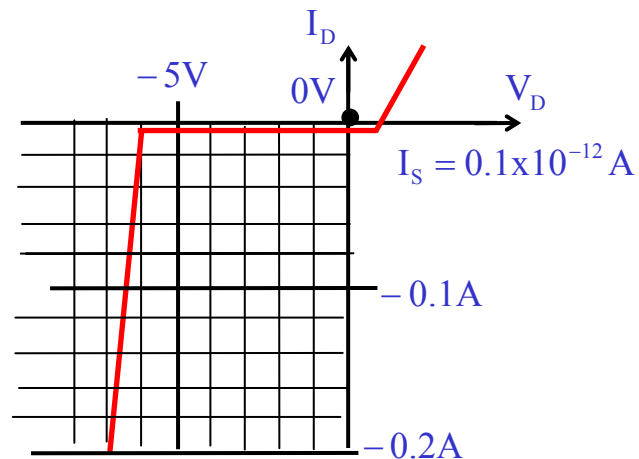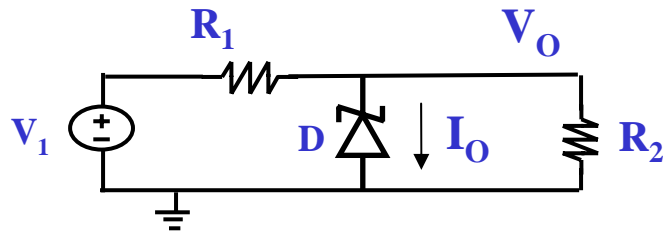

a

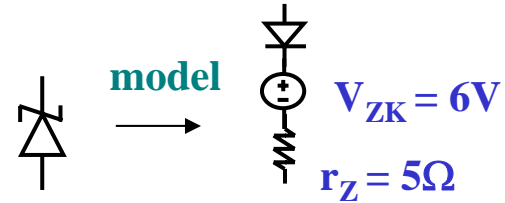

b

$$V_O = V_1 * \frac{R_2}{R_1 + R_2} = 4\text{V} * \frac{1\text{k}\Omega}{1\text{k}\Omega + 1\text{k}\Omega} = 2\text{V}$$

diode is OFF

$$\therefore I_O = I_S = 0.1 \times 10^{-12} \text{ A}$$

c

$$V_o = V_1 * \frac{R_2}{R_1 + R_2} = -5.6V * \frac{0.1\Omega}{0.7\Omega + 0.1\Omega} = -0.7V$$

diode is ON

$$\begin{aligned}\therefore I_o &= -I_s (e^{\frac{0.7V}{25mV}} - 1) \\ &= -0.1 \times 10^{-12} A (e^{\frac{700m}{25m}} - 1) \cong -0.145A\end{aligned}$$

d

$$V_o = V_1 * \frac{R_2}{R_1 + R_2} = 16V * \frac{2k\Omega}{2k\Omega + 2k\Omega} = 8V$$

diode is BREAKDOWN

$$\begin{aligned}\frac{16V - V_o}{2k\Omega} &= \frac{V_o - 6V}{5\Omega} + \frac{V_o}{2k\Omega} \\ 16V - V_o &= 400(V_o - 6V) + V_o \\ V_o &= \frac{2400V + 16V}{402} \cong 6.01V\end{aligned}$$






7


7. (a) Plot the waveform of  $V_O(t)$ . Show clearly the voltage and time in your plot.

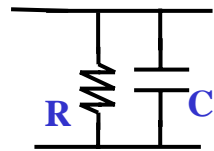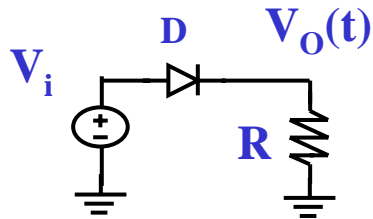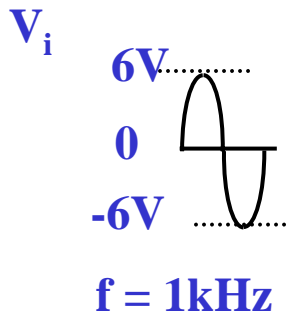(b) If a **capacitance C** is connected **in parallel** to  $R$ , sketch the waveform of  $V_O(t)$ . Show also that the ripple voltage  $V_r$  of  $V_O(t)$  is about 0.18V.


Given that  $R = 3k\Omega$ ,  $C = 10 \mu F$ , diode is an **offset diode** and threshold voltage  $V_F$  is 0.7V. (24)



a

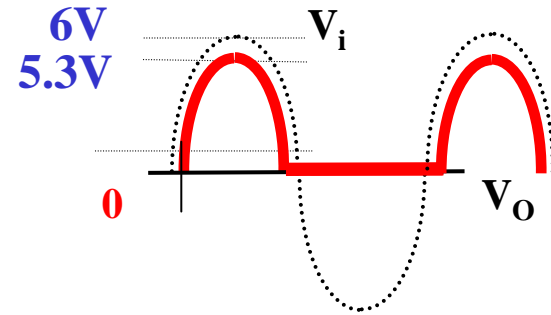

b

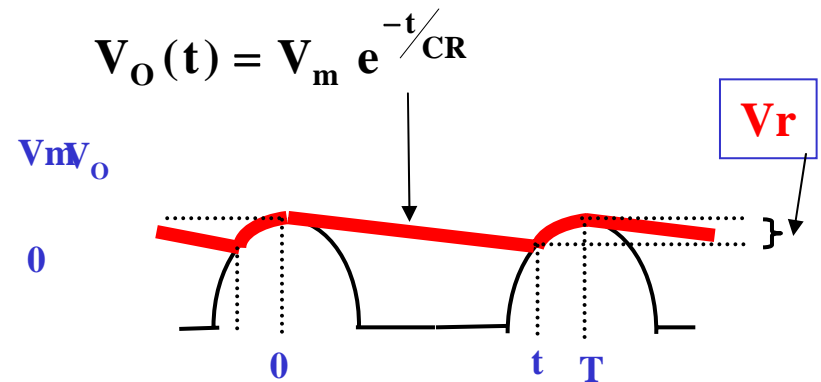

$$V_r = V_m(1 - e^{-T/CR}) \cong V_m(T/CR)$$

$$= (6V - 0.7V)(1\text{ms}/30\text{ms}) \cong 0.18V$$