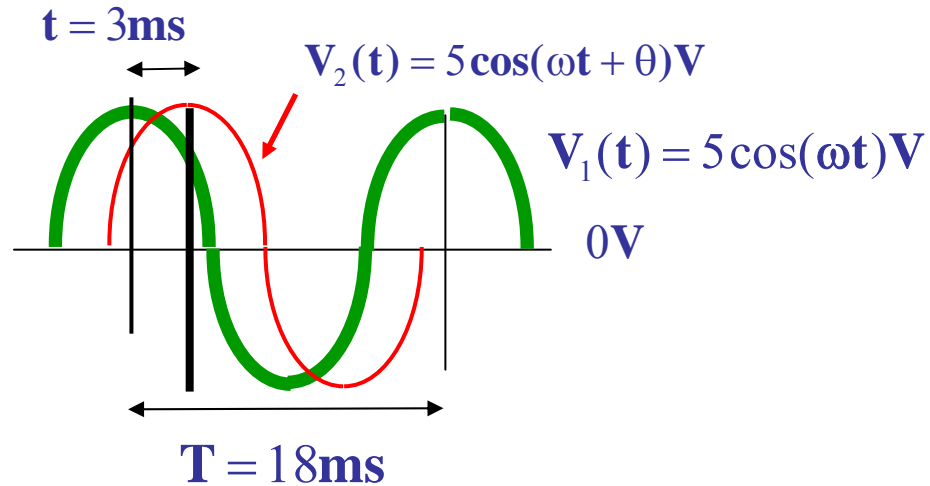


1

Find ω and θ . Does $V_2(t)$ lag $V_1(t)$? Given period of $V_2(t)$ is 18ms, and difference between the peaks of $V_1(t)$ and $V_2(t)$ is 3 ms. (12)



$V_2(t)$ lags $V_1(t)$ (3.5)

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{18\text{ms}} \quad (3.5)$$

$$\theta = -\frac{t}{T} * 360^\circ = -\frac{3\text{ms}}{18\text{ms}} * 360^\circ = -60^\circ \quad (5)$$


(20)

2

(20)

(a) If $X = 2\text{k}\Omega$, $I_m = 5\text{mA}$, $\theta = 60^\circ$, find V_m , ϕ , power factor of X , power stored in X .

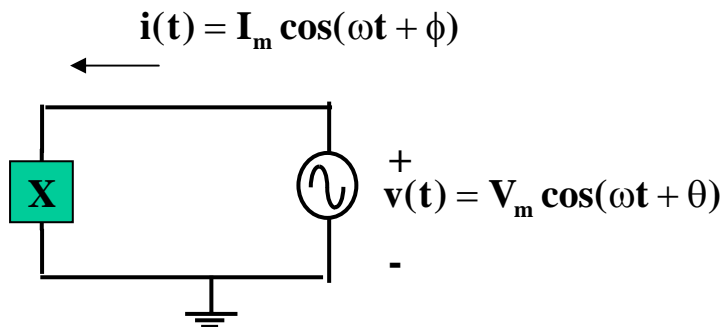(b) If $X = -j4\Omega$, $V_m = 8\text{V}$, $\theta = -10^\circ$, find I_m , ϕ , power factor of X .



(a) $V_m = 10\text{V}$ (2.5)

$\phi = 60^\circ$ (2.5)

$\text{PF} = 1$ (2)

$Q_R = 0$ (2.5)



(b) $I_m = 2\text{A}$ (3.5)

$\phi = 80^\circ$ (5)


$\text{PF} = 0$ (2)

3 Explain briefly why the voltage of capacitor is continuous with time.

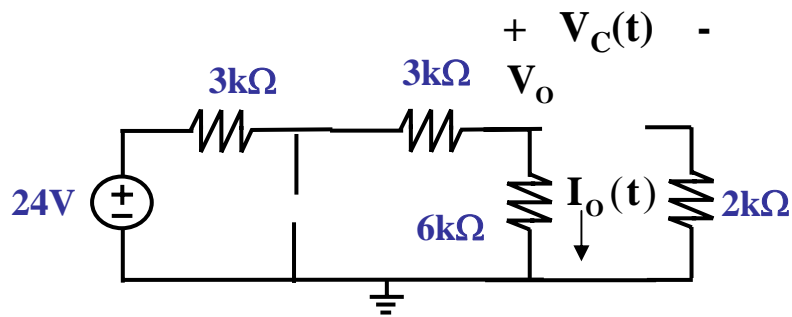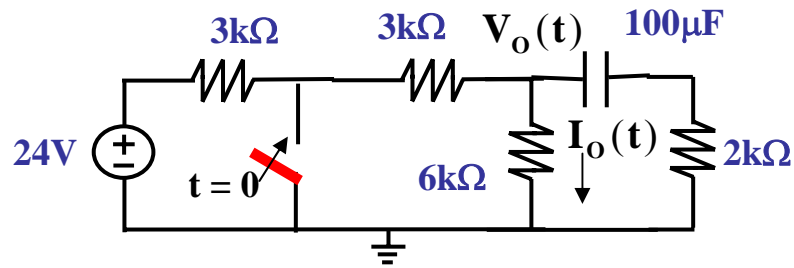(b) circuit is at steady state for $t < 0$. At $t = 0$, the switch is closed. Find $I_o(0)$. (17)



$$\therefore V_C(0) = 12V$$

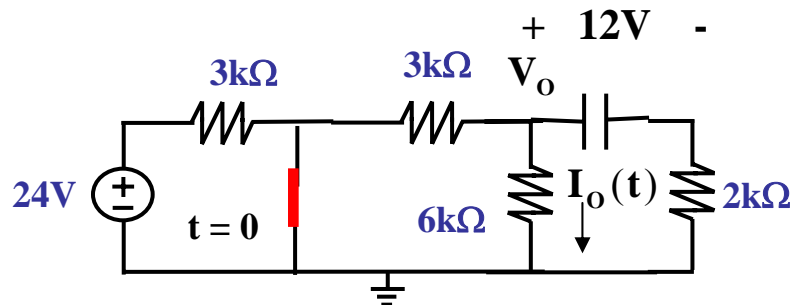

(a)

$$E_C = \frac{CV_C(t)^2}{2} \quad (8)$$

E_C (hence V_C) must be continuous with time

(b)

$$\therefore I_o(0) = \frac{12V}{3k\Omega // 6k\Omega + 2k\Omega} * \frac{3k\Omega}{3k\Omega + 6k\Omega} = 1mA \quad (9)$$

4


In the circuit,

$$V(t) = 2\sqrt{2} \cos(1kt) \text{ V}$$

$$I(t) = 40\sqrt{2} \cos(1kt) \text{ mA}$$

Find V_o in V_{rms}

(13)

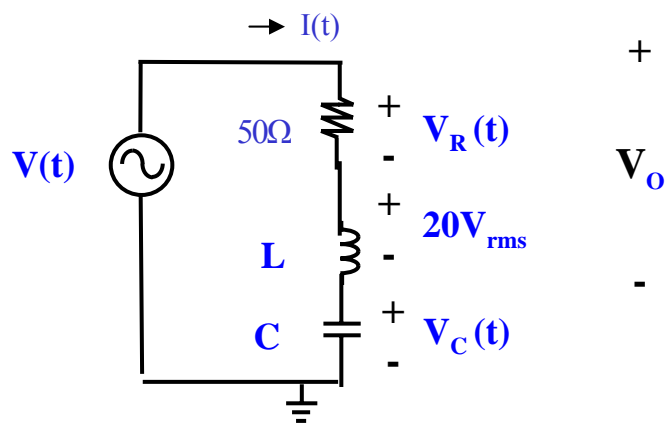

(13)

$$\therefore I = 40\text{mA}_{\text{rms}} \quad (3)$$


$$\therefore V_R = 40\text{mA}_{\text{rms}} * 50\Omega = 2V_{\text{rms}} \quad (4.5)$$

$$\therefore V_o = \sqrt{2^2 + 20^2} \cong 20.1V_{\text{rms}} \quad (5.5)$$

$$\therefore V_C = -20V_{\text{rms}}$$

5

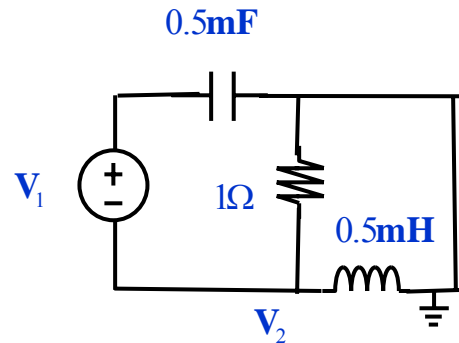
In the circuit, $V_1(t) = 4\cos(2kt)V$ find V_2 in phasor form. (23)



$$\therefore V_1 = 4\angle 0^\circ V \quad (3)$$

$$\frac{1}{j\omega C} = \frac{1}{j(2k)0.5mF} = -j\Omega \quad (3)$$
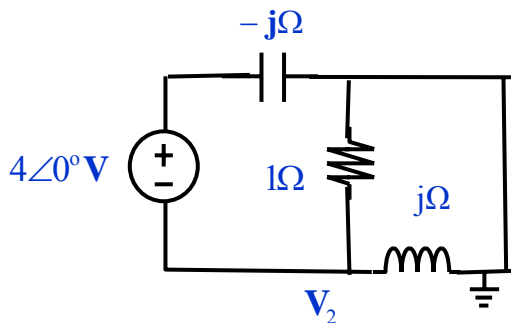
$$j\omega L = j(2k)0.5mH = j\Omega \quad (3)$$




$$\frac{0 - V_2}{j\Omega} = \frac{V_2}{1\Omega} + \frac{V_2 + 4}{-j\Omega} \quad (6.5)$$

$$-V_2 = jV_2 - (V_2 + 4)$$

$$V_2 = -j4V = 4\angle -90^\circ V \quad (7.5)$$


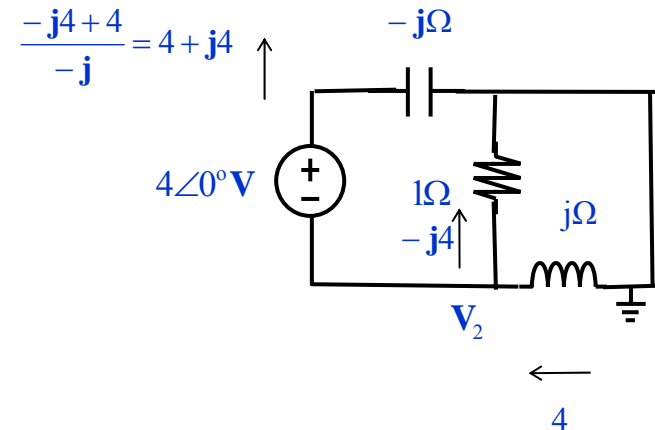
$$\therefore V_2(t) = 4\cos(2kt - 90^\circ)V$$



6

Show that the **open circuit voltage** at terminal ab is $6\angle 0^\circ$ V. Find the Thevenin impedance and hence use Thevenin's Theorem to find V_2 .

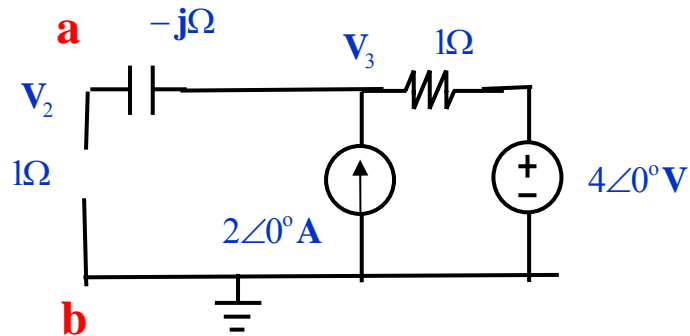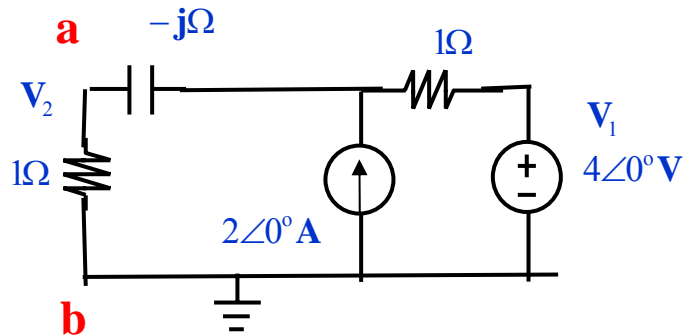Draw also V_1 and V_2 in a **phasor diagram**. (25)




$$\therefore V_{oc} = V_3 = 4\angle 0^\circ + 2\angle 0^\circ * 1\Omega = 6\angle 0^\circ \text{ V} \quad (4.5)$$


$$\text{Thevenin impedance, } Z = 1 - j\Omega \quad (5.5)$$

$$\therefore V_2 = \frac{1}{1 + 1 - j\Omega} * 6\angle 0^\circ \text{ V} \quad (5)$$
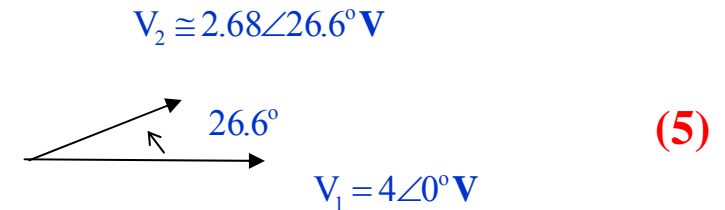
$$= \frac{6\angle 0^\circ}{\sqrt{5}\angle -26.6^\circ} \quad (5)$$
$$\cong 2.68\angle 26.6^\circ \text{ V}$$



7

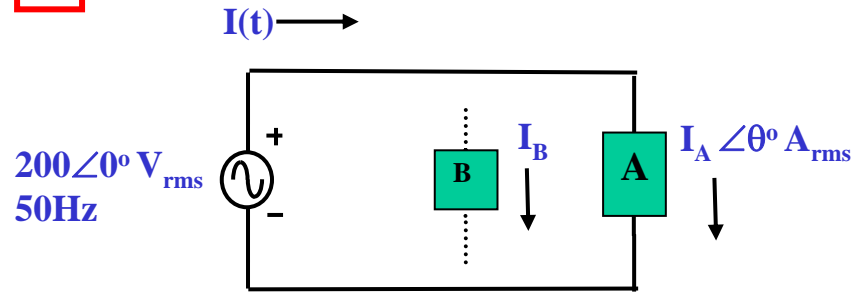

- (a) P = real (or average) power dissipated by load (3)
 S = power supplied by source to load Z (3)
 Q = power stored in Z (3)

(b)

$$Q = S \sin \theta = 5\text{k} \sin(\cos^{-1} 0.8) = 3\text{kVAR(L)} \quad (6)$$

$$(c) \quad I_A = \frac{S}{V} = \frac{5\text{k}}{200} = 25\text{A}_{\text{rms}} \quad (6.5)$$

$$L = \frac{Q}{\omega I^2} = \frac{3\text{k}}{2\pi 50 (25^2)} \cong 15.3\text{mH} \quad (6)$$

$$\theta = -\cos^{-1} 0.8 \cong -37^\circ \quad (6)$$

$$(d) \quad \therefore C = \frac{|Q_c|}{V^2 \omega} = \frac{3\text{k}}{(200^2) 2\pi 50} \cong 0.24\text{mF} \quad (7)$$



$$I = \frac{S}{V} = \frac{4\text{k}}{200} = 20\text{A}_{\text{rms}}$$

$$I_B = \frac{Q}{V} = \frac{3\text{k}}{200} = 15\text{A}_{\text{rms}} \quad (6.5)$$

Load A is connected in parallel to a 200V_{rms}, 50 Hz supply as shown. Power factor PF of load A is 0.8 lagging. $S = 5\text{kVA}$.
 (a) Explain very briefly the physical meaning of apparent power S , reactive power Q and average power P .
 (b) Show that Q of load A = 3kVAR.
 (c) If load A consists of R and L in series, find I_A (in Arms), L and θ .
 (d) If load B is connected in parallel to load A such that the power factor (PF) of the combined load is 1, find the element and value of load B. Find also I_B in Arms. (47)

8

Find V_2 (15)

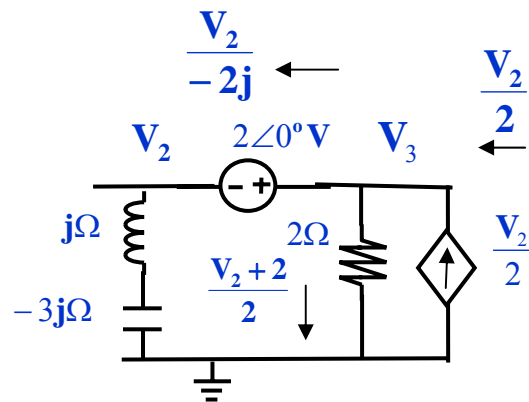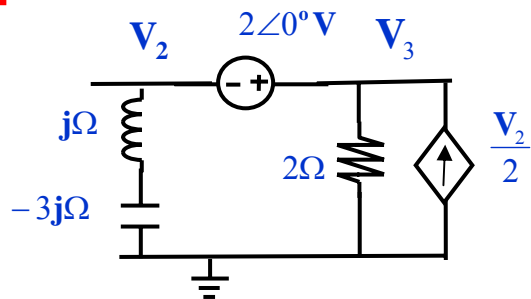


$$\frac{V_2}{2\Omega} = \frac{V_2 + 2V}{2\Omega} + \frac{V_2}{-2j\Omega} \quad (8)$$


$$0 = 1 - \frac{V_2}{2j}$$

$$\therefore V_2 = 2j \quad (7)$$

9

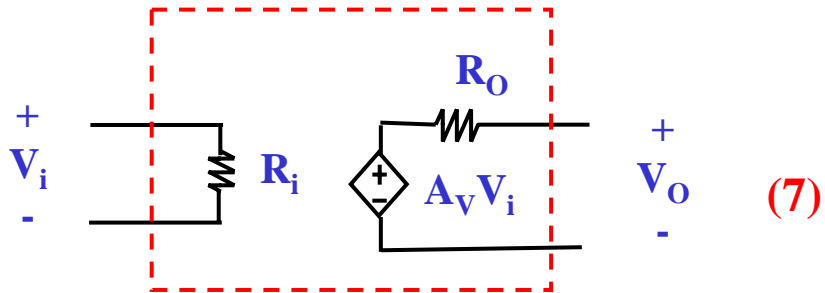

$$R_o = 0 \quad (3)$$

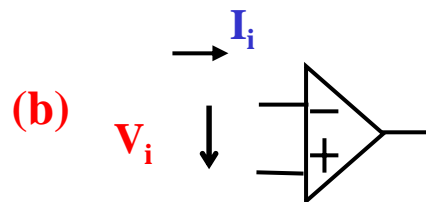

$$V_i = \frac{V_o}{A} \cong \frac{\pm 15V}{\infty} = 0V \quad (6)$$

$$I_i = \frac{V_i}{R_i} \cong \frac{0V}{\infty \Omega} = 0A \quad (5)$$


(a)

Draw the circuit model for a **voltage amplifier**.
What is the ideal value of the output resistance?

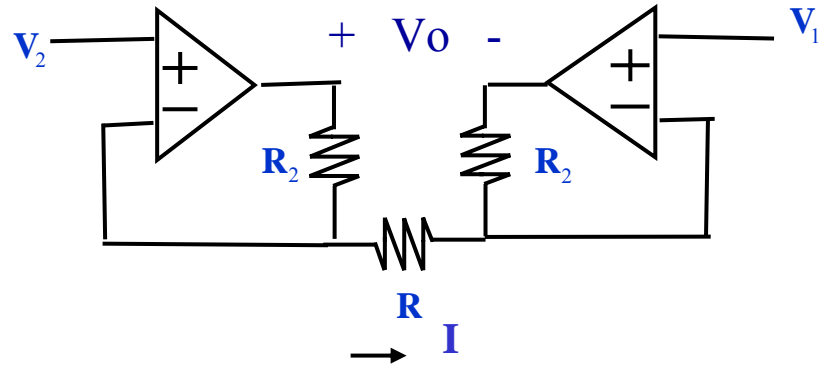(b) Explain briefly why for ideal op amp,
the V_i and I_i are ~ 0 . (21)

10

In the instrumentation amplifier,
find $V_o / (V_2 - V_1)$ in terms of R_2 and R .
Name also two advantages of this amplifier.
Assume the op amps are ideal. (17)



$$\therefore V_o = I * (2R_2 + R) = \frac{V_2 - V_1}{R} (2R_2 + R) \quad (10)$$

High input resistance
Change voltage gain by only 1 R (7)