

(15)

1


(a) Name two advantages of MOSFET. (b) Draw the cross sectional diagram for an enhancement NMOSFET and describe very briefly the structure. Are  $I_G = 0$  and  $I_D = I_S$ ? (15)

(a)

small size (scaled down easily)  
and low power consumption.

(4)

(b)

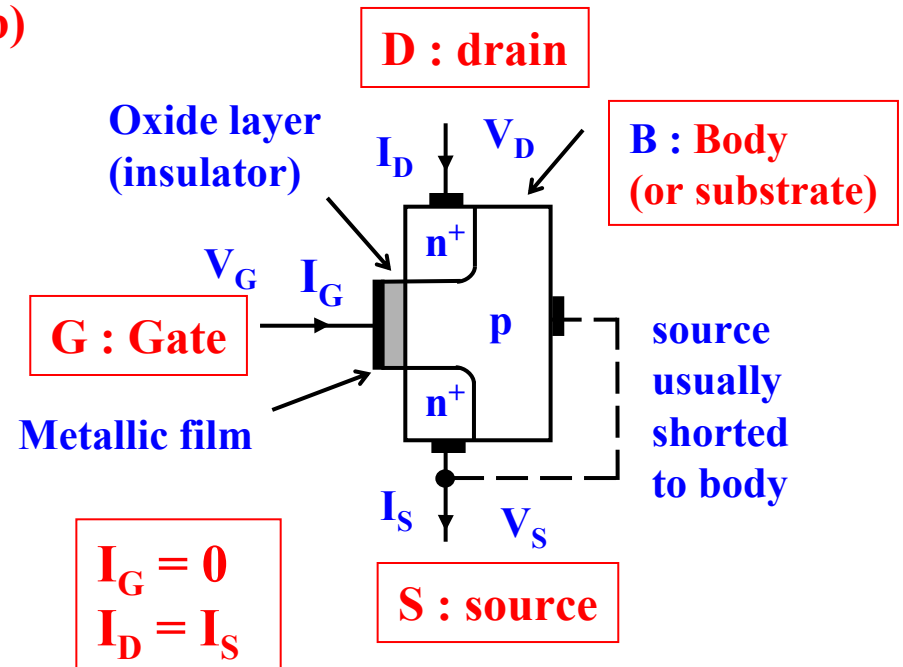

(1)

An NMOSFET consists of a **metal gate** insulated from a **p-type semiconductor** substrate (or body) by an insulating layer of **silicon dioxide**. On either side of the gate there are **n type** regions forming the **drain and source**.

(10)

(16)

1


In the circuit, find  $V_1$ . Show clearly your reasons .  
(16)

Given that  $V_T = 1V$ ,  $K = 2 \text{ mA/V}^2$ .


(c)

At triode region,  $V_{GS} \geq V_T$ ,  $V_{DS} < V_{GS} - V_T$ ,  $I_D = 2K(V_{GS} - V_T)V_{DS} - KV_{DS}^2$

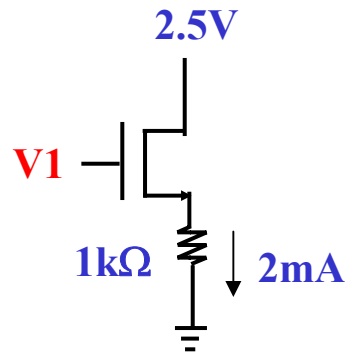At saturation region,  $V_{GS} \geq V_T$ ,  $V_{DS} \geq V_{GS} - V_T$ ,  $I_D = K[(V_{GS} - V_T)^2]$



(c)

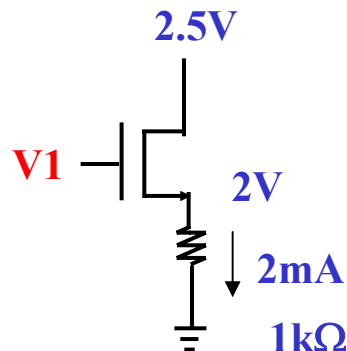

$$V_{GS} = V_1 - 2 \quad V_{DS} = 0.5V$$

NMOS may be triode since  $V_{DS} \sim 0$  (4)

$$\therefore I = 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}]$$

$$\therefore 2\text{mA} = 2 * 2[(V_1 - 2 - 1) * 0.5 - \frac{0.5^2}{2}]$$

$$\therefore V_1 = (\frac{2\text{mA}}{4} + 0.125) * 2 + 3 = 4.25V \quad (8)$$

Hence NMOS is triode since

$$\begin{aligned} 1. & V_{GS} > V_T \quad 2.25 > 1 \\ 2. & V_{DS} < V_{GS} - V_T \quad 0.5 < 2.25 - 1 \end{aligned} \quad (4)$$

$$\therefore I = 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}]$$

$$= 2 * 2\text{m}[(4.25 - 2 - 1) * 0.5 - \frac{0.5^2}{2}] = 2\text{mA}$$

(18)

2


Find  $I$ . Show clearly your reasons. (18)

Given the NMOS are identical,

$$V_T = 1V, K = 0.25m \text{ A/V}^2.$$

At triode region,  $V_{GS} \geq V_T$ ,  $V_{DS} < V_{GS} - V_T$ ,  $I_D = 2K(V_{GS} - V_T)V_{DS} - KV_{DS}^2$

At saturation region,  $V_{GS} \geq V_T$ ,  $V_{DS} \geq V_{GS} - V_T$ ,  $I_D = K[(V_{GS} - V_T)^2]$

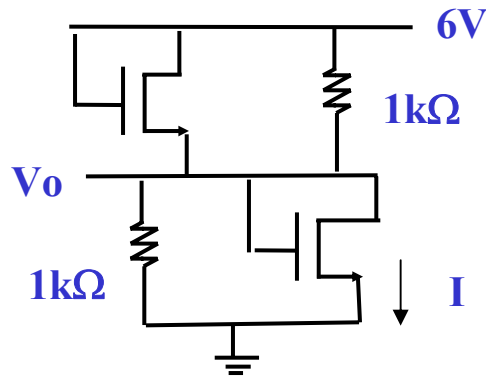Assume 2 NMOS are in saturation and use KCL

(4)

$$\therefore I_D = K(V_{GS} - V_T)^2$$

$$\therefore 0.25m * (6 - V_o - 1)^2 + \frac{6 - V_o}{1k\Omega} = 0.25m * (V_o - 1)^2 + \frac{V_o}{1k\Omega}$$

(4)

From symmetry,  $V_o = 3V$  (5)

$$\therefore I = 0.25m * (6 - 3 - 1)^2 = 1mA \quad (2)$$


$$V_{GS1} = 3V \quad V_{DS1} = 3V$$

$$V_{GS2} = 3V \quad V_{DS2} = 3V$$

Hence NMOS is saturate since

$$1. V_{GS} > V_T \quad 3 > 1$$
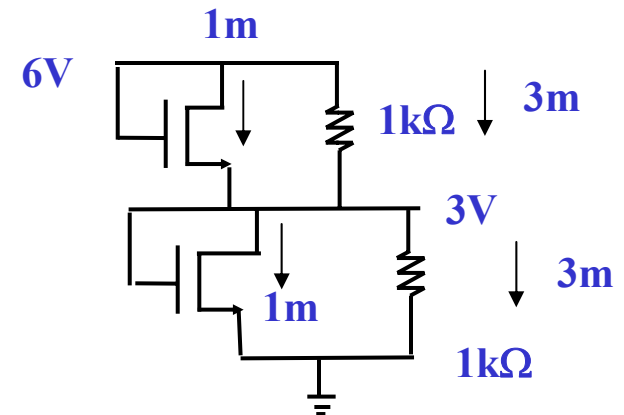
$$2. V_{DS} > V_{GS} - V_T \quad 3 > 3 - 1 \quad (4)$$





(17)

3


In the diode circuit, find  $V_C$ . Hence sketch and label clearly  $V_o(t)$ .

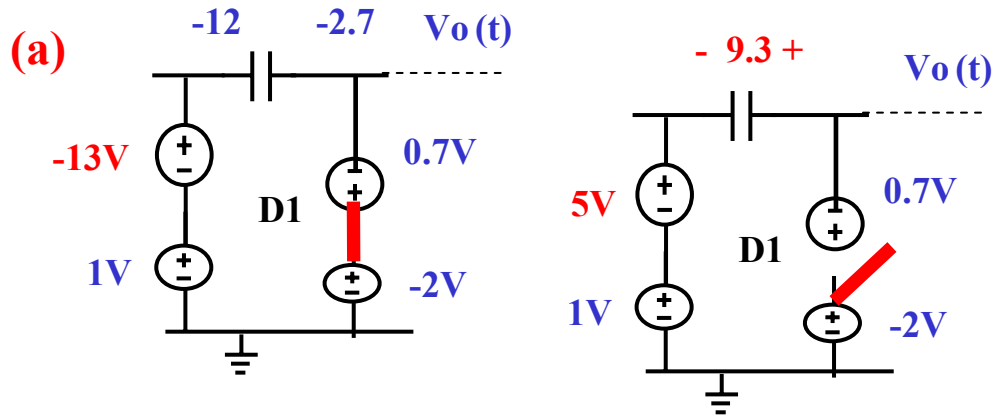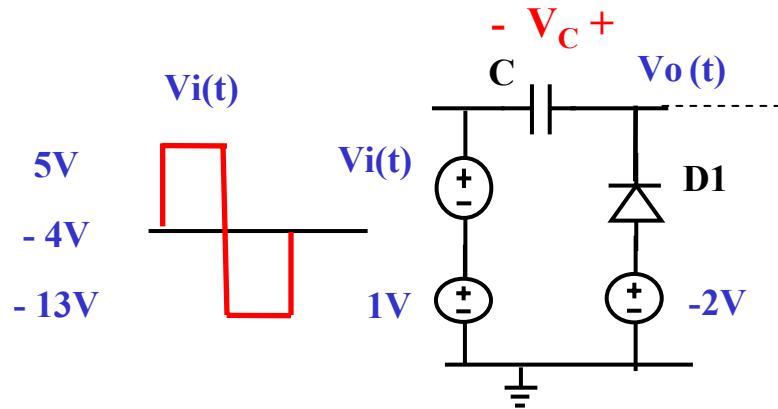(a) D1 is an offset diode with  $V_F = 0.7V$ . (17)




$$V_C = 9.3V \quad (11)$$
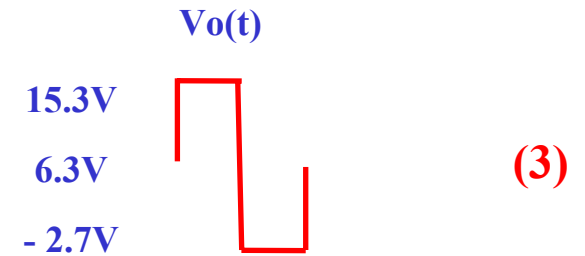
$$V_o = V_i + 1 + V_C = V_i + 10.3V \quad (3)$$



OR

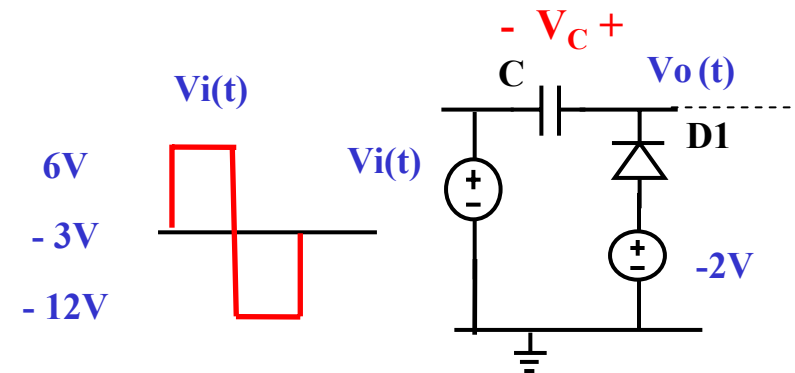






$$V_o = V_i + V_C = V_i + 9.3V \quad (3)$$

(24)

3

In the ideal diode circuit, plot  $V_3$  versus  $V_2$  for  $18V \geq V_2 \geq 0V$ . (24)

(b)

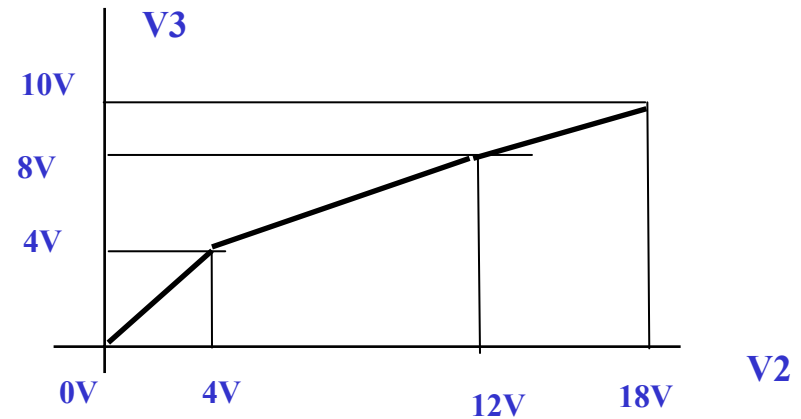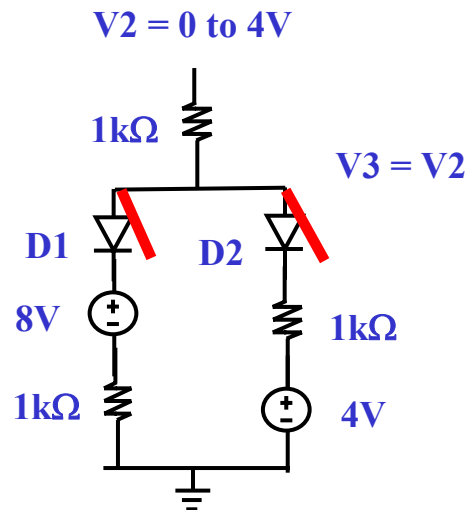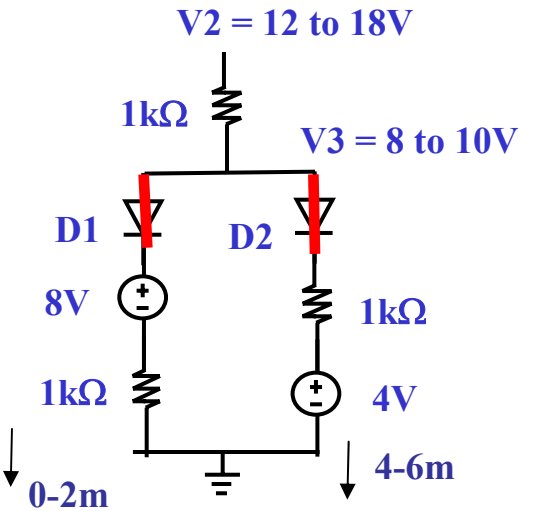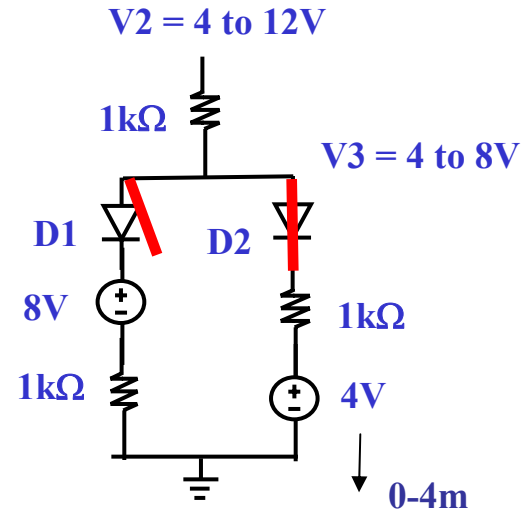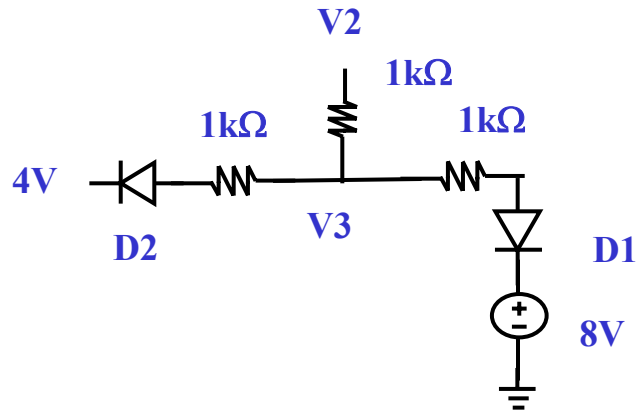

(8)

(8)

(8)

(15)

4

- (a) Find the model of the diode D1 at breakdown.  
 (b) Find I1 if  $R_3 = 1\text{k}\Omega$ ,  $I_2 = 5\text{mA}$ ,  $R_1 = R_2 = 4\text{k}\Omega$ ,  $V_1 = 3\text{V}$ .  
 (c) Find  $V_2$  if  $V_1 = 4.7\text{V}$ ,  $R_1 = R_2 = 1\text{k}\Omega$ ,  $R_3 = 2\text{k}\Omega$ ,  $I_1 = -1\text{mA}$ ,  $V_4 = 3\text{V}$ .



Show clearly your reasons. (30)

Given that D1 and D2 are identical.


Diode equation is

$$I_D = I_0 * [e^{\frac{V_D}{25\text{mV}}} - 1]$$

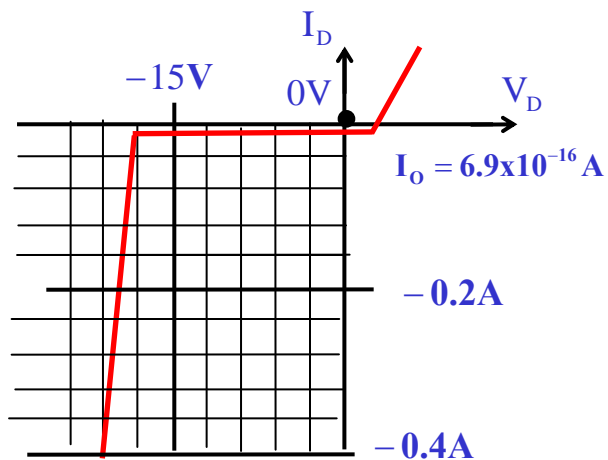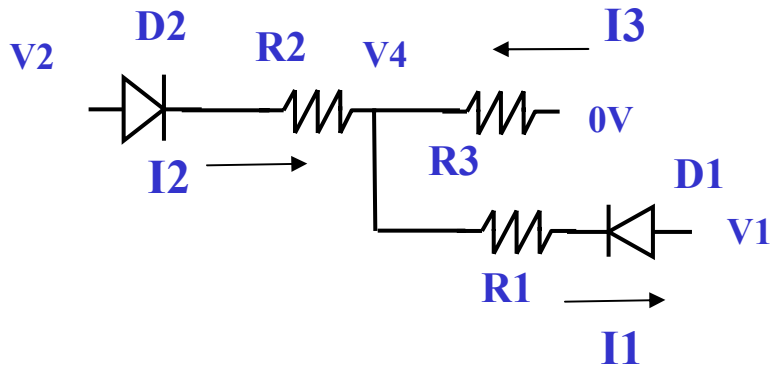
and the diode has the I-V curve as shown.



(a)

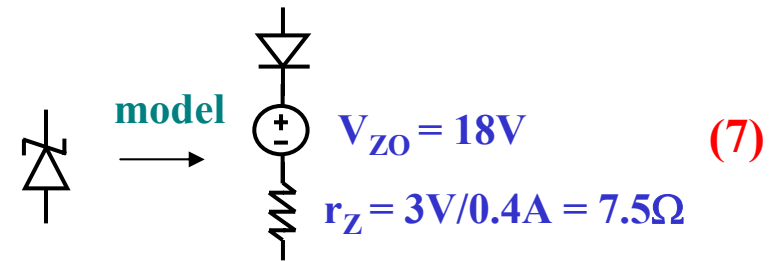

(b)

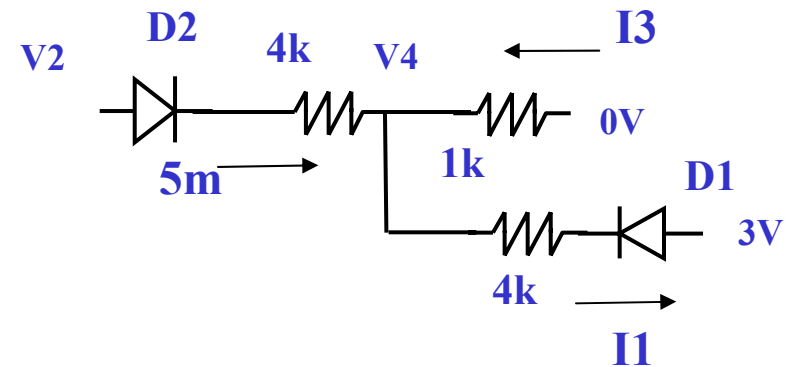

$$V_4 = 5\text{V} > 3\text{V}$$

D1 is OFF (5)

$$I_1 = I_0 = 6.9 \times 10^{-16} \text{A} \quad (3)$$

$$\frac{3 - v_4}{4\text{k}} + 5\text{m} = \frac{v_4}{1\text{k}}$$

$$3 - v_4 + 20 = 4v_4$$


$$v_4 = 4.6\text{V}$$

Use KCL and D1 is OFF

(15)

4

(c)

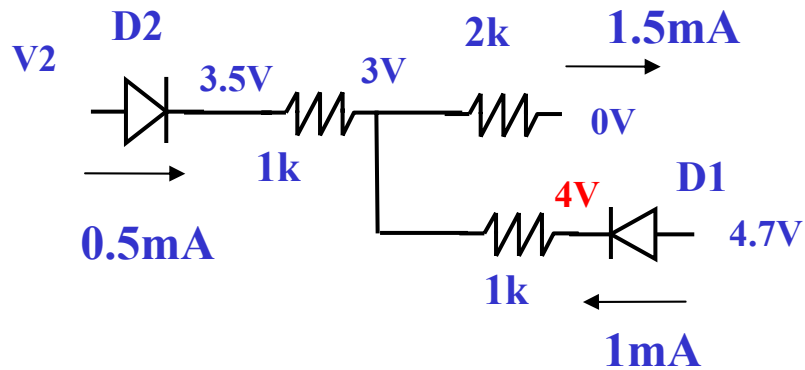

$$\therefore I_2 = 0.5\text{mA} \quad (5)$$

$$\therefore 0.5\text{mA} \cong I_o(e^{\frac{V_D}{25\text{mV}}}) \quad (2)$$

$$\therefore V_D = 25\text{mV} * \log_e \frac{0.5\text{mA}}{6.9 \times 10^{-19} \text{A}} \cong 682.7\text{mV} \quad (5)$$

$$\therefore V_2 \cong 3.5 + 0.683 = 4.183\text{V} \quad (3)$$

OR

$$\therefore 1\text{mA} = I_o(e^{\frac{V_D}{25\text{mV}}} - 1) \cong I_o(e^{\frac{700\text{mV}}{25\text{mV}}})$$

$$\therefore 0.5\text{mA} \cong I_o(e^{\frac{V_D}{25\text{mV}}})$$


$$\therefore \log_e 2 = \frac{700\text{mV} - V_D}{25\text{mV}}$$

$$\therefore V_D \cong 682.7\text{mV}$$

$$\therefore V_2 \cong 3.5 + 0.683 = 4.183\text{V}$$


(18)

5

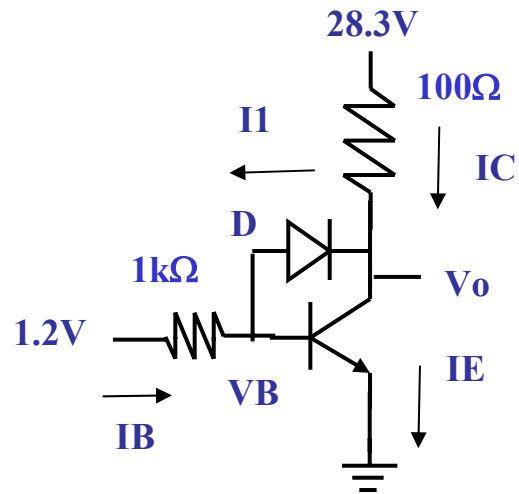Find  $I_E$ . Given  $V_o = 5.8V$ .Show clearly your reasons. For the BJT, given  $V_{BE(ON)} = 0.7V$ ,  $\beta = 10$ ,  $V_{CESAT} = 0.2V$ .For the diode, the diode equation is  $I_D = I_0 * [e^{\frac{V_D}{25mV}} - 1]$  and  $I_0 = 10^{-13}A$ . In breakdown,  $V_{zo} = 5V$ ,  $r_z = 5\Omega$ . (18)

$$\therefore V_B = 0.7V \quad (3)$$

D is breakdown since  $V_o = 5.8V$  (4)

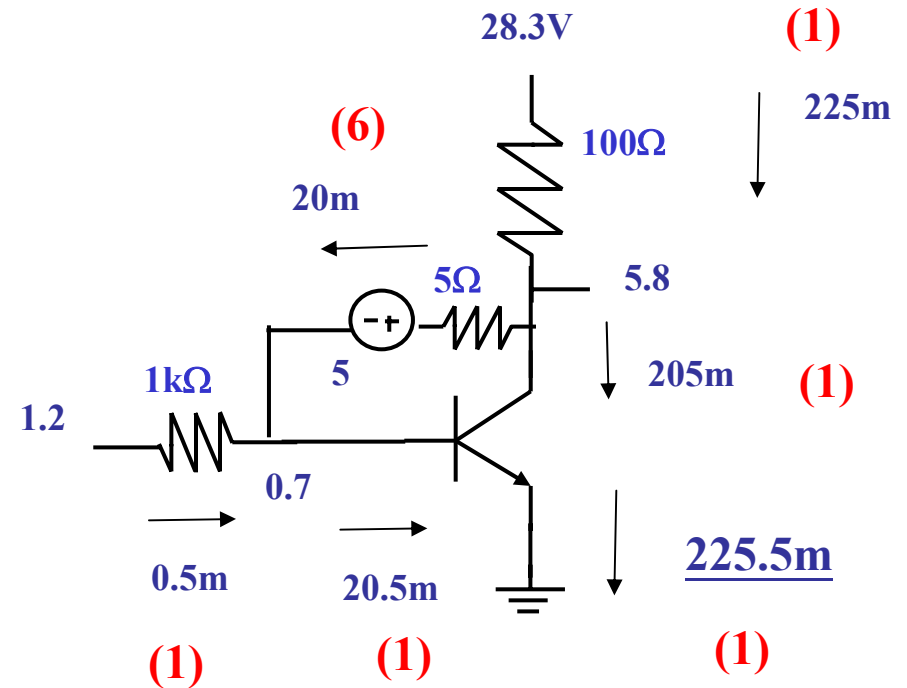



(40)

6

- (a) Name two III-V compound semiconductors.  
 (b) Find the conductivity of intrinsic (pure) Germanium (Ge).  
 Find also the resistivity.  
 (c) The pure Ge is doped to n-type Ge with a dopant of  $1 \times 10^{22}/\text{m}^3$ .  
 Find the conductivity. Find also the hole concentration (in atoms /  $\text{m}^3$ ) .  
 (d)  $5 \times 10^{20} / \text{m}^3$  indium atoms are used to dope the pure Si.  
 Find the electron density  $n$ , hole density  $p$ , and conductivity  $\sigma$ . Is the doped Si n-Si or p-Si ?

Given that  $\sigma = e(n\mu_n + p\mu_p)$ ,  $\rho = 1/\sigma$ ,  $np = n_i^2$ ,  $e = 1.6 \times 10^{-19} \text{ C}$   
 For Ge :  $n_i = 2.4 \times 10^{19}/\text{m}^3$ ,  $\mu_p = 0.19 \text{ m}^2/\text{Vs}$ ,  $\mu_n = 0.39 \text{ m}^2/\text{Vs}$ .  
 For Si :  $n_i = 1.5 \times 10^{16}/\text{m}^3$ ,  $\mu_p = 0.048 \text{ m}^2/\text{Vs}$ ,  $\mu_n = 0.135 \text{ m}^2/\text{Vs}$ .  
 Some atoms : group 3 (boron B, gallium Ga, indium In) ; group 5 (nitrogen N, phosphorus P, arsenic As) (40)

(a) III-V compound  
GaAs, InP etc (4)

(b) The conductivity of intrinsic (pure) Ge

$$\sigma_i = e(\mu_n n_i + \mu_p n_i) = en_i(\mu_p + \mu_n)$$

$$= 1.6 \times 10^{-19} \times 2.4 \times 10^{19} \times (0.19 + 0.39) \cong 2.227 / \Omega\text{m}$$

(7)

$$\rho_i = \frac{1}{\sigma_i} \cong \frac{1}{2.227} \cong 0.45 \Omega\text{m} \quad (4)$$

(b)

$$\begin{aligned} \therefore \sigma_N &= e(\mu_p p + \mu_n n) \cong e(\mu_n n) \\ &= 1.6 \times 10^{-19} * (0.39 * 1 \times 10^{22}) \cong 624 / \Omega\text{m} \end{aligned} \quad (7)$$

$$\begin{aligned} \therefore p &= \frac{n_i^2}{n} = \frac{(2.4 \times 10^{19})^2}{1 \times 10^{22}} \\ &\cong 5.76 \times 10^{16} \text{ holes} / \text{m}^3 \end{aligned} \quad (6)$$

(c) P-type (2)

$$\therefore p \cong 5 \times 10^{20} \text{ holes} / \text{m}^3 \quad (4)$$

$$\begin{aligned} \therefore n &= \frac{n_i^2}{p} = \frac{(1.5 \times 10^{16})^2}{5 \times 10^{20}} \\ &\cong 4.5 \times 10^{11} \text{ electrons} / \text{m}^3 \end{aligned} \quad (6)$$

$$\begin{aligned} \therefore \sigma_p &= e(\mu_p p + \mu_n n) \cong e(\mu_p p) \\ &= 1.6 \times 10^{-19} * 0.048 * 5 \times 10^{20} \\ &= 3.84 / \Omega\text{m} \end{aligned}$$



(21)

7


(a) If  $X = 1\text{k}\Omega$ ,  $Y = 2\text{k}\Omega$ ,  $V_2 = 0\text{V}$ ,  $V_1 =$  given waveform, draw the waveform of  $V_o$ .

(b) If  $Y = 1\mu\text{F}$ ,  $X = 1\text{k}\Omega$ ,  $V_1 = 0$ ,  $V_2 =$  given waveform. Derive the equation for the output voltage  $V_o$ , and hence draw the waveform of  $V_o$ . Given  $V_o(0) = 0\text{V}$ .

Assume the op amp is ideal. (21)

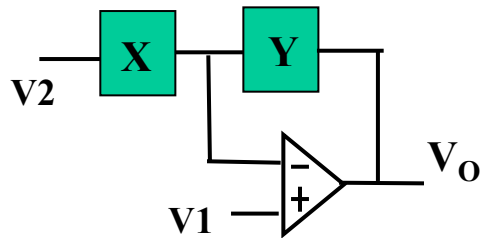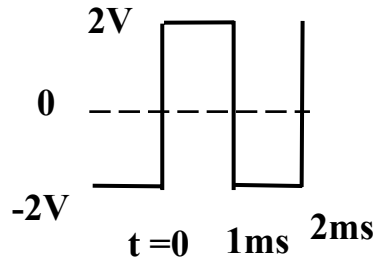


(a)

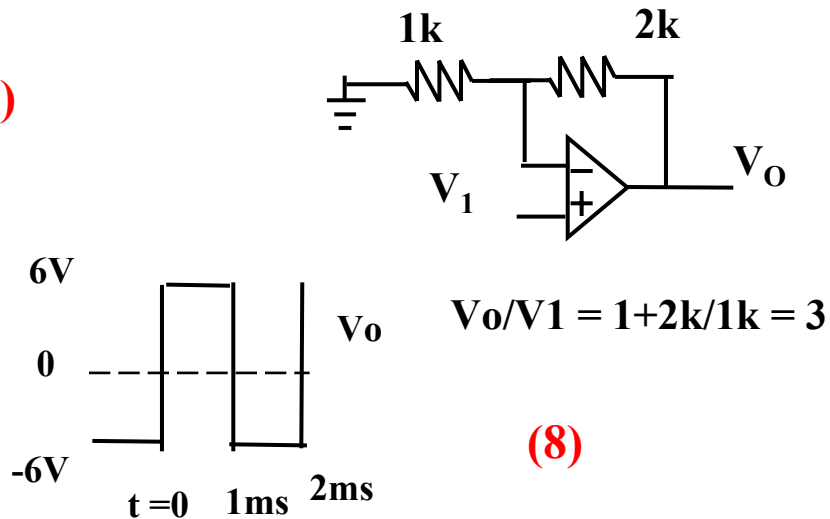

(8)

(b)

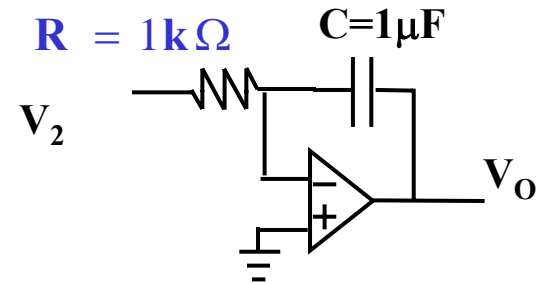


$$\frac{V_2}{R} = C \frac{d(0 - V_o)}{dt}$$

$$\frac{dV_o}{dt} = \frac{-V_2}{CR} = \frac{-2\text{V}}{1\text{ms}}$$

given  $V_o(0) = 0\text{V}$

(8)

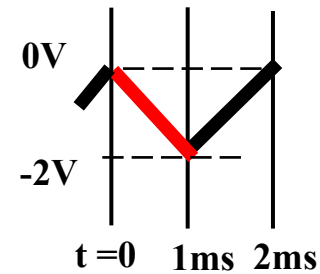

(5)



(22)

8

(a) Find the complex transfer function  $G (= V_o / V_s)$  in terms of  $R_1$ ,  $C$ ,  $R_2$  and  $j\omega$ .

(b) If  $R_1 = 2\text{k}\Omega$ ,  $R_2 = 5\text{k}\Omega$ ,  $C = 0.01\mu\text{F}$ , plot the magnitude of  $G$  ( $|G|$ ) versus  $\omega$ . Show clearly the value of  $|G|$  when  $\omega = 0$ ,  $\omega = \infty$ , and  $\omega = \omega_0$  (cut-off frequency) in your plot. Find also  $\omega_0$ . Assume op amp is ideal.

(22)

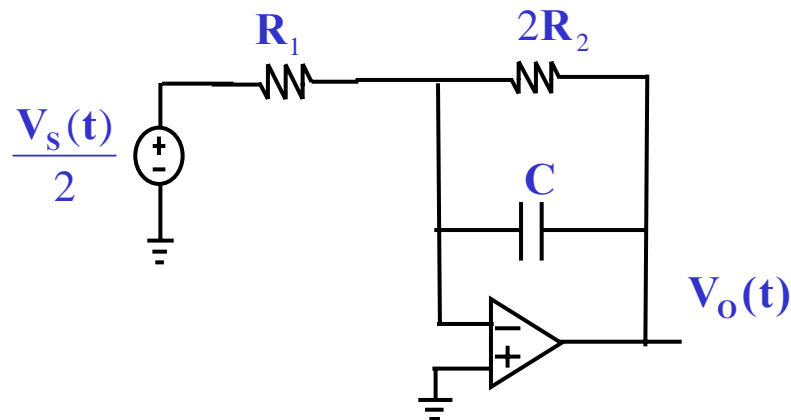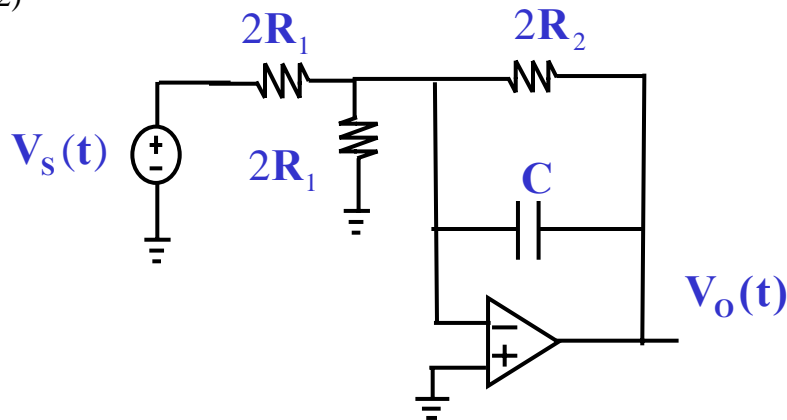

$$\frac{V_o}{0.5V_s} = -\frac{Z_2}{Z_1} = -\frac{2R_2 \parallel \frac{1}{j\omega C}}{R_1}$$

$$\frac{V_o}{V_s} = -\frac{2R_2 * \frac{1}{j\omega C}}{2R_1 (2R_2 + \frac{1}{j\omega C})} = -\frac{2R_2 * \frac{1}{j\omega C}}{2R_1 (1 + j\omega C * 2R_2)}$$


$$= -\frac{R_2 * \frac{1}{j\omega C}}{R_1 (1 + j\omega C * 2R_2)}$$

(10)

$$2\omega CR_2 = 1$$

$$\omega = \omega_0 = \frac{1}{2CR_2} = \frac{1}{2 * 0.01\mu * 5k} = 10\text{krad/s} \quad (5)$$

$$\left| \frac{V_o(\omega)}{V_s(\omega)} \right|$$

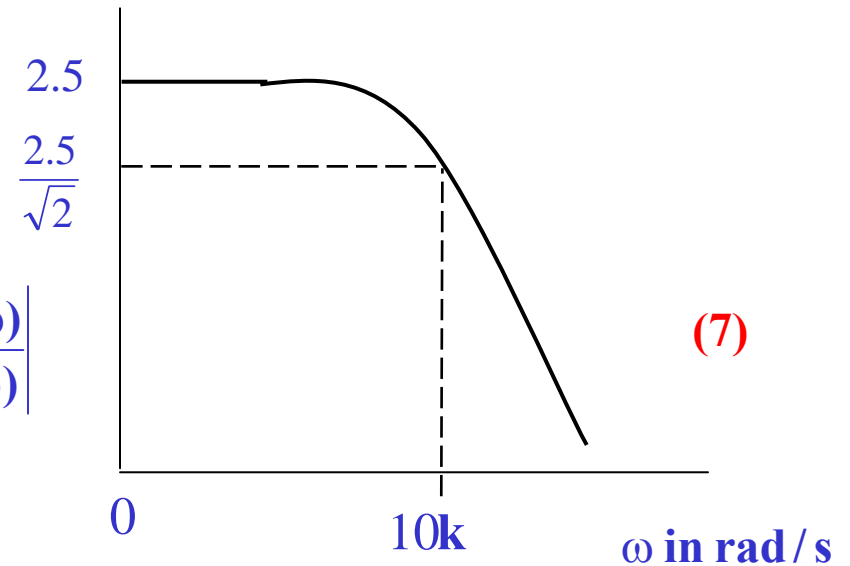

(7)

(20)

9

In an ideal op amp filter circuit, the complex transfer function  $G (= V_O / V_S)$  is given as.  $\frac{-20}{1 - \frac{2j}{\omega CR}}$

(a) If  $V_O(t) = \frac{-10}{\sqrt{17}} \cos(200kt + 66^\circ) \text{ V}$ , find  $V_S(t)$ .

(b) Find the cut-off frequency  $\omega = \omega_O$ . Is the ideal op amp circuit a low pass filter?

Given that  $1/CR = 400 \text{ krad/s}$ . (20)

(b)

$$G = \frac{-20}{1-j} \Rightarrow 2/\omega CR = 1$$

$$\omega = \omega_O = \frac{2}{CR} = 800 \text{ krad/s} \quad (4)$$

(a)

$$G = \frac{-20}{1 - 2j/200k * CR} = \frac{-20}{1 - 4j} = \frac{-20}{\sqrt{17} \angle -76^\circ} \quad (5)$$

$$\therefore V_S = \frac{-10}{\sqrt{17}} \angle 66^\circ / \frac{-20}{\sqrt{17}} \angle 76^\circ = 0.5 \angle -10^\circ \text{ V} \quad (5)$$

$$\therefore V_S(t) = 0.5 \cos(200kt - 10^\circ) \text{ V} \quad (3)$$

Circuit is a high pass filter


(3)

(17)

10

Draw the cross sectional structure of a NPN BJT transistor operated in the amplifier mode. Describe the movement of electrons, the designs in the emitter/base/collector, and explain briefly the equation  $I_E \approx I_C / \alpha$ . Given  $I_C \cong \beta I_B$ , find  $\alpha$  if  $\beta = 200$ . (17)

(a)

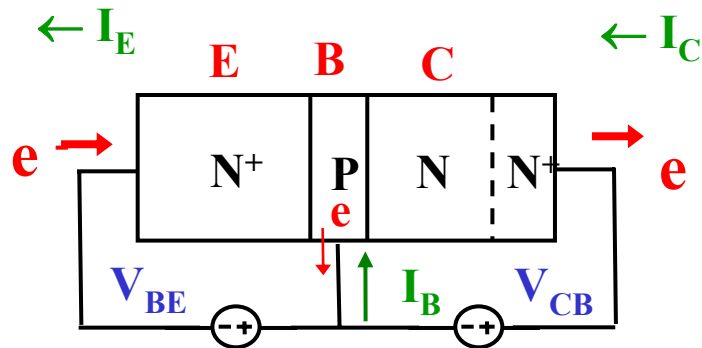

(4)

1. EB Junction is a forward bias (on) diode and BC is reverse bias (off) diode

2. E is very heavily doped ( $N^+$  for NPN). E has many electrons,

3. B is very thin. So most electrons injected from E (to B) are attracted to C and

$$I_C \cong \alpha I_E \quad (7)$$

$$I_E \cong \frac{I_C}{\alpha} = I_B + I_C = \frac{I_C}{\beta} + I_C$$

$$\text{hence } \frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\beta = \frac{\alpha}{1 - \alpha}$$



$$\alpha = \frac{\beta}{\beta + 1} = \frac{200}{201} \quad (6)$$

(19)

11

Draw the small signal (AC) equivalent circuit of the BJT amplifier and find the voltage gain  $A_v (= V_o / V_i)$ .

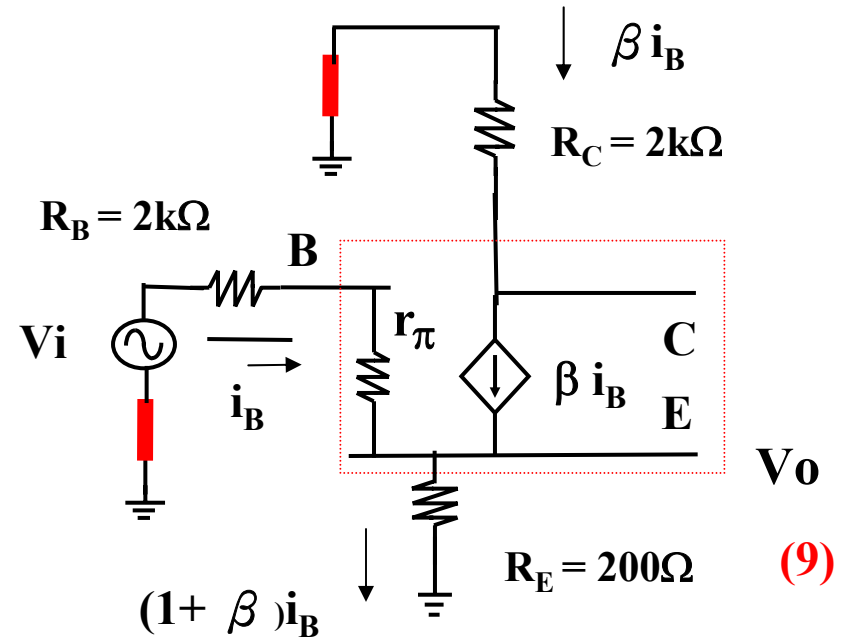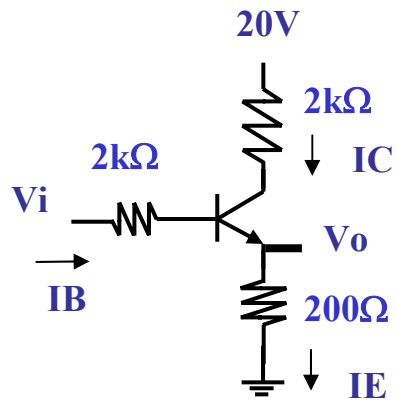Given  $r_\pi = 10\Omega$ ,  $r_o = \infty\Omega$ ,  $\beta = 100$ , and  $V_{CESAT} = 0.2V$ ,  $V_{BE(ON)} = 0.7V$ . (19)



$$\therefore A_v = \frac{V_o}{V_i} = \frac{(1+\beta)i_B R_E}{i_B (R_B + r_\pi) + (1+\beta)i_B R_E} \quad (6)$$

$$= \frac{(1+\beta)R_E}{R_B + r_\pi + (1+\beta)R_E}$$

$$= \frac{101 * 200\Omega}{2010 + 101 * 200\Omega} \cong 0.91 \quad (4)$$


(20)

12

If  $I_B = 0.2\text{mA}$ , find  $I_C/I_B$ .

Show clearly your reasons. For the BJT, given

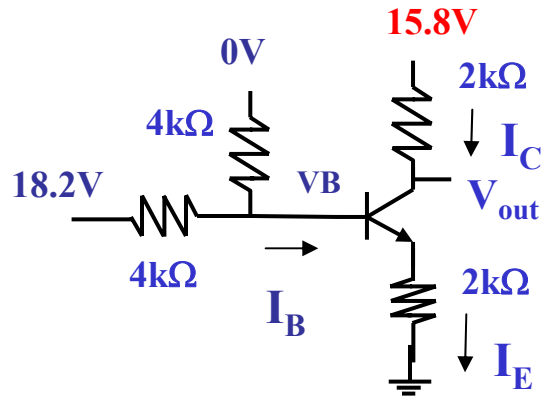
$$V_{BE(ON)} = 0.7\text{V}, \beta = 100, V_{CESAT} = 0.2\text{V}. \quad (20)$$



(a)

when  $V_{CE} = V_{CESAT}$
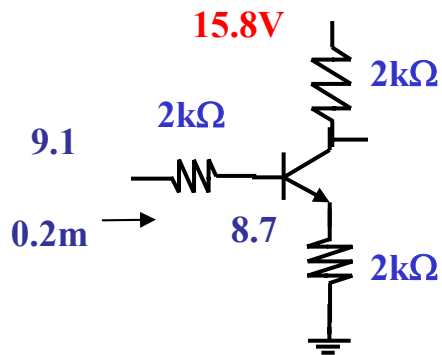
$$I_C \cong I_E \cong \frac{15.8\text{V} - 0.2\text{V}}{4\text{k}\Omega} = 3.9\text{mA}$$



Now  $I_B = 0.2\text{mA}$ ,  $V_B = 8.7\text{V}$ ,  $V_E = 8\text{V}$ ,


$I_E = 4\text{mA}$ , hence BJT is SAT

( OR  $I_B \sim I_C / \beta \sim 0.04\text{mA}$

But now  $I_B \sim 0.2\text{mA}$ , hence BJT is SAT )

Hence  $V_{out} = 8.2\text{V}$ ,  $I_C = 3.8\text{mA}$  (17)
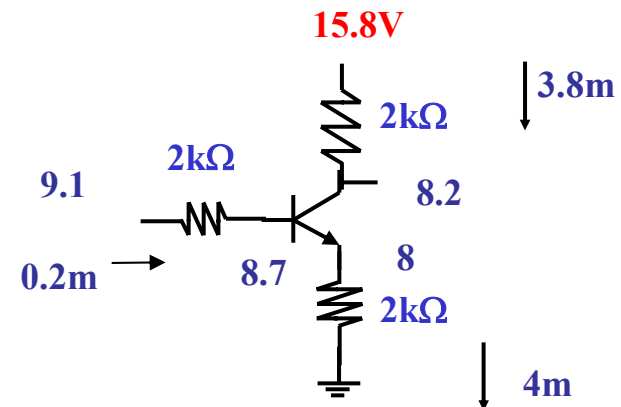
$$\therefore \beta' = \frac{I_C}{I_B} = \frac{3.8\text{mA}}{0.2\text{mA}} = 19 \quad (3)$$



13



Given the BJT circuit below and the  $I_C$ - $V_{CE}$  curve of the BJT.

Given the  $V_B$  waveform and  $V_{CEQ} = 10V$ . (a) Find  $V_{CC}$ , draw the load line  $V_{CE} = V_{CC} - I_C R_C$  and locate the Q point on the load line.

(b) Estimate the voltage gain ( $V_{CE} / V_{IN}$ ) from the load line and  $I_C$  - $V_{CE}$  curves. Show also on the load line the range of movement of the bias point. Draw and label also the waveform of  $V_{CE}$ .

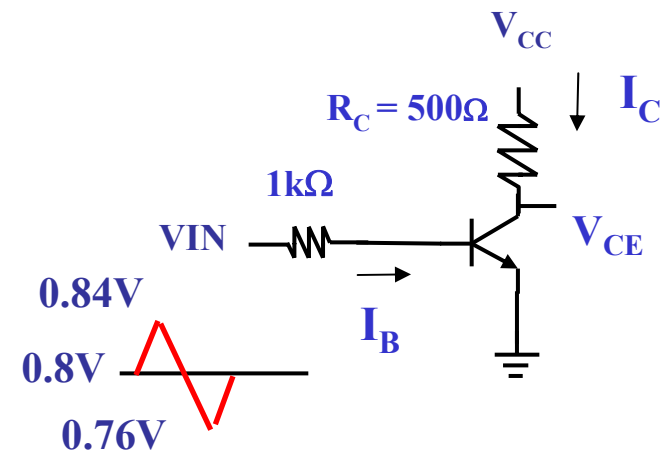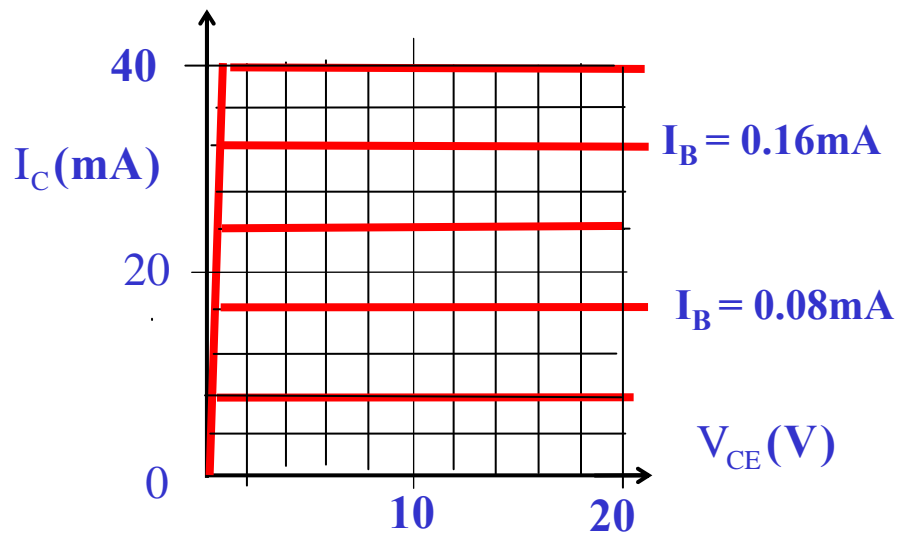(c) If  $V_{BE(ON)}$  is changed from  $0.7V$  to  $0.62V$ , draw roughly and label the waveform of  $I_C$ . (33)

For the BJT, given  $V_{BE(ON)} = 0.7V$ ,  $V_{CESAT} = 0.2V$ .






(33)

Draw load line, Draw Q point,

$$(a) \quad \therefore I_{BQ} = \frac{0.8V - 0.7V}{1k\Omega} = 0.1mA$$


$$\therefore I_{CQ} = 20mA \quad (6)$$
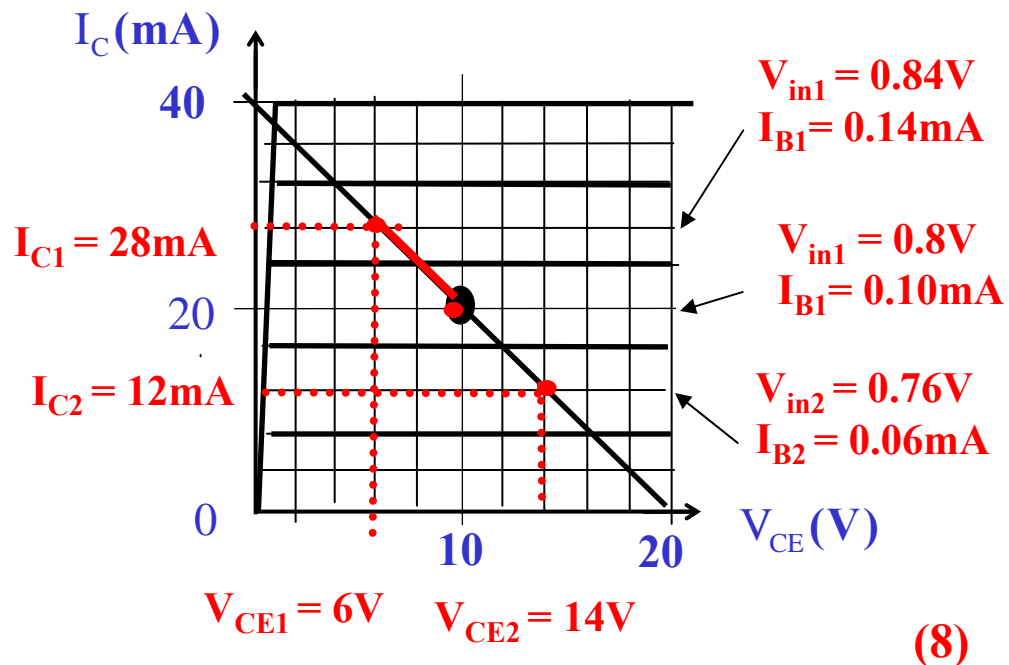
$$\therefore V_{CC} = 10V + 20mA * 500\Omega = 20V \quad (4)$$



(b)
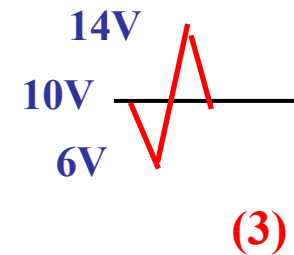
$$\text{voltage gain } A_v = \frac{V_{CE}}{V_B} = \frac{V_{CE2} - V_{CE1}}{V_{in2} - V_{in1}} \\ \cong \frac{14V - 6V}{0.76V - 0.84V} \cong -100 \quad (5)$$



If  $V_{BE(ON)}$  is changed to  $0.62V$ , Q point moves to  $I_B = 0.18mA$ ,  $I_C = 36mA$ ,  $I_C$  waveform ~

