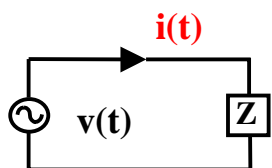


(23)

1





$$v(t) = 250 \cos(100t + 20^\circ) \text{ V}$$

$$i(t) = 10 \cos(100t + 40^\circ) \text{ A}$$

$$\begin{aligned} \therefore Z &= 25 (\cos -20^\circ + j \sin -20^\circ) \Omega \\ &= 23.5 - j8.55 \Omega \\ &= R - j(1/\omega C) \end{aligned}$$

$$\therefore R = 23.5 \Omega \quad (4)$$
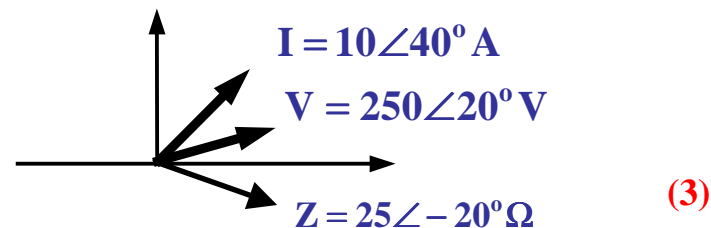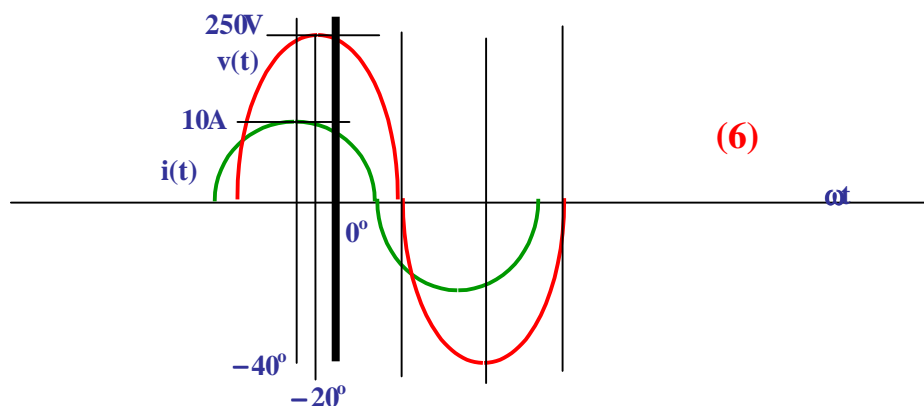
$$\therefore C = \frac{1}{8.55\omega} = \frac{1}{8.55(100)} = 1.17 \text{ mF} \quad (5)$$




$i(t)$ leads $v(t)$ (2)

Capacitive element (C in series with R)

$$\begin{aligned} \therefore Z &= \frac{V}{I} = \frac{250 \angle 20^\circ \text{ V}}{10 \angle 40^\circ \text{ A}} \\ &= 25 \angle -20^\circ \Omega \end{aligned} \quad (3)$$

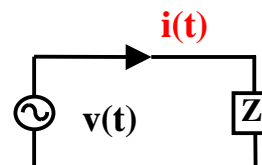1. In the following circuit, $v(t) = 250 \cos(100t + 20^\circ) \text{ V}$, $i(t) = 10 \cos(100t + 40^\circ) \text{ A}$.
- (a) Sketch $v(t)$ and $i(t)$ together. Show clearly the phase angles and amplitudes. Does $v(t)$ lead $i(t)$?
- (b) If Z is two elements in series, find the two elements and the values.
- (c) Sketch impedance Z and phasors V , I in a complex plane. (23)



(31)

2

$$\therefore P = VI \cos \theta = (250)\left(\frac{10}{2}\right) \cos(20) = 1174.62 \text{ W} \quad (3)$$

$$\therefore Q = VI \sin \theta = (250)\left(\frac{10}{2}\right) \sin(-20) = -427.53 \text{ VAR} \quad (3)$$

$$\therefore S = VI = \left(\frac{10}{2}\right)(250) = 1250 \text{ VA} \quad (3)$$

$$\therefore \text{PF} = \cos(-20^\circ) = 0.94 \text{ leading} \quad (3)$$

When L is connected (PF = 1),
 $S = P = 1174.62 \text{ VA}$, hence

$$\therefore I = \frac{S}{V} = \frac{1174.62}{250/\sqrt{2}} = 4.7\sqrt{2} \text{ Arms} \quad (5)$$

If V is 500V (2x of original V)

I is 2x of original I

but R and C are unchanged

hence P and Q ($\propto I^2$) are 4x of original P and Q

Hence new $L \propto V^2 / Q = \text{original } L = 0.73 \text{ H}$

(5)

P = real (or average) power dissipated by load Z

S = power supplied by source to load Z

Q = maximum reactive power stored in Z

(4)

Connect L in parallel to improve PF = 1

$$\therefore L = \frac{V^2}{\omega_0 Q} = \frac{(250/\sqrt{2})^2}{100(427.53)} = 0.73 \text{ H} \quad (5)$$

2. Using the same circuit in question (1),

(a) find the apparent power S, reactive power Q, average power P and power factor PF of load Z.


(b) What are the physical meanings of S, P, Q?

(c) A load B is now connected in parallel to Z to make the total power factor = 1. Find the load B and the value. Find also the current (in rms) supplied by v(t) when PF is 1.

(d) If v(t) is now changed to $500 \cos(100t + 20^\circ) \text{ V}$, find the new load B required.

(31)

(37)

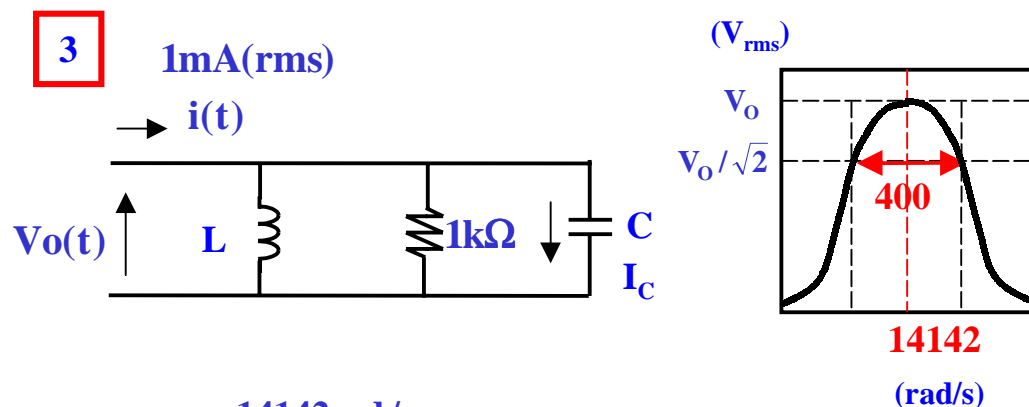

$$\therefore \omega_0 = 14142 \text{ rad/s}$$

$$f_0 = \frac{\omega_0}{2\pi} = 2250.8 \text{ Hz} \quad (3)$$

$$\therefore \text{BW} = 400 \text{ rad/s} \quad (2)$$

$$\therefore \omega_2 = \omega_0 + \frac{\text{BW}}{2} = 14142 + 200 = 14342 \text{ rad/s} \quad (2)$$

$$\therefore \omega_1 = \omega_0 - \frac{\text{BW}}{2} = 14142 - 200 = 13942 \text{ rad/s} \quad (2)$$

$$\therefore Q = \frac{\omega_0}{\text{BW}} = \frac{14142}{400} = 35.355 \quad (3)$$

$$Q > 10, \text{ good resonant circuit} \quad (2)$$

$$\text{Vo is max at resonance, hence circuit is parallel LCR} \quad (2)$$

$$\therefore L = \frac{R}{\omega_0 Q} = \frac{1\text{k}}{14142(35.355)} = 2\text{mH} \quad (4)$$


$$\therefore C = \frac{Q}{\omega_0 R} = \frac{35.355}{14142(1\text{k})} = 2.5\mu\text{F} \quad (3)$$

$$\therefore \max V_0 = iR = 1\text{m}(1\text{k}) = 1\text{Vrms} \quad (3)$$

$$\therefore \max i_C = \frac{\max V_0}{1/j\omega_0 C} = IR(j\omega_0 C) = jIQ$$

$$\therefore \max i_C(t) = 35.355(\sqrt{2})\cos(14142t + 90^\circ)\text{mA} \quad (6)$$

If R is changed to 2k

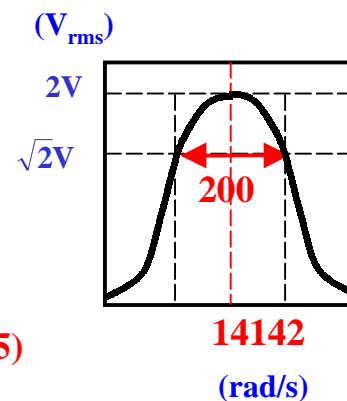

(5)

3. A LCR circuit has the following resonance curve (magnitude of Vo(t) versus frequency ω).


(a) Find the resonant frequency (in rad/s and in Hz), bandwidth (BW), upper and lower cut-off frequencies (in rad/s), and the Q-factor of the LCR circuit. Is the circuit a good resonant circuit and why?

(b) If R = 1kΩ, find the values of C and L. Find also the maximum Vo (in rms) and maximum current flowing in C (i_C(t)).

(c) If R is now changed to 2kΩ (C and L are unchanged), sketch the new resonance curve. Show clearly all intercepts. (37)


(29)

4

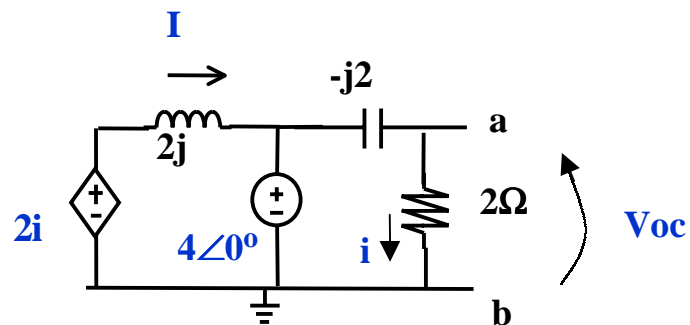


$$i = \frac{4}{2-2j} = \frac{2}{1-j} = \frac{2}{\sqrt{2}\angle-45^\circ} = \sqrt{2}\angle 45^\circ \text{ A}$$
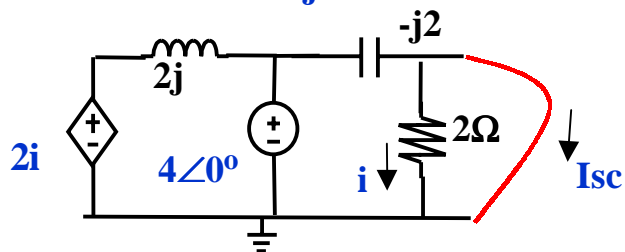
$$\therefore V_{oc} = 2i = \frac{4}{1-j} = 2\sqrt{2}\angle 45^\circ \text{ V} \quad (6)$$



$$I_{sc} = \frac{4}{-2j} = 2j = 2\angle 90^\circ \text{ A} \quad (5)$$

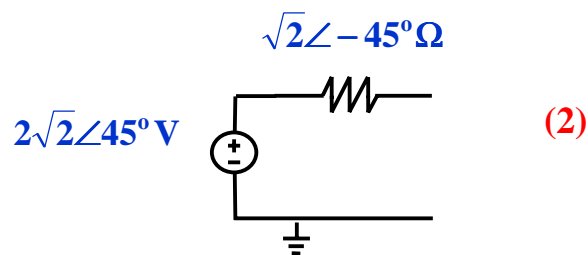
$$\therefore Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{2\sqrt{2}\angle 45^\circ}{2\angle 90^\circ} = 1-j = \sqrt{2}\angle -45^\circ \Omega \quad (3)$$



use KVL:

$$2i = I(2j) + i(2 - 2j)$$

$$I = i \quad (5)$$

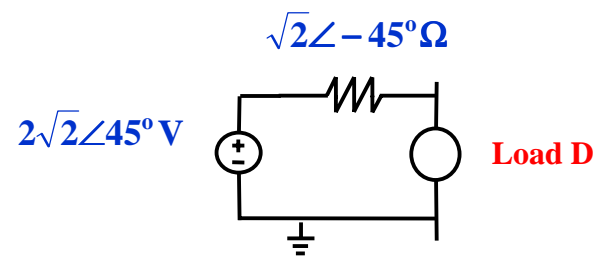

$$\text{load } D = \sqrt{2}\angle 45^\circ \Omega \quad (3)$$

$$I = \frac{V_{oc}}{Z} = \frac{4}{1-j} = \frac{4(1+j)}{1-j+j} = 2 \quad (5)$$

$$\therefore \text{load } D = 1+3j$$

4. In the following circuit,

(a) find the complex open circuit voltage and the short circuit current at terminals ab. Hence sketch the Thevenin equivalent at ab.

(b) Find I in terms of i.


(c) A load D is now connected across ab. Find load D (i) if it has maximum power dissipation, (ii) if current in load D is $2\angle 0^\circ$ A. (29)

(40)

5


$$\therefore A \sim \infty \quad \therefore V_i = \frac{V_o}{A} \sim 0$$
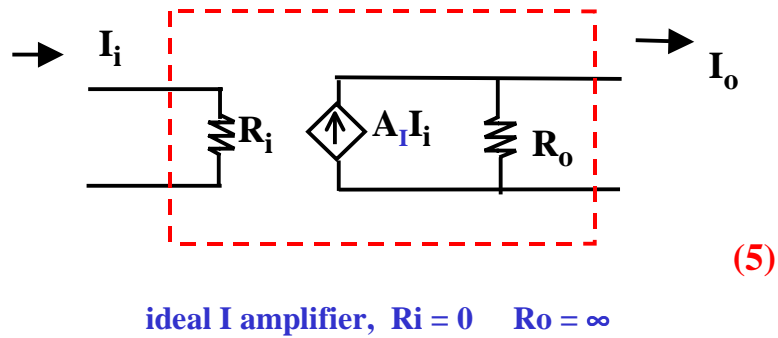
$$\therefore R_i \sim \infty \quad \therefore I_i = \frac{V_i}{R_i} \sim 0$$



(5)

(5)

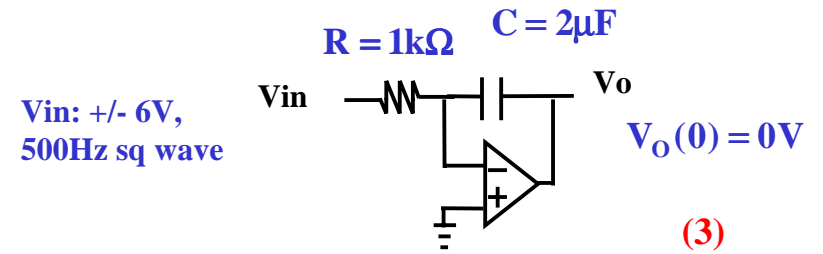



(3)

$$\therefore \frac{V_{in} - 0}{R} = -C \frac{dV_o}{dt}$$

$$\therefore \frac{dV_o}{dt} = -\frac{V_{in}}{RC} \quad (3)$$

$$= \frac{-6V}{2ms} = -3V/ms \quad (2)$$

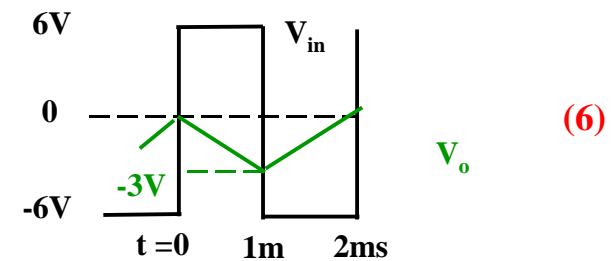

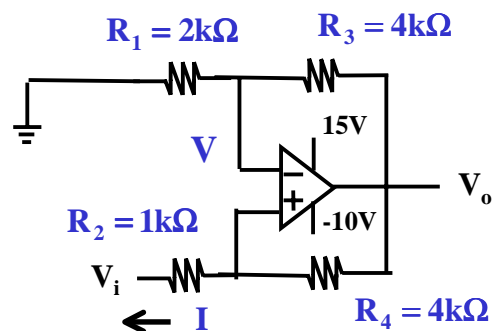

$$\therefore V_- = V_+ = V$$

$$\therefore V_- = V_o \frac{2k}{2k + 4k} = \frac{V_o}{3}$$

$$\therefore \frac{V_i - V}{1k} = \frac{V - V_o}{4k}$$

$$\therefore 4V_i - 4V = V - V_o \quad \therefore 4V_i = \frac{2}{3}V_o$$

$$\therefore A_v = \frac{V_o}{V_i} = 6 \quad (8)$$

$$\text{If } V_i = 3V, \quad V_o = 15V \quad (3)$$

$$\text{If } V_i = -1V, \quad V_o = -6V \quad (2)$$

$$\therefore I = \frac{V_o - V_i}{5k} = \frac{-6 - (-1)}{5k} = -1mA \quad (3)$$

5. (a) An ideal op amp assumes $V_i = 0$ and $I_i = 0$ (voltage across and current flow into input terminals are zero). Explain briefly the reasons.

(b) Sketch the equivalent circuit of an ideal current amplifier. What are the values of the input and output resistances?

(c) Sketch the circuit of an ideal op amp RC integrator. If $C = 2\mu F$, $R = 1k\Omega$, $V_{in}(t)$ is a $\pm 6V$ 500Hz square wave, sketch $V_{out}(t)$ and $V_{in}(t)$ together. Show clearly all voltage and time. Given at $t = 0$, $V_{in} = 6V$, $V_{out} = 0V$.

(d) In the following circuit, assume ideal op amp, (i) find V_o if $V_i = 3V$, (ii) find I if $V_i = -1V$. (40)