



(300)

(17)

1

Find  $V_s(t)$  in terms of  $C$ ,  $R$ , and  $V_o(t)$ .If  $C = 1\mu\text{F}$  and  $R = 2\text{k}\Omega$ , find and plot  $V_s(t)$ . Assume the op amp is ideal.

(17)

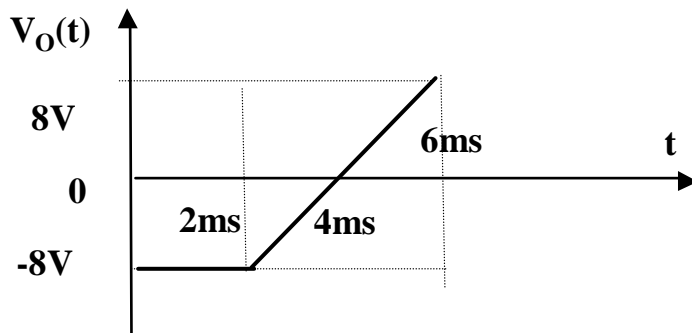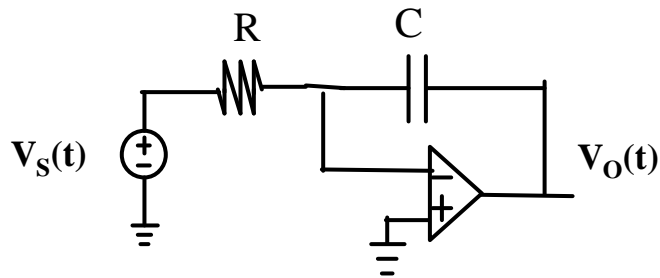


$$\text{apply KCL} \Rightarrow \frac{V_s}{R} \cong -C \frac{dV_o}{dt} \quad (6)$$

$$CR = 0.5\text{mF} * 2\text{k}\Omega = 1\text{ms}$$

$$\therefore V_s \cong -CR \frac{dV_o}{dt} = -2\text{ms} * \frac{8\text{V} - -8\text{V}}{4\text{ms}} = -8\text{V}$$


(7)

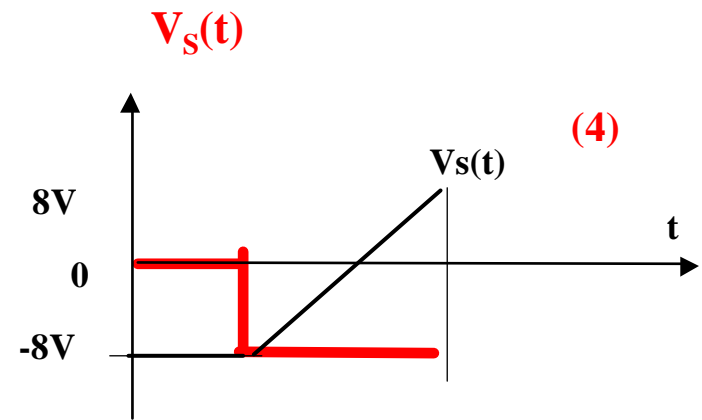

(17)


2

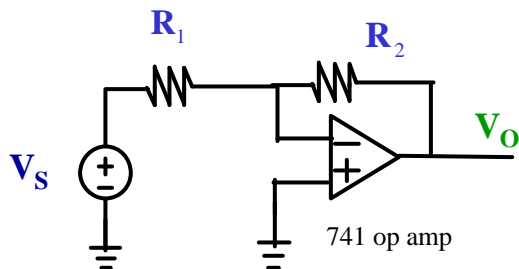- a. In the circuit, replace the 741 op amp by the op amp circuit model and redraw the circuit. Given that  $R_i = 2\text{M}\Omega$ ,  $R_o = 75\Omega$ ,  $A = 200\text{k}$ . (8)



2

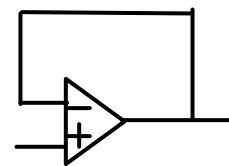- b. Draw the circuit of an op amp **voltage follower** and name two advantages of the circuit. (9)




**voltage  
follower**

(4)

1. Very high input resistance
2. Very low output resistance

(5)

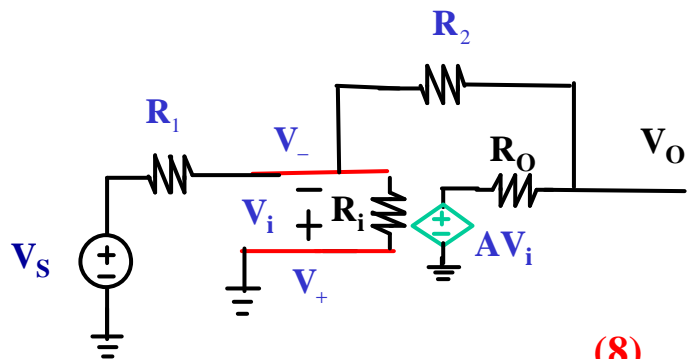


(8)

(13)

3

Given that  $V_s(t) = V_m \cos \omega t$  and  $V_O / V_1 = 21$ , find  $V_1 / V_s$  in terms of  $R$ ,  $C$  and  $j\omega$ . If  $C = 1\mu\text{F}$  and  $R = 1\text{k}\Omega$ , find the complex transfer function  $G$  ( $= V_O / V_s$ ). Is the op amp circuit a low pass filter? Assume the op amp is ideal.

(13)

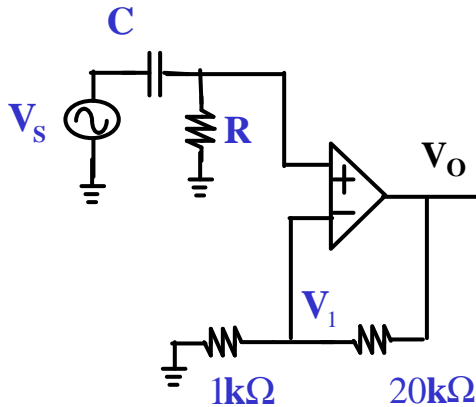

$$V_1 = V_s * \frac{R}{R + \frac{1}{j\omega C}} = V_s * \frac{1}{1 + \frac{1}{j\omega CR}}$$

$$V_O = 21V_1 = 21 * V_s \frac{1}{1 + \frac{1}{j\omega CR}} = \frac{21V_s}{1 + \frac{1}{j\omega(1\text{mF} * 1\text{k}\Omega)}}$$

$$G = \frac{V_O}{V_s} = \frac{21}{1 + \frac{1}{j\omega * 1\text{ms}}}$$

(10)

Circuit is a high pass filter

(3)

(21)

4

In an ideal op amp filter circuit, the complex transfer function  $G$  ( $= V_o / V_s$ ) is given as.  $\frac{-11}{1 + j\omega CR}$


$C = 1 \times 10^{-8} \text{ F}$  and  $R = 1 \text{ k}\Omega$ .

(a) Show that the cut off frequency  $\omega_o$  is  $100 \text{ k rad/s}$ .

(b) Plot the magnitude of  $G$  ( $|G|$ ) versus  $\omega$ . Show clearly the value of  $|G|$  when  $\omega = 0$  and  $\omega = \omega_o$  in your plot.

(c) If  $V_s(t) = 2 \cos 100 \text{ kt}$  V find  $V_o(t)$ .

(b)

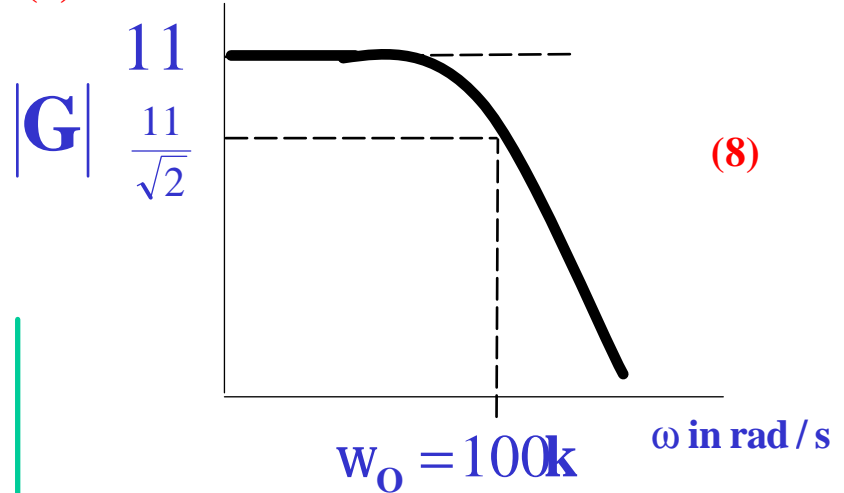

(8)

(a)

$$\omega_o = \frac{1}{CR} = \frac{1}{10 \text{ nF} * 1 \text{ k}\Omega} = 100 \text{ krad/s}$$

(5)

(c)

$$V_o = 2 \angle 0^\circ * \frac{-11}{1 + j} = \frac{-11}{\sqrt{2} \angle 45^\circ}$$

(8)



$$V_o(t) = -\frac{22}{\sqrt{2}} \cos(100 \text{ kt} - 45^\circ) \text{ V}$$

(22)


5

In the ideal op amp circuit, the diode has the forward, reverse and breakdown characteristics as shown.

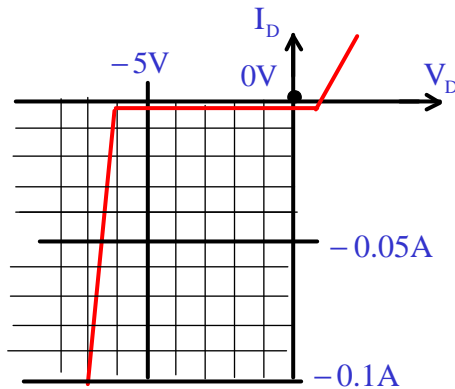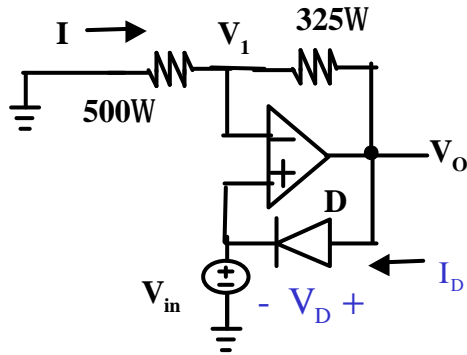- (a) Draw the circuit model of the diode at breakdown.  
 (b) If  $I = 20\text{mA}$ , show that  $V_o = -16.5\text{V}$ . Hence find  $I_D$ .  
 (22)



(a)

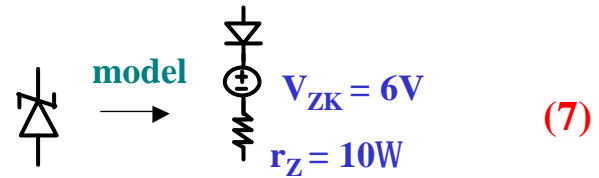(b) When  $I = 10\text{mA}$ 

$$V_o = -I * (500\Omega + 325\Omega) = -16.5\text{V} \quad (3)$$

$$\therefore V_{in} = V_1 = -10\text{V} \quad (4)$$

Dis breakdown (2)

$$I_D = -\frac{-10\text{V} - (-16.5\text{V}) - 6\text{V}}{10\Omega} = -0.05\text{A} \quad (6)$$


(13)

6

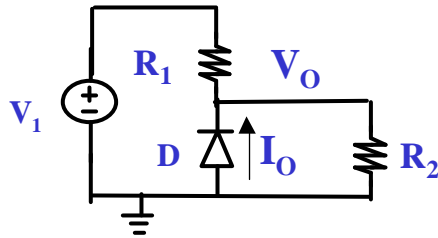(a) In the diode circuit, if  $V_1 = -7V$ ,  $R_1 = 18k\Omega$ ,  $R_2 = 2k\Omega$ ,  
find  $I_O$ .

Given that the diode equation is

$$I = (1pA) \exp [(VD/25mV) - 1]. \quad (13)$$



$$V_O = V_1 * \frac{R_2}{R_1 + R_2} = -7V * \frac{2k\Omega}{18k\Omega + 2k\Omega} = -0.7V$$


diode is ON (5)

$$\begin{aligned} \therefore I_O &= I_s \left( e^{\frac{0.7V}{25mV}} - 1 \right) \\ &= 1 \times 10^{-12} A \left( e^{\frac{700m}{25m}} - 1 \right) \cong 1.45A \end{aligned} \quad (8)$$

(15)

6

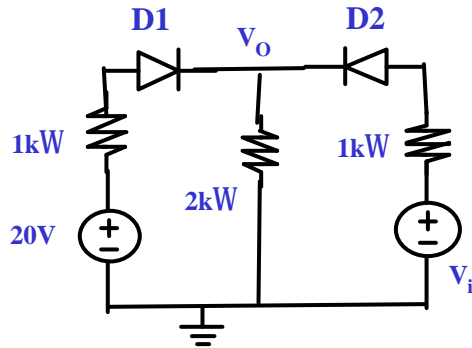(b) In the diode circuit, find  $V_o$  when  $V_i = 18V$ . Assume the diodes are ideal. (15)



$V_i = 18V$ , D1 and D2 ON,

(4)

$$\therefore \frac{V_i - V_o}{1k\Omega} + \frac{20 - V_o}{1k\Omega} = \frac{V_o}{2k\Omega}$$


$$\therefore V_i - V_o + 20 - V_o = 0.5V_o$$

$$\therefore V_o = \frac{V_i + 20}{2.5} = \frac{18V + 20}{2.5} = 15.2V \quad (11)$$

(10)


7

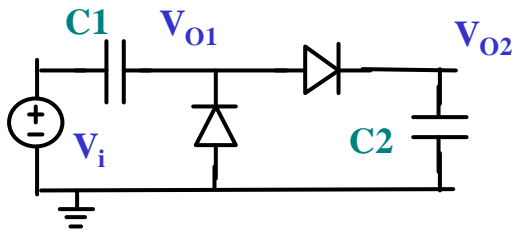(a) Given that  $V_i(t) = 6 \cos 2\pi 1kt$  V, plot and label clearly  $V_{O1}$  and  $V_{O2}$ . Assume the diodes are ideal. (10)



$V_{O1}$


12V  
6V  
0

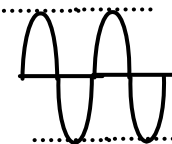

(5)

$V_{O2}$

12V  
6V  
0

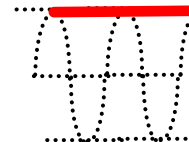





(5)



(12)

7

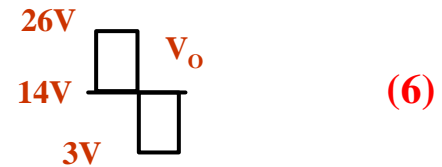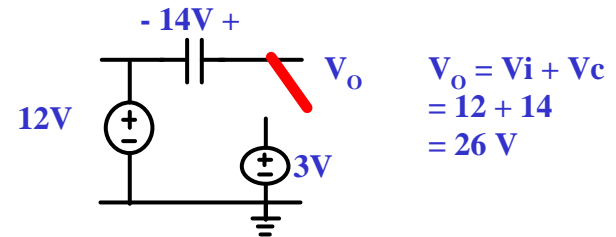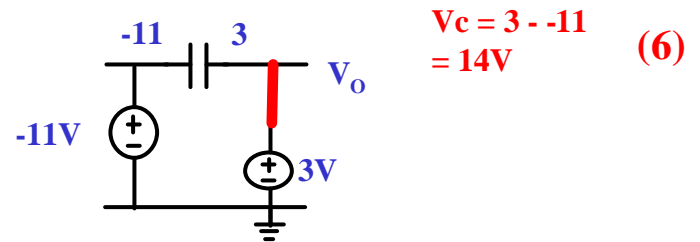
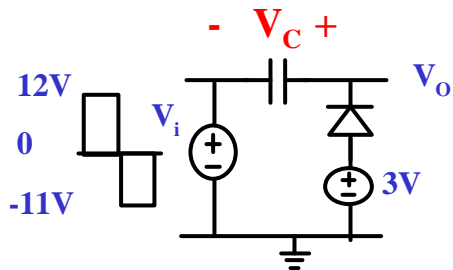
(b) In the diode circuit, find  $V_c$  and sketch  $V_o(t)$ . Label clearly  $V_o(t)$ . Assume the diode is ideal. (12)



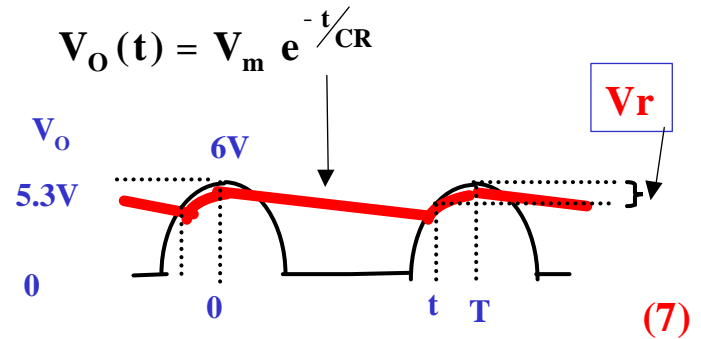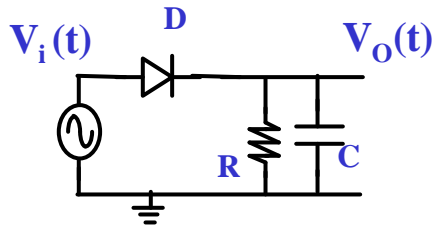(14)

8

. If  $V_i(t) = 6 \cos 2\pi 1kt$  V, sketch the waveform of  $V_i(t)$  and  $V_o(t)$ . Find also the ripple voltage  $V_r$  of  $V_o(t)$ . Given that  $R = 30k\Omega$ ,  $C = 1\mu\text{F}$  and diode is an offset diode where  $V_F = 0.7\text{V}$ . Given also that  $V_r \cong V_m T / CR$ . (14)



$$V_r \cong V_m(T/CR)$$


$$= (6\text{V} - 0.7\text{V})(1\text{ms}/30\text{ms}) \cong 0.18\text{V}$$

(7)

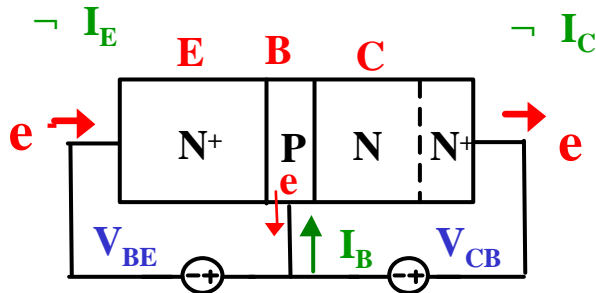(16)

9

Draw the cross sectional structure of a NPN BJT transistor operated in the amplifier mode, describe the movement of electrons, and explain briefly why  $I_C \cong \alpha I_E$ . If  $I_C \cong \beta I_B$ , find  $\alpha$  in terms of  $\beta$ . (16)



1. EB Junction is a forward bias (on) diode and BC is reverse bias (off) diode

2. E is very heavily doped ( $N^+$  for NPN). E has many electrons,

3. B is very thin. So most electrons injected from E (to B) are attracted to C and

$$I_C \cong \alpha I_E \quad (10)$$

$$I_E \cong \frac{I_C}{\alpha} = I_B + I_C = \frac{I_C}{\beta} + I_C$$



$$\text{hence } \frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\alpha = \frac{\beta}{\beta + 1} \quad (6)$$

10

Given the BJT circuit below and the  $I_C$ - $V_{CE}$  curve of the BJT. (a) Draw the load line  $V_{CE} = V_{CC} - I_C R_C$  and locate the Q point on the load line. (b) If  $v_i(t) = 0.02 \sin \omega t$  V, estimate the voltage gain from the I-V curve and sketch  $V_O(t)$ .  
(22)

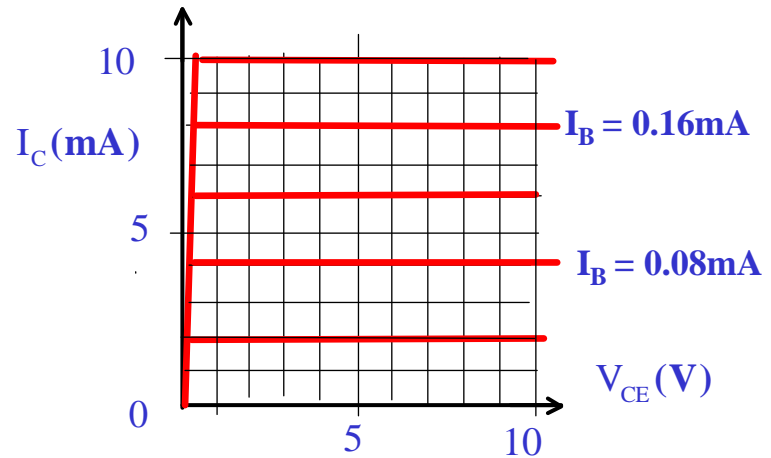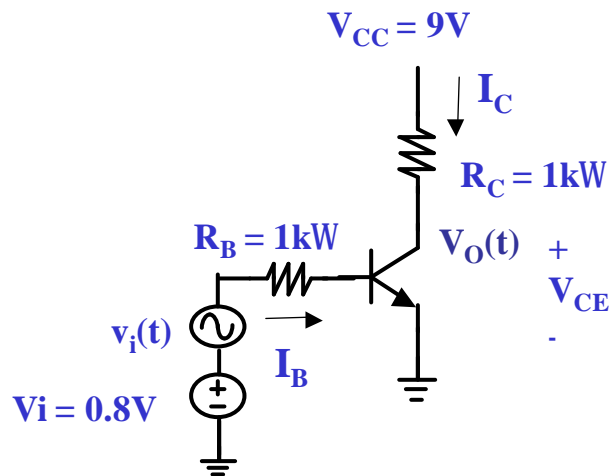
For the BJT, given  $\beta = 50$ ,  $V_{BE(ON)} = 0.7$  V,  $V_{CESAT} = 0.2$  V,  $r_{\pi} = 0 \Omega$



(22)

Draw load line, Q point,

(a)

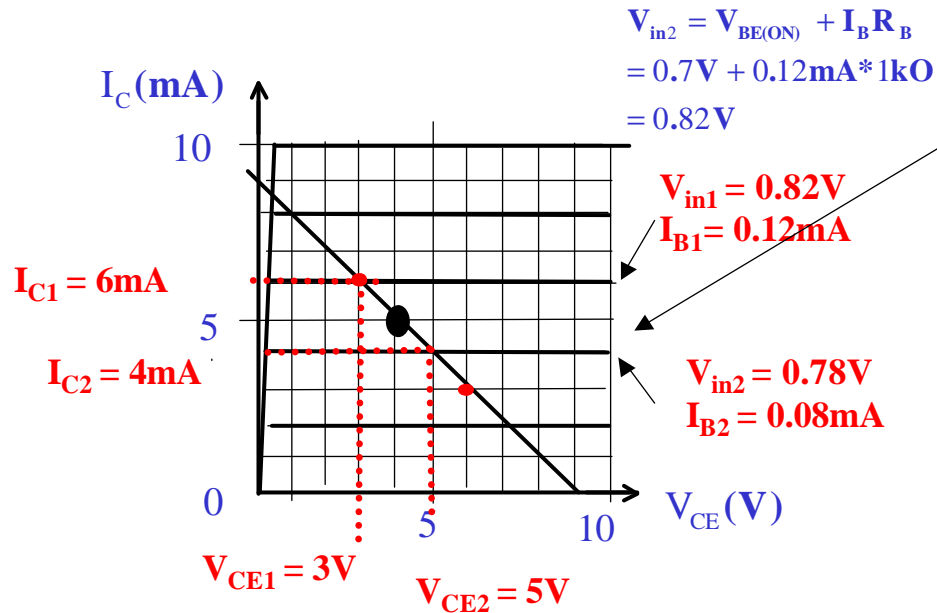


(11)

$$I_B = \frac{V_i - V_{BE(ON)}}{R_B} = \frac{0.8V - 0.7V}{1k\Omega} = 0.1mA$$

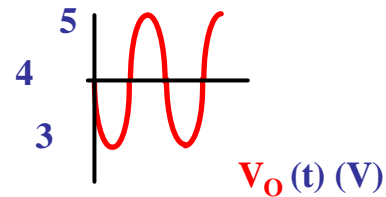(b) and find voltage gain

$$\text{voltage gain } A_v = \frac{dV_{CE}}{dV_{in}} = \frac{V_{CE2} - V_{CE1}}{V_{in2} - V_{in1}}$$

$$\cong \frac{5V - 3V}{0.78V - 0.82V} = -50$$





(11)

(16)

11

Draw the small signal (AC) equivalent circuit of the BJT amplifier and find the voltage gain  $A_V (= v_{out} / v_{in})$ .

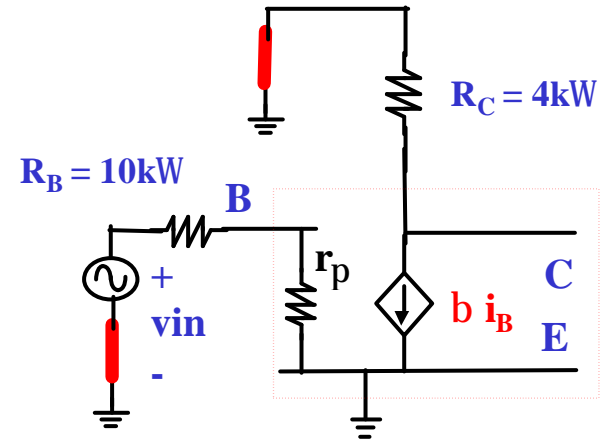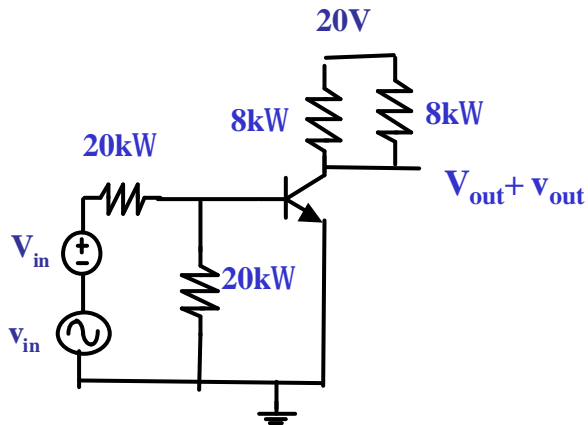Given  $\beta = 100$ , and  $V_{CESAT} = 0.2V$ ,  $V_{BE(ON)} = 0.7V$ ,  $r_{\pi} = 0\Omega$ . (16)



(8)


$$\begin{aligned} \therefore A_V &= \frac{v_{OUT}}{v_{in}} = \frac{-\beta i_B R_C}{i_B (R_B + r_p)} \\ &= \frac{-\beta R_C}{R_B + r_p} = \frac{-(100)(4k\Omega)}{10k\Omega + 0\Omega} = -40 \end{aligned}$$

(8)

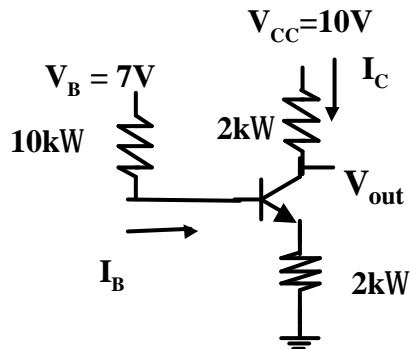(17)

12

Given that the BJT is in saturation. Write down the equation relating  $I_B$  and  $V_B$ , and the equation relating  $I_B$  and  $V_{CC}$ , and show that the forced beta  $\beta^*$  ( $= I_C / I_B$ ) is about 18.8. Given that  $V_{CESAT} = 0.2V$ ,  $V_{BE(ON)} = 0.7V$ . (17)




$$\therefore I_B = \frac{V_B - V_{BE}}{R_B + (1 + \beta^*)R_E} = \frac{V_{CC} - V_{CESAT}}{\beta^* R_C + (1 + \beta^*)R_E}$$

$$\therefore I_B = \frac{7 - 0.7}{10k + (1 + \beta^*)2k} = \frac{10 - 0.2}{2k(1 + 2\beta^*)} \quad (10)$$

$$\therefore 6.3(1 + 2\beta^*) = 9.8(1 + \beta^*)$$

$$\therefore 12.6\beta^* + 6.3 = 9.8\beta^* + 9.8$$
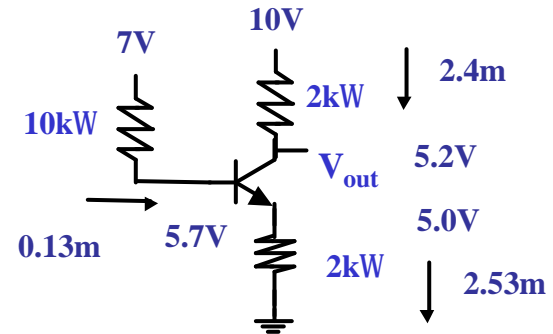
$$\therefore \beta^* = \frac{58.8 - 6.3}{12.6 - 9.8} \approx 18.75 \quad (7)$$



(31)


13

(a) If  $V_i = 8V$ , find  $I_B$ ,  $I_C$ ,  $V_{out}$  and the mode of BJT.

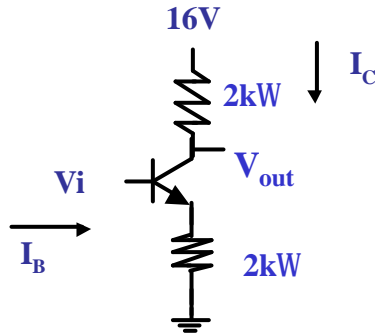(b) If  $V_i = 10V$ , find  $V_{out}$

Show clearly your reasons.

Given  $\beta = 100$ , and  $V_{CESAT} = 0.2V$ ,  $V_{BE(ON)} = 0.7V$ .  
(31)



BJT is not OFF since  $V_{BE}$  can be  $0.7V$

$$\therefore I_B = \frac{8V - 0.7V}{(100 + 1)(2k\Omega)} \cong 36\mu A \quad (6)$$

$$\therefore I_C = \beta I_B \cong 100 * 36\mu A = 3.6mA \quad (3)$$

$$I_C < \max I_C = \sim 15.8V / 4k\Omega \sim 4mA \quad (3)$$

Hence BJT is in amplifier mode (2)

$$\therefore V_{out} = 16V - I_C(2k\Omega) = 16V - 7.2V = 8.8V \quad (4)$$

$$V_i = 10V, I_B \sim 46\mu A \quad (6)$$

hence  $I_C > \max I_C$

Hence BJT is in saturation mode (2)

$$\therefore V_{out} = 9.3V + 0.2V = 9.5V \quad (5)$$



(15)


14

(a) Name two advantages of MOSFET. (b) Draw the cross sectional diagram for an enhancement NMOSFET and describe very briefly the structure.

(15)

small size (scaled down easily)  
and low power consumption.

(5)

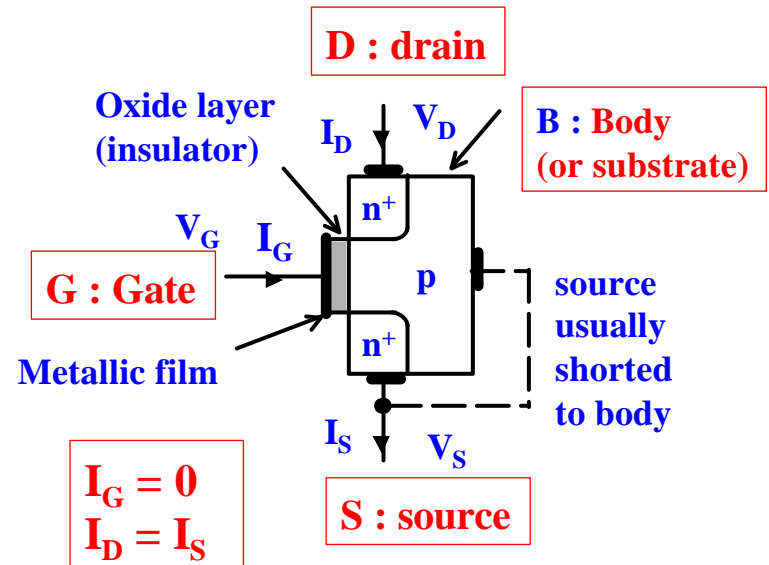

An NMOSFET consists of a **metal gate** insulated from a **p-type semiconductor** substrate (or body) by an insulating layer of **silicon dioxide**. On either side of the gate there are **n type** regions forming the **drain and source**.

(10)

(14)


15

(a) Find the mode of the MOSFET. Find also  $I_{DS}$ . Show clearly the reasons for your answers. (14)

Given that  $V_T = 1V$ ,  $K = 0.5 \text{ mA/V}^2$ .

At triode region,  $V_{GS} \geq V_T$ ,  $V_{DS} < V_{GS} - V_T$ ,  $I_{DS} = 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}]$

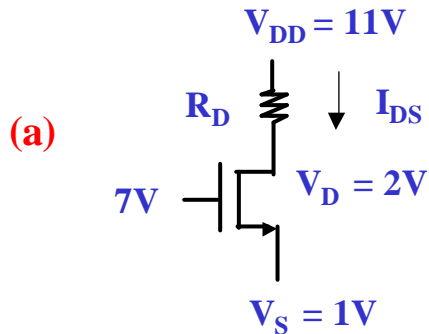At saturation region,  $V_{GS} \geq V_T$ ,  $V_{DS} \geq V_{GS} - V_T$ ,  $I_{DS} = K[(V_{GS} - V_T)^2]$



$$V_{GS} = V_G - V_S = 7V - 1V = 6V$$

$$V_{GS} > V_T$$

$$K = 0.5 \text{ mA/V}^2$$

$$V_T = 1V$$

$$V_{DS} = V_D - V_S = 2 - 1 = 1V$$

$$V_{GS} - V_T > V_{DS} \quad (6)$$

NMOSFET is in triode mode (2)

$$\therefore I_{DS} = 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}]$$

$$= 1\text{m}[(6V - 1V)1V - \frac{1V^2}{2}]$$

$$= 1\text{m}(\frac{9}{2}) = 4.5\text{mA} \quad (6)$$

(15)

15. (b) Show that  $V_O = 0.5 V_i$  . (15)


Given that

M1 and M2 are in saturation .

$V_T = 1V$  ,  $K = 0.5 \text{ mA/V}^2$  .

At triode region,  $V_{GS} \geq V_T$  ,  $V_{DS} < V_{GS} - V_T$  ,  $I_{DS} = 2K[(V_{GS} - V_T)V_{DS} - V_{DS}^2/2]$  .

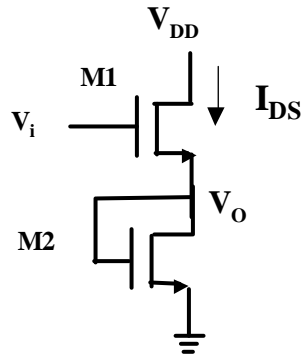At saturation region  $V_{GS} \geq V_T$  ,  $V_{DS} > V_{GS} - V_T$  ,  $I_{DS} = K[(V_{GS} - V_T)^2]$  .



$$\therefore I_{DS} = K (V_{GS1} - V_T)^2 = K (V_{GS2} - V_T)^2 \quad (6)$$

$$\therefore (V_{GS1} - V_T) = (V_{GS2} - V_T)$$

$$\therefore V_{GS1} = V_{GS2}$$

$$\therefore V_i - V_O = V_O$$

$$\therefore V_O = \frac{V_i}{2} \quad (9)$$