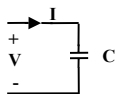


(15)


1

$$\therefore \omega = \frac{2\pi}{T} = \frac{2\pi}{\pi} = 2 \text{ rad/s}$$

$$\therefore V(t) = V_m \sin \omega t = 10 \sin 2t \text{ V}$$



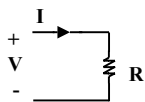
$$\therefore I(t) = C \frac{dV(t)}{dt} = 1 \text{ mF} \frac{d}{dt} 10 \sin 2t = 20 \cos 2t \text{ mA}$$



$$\therefore P = \frac{V_{rms}^2}{R} = \left(\frac{10}{\sqrt{2}}\right)^2 \frac{1}{10\Omega} = 5 \text{ W}$$


$$\therefore E = Pt = 5 \text{ W}(10 \text{ s}) = 50 \text{ J}$$

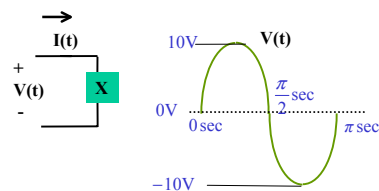1. In the circuit, $V(t)$ is given as shown.
 (a) If $X = 1 \text{ mF}$, find $I(t)$.
 (b) If $X = 10 \Omega$, find the total energy dissipated by X in 10 sec.
 Given $d(\sin x)/dx = \cos x$, $d(\cos x)/dx = -\sin x$. (15)



(24)

2

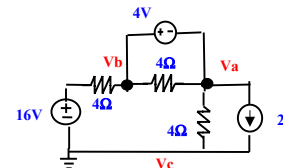

$$V_b = V_a + 4 \text{ V}$$

$$V_c = 0 \text{ V}$$

$$\text{KCL: } \frac{16 - V_b}{4} = \frac{16 - V_a - 4}{4} = \frac{V_a}{4} + 2$$

$$\therefore 16 - V_a - 4 = V_a + 8$$

$$\therefore V_a = 2 \text{ V}$$

$$\therefore V_b = 6 \text{ V}$$

$$V_{bc} = V_b - V_c = 6 - 0 \text{ V} = 6 \text{ V}$$

$$\text{KCL:}$$


$$\frac{16 - V_b}{4} = i + \frac{4 \text{ V}}{4\Omega} = \frac{16 - 6}{4}$$

$$\therefore i + 1 = 2.5$$


$$\therefore i = 1.5 \text{ A}$$

$$P = iv = 4 \text{ V}(1.5 \text{ A}) = 6 \text{ W}$$

Power is absorbed by 4V source


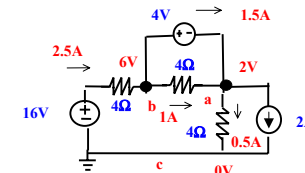


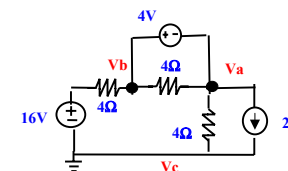2. In the circuit, find V_a , V_b and V_{bc} . Find also the power delivered or absorbed by the 4V supply. (24)




(32)

3

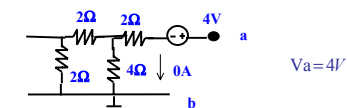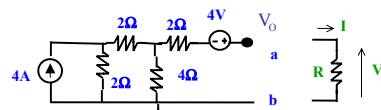


$$V_a = 4 \text{ V}$$

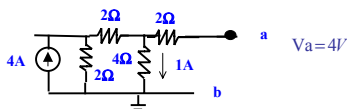


$$V_a = 4 \text{ V}$$
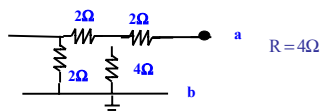
$$\therefore V_o = V_a + V_b = 8 \text{ V}$$



$$R = 4\Omega$$

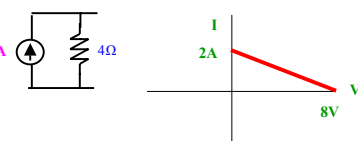


Norton equivalent

Maximum power delivered when $R = 4\Omega$




$$\therefore P = I^2 R = (1 \text{ A})^2 4\Omega = 4 \text{ W}$$

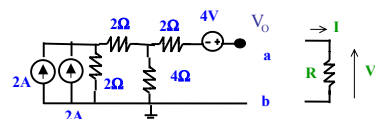3. (a) Use **superposition method** to show that $V_o = 8 \text{ V}$.
 (b) Hence find the **Norton equivalent** of the network at terminals ab.
 (c) If a load R is connected to ab, plot I versus V for all values of R (0 to ∞ ohm). Find also the maximum power that can be dissipated by R (32).





(16)

4

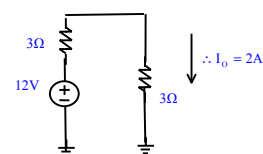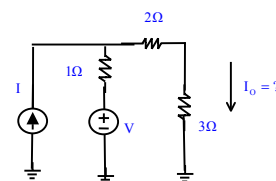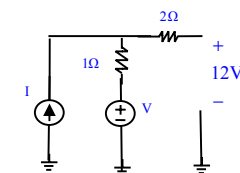


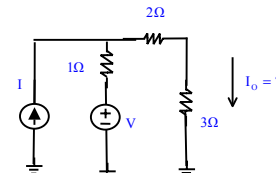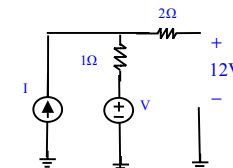4. In the network, find current I_o . Voltage V and current I are not known. Hint: can use Thevenin's Theorem. (16)



(28)


5

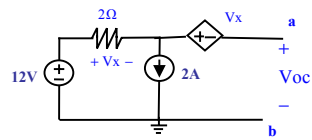

$$\therefore V_x = (2A)2\Omega = 4V$$

KVL:
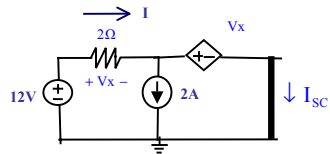
$$V_{oc} = 12 - V_x - V_x \\ = 12 - 2V_x = 4V$$



$$\text{KVL: } 12 - V_x = V_x$$



$$\therefore V_x = 6V$$

$$\therefore I = \frac{6V}{2\Omega} = 3A$$


$$\therefore I_{sc} = 1A$$

Thevenin resistance
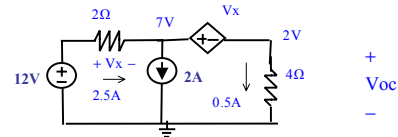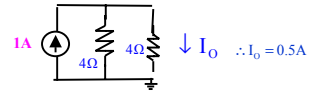
$$R_{th} = \frac{V_{oc}}{I_{sc}} \\ = \frac{4V}{1A} = 4\Omega$$



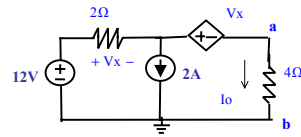5. In the circuit, find I_o using **Norton's Theorem**. The **voltage controlled voltage source** is in volt and equal to V_x . Hint: find V_{oc} , I_{sc} at terminals ab and $R_N = V_{oc}/I_{sc}$. (28)







(24)

6

6. In the circuit, the switch has been closed for a long time. At $t = 0$ sec, the switch is opened. Find $V(t)$ for $t \geq 0$. Find also the maximum energy stored in the inductor.

Given that $V_L = L (dI_L / dt)$, $i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$ and $v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$ (24)

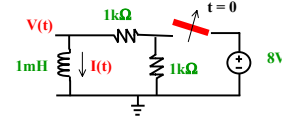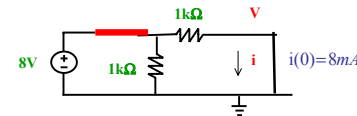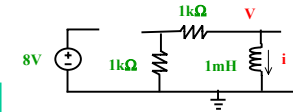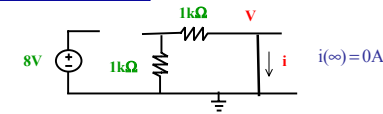 $t < 0$, S is closed $t \geq 0$, S is opened

$$\tau = \frac{L}{R} = \frac{1mH}{2k\Omega} = 0.5\mu s$$

$$\therefore i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau} \\ = 0 + [8m - 0] e^{-t/0.5\mu s} \\ = 8e^{-t/0.5\mu s} mA$$

$$\therefore v(t) = L \frac{di(t)}{dt} = 1m \frac{d}{dt} [8me^{-t/0.5\mu s}] \\ = 1m(8m) \left(\frac{-1}{0.5\mu} \right) e^{-t/0.5\mu s} A \\ = -16e^{-t/0.5\mu s} V$$

Maximum energy stored in L





$$= \frac{1}{2} Li^2 = \frac{1}{2} (1mH)(8mA)^2 = 32 \times 10^{-9} J$$

(22)

7


7. At $t < 0$, the switch is at terminal a and the circuit is steady. At $t = 0$ sec, the switch is switched to terminal b. Find $V(t)$ for $t \geq 0$. Plot $V(t)$ also and show clearly the voltage and time. Find also the maximum energy stored in the capacitor.

Given that $i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$, $v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$ (22)

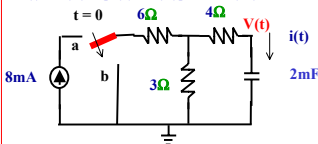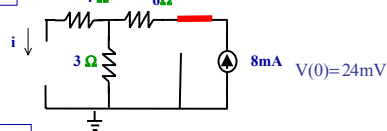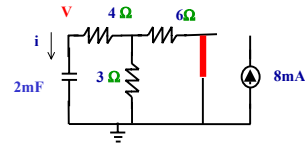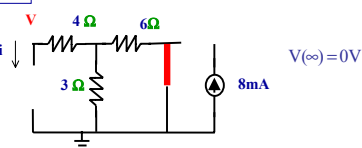 $t < 0$  $t \geq 0$ 

$$\tau = CR = 2mF * 6\Omega = 12ms$$
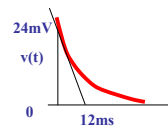
$$\therefore V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau} \\ = 0 + [24m - 0] e^{-t/12ms} \\ = 24e^{-t/12ms} mV$$



Maximum energy stored in C

$$= \frac{1}{2} CV^2 = \frac{1}{2} (2mH)(24mV)^2 = 576 \times 10^{-9} J$$