

(321)

1

(a) Name two advantages of MOSFET. (b) Draw the cross sectional diagram for an enhancement NMOSFET and describe very briefly the structure.

(16)


(a)

small size (scaled down easily)
and low power consumption.

(4)

(16)

(b)

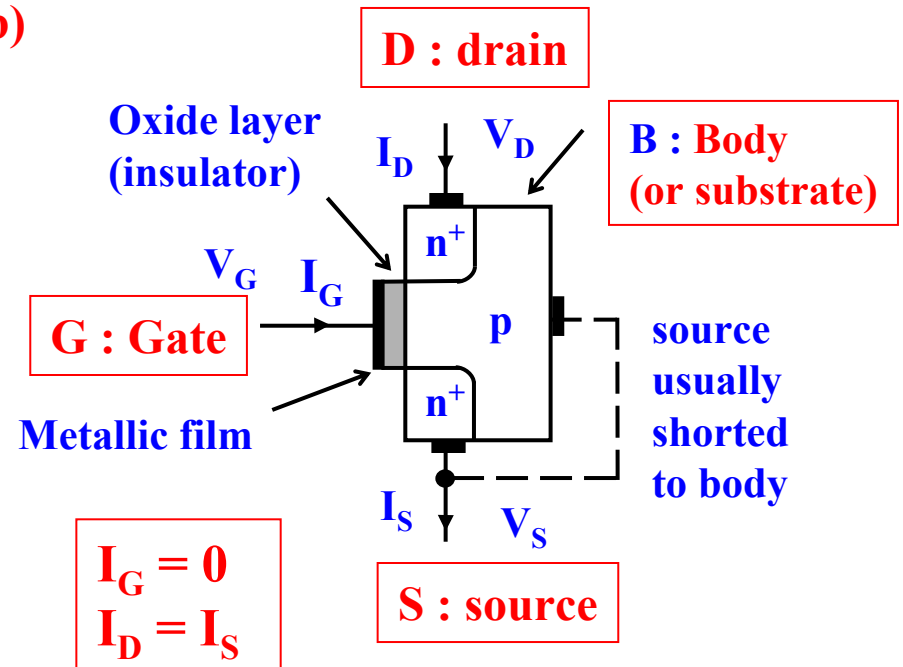

An NMOSFET consists of a **metal gate** insulated from a **p-type semiconductor** substrate (or body) by an insulating layer of **silicon dioxide**. On either side of the gate there are **n type** regions forming the **drain and source**.


(12)

(12)

(c) Draw the cross sectional structure and draw the n-channel conditions when the NMOS is in Triode ($V_{DS} \ll V_{GS} - V_T$) and Saturation ($V_{DS} > V_{GS} - V_T$) mode. Sketch also the I_D - V_{DS} curve in each mode. (12)

(c)


Triode (ohmic)

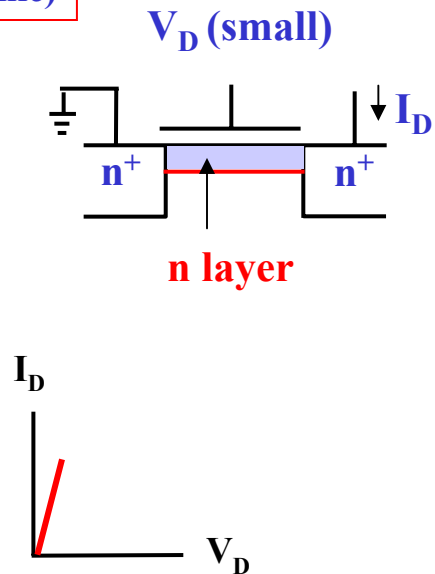

(5)

saturation

electrons

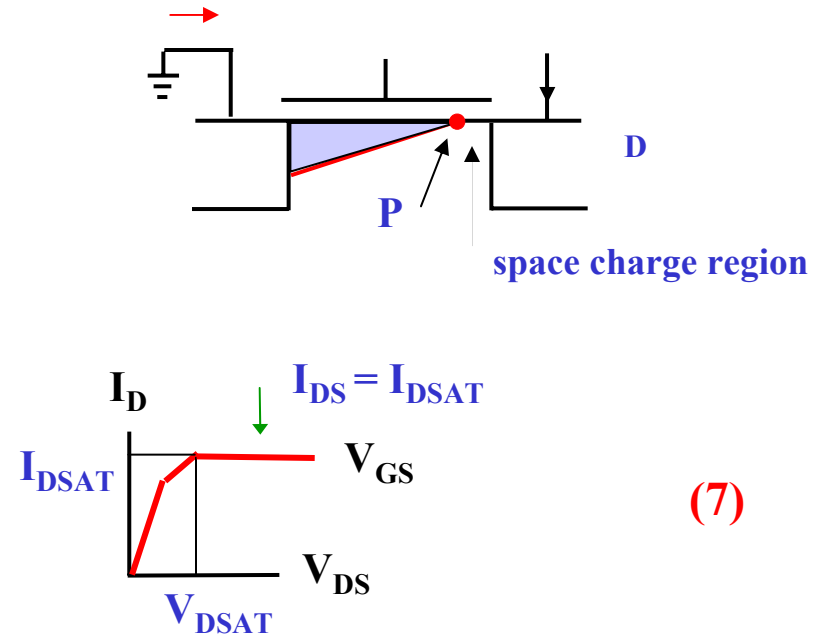

(7)


(22)

2

Find V_o . (20)

Show clearly your reasons.

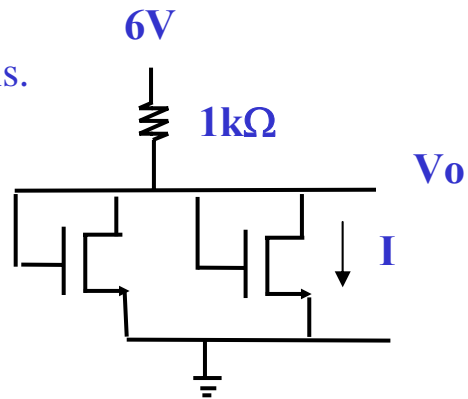Given the NMOS are all identical, $V_T = 1V$
 $K = 0.25mA/V^2$.



Assume 2 NMOS are in saturation (2)

At triode region, $V_{GS} \geq V_T$, $V_{DS} < V_{GS} - V_T$, $I_D = 2K(V_{GS} - V_T)V_{DS} - KV_{DS}^2$

At saturation region, $V_{GS} \geq V_T$, $V_{DS} \geq V_{GS} - V_T$,
 $I_D = K[(V_{GS} - V_T)^2]$

$$\therefore I_D = K (V_{GS} - V_T)^2$$

$$\therefore I = 0.25m * (V_o - 1)^2 = \frac{6 - V_o}{1k\Omega} * \frac{1}{2} \quad (8)$$

$$0.5(1 - 2V_o + V_o^2) = 6 - V_o$$


$$1 - 2V_o + V_o^2 = 12 - 2V_o$$

$$V_o^2 = 11$$

$$V_o = \sqrt{11} \cong 3.31V \quad (8)$$

NMOS is saturate since

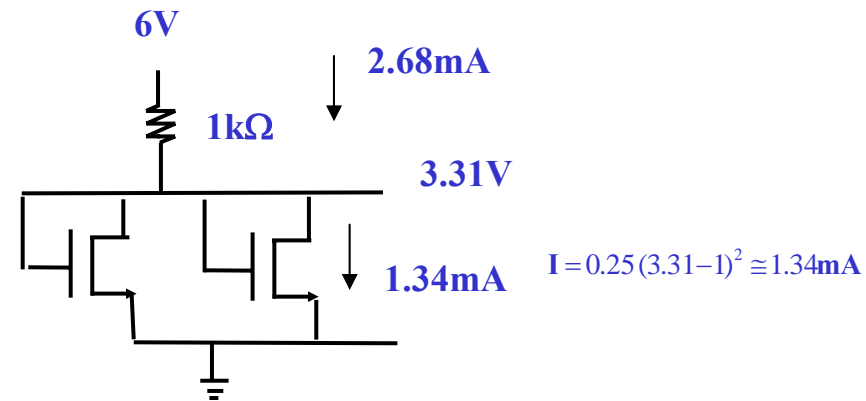
1. $V_{GS} > V_T$ $3.31 > 1$
 2. $V_{DS} > V_{GS} - V_T$ $3.31 > 3.31 - 1$
- (4)



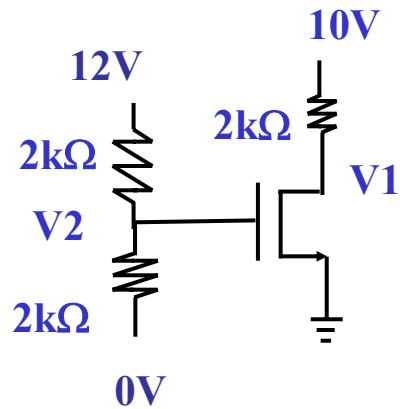(22)

3


Show that $V_2 = 6V$.
Hence find V_1 . Show clearly your reasons. (22)



Given

$$V_T = 1V$$

$$K = 0.5mA/V^2$$

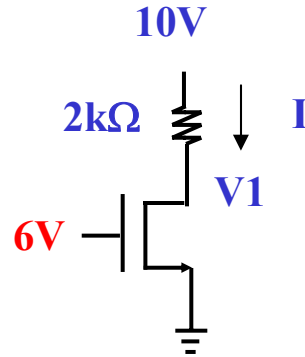

$$V_2 = 6V \text{ since } I_G = 0. \quad (4)$$

Assume NMOS is triode

$$\therefore I = \frac{10V - V_1}{2k\Omega} = 2 * 0.5m * [(6V - 1V)V_1 - \frac{V_1^2}{2}]$$

$$\therefore 10V - V_1 = 2 * [5V_1 - \frac{V_1^2}{2}] \quad (8)$$

$$\therefore V_1^2 - 11V_1 + 10 = 0$$

$$\therefore V_1 = 10V \quad \text{or} \quad 1V \quad (6)$$


When $V_o = 10V$, MOS is OFF

But MOS is not OFF ($V_{GS} > V_T$). Hence $V_o = 1V$ (2)

NMOS is triode since

$$1. V_{GS} > V_T \quad 6 > 1 \quad (2)$$
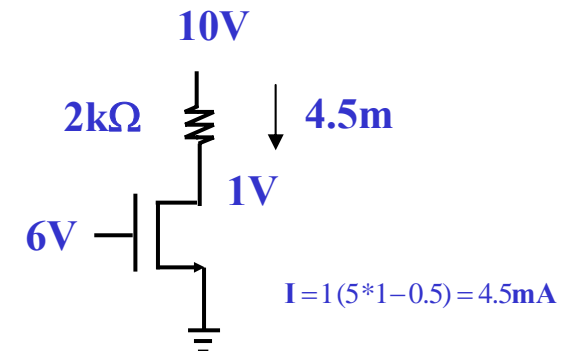
$$2. V_{DS} < V_{GS} - V_T \quad 1 > 6 - 1$$




At triode region, $V_{GS} \geq V_T$, $V_{DS} < V_{GS} - V_T$, $I_D = 2K(V_{GS} - V_T)V_{DS} - KV_{DS}^2$
At saturation region, $V_{GS} \geq V_T$, $V_{DS} \geq V_{GS} - V_T$, $I_D = K[(V_{GS} - V_T)^2]$

(17)

4

Draw the cross sectional structure of a NPN BJT transistor operated in the amplifier mode, Describe the movement of electrons, the designs in the emitter/base/collector, and explain briefly the equation $I_E \approx I_C / \alpha$. If $I_C \cong \beta I_B$, find β in terms of α . (17)

(a)

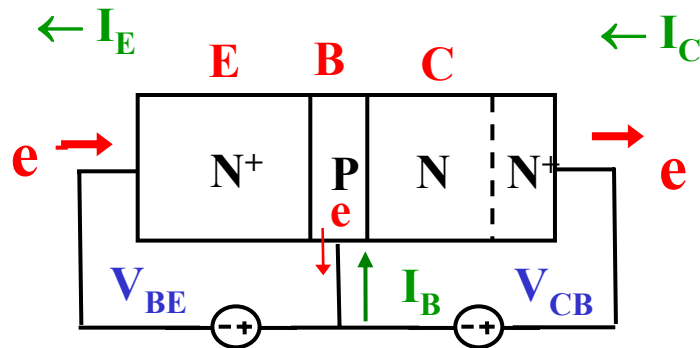

1. EB Junction is a forward bias (on) diode and BC is reverse bias (off) diode

2. E is very heavily doped (N^+ for NPN). E has many electrons,

3. B is very thin. So most electrons injected from E (to B) are attracted to C and

$$I_C \cong \alpha I_E \quad (12)$$

$$I_E \cong \frac{I_C}{\alpha} = I_B + I_C = \frac{I_C}{\beta} + I_C$$

$$\text{hence } \frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha} \quad (5)$$

5



Given the BJT circuit below and the I_C - V_{CE} curve of the BJT. Given $V_{CC} = 9V$, $R_C = 500\Omega$, $R_B = 1k\Omega$, $V_i = 0.8V$.

(a) Draw the load line $V_{CE} = V_{CC} - I_C R_C$, and locate the Q point on the load line.

(b) If $V_i(t) = 0.02\cos\omega t$ V, sketch and label $I_b(t)$, $I_c(t)$ and $V_o(t)$.

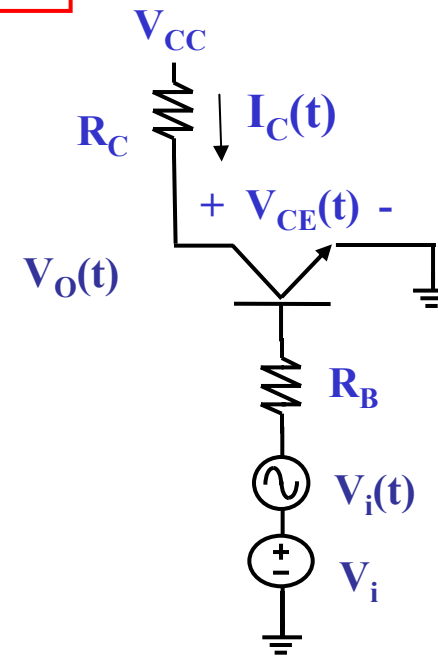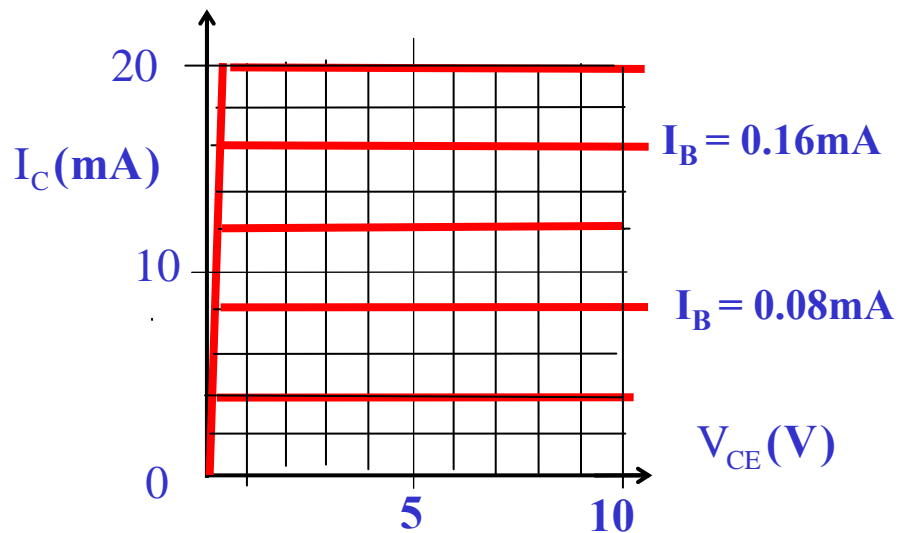(c) If V_i is changed from 0.8V to 0.76V, sketch and label $V_{CE}(t)$. Estimate also the voltage gain $\Delta V_O / \Delta V_i$. $V_i(t) = 0.02\cos\omega t$ V (32)

For the BJT, given $V_{BE(ON)} = 0.7V$, $V_{CESAT} = 0.2V$.




(32)

Draw load line,


(a)

$$\therefore I_C = \frac{V_{CC}}{R_C} = \frac{9V}{500\Omega} = 18mA \quad (6)$$

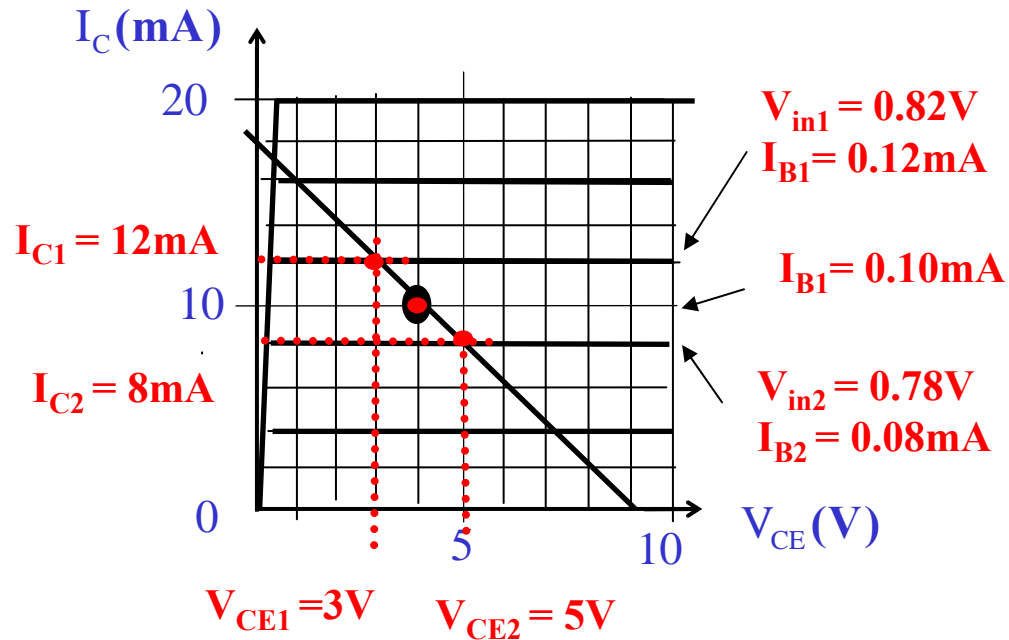
Draw Q point,

$$\therefore I_{BQ} = \frac{0.8V - 0.7V}{1k\Omega} = 0.1mA \quad (6)$$

(b)

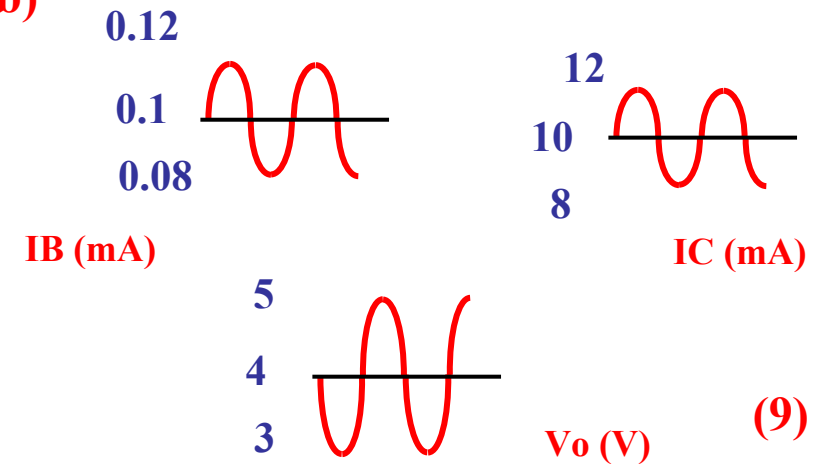 $V_{CE}(t)$ roughly ~

$$(c) \quad \therefore I_{BQ} = \frac{0.76V - 0.7V}{1k\Omega} = 0.06mA$$

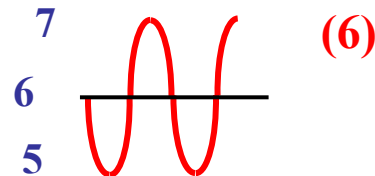
voltage gain A_v (5)

$$\cong \frac{7V - 5V}{0.74V - 0.78V} = -50$$

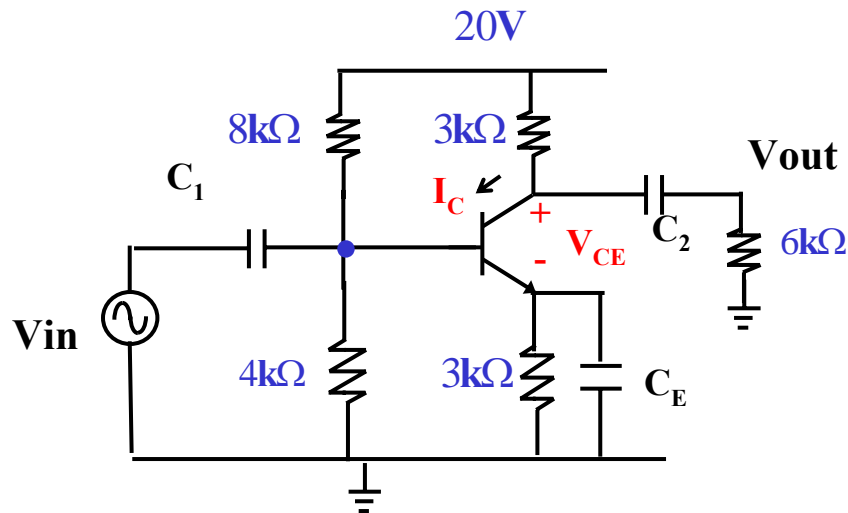
(17)

6

Sketch the small signal (AC) equivalent circuit of the BJT amplifier and find the voltage gain $A_v (= V_{out} / V_{in})$.
 Given $r_\pi = 1\text{k}\Omega$, $\beta = 100$, $V_{CESAT} = 0.2\text{V}$, $V_{BE(ON)} = 0.7\text{V}$. Assume C_1 , C_2 and C_E are very large in your calculation. . (17)



Replace BJT by model.

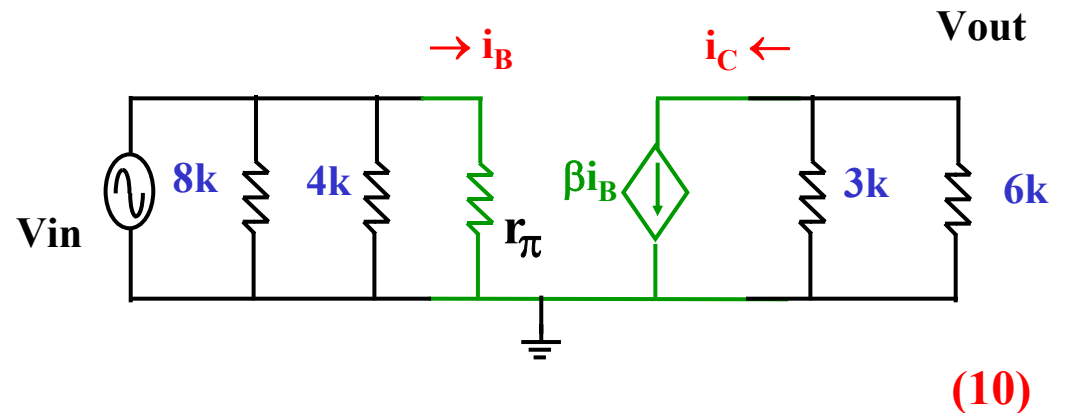

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{-\beta i_B (6\text{k}\Omega // 3\text{k}\Omega)}{i_B r_\pi} \\ &= \frac{-\beta (2\text{k}\Omega)}{r_\pi} = -\frac{100 * 2\text{k}\Omega}{1\text{k}\Omega} = -200 \end{aligned}$$

(7)

Answer with 3kohm (not 6k//3k) also accepted


(33)

7

If $I_B = 0.097\text{mA}$, find V_{in} and I_E . Show clearly your reasons.

For the BJT, given $V_{BE(ON)} = 0.7\text{V}$, $\beta = 100$, $V_{CESAT} = 0.2\text{V}$.

(33)

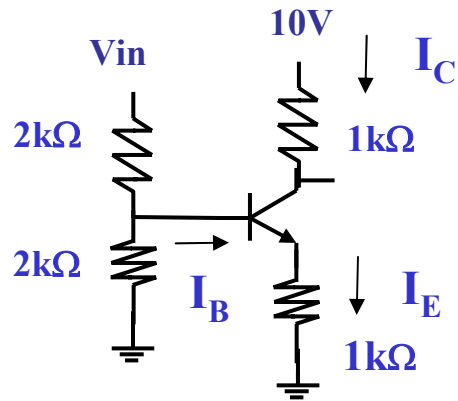


$$\therefore V_B = V_{in} * \frac{2\text{k}\Omega}{2\text{k}\Omega + 2\text{k}\Omega} = \frac{V_{in}}{2}$$

$$\therefore R_B = 2\text{k}\Omega // 2\text{k}\Omega = 1\text{k}\Omega \quad (6)$$

$$\therefore I_C = \beta I_B = 100 * 97\mu\text{A} = 9.7\text{mA}$$

BJT is SAT, since I_C when $V_{CE} = 0.2\text{V}$ is only $\sim 5\text{mA}$

(7)

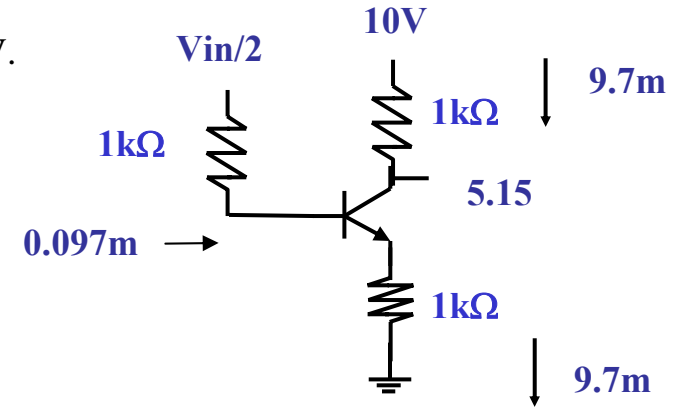

$$\begin{aligned} \therefore 10\text{V} &= I_C R_C + V_{CE} + I_E R_E \\ &= \beta I_B R_C + V_{CE} + (1 + \beta) I_B R_E = (1 + 2\beta) 0.097\text{m} * 1\text{k}\Omega + 0.2\text{V} \\ \therefore \beta &= \left(\frac{10\text{V} - 0.2\text{V}}{0.097\text{m} * 1\text{k}\Omega} - 1 \right) * \frac{1}{2} \cong 50 \end{aligned} \quad (10)$$



$$\therefore I_C \cong \beta I_B \cong 50 * 97\mu\text{A} \cong 4.85\text{mA}$$

$$\therefore I_E \cong (1 + \beta) I_B \cong 51 * 97\mu\text{A} \cong 4.95\text{mA} \quad (3)$$

$$\begin{aligned} \therefore \frac{V_{in}}{2} &= I_B R_B + V_{BE} + I_E R_E \\ &\cong 0.097\text{m} * 1\text{k}\Omega + 0.7\text{V} + 4.95\text{V} \cong 5.75\text{V} \end{aligned} \quad (7)$$

$$\therefore V_{in} \cong 11.5\text{V}$$


(33)

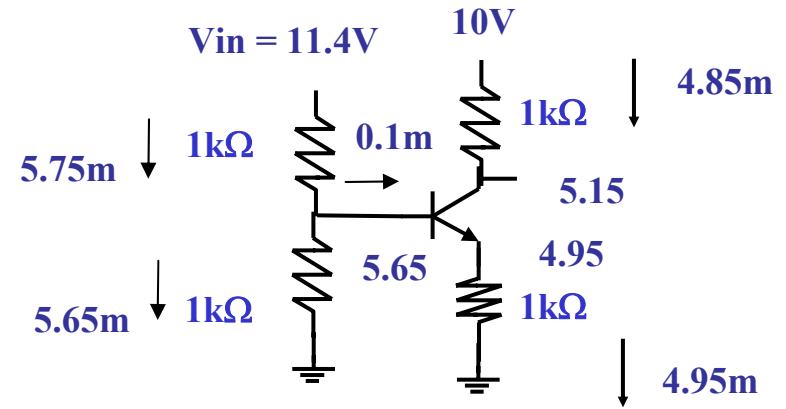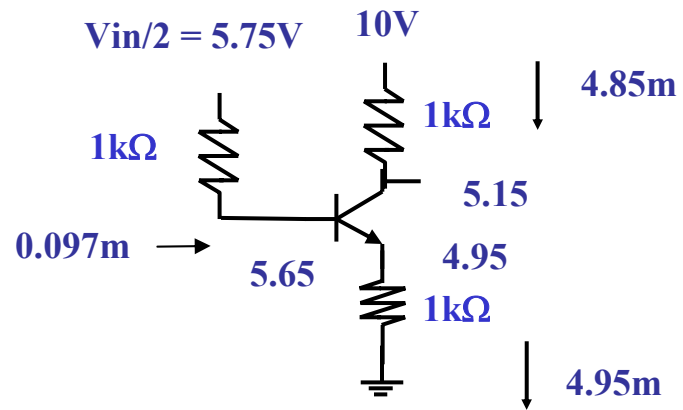

(16)

8

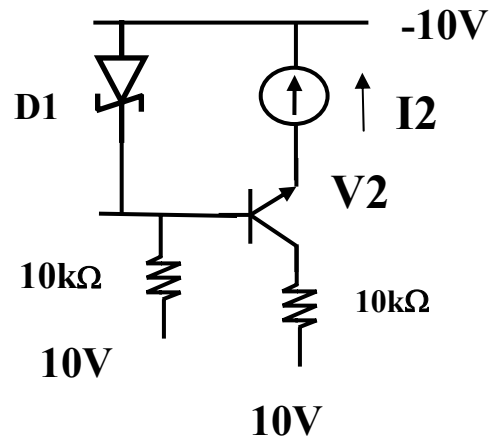8. In the BJT circuit, if transistor is just in saturation and diode is at breakdown, find I_2 . Given $V_{CESAT} = 0.1V$, $V_{BEON} = 0.7V$, β is large for BJT, breakdown voltage = $5V$ for zener diode, $r_z = 0$.
(15)



Base of BJT = $-5V$


Hence $V_2 = -5.7V$

$$\therefore 10V \cong V_2 + V_{CESAT} + I_2 * 10k\Omega$$

$$= -5.7V + 0.1V + I_2 * 10k\Omega$$

$$\therefore I_2 \cong \frac{15.6V}{10k\Omega} = 1.56mA$$


(15)

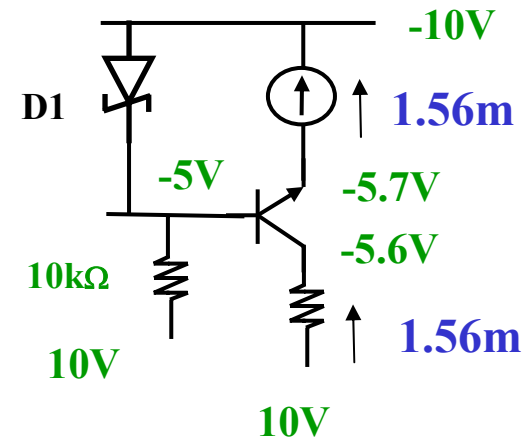



(15)

9

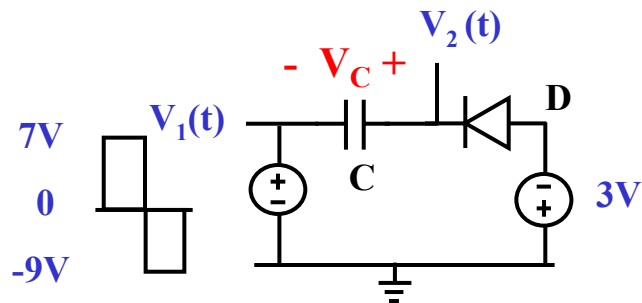
(a) In the diode circuit, find V_c . Hence sketch and label clearly $V_2(t)$. D is an offset diode with $V_F = 0.7V$. (15)



(a)

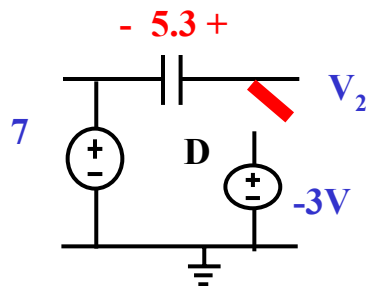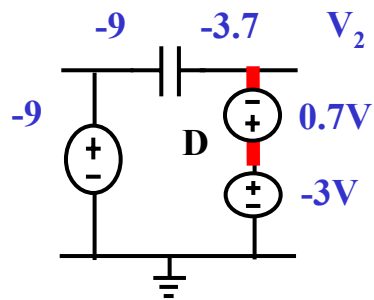

$$V_2 = V_1 + V_c = V_1 + 5.3V$$

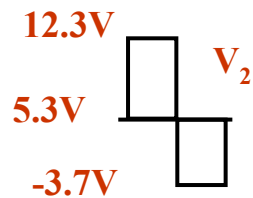


(15)

(22)

9

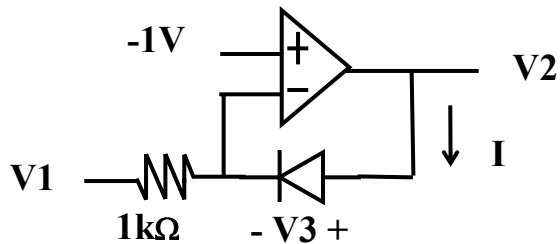9. (b) In the ideal op amp circuit, the diode equation is

$$I_D = I_0 \left[e^{\frac{V_D}{25\text{mV}}} - 1 \right]$$



Find V_3 if $V_1 = -2\text{V}$

Given that $I = 0.135\text{ mA}$ when $V_2 = -0.35\text{V}$. (22)

9(b)

$$V_2 = -0.35\text{V}$$

$$\therefore V_3 = -0.35 - (-1\text{V}) = 0.65\text{V}$$

$$\therefore I = 0.135\text{mA} = I_0 \left(e^{\frac{0.65\text{V}}{25\text{mV}}} - 1 \right)$$

(7)

$$\therefore V_1 = -2\text{V}$$



$$\therefore I = 1\text{mA}$$

$$\therefore I = 1\text{mA} = I_0 \left(e^{\frac{V_3}{25\text{mV}}} - 1 \right) \quad (7)$$

$$\frac{1\text{mA}}{0.135\text{mA}} = \frac{e^{\frac{V_3}{25\text{m}}} - 1}{e^{\frac{650\text{m}}{25\text{m}}} - 1} \cong e^{(V_3 - 650\text{m})/25\text{m}} \cong 0.135$$

$$\therefore V_3 = 650\text{m} + 25\text{m} \ln \frac{1}{0.135} = 700\text{mV}$$

(8)

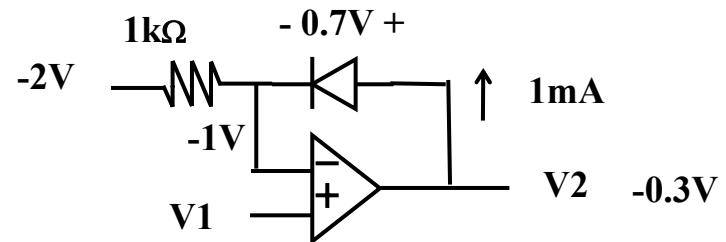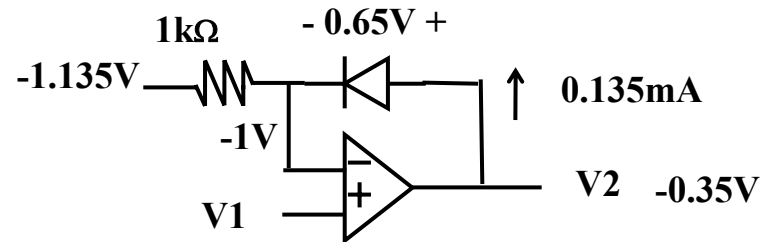

(17)

10

In the diode circuit, the diode has the forward, reverse and breakdown characteristics as shown.

(a) Find the model of the diode at breakdown.



(b) Find I_2 , V_1 and V_2 if $V_3 = 20\text{V}$

(c) Find V_1 and I_2 if $V_3 = 30\text{V}$.


Show clearly your reasons. (34)

The diode equation is
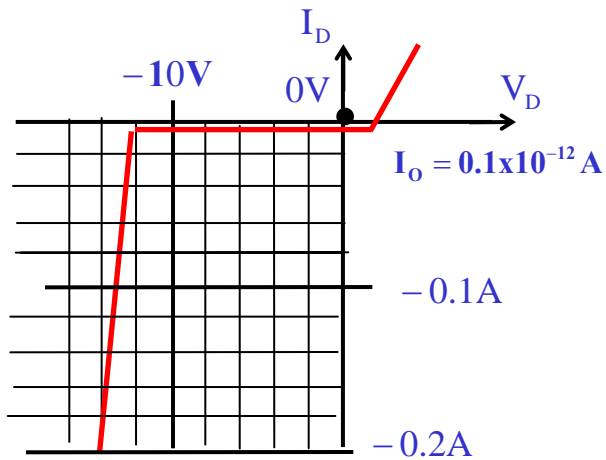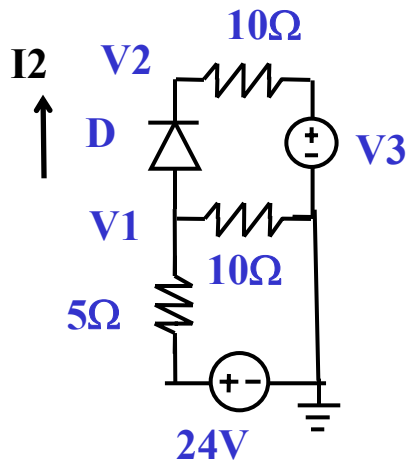
$$I_D = I_0 * [e^{\frac{V_D}{25\text{mV}}} - 1]$$




(a)

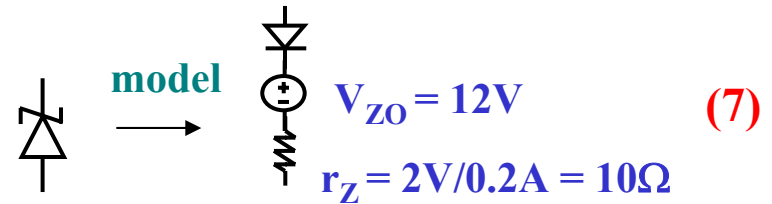

(b)

If $V_3 = 20\text{V}$, D is OFF, $V_1 = 16\text{V}$, $V_2 = 20\text{V}$ (6)


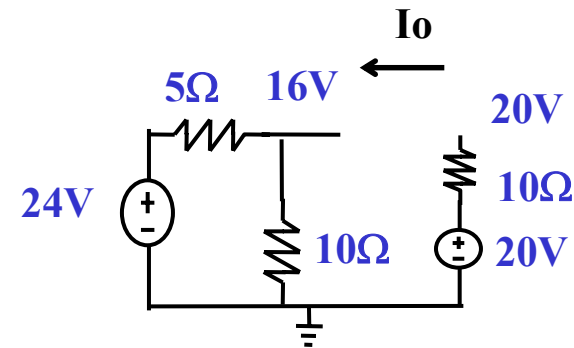
$$\therefore I_2 = -I_0 = -0.1 \times 10^{-12} \text{ A} \quad (4)$$



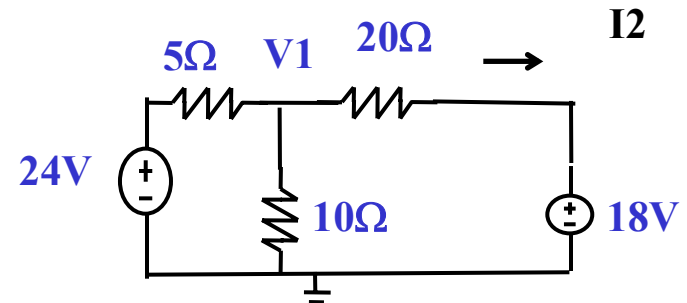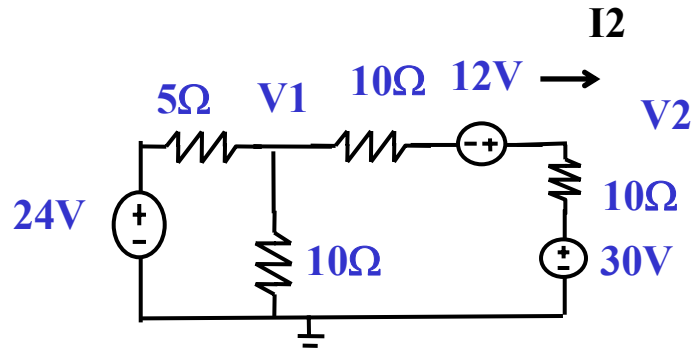(17)

(c)

If $V_3 = 30\text{V}$, D is breakdown,
replace D by model




$$\frac{24\text{V} - V_1}{5\Omega} = \frac{V_1}{10\Omega} + \frac{V_1 - 18\text{V}}{20\Omega} \quad (8)$$

$$\therefore 96\text{V} - 4V_1 = 2V_1 + V_1 - 18\text{V}$$

$$V_1 = \frac{114\text{V}}{7} \cong 16.29\text{V} \quad (5)$$


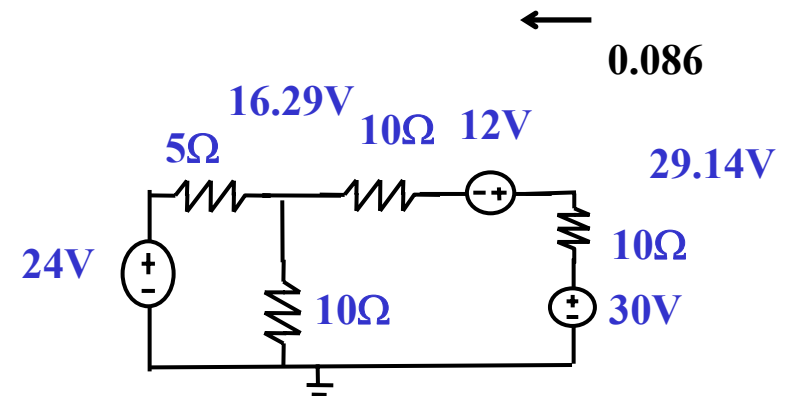
$$I_2 \cong \frac{16.29\text{V} - 18\text{V}}{20\Omega} = -0.0857\text{A} \quad (4)$$



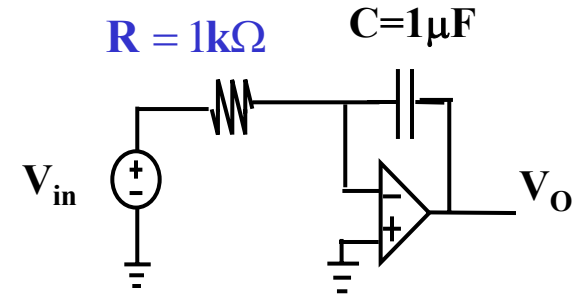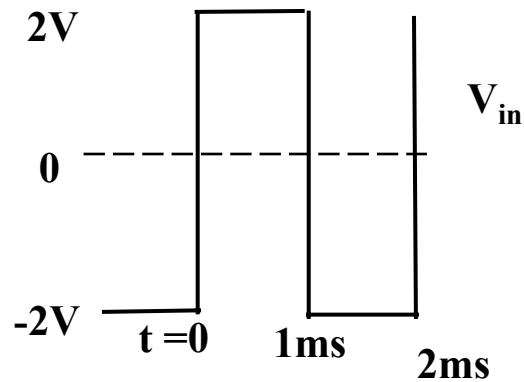(18)

11

. An ideal op amp RC integrator circuit has the following input voltage V_{in} . Draw the integrator circuit, derive the equation for the output voltage V_o , and hence draw the waveform of V_o . Given $R = 1k\Omega$ and $C = 1\mu F$. (18)




(6)

$$-C \frac{dV_o}{dt} \cong \frac{V_{in}}{R}$$

$$V_{in} \cong -CR \frac{dV_o}{dt}$$

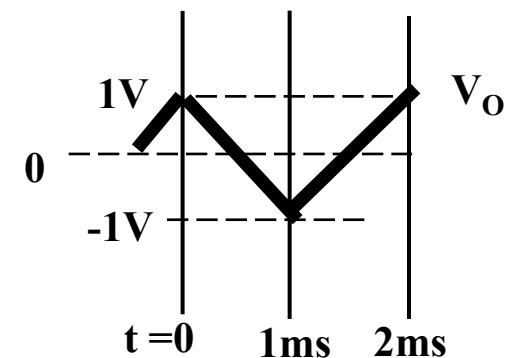(6)

$$V_{in} \cong -(1\mu F * 1k\Omega) \frac{\Delta V_o}{1ms} = 2V \Rightarrow \Delta V_o = -2V$$



(6)

Can have other answers with $\Delta V_o = -2V$

(21)


12

Given the ideal op amp filter circuit .

(a) Find the complex transfer function $G (= V_o / V_s)$ in terms of R , C , R_1 , R_2 and $j\omega$.

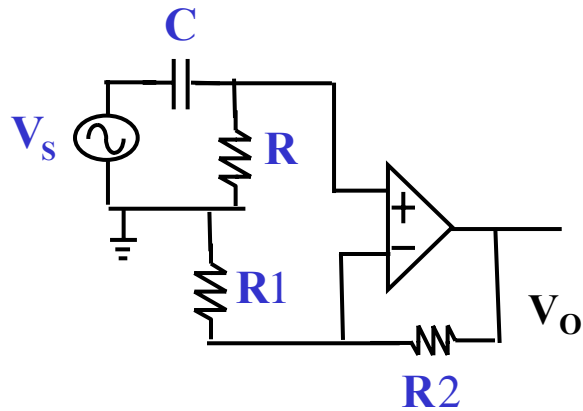(b) Find the cut-off frequency . Estimate also $V_o(t)$ if $V_s(t) = 2\cos t$ V. Is the op amp circuit a low pass filter?

Given that $R = 1\text{k}\Omega$, $C = 1\mu\text{F}$, $R_1 = 1\text{k}\Omega$, $R_2 = 20\text{k}\Omega$, and $\omega_0 = 1/CR$. (21)



a

$$V_o = V_s * \frac{R}{R + \frac{1}{j\omega C}} \left(1 + \frac{R_2}{R_1}\right)$$

$$G = \frac{V_o}{V_s} = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + \frac{1}{j\omega CR}}$$

(8)

b

$\omega_0 = \text{cut-off frequency}$

$$\omega_0 = \frac{1}{RC} = \frac{1}{1\text{k}\Omega * 1\mu\text{F}} = 1\text{krad/s} \quad (4)$$

when $\omega = 1$

$$\omega CR = \frac{1}{1\text{k}} \cong 0.001 \quad (6)$$

$$V_o = V_i * |G| \cong 0.021 V_i \cong 0$$

Circuit is a high pass filter (3)

(28)

13

In an ideal op amp filter circuit, the complex transfer function G ($= V_O / V_S$) is given as. $\frac{-10}{1 + 2j\omega CR}$

(a) Plot the magnitude of G **in dB** ($= |G|$ in dB) versus ω .

Given $|G|$ **in dB** = $20 \log_{10} |G|$.

Show clearly the value of $|G|$ when $\omega = 0$, **cut-off frequency**, and ω in your plot.

(b) If $V_S(t) = 1 \cos 400kt$ V, find $V_O(t)$.

Given that $1/CR = 200 \text{krad/s}$. (28)


(a)

$$|G| \text{ in dB} = 20 \log_{10} 10 \cong 20.0 \text{ dB} \quad (4)$$

At cut-off frequency, $|G| = \frac{10}{\sqrt{2}}$

$$|G| \text{ in dB} = 20 \log_{10} \frac{10}{\sqrt{2}} \cong 17.0 \text{ dB} \quad (4)$$

(a)

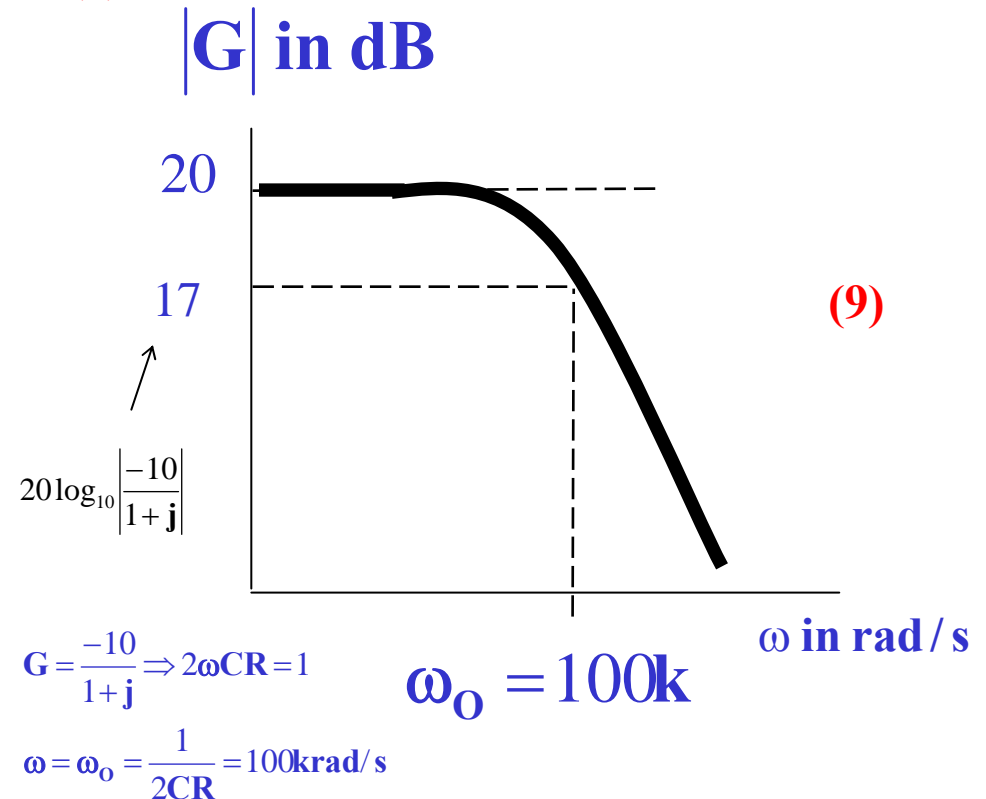

$$G = \frac{-10}{1+j} \Rightarrow 2\omega CR = 1$$

$$\omega_o = 100k$$

$$\omega = \omega_o = \frac{1}{2CR} = 100 \text{krad/s}$$

$$G = \frac{-10}{1 + 2j * 400k * CR} = \frac{-10}{1 + j4} \quad (11)$$

$$\therefore V_O = 1 \angle 0^\circ * \frac{-10}{1 + 4j} \cong \frac{-10}{\sqrt{17} \angle 76^\circ}$$

$$V_O(t) = -\frac{10}{\sqrt{17}} \cos(400kt - 76^\circ) \text{ V}$$