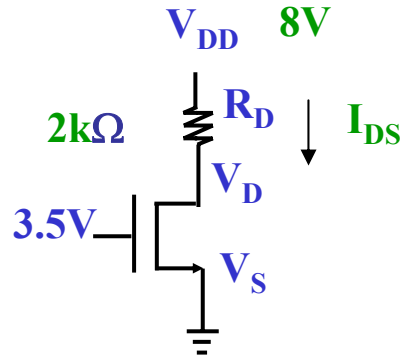


2

Given  $V_T = 1\text{V}$   
 $K = 0.25\text{mA/V}^2$



Find  $V_{DS}$  and  $I_{DS}$  for  $V_G = 3.5\text{V}$

**MOS is in saturation mode**

$$\therefore I_{DS} = K (V_{GS} - V_T)^2 = 0.25\text{m}(3.5 - 1)^2 = 1.5625\text{mA}$$


$$\therefore V_{DS} = V_{DD} - I_{DS} R_D = 8 - (1.5625\text{m})2\text{k} \cong 4.875\text{V}$$

$$\therefore I_{DS} = \frac{8 - 4.875}{2\text{k}} = 1.5625\text{mA}$$

4

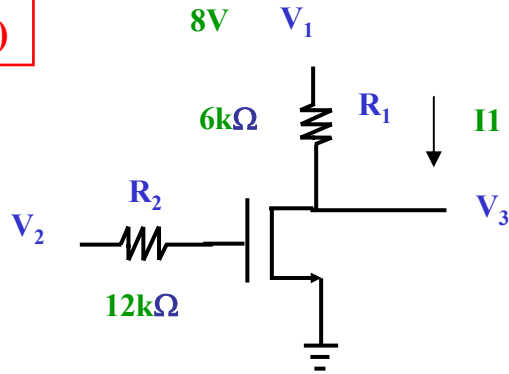(18)

Given  
 $V_T = 1\text{V}$   
 $K = 0.25\text{mA/V}^2$



a

If  $V_2 = 0.5\text{V}$ 

$$V_{GS} < V_T$$

$$0.5 < 1$$

$$\therefore I_1 = 0$$

NMOS cut off

$$\therefore V_3 = 8\text{V}$$

b

If  $V_2 = 3\text{V}$ 

Assume NMOS is in saturation

$$\therefore I_1 = K (V_{GS} - V_T)^2 = 0.25\text{m}(3-1)^2 = 1\text{mA}$$


$$\therefore V_3 = 8 - I_1 R_1 = 8 - 1\text{m}(6\text{k}) = 2\text{V}$$

NMOS is saturated since

1.  $3 > 1$
2.  $2 = 3 - 1$

NMOS is saturated since

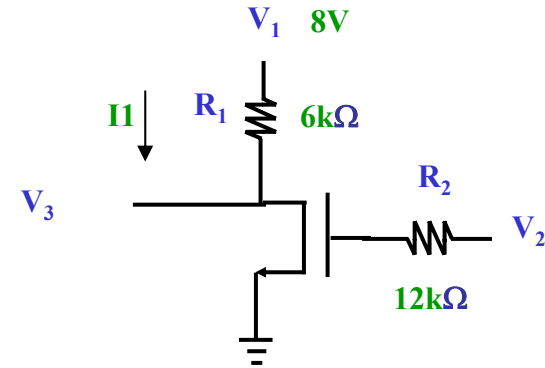1.  $V_{GS} > V_T$
2.  $V_{DS} = V_{GS} - V_T$



4. (a) If  $V_2 = 0.5\text{V}$ , find  $I_1$  and  $V_3$ . (b) If  $V_2 = 2\text{V}$ , find  $I_1$  and  $V_3$ . State clearly the reasons for your answer.

Given  $V_T = 1\text{V}$ ,  $K = 0.25\text{mA/V}^2$ .

Given that


at triode region,  $I_{DS} = 2K[(V_{GS} - V_T)V_{DS} - V_{DS}^2/2]$

at saturation region,  $I_{DS} = K[(V_{GS} - V_T)^2]$  (19).

5

(26)

Given  
 $V_T = 1V$   
 $K = 0.5mA/V^2$

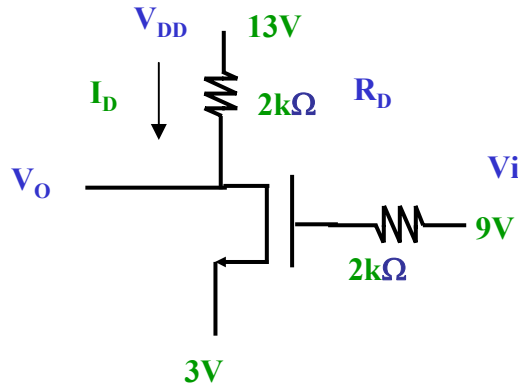

$$\begin{aligned}\therefore I_D &= \frac{V_{DD} - V_{DS}}{R_D} = \frac{10 - V_{DS}}{2k} \\ &= 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}] = 1m[(8 - 2 - 1)V_{DS} - \frac{V_{DS}^2}{2}] \\ \therefore \frac{10 - V_{DS}}{2k} &= 1m[5V_{DS} - \frac{V_{DS}^2}{2}] \\ \therefore 10 - V_{DS} &= 2[5V_{DS} - \frac{V_{DS}^2}{2}] \\ \therefore V_{DS}^2 - 11V_{DS} + 10 &= 0 \\ \therefore V_{DS} &= 10V \quad \text{or} \quad 1V\end{aligned}$$

hence  $V_O = 3 + 1 = 4V$

$V_{DS} = 12V = V_{DD}$  is impossible since MOS is not cut off ( $V_{DGS} > V_T$ )

NMOS is in triode since

1.  $V_{GS} > V_T$
2.  $V_{DS} < V_{GS} - V_T$

NMOS is triode since

1.  $6 > 1$
2.  $1 < 6 - 1$

$$\begin{aligned}\therefore I_D &= 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}] \\ &= 1m[(6 - 1)1 - \frac{1}{2}] = 4.5mA\end{aligned}$$

5. In the circuit, find  $V_O$ . State clearly the reasons for your answer.

Given  $V_T = 1V$ ,  $K = 0.5mA/V^2$ .

Given that

at triode region,  $I_{DS} = 2K[(V_{GS} - V_T)V_{DS} - V_{DS}^2/2]$



at saturation region,  $I_{DS} = K[(V_{GS} - V_T)^2]$  (26).

8


8. A BJT with the following  $I_C$ - $V_{CE}$  characteristics is used in the following circuit. (a) Sketch the load line  $V_{CE} = V_{CC} - I_C R_C$  and the Q point on the graph.

(b) If  $v_{in} = 0.1 \cos \omega t$  V, sketch the base current  $I_B$ , the collector current  $I_C$  and the output voltage  $V_{out}$ . Show clearly the DC value, the maximum and minimum value in your sketch. Estimate also the current gain  $dI_C / dI_B$  and voltage gain  $dV_{out} / dV_{in}$ .

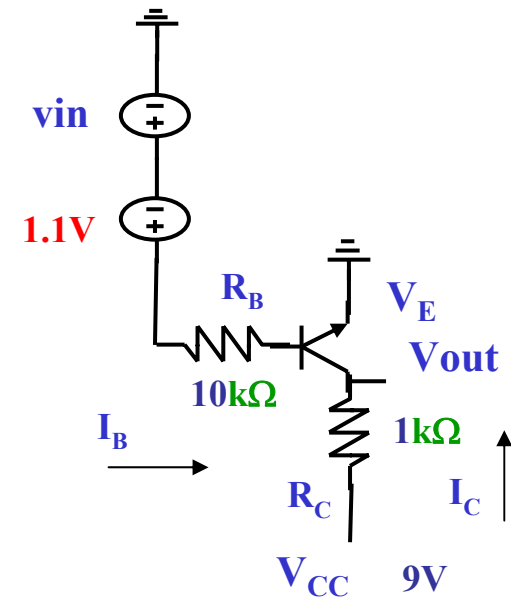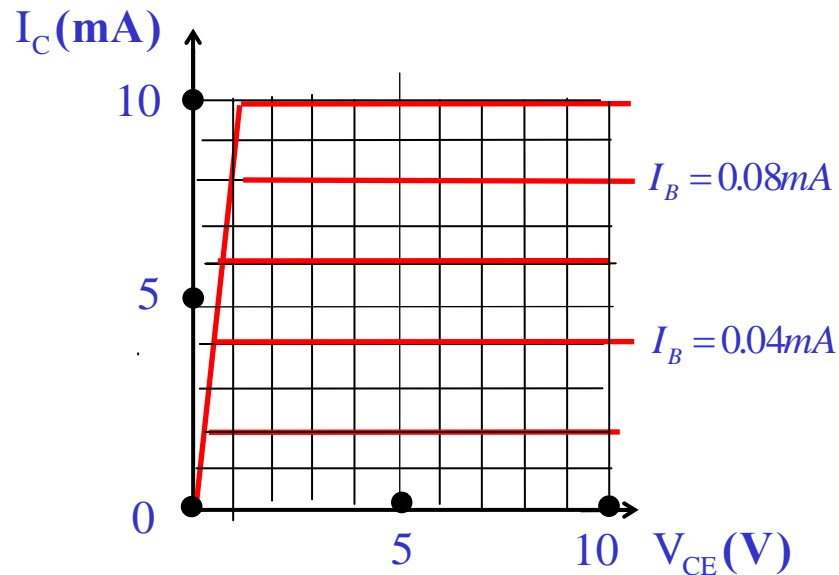
(c) Sketch the small signal (AC) equivalent circuit of the amplifier and find the voltage gain  $A_v (= V_{out}/V_{in})$ . For the BJT, given  $r_{\pi} = 0\Omega$ ,  $V_{BE(ON)} = 0.7V$ . (49)





**b** Find  $I_C$  from graph

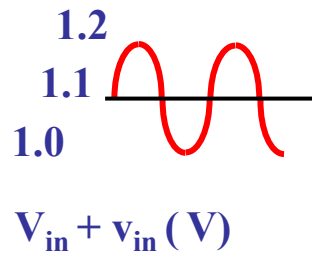

**a** Find  $I_B$  from equation

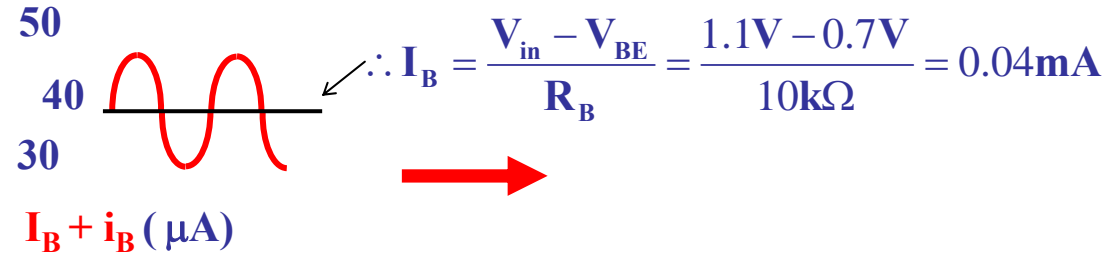

**c** Find  $V_{CE}$  from graph

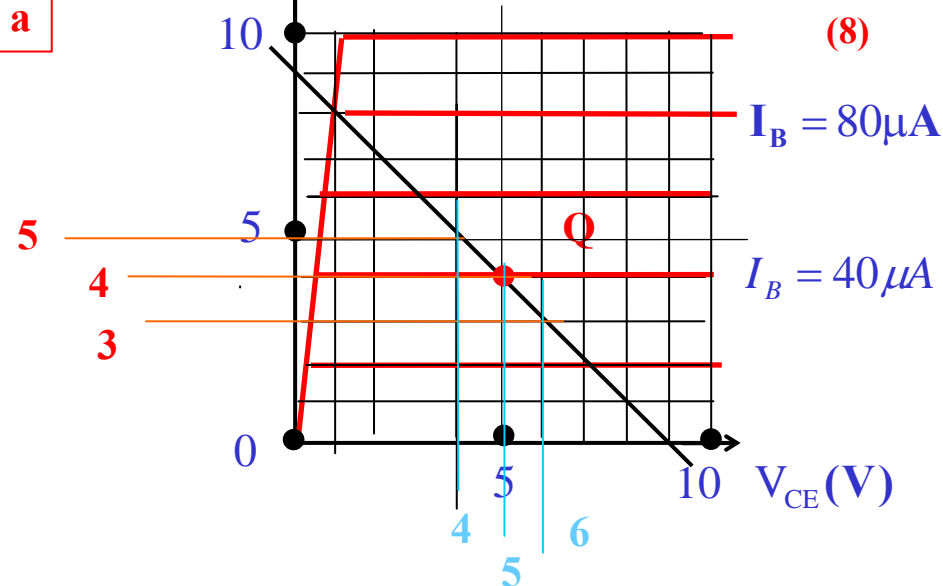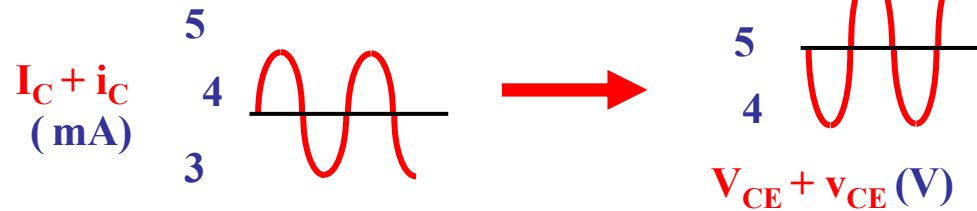


Estimate current and voltage gain

$$\therefore A_I = \beta_F = \frac{\Delta I_C}{\Delta I_B} \approx \frac{5m - 3m}{50\mu - 30\mu} = \frac{2mA}{20\mu A} = 100$$

$$\therefore A_V = \frac{\Delta V_{out}}{\Delta V_{in}} = \frac{6V - 4V}{1.0V - 1.2V} = \frac{2V}{-0.2V} = -10$$

c

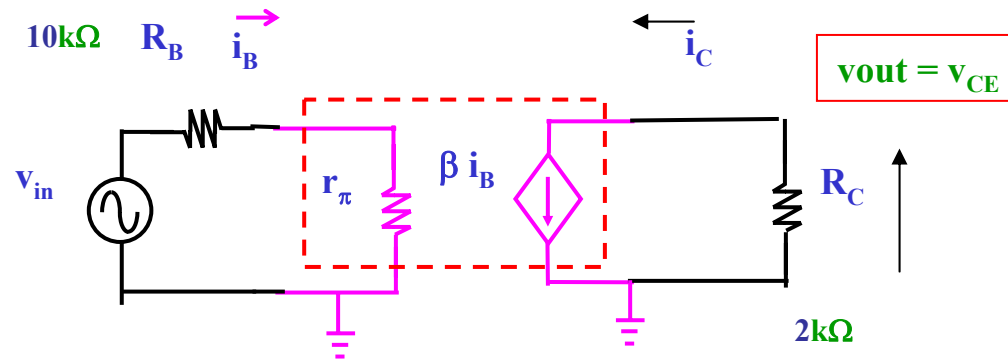

$$\therefore A_V = \frac{V_{OUT}}{V_{in}} = \frac{-\beta i_B R_C}{i_B (R_B + r_\pi)} = \frac{-\beta R_C}{R_B + r_\pi} = \frac{-(100)(1k)}{10k} \cong -10$$


9

9. Given the BJT circuit.

Given that  $I_B$  is about  $1.57\text{mA}$ . Show that the BJT is in saturation.


Hence show that the forced beta is about 2.7.

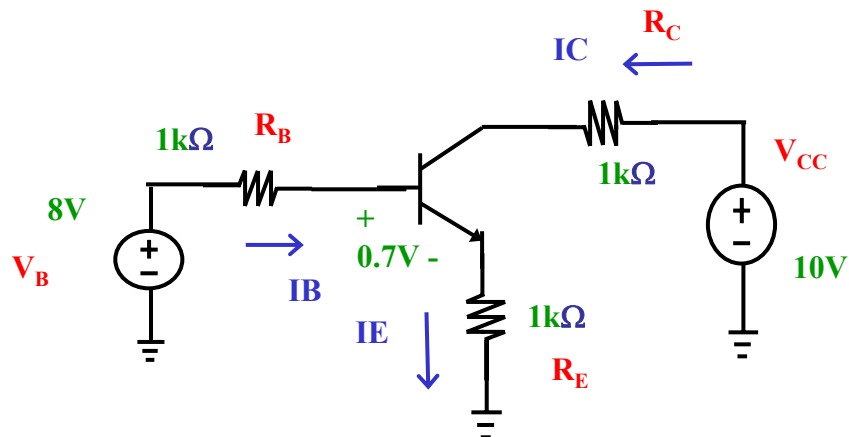For the BJT, given  $V_{BE} = 0.7\text{V}$ ,  $\beta = 100$ ,  $V_{CESAT} = 0.1\text{V}$ . (30)



$$\therefore I_C = \beta I_B = 100(1.57\text{m}) = 157\text{mA}$$
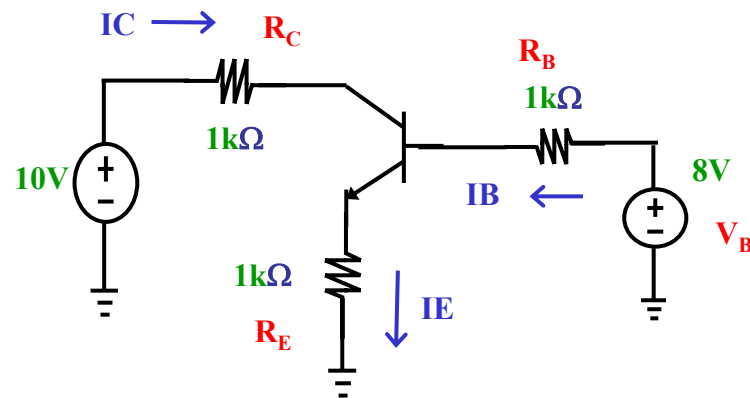
$$\gg I_C \text{ (when } V_{CE} = 0\text{V)} = \frac{10\text{V}}{2\text{k}\Omega} = 5\text{mA}$$



$$\therefore I_B = \frac{V_B - V_{BE}}{R_B + (1 + \beta^*)R_E} = \frac{V_{CC} - V_{CESAT}}{\beta^* R_C + (1 + \beta^*)R_E}$$

$$\therefore I_B = \frac{8 - 0.7}{1\text{k} + (1 + \beta^*)1\text{k}} = \frac{10 - 0.1}{1\text{k}(1 + 2\beta^*)}$$




$$\therefore 7.3(1 + 2\beta^*) = 9.9(2 + \beta^*)$$

$$\therefore 14.6\beta^* + 7.3 = 9.9\beta^* + 19.8$$

$$\therefore \beta^* = \frac{19.8 - 7.3}{14.6 - 9.9} \cong 2.66$$


11

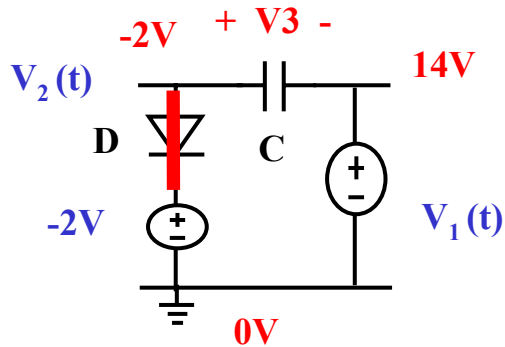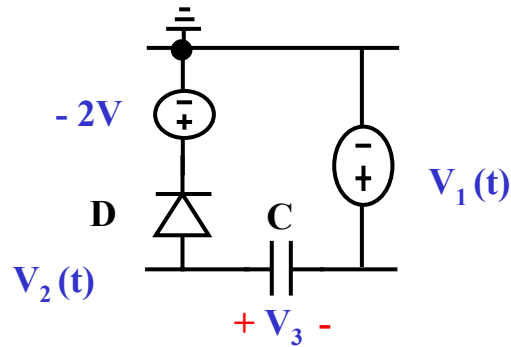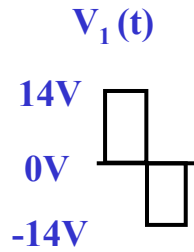11. (a) In the ideal diode circuit, find  $V_3$  and sketch  $V_2(t)$ . (15)



Hence  $V_3 = -16V$

Hence  $V_2 = V_1 + V_3 = V_1 - 16V$


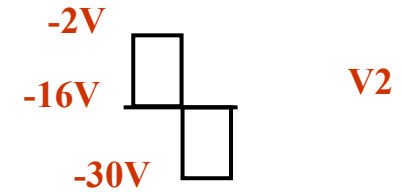




11

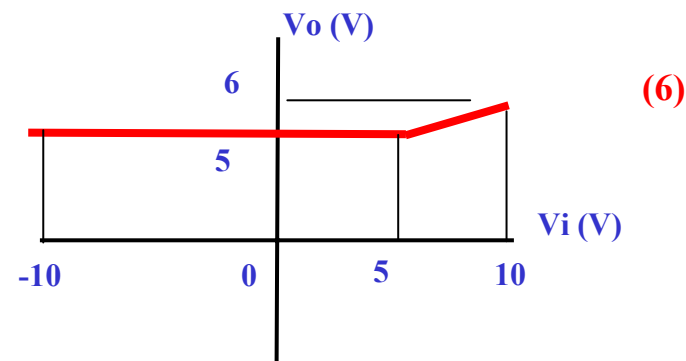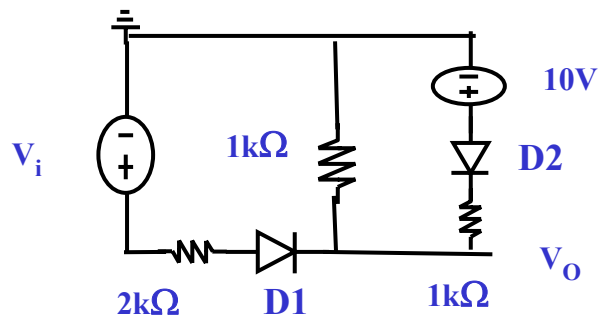(b) In the ideal diode circuit, plot  $V_o$  versus  $V_i$  for  $-10V \leq V_i \leq 10V$ .

Show clearly all voltages in your sketch. (20)



$V_i < 5V$ , D1 OFF and D2 ON

$\therefore V_o = 5V$

$V_i > 5V$ , D1 and D2 ON,

$$\therefore \frac{V_i - V_o}{2k} + \frac{10 - V_o}{1k} = \frac{V_o}{1k}$$


$$\therefore V_i - V_o + 20 - 2V_o = 2V_o$$

$$\therefore V_o = \frac{V_i + 20}{5}$$


12

12. In the diode circuit, the diode has the reverse characteristics as shown. The diode equation is  $I = I_o \exp [(V/25\text{mV}) - 1]$ .

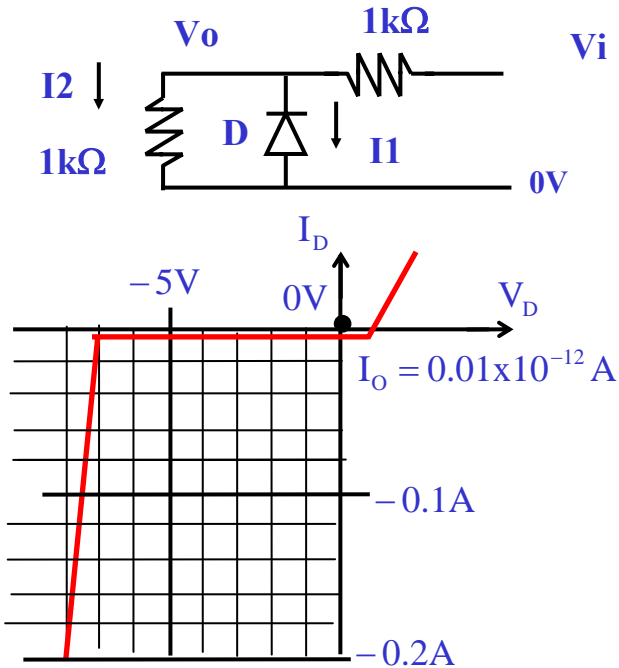- (a) Sketch the circuit model of the diode at breakdown.  
 (b) Find  $I_1$  if  $V_i = -1\text{V}$ .  
 (c) Find  $I_1$  if  $V_i = 2\text{V}$ .  
 (d) Find  $I_2$  if  $V_i = 16\text{V}$ . (35)



a

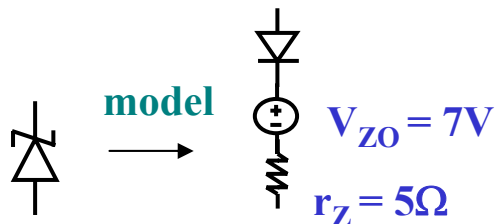

b

$$V_i = -1\text{V}, \therefore V_o = -0.5\text{V}$$

$$\therefore I_1 = -I_o (e^{\frac{0.5\text{V}}{25\text{mV}}} - 1)$$

$$= -0.01 \times 10^{-12}\text{A} (e^{\frac{500\text{m}}{25\text{m}}} - 1) = -4.85 \times 10^{-6}\text{A}$$

c

$$\therefore I_1 = I_o = 0.01 \times 10^{-12}\text{A}$$

d

$$V_i = 16\text{V}, \therefore V_o = 8\text{V}, D \text{ breakdown}$$


$$\frac{16 - V_o}{1\text{k}} = \frac{V_o - 7}{5} + \frac{V_o}{1\text{k}}$$

$$16 - V_o = 200(V_o - 7) + V_o$$

$$V_o = \frac{1400 + 16}{202} \cong 7.01\text{V}$$

$$\therefore I_2 = \frac{V_o}{R_L} \cong \frac{7.01}{1\text{k}} = 7.01\text{mA}$$

13

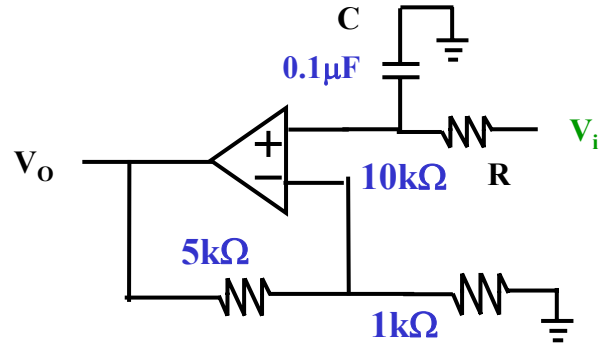

a

$$V_2 = V_i \frac{1/j\omega C}{R + 1/j\omega C} = \frac{V_i}{1 + j\omega CR}$$

$$\therefore V_o = V_2 \left(1 + \frac{5k}{1k}\right) = 6V_2 = 6 \frac{V_i}{1 + j\omega CR}$$

$$\therefore G = \frac{V_o}{V_i} = \frac{6}{1 + j\omega CR}$$

13. Given the filter circuit. The op amp is ideal.

(a) Obtain the complex transfer function  $G (=V_o/V_i)$  in terms of  $j\omega$ ,  $C$  and  $R$ .

(b) Find the cut-off frequency (in rad/s) and the DC gain (value of  $G$  when  $V_i$  is a DC voltage) of the filter.

(c) Sketch  $|V_o/V_i|$  in dB versus angular frequency  $\omega$ . Label clearly all intercepts. Given  $|G|$  in dB  $= 20\log_{10} |G|$ .

(d) Is it a low pass filter? Find also the pole and zero of the filter.

(38)

b

At cut off frequency  $\therefore G = \frac{V_o}{V_i} = \frac{6}{1 + j}$


$$\omega_o CR = 1$$

$$\therefore \omega_o = \frac{1}{CR} = \frac{1}{0.1\mu(10k)} = 1\text{krad/s}$$

DC gain  $G = 6$

c

At low frequency,  $\omega \sim 0$   $|G|$

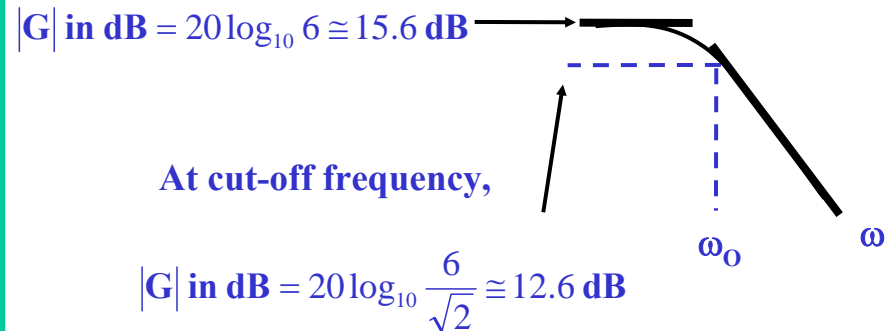


d

low pass filter

15

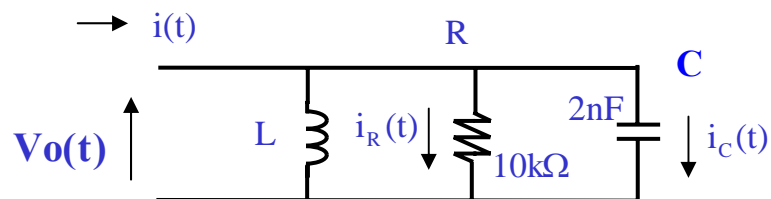15. In the following LCR circuit,  
 (a) find the resonant frequency (in rad/s and in Hz), Q-factor, bandwidth, upper and lower cut-off frequencies (all in rad/s) of the LCR circuit.  
 (b) If  $i(t) = \sqrt{8}\cos\omega t$  mA find  $V_o(t)$  and  $i_C(t)$  at resonance. (36)



a

$$\therefore \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{L * 2n}} = 5M \text{ rad/s and } 795.78 \text{ kHz}$$

$$\text{Hence } L = \frac{1}{(5M)^2 * 2n} = 0.02 \text{ mH}$$

$$\therefore Q \text{ factor} = \frac{Q}{P} = \frac{R}{\omega_0 L} = \frac{10k}{5M(0.02m)} = 100$$

$$\therefore BW = \frac{\omega_0}{Q \text{ factor}} = \frac{5M}{100} = 50k \text{ rad/s or } 7.96 \text{ kHz}$$

$$\text{Lower } f \therefore \omega_1 = \omega_0 - \frac{BW}{2} = 4950k \text{ rad/s}$$

$$\text{Upper } f \therefore \omega_2 = \omega_0 + \frac{BW}{2} = 5050k \text{ rad/s}$$

If i is 2mA rms

b

$$\begin{aligned} \therefore i_R &= 2 \text{ m Arms} \\ \therefore V_o &= 2 \text{ mA} * 10k\Omega = 20 \text{ Vrms} \\ \therefore i_C &= Q \text{ factor} * i_R = 200 \text{ mArms} \end{aligned}$$

$$\therefore V_o(t) = 20\sqrt{2}\cos 5Mt \text{ V}$$

$$\therefore i_C(t) = 200\sqrt{2}\cos(5Mt + 90^\circ) \text{ mA}$$

