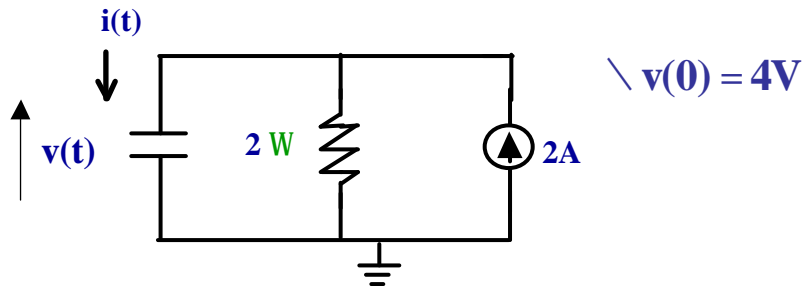
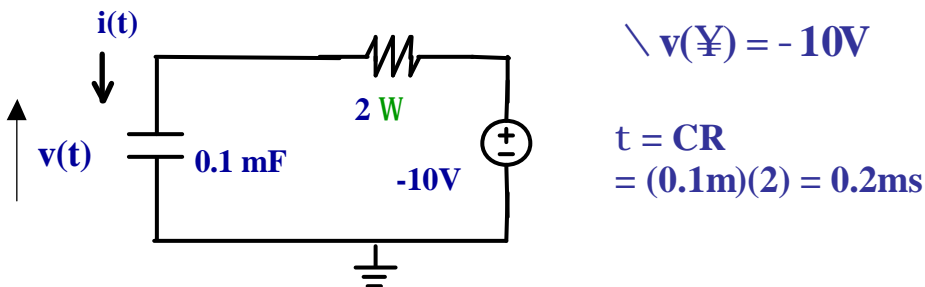




1

(35)

 $t < 0$, S is at a, $v = 4V$ At $t = 0$, S is switched to b

$$\backslash v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/CR} = -10 + [4 + 10]e^{-t/0.2ms} V$$

$$\backslash i(t) = \frac{-10 - v(t)}{R} = \frac{-10 + 10 - 14e^{-t/0.2ms}}{2} = -7e^{-t/0.2ms} A$$

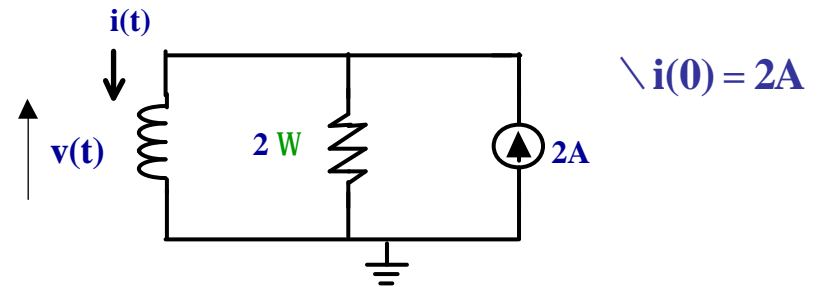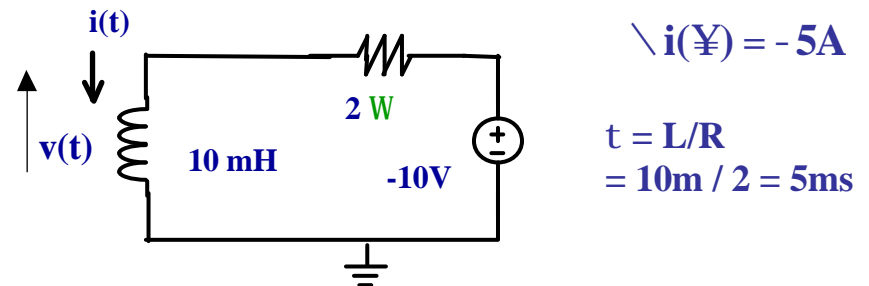 $t < 0$, S is at a, $i = 2A$ At $t = 0$, S is switched to b

$$\backslash i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} = -5 + [2 + 5]e^{-t/0.2ms} A$$

$$\backslash v(t) = -10 - i(t)2 = -10 - [-5 + 7e^{-t/0.2ms}]2 = -14e^{-t/0.2ms} V$$

1. In the circuit, the switch has been at **terminal a** for a long time.At $t = 0$, the switch is switched to **terminal b**.(a) If X is a 0.1mF capacitor, find $i(t)$ for $t \geq 0$. Find also the power supplied or absorbed by the $-10V$ source at $t = 0$.(b) If X is a 10 mH inductor, find $v(t)$ for $t \geq 0$.Given that $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$ and $v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}$ (35)


2

(33)

$$\frac{1}{j\omega C} = \frac{1}{j(1k)\frac{1}{2}m} = -2j$$

$$j\omega L = j(1k)10m = 10j$$
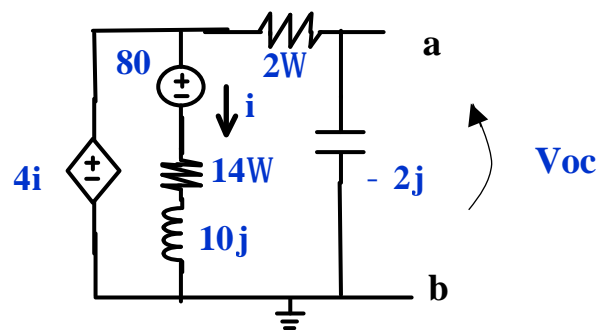
$$v(t) = 80\cos(1kt)V \Rightarrow V = 80$$



$$\therefore 4i = 80 + i(14 + 10j)$$


$$\therefore i = \frac{-80}{10 + 10j} = \frac{-8}{1 + j}$$

$$\therefore V_{oc} = 4i \frac{-2j}{2 - 2j}$$

$$= 4i \frac{-j}{1 - j} = 4 \frac{-8}{1 + j} \frac{-j}{1 - j} = \frac{32j}{2} = 16j$$

$$\therefore V_{oc}(t) = 16\cos(1000t + 90^\circ)V$$

Hence $V_{oc}(t)$ leads $v(t)$

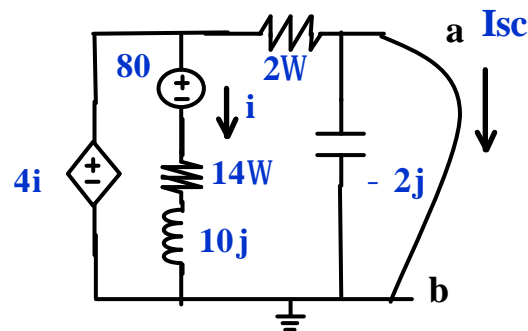

$$\therefore I_{sc} = \frac{4i}{2} = 2i$$

$$= 2 \frac{-8}{1 + j} = -16 \frac{1}{1 + j} \frac{1 - j}{1 - j}$$

$$= -16 \frac{1 - j}{2} = -8(1 - j) = -8 \frac{\sqrt{2} - 45}{\sqrt{2}}$$

$$\therefore I_{sc}(t) = \frac{-8}{\sqrt{2}} \cos(1000t - 45^\circ)A$$


2. In the circuit, $v(t) = 80 \cos(1k t) V$. Find $V_{oc}(t)$ and $I_{sc}(t)$ at terminals ab . Does $V_{oc}(t)$ lead $V(t)$? (33)

3**(33)**

3. In the circuit, load A is 50 kW at 0.866 lagging power factor. Load B is 100 kW at 0.5 leading power factor.

(a) Find the total apparent power S , reactive power Q , average power P and power factor PF of the combined load (load A and B).

(b) If a load X is connected to terminals ab to make the total power factor = 1, find the element and value of load X. Find also the new load current I in Arms. (33)

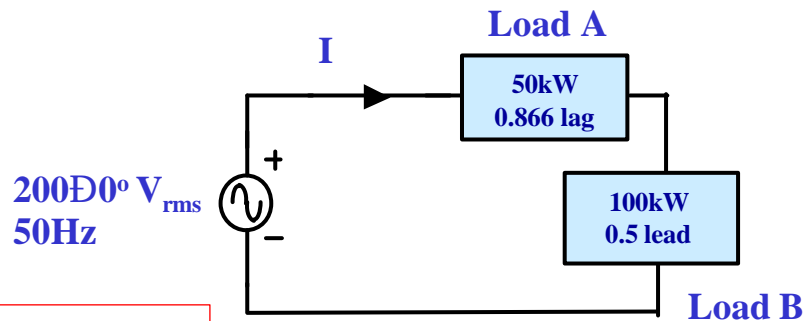**For load A**

$$P = 50\text{kW}$$

$$Q = P \tan q = 50\text{k} \tan(\cos^{-1} 0.866) = 28.87\text{kVAR (L)}$$

For load B

$$P = 100\text{kW}$$

$$Q = P \tan q = 100\text{k} \tan(\cos^{-1} 0.5) = 173.2\text{kVAR (C)}$$

For load A and B

$$\text{total } P = 50\text{k} + 100\text{k} = 150\text{kW}$$

$$\text{total } Q = 28.87\text{k} - 173.2\text{k} = -144.33\text{kVAR}$$

$$\text{total } S = \sqrt{P^2 + Q^2} = \sqrt{150\text{k}^2 + 144.33\text{k}^2} = 208.16\text{kVA}$$

$$\text{total } PF = \frac{P}{S} = \frac{150\text{k}}{208.16\text{k}} = 0.72\text{leading}$$

Add Load X (inductance L)

$$Q_L = \frac{V^2}{\omega L}$$


$$L = \frac{V^2}{\omega Q_L} = \frac{200^2}{2\pi 50(144.33\text{k})} = 0.88\text{mH}$$

New I

$$I = \frac{S}{V} = \frac{150\text{k}}{200} = 750\text{A}_{\text{rms}}$$

4

(30)

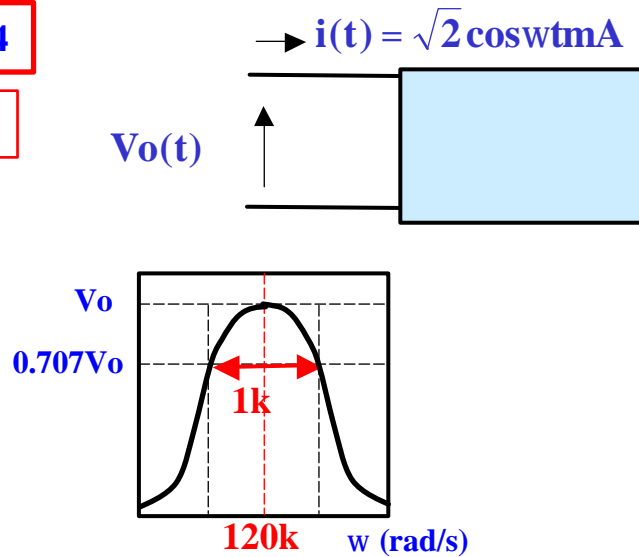

$$\omega_0 = 120k \text{ rad/s}$$

$$BW = 1k \text{ rad/s}$$

$$\omega_2 = \omega_0 + \frac{BW}{2} = 120.5k \text{ rad/s}$$

$$\omega_1 = \omega_0 - \frac{BW}{2} = 119.5k \text{ rad/s}$$

$$Q = \frac{\omega_0}{BW} = \frac{120k}{1k} = 120$$

V_o is maximum at resonance,
hence network is parallel LCR

$$Q = \frac{R}{\omega_0 L}$$

$$R = Q \omega_0 L = 120(120k)(0.4m) = 5.76k\Omega$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(120k)^2(0.4m)} = 0.174mF$$

$$\max V_o(t) = i(t)R$$

$$= \sqrt{2} \cos(\omega_0 t) \text{ mA} * 5.76k\Omega = 5.76\sqrt{2} \cos(\omega_0 t) \text{ V}$$

$$\max i_L = \frac{\max V_o}{j\omega_0 L} = \frac{IR}{j\omega_0 L} = \frac{QI}{j}$$

$$\max i_L(t) = 120\sqrt{2} \cos(\omega_0 t - 90^\circ) \text{ mA}$$

4. A LCR circuit (band pass filter) has the following frequency response curve (magnitude of $V_o(t)$ versus frequency ω).

(a) Find the resonant frequency, bandwidth (BW), upper and lower cut-off frequencies (in rad/s), and the Q-factor of the LCR circuit.

(b) If $L = 0.4mH$, find the values of C and R . Find also the maximum $V_o(t)$ and maximum current flowing in L ($i_L(t)$). (30)

5**(30)**


5. An ideal op amp filter circuit is composed of filter 1 in series with filter 2.

(a) Obtain the complex transfer function $H (=V_o/V_i)$ in terms of $j\omega$, C , R_1 , R_2 , R_3 and R_4 .

(b) Obtain the cut-off frequency (in rad/s) for filter1 and filter 2.

(c) Sketch $|V_o/V_i|$ in dB versus angular frequency ω . Label clearly all intercepts.

(d) What type of filter is it?

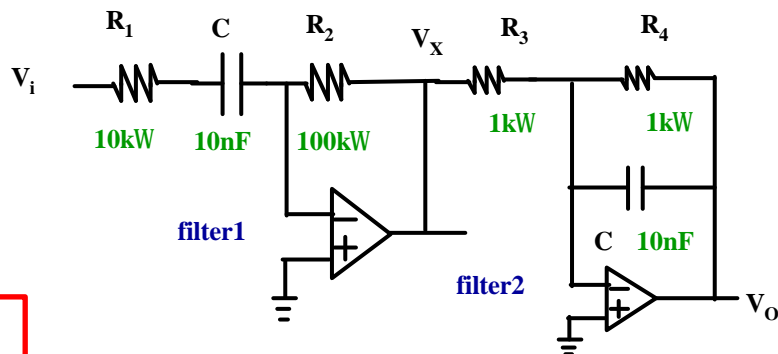(30)**a**

$$G_1 = \frac{V_x}{V_i} = -\frac{R_2}{R_1 + 1/j\omega C} = -\frac{R_2}{R_1} \frac{1}{1 - j/\omega CR_1}$$

$$G_2 = \frac{V_o}{V_x} = -\frac{R_4 // \frac{1}{j\omega C}}{R_3} = -\frac{R_4 (\frac{1}{j\omega C})}{R_3 (R_4 + \frac{1}{j\omega C})} = -\frac{R_4}{R_3} \frac{1}{(1 + j\omega CR_4)}$$

b


$$\frac{V_o}{V_i} = \frac{V_o}{V_x} \frac{V_x}{V_i} = \frac{R_2}{R_1} \frac{R_4}{R_3} \frac{1}{(1 + j\omega CR_4)} \frac{1}{(1 - j/\omega CR_1)}$$

$$\omega_1 = \frac{1}{CR_1} = \frac{1}{10n(10k)} = 10 \text{krad/s}$$

$$\omega_2 = \frac{1}{CR_4} = \frac{1}{10n(1k)} = 100 \text{krad/s}$$

$$|G_1| = \left| \frac{R_2}{R_1} \right| = \frac{100k}{10k} = 10 \quad 20 \log 10 = 20 \text{dB}$$

$$|G_2| = \left| \frac{R_4}{R_3} \right| = \frac{1k}{1k} = 1$$

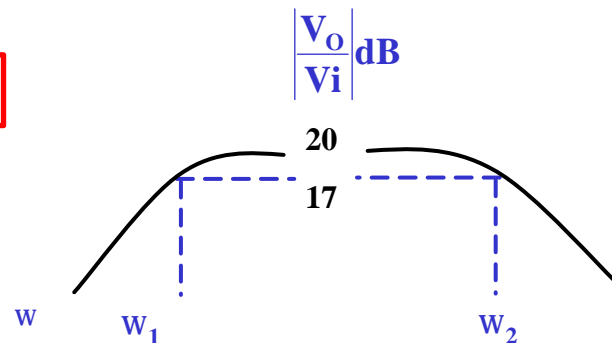c**d**

Circuit is a band pass filter

6

(41)

a

Model of zener diode

b




 V_s in terms of I_Z

$$\therefore \frac{V_s - V_Z}{R_s} = \frac{V_Z}{R_1} + I_Z$$

$$\therefore \frac{V_s}{R_s} = V_Z \left(\frac{1}{R_1} + \frac{1}{R_s} \right) + I_Z = (V_{ZK} + I_Z r_Z) \left(\frac{1}{R_1} + \frac{1}{R_s} \right) + I_Z$$

$$\therefore V_s = (V_{ZK} + I_Z r_Z) \left(\frac{R_s}{R_1} + 1 \right) + I_Z R_s$$
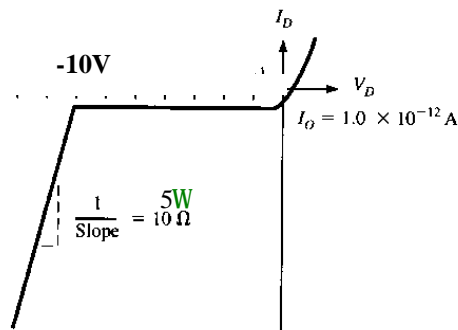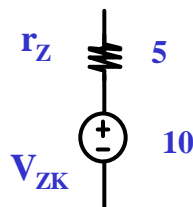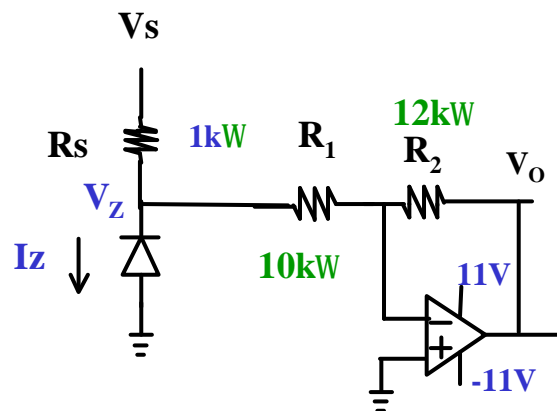
$$= (10 + I_Z 5) \left(\frac{1k}{10k} + 1 \right) + I_Z 1k = 11 + I_Z (1005.5)$$



c

 $V_Z = -0.5V$ Zener is a on diode

$$\therefore I_Z = -I_0 \exp\left(\frac{V_Z}{25m}\right) = -(1p) \exp\left(\frac{700}{25}\right) = -0.49mA$$

d (i)

 $V_s = 10V$ Zener is not breakdown and is an off diode (open)

$$\therefore V_o = -\frac{R_2}{R_1 + R_s} V_s = -\frac{12k}{10k + 1k} 10 = -10.91V$$

d (ii)

 $V_s = 25V$ Zener is breakdown

$$\begin{aligned} \therefore V_Z &= V_{ZK} + I_Z r_Z = 10 + I_Z (5) \\ &= 10 + \frac{V_s - 11}{1005.5} (5) = 10 + \frac{25 - 11}{1005.5} (5) = 10.07V \end{aligned}$$

$$\therefore V_o = -\frac{R_2}{R_1} V_Z = -\frac{12k}{10k} (10.07) = -12.1V \approx -11V$$

6. In the ideal op amp circuit, the diode has the reverse characteristics as shown. The diode equation is .

$$I_D = I_0 \exp \frac{V_D}{25mV}$$


- (a) Sketch the model of the diode at breakdown.
 (b) When diode is at breakdown, find V_s in terms of I_Z only.
 (c) Find I_Z if $V_Z = -0.5V$.
 (d) Find the output voltage V_o if $V_s =$ (i) $10V$, (ii) $25V$. (41)

7

(30)


a

9V
0
-9V

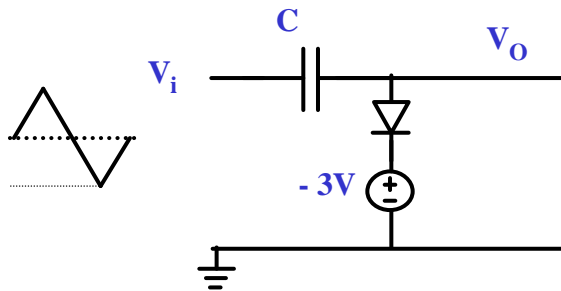

$$V_o = V_i + V_c = V_i - 12$$



-3V
Vo
-21V

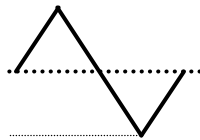

7. In the ideal diode circuit, sketch $V_o(t)$. Show clearly the voltages in your sketch. (12)

(b) In the ideal diode circuit, plot V_o versus V_i for $0V \leq V_i \leq 35V$. Show clearly all voltages in your sketch. (18)

b

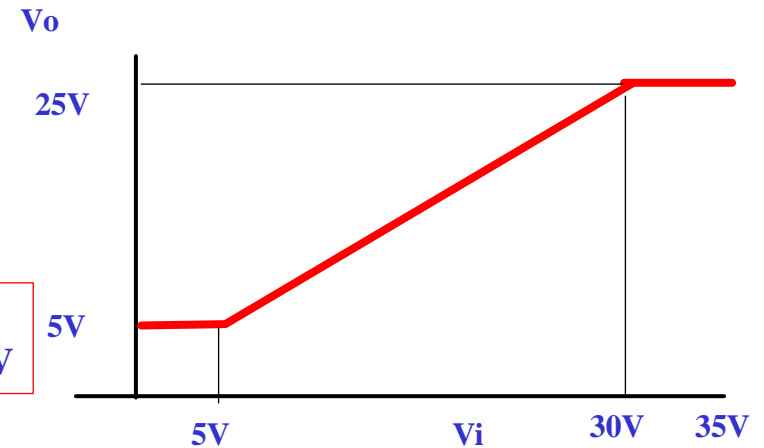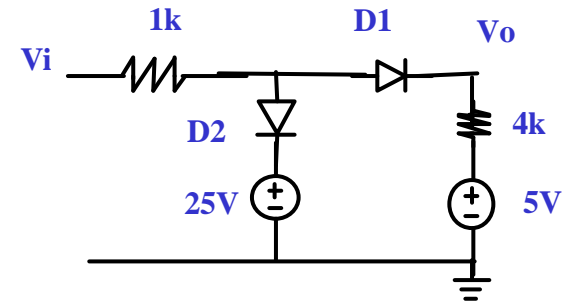

$V_i < 5V$, D1 and D2 OFF, $V_o = 5V$


$V_i > 5V$, D1 ON,
 $V_o = 5 + I(4k)$
 $= 5 + (V_i - 5)4k/(4k + 1k)$
 $= 5 + (V_i - 5)4/5$
 $V_i = 30, V_o = 5 + 25*4/5 = 25$

$V_i = 30V, V_o = 25, D2$
 ON, V_o is fixed at 25V

8

(20)

a

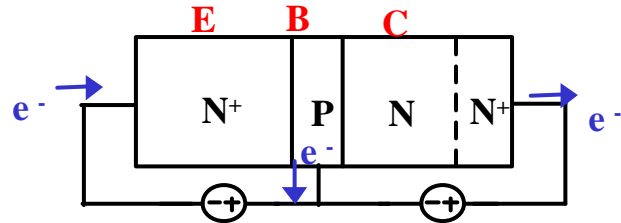

1. EB Junction is a forward (on) diode and BC is reverse (off) diode
2. E is made very heavily doped (N^+ for NPN)
Hence I_E mainly are electrons diffusing from E to B.
3. But B is made very thin and has a wide depletion region near C.
4. Hence most electrons will arrive C.

$$I_C \gg \alpha_F I_E$$

$$\text{Since } I_E = I_B + I_C$$


$$\text{Hence } I_C \gg \beta_F I_B, \quad \text{where } \beta_F = \frac{\alpha_F}{1 - \alpha_F}$$

8. (a) Sketch the cross section of a NPN transistor operated in the active region, describe the movement of electrons and explain briefly why $I_C \sim \alpha I_E$ and $I_C \sim \beta I_B$.
(b) Sketch the cross section of an enhancement NMOSFET, describe the movement of electrons and the change of the channel, and explain the linear and saturation regions. (20)

b

Cut-off


$$V_{GS} < V_T$$

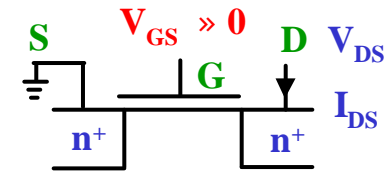

triode



$$V_{GS} \geq V_T$$

$$V_{DS} \ll V_{GS} - V_T$$

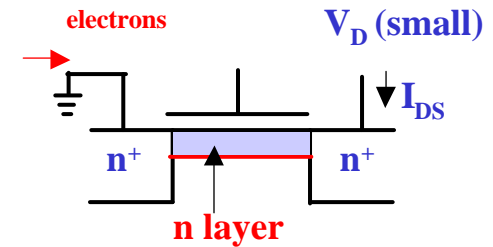


saturation

$$V_{DS} \geq V_{GS} - V_T$$

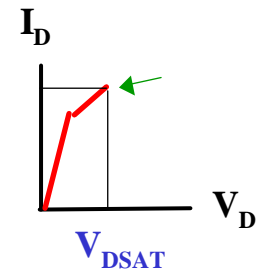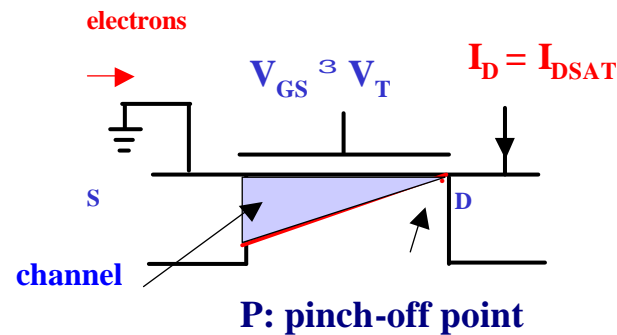


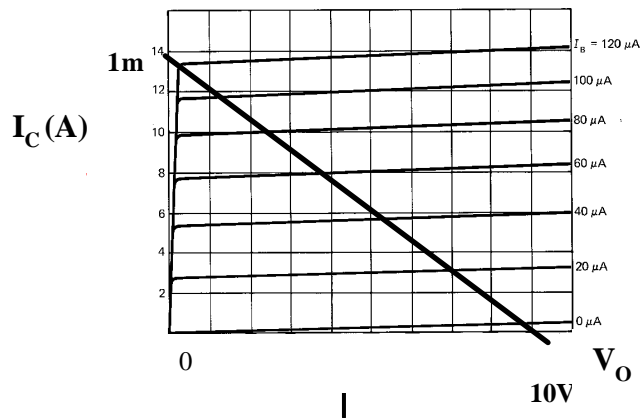9. The BJT amplifier has the output characteristic curves and DC load line as shown. (a) Assume $I_C \sim I_E$, write the load line equation, find V_{CC} and show that $R_C = 5k\Omega$. (b). If the amplifier is to have maximum symmetrical output, find the value of the Q-point and sketch the Q point on the load line. (c) At the Q-point in (b), find the value of R_1 if $R_2 = 10k\Omega$. You can assume $I_B \sim 0$ in your calculation. (d) Sketch the AC equivalent circuit and find the voltage gain $A_v (= \Delta V_o / \Delta V_{in})$ of the amplifier. Given that for the BJT, $V_{BE} = 0.7V$, $r_\pi = 5k\Omega$, $r_o = \infty$, $\beta = 100$. (44)



9

(44)

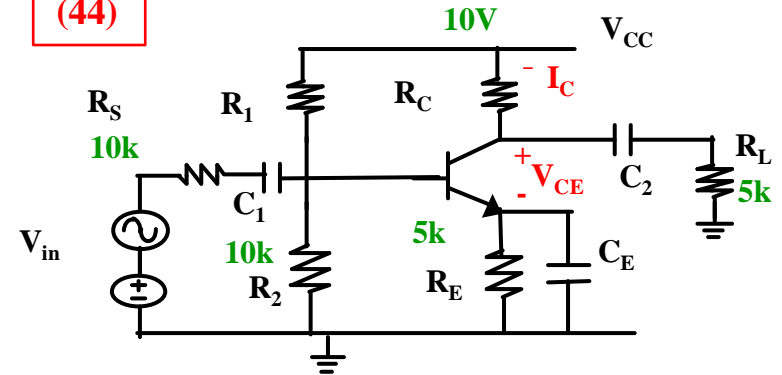

Given $I_C = 0.5mA$, $\beta = 100$, $V_{BE} = 0.7V$, $r_\pi = 5k$

a

Find R_C

$$\setminus V_{CC} \gg V_{CE} + I_C R_C + I_E R_E = 10$$

Since $I_C \sim I_E = 1mA$ when $V_{CE} = 0$

$$\setminus R_C = \frac{V_{CC}}{I_C} - R_E = \frac{10}{1m} - 5k = 5kW$$

9

b

Q-point at middle of load line :
 $I_C \sim 0.5\text{mA}$, $V_{CE} \sim 5\text{V}$

c

$$\searrow V_B = V_{BE} + I_B R_B + I_E R_E$$

$$\searrow V_{CC} \frac{R_2}{R_1 + R_2} = 0.7 + \frac{I_C}{b} \frac{R_1 R_2}{R_1 + R_2} + 0.5\text{m}(5\text{k})$$

$$\searrow 10 \frac{R_2}{R_1 + R_2} = 0.7 + \frac{0.5\text{m}}{100} \frac{R_1 R_2}{R_1 + R_2} + 0.5\text{m}(5\text{k})$$

$$\searrow 10R_2 = 0.7(R_1 + R_2) + 5\text{m}(R_1 R_2) + 2.5(R_1 + R_2)$$


$$\searrow R_2(10 - 0.7 - 2.5) = R_1(0.7 + 2.5) + 5\text{m}R_1 R_2$$

$$\searrow R_1 = \frac{R_2(6.8)}{3.2 + 5\text{m}R_2} = \frac{10\text{k}(6.8)}{3.2 + 5\text{m}10\text{k}} = 21\text{k}\Omega$$

d

$$\searrow R_B = 10\text{k} // 21\text{k} = 6.78\text{k}\Omega$$
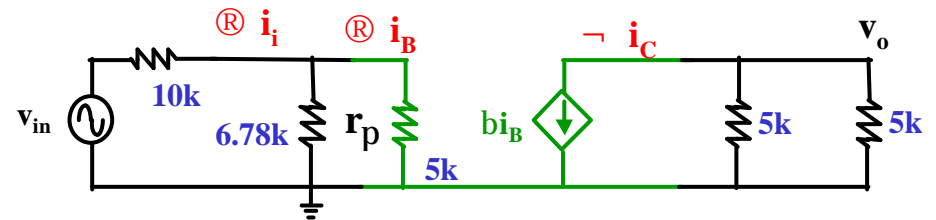
$$\searrow i_i = \frac{i_B r_p}{r_p // R_B} = i_B \frac{5\text{k}}{5\text{k} // 6.78\text{k}} = i_B \frac{5\text{k}}{2.88\text{k}} = 1.74 i_B$$



voltage gain

$$\begin{aligned} A_v &= \frac{v_o}{v_{in}} = \frac{-b i_B (R_C // R_L)}{i_B r_p + i_i R_S} \\ &= \frac{-b i_B (5\text{k} // 5\text{k})}{i_B 5\text{k} + 1.74 i_B 10\text{k}} \\ &= \frac{-100 (2.5\text{k})}{22.4\text{k}} = -11.16 \end{aligned}$$


10. Using the same BJT circuit in question (9),
(a) Explain briefly why the circuit can have stable I_C .
(b) Explain briefly the importance of having a stable Q-point.
Explain also briefly the difference between normal β and forced β .
(18)

10

a

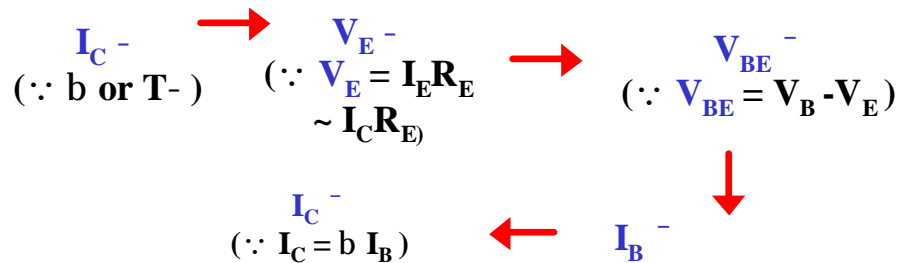(18)

Circuit can maintain stable I_C (Q-point).



b


Stable Q-point can maintain stable output

Forced beta is dI_C / dI_B at saturation region
Beta is dI_C / dI_B at active region

11

(30)

Given
 $V_T = 1V$
 $K = 0.02mA/V^2$

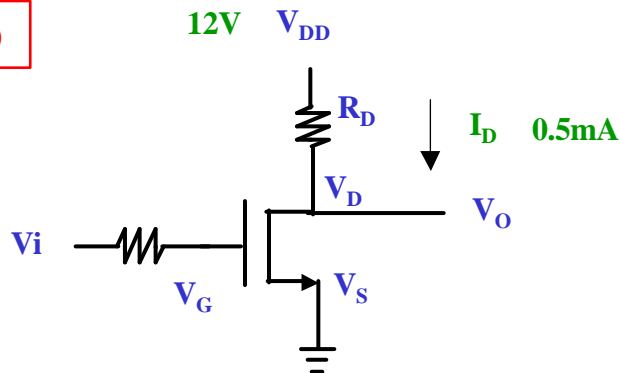

1

Find R_D such that $V_i = V_O$

When $V_i = V_O$,
 i.e. $V_{GS} = V_{DS}$
 NMOS is saturate

$$\therefore I_{DS} = K (V_{GS} - V_T)^2 = 0.02m(V_{GS} - 1)^2 = 0.5mA$$

$$\therefore V_{GS} = \sqrt{\frac{0.5m}{0.02m}} + 1 = 6V$$

$$\therefore V_{DD} = I_{DS}R_D + V_{DS}$$

$$\therefore R_D = \frac{V_{DD} - V_{DS}}{I_{DS}} = \frac{12 - 6}{0.5m} = 12kW$$

2

Find V_O such that $V_i = V_{DD}$

When $V_i = V_{DD}$
 i.e. $V_{GS} = 12V$,
 hence $V_{GS} - V_T > V_{DS}$ and NMOS is in triode mode

$$\begin{aligned} I_{DS} &= 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}] \\ &= 2(0.02m)[(12 - 1)V_{DS} - \frac{V_{DS}^2}{2}] \end{aligned}$$

$$\therefore I_{DS} = \frac{V_{DD} - V_{DS}}{R_D} = \frac{12 - V_{DS}}{12.5k} = 0.04m(11V_{DS} - \frac{V_{DS}^2}{2})$$

$$\therefore 12 - V_{DS} = 0.5[11V_{DS} - \frac{V_{DS}^2}{2}]$$

$$\therefore 12 - 6.5V_{DS} + 0.25V_{DS}^2 = 0$$

$$\therefore V_{DS}^2 - 26V_{DS} + 48 = 0$$


$$\therefore V_{DS} = 24V \quad \text{or} \quad 2V$$

hence $V_O = V_{DS} = 2V$
 $(V_O = 24V > V_{DS} \text{ is impossible})$

12

(20)

Given
 $V_T = 1V$
 $K = 0.02mA/V^2$

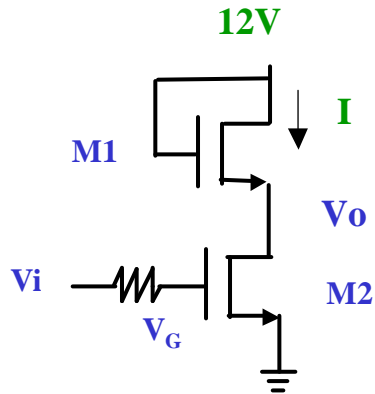

Find the maximum V_i such that M2 still operates in saturation region

1

M1 is also saturate, since

$$\begin{aligned} V_{DS} &= V_{GS} \\ V_{DS} &> V_{GS} - V_T \end{aligned}$$

$$\setminus I_{DS} = K (V_{GS1} - V_T)^2 = K (V_{GS2} - V_T)^2$$

$$\setminus (V_{GS1} - V_T) = (V_{GS2} - V_T)$$

$$\setminus V_{GS1} = V_{GS2} = V_i$$

2

If M2 is saturate, then

$$V_{DS} \geq V_{GS} - V_T$$

When $V_i (= V_G)$ is maximum and M2 is still saturate, then

$$V_{DS} = V_{GS} - V_T$$

$$\setminus V_{DS2} = V_{GS2} - V_T$$

$$\setminus V_{DD} - V_{GS1} = V_{GS2} - V_T$$

$$\setminus V_{DD} + V_T = V_{GS2} + V_{GS1} = 2V_{GS2} = 2V_i$$

$$\setminus V_i = \frac{V_{DD} + V_T}{2} = \frac{12+1}{2} = 6.5V$$