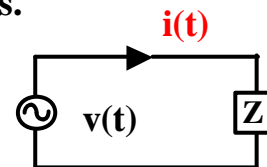



1. In the following circuit, $v(t) = 250 \cos(100t + 20^\circ) \text{ V}$, $i(t) = 10 \cos(100t + 40^\circ) \text{ A}$.
- (a) Sketch $v(t)$ and $i(t)$ together. Show clearly the phase angles and amplitudes. Does $v(t)$ lead $i(t)$?
- (b) If Z is two elements in series, find the two elements and the values.
- (c) Sketch impedance Z and phasors V , I in a complex plane. (23)



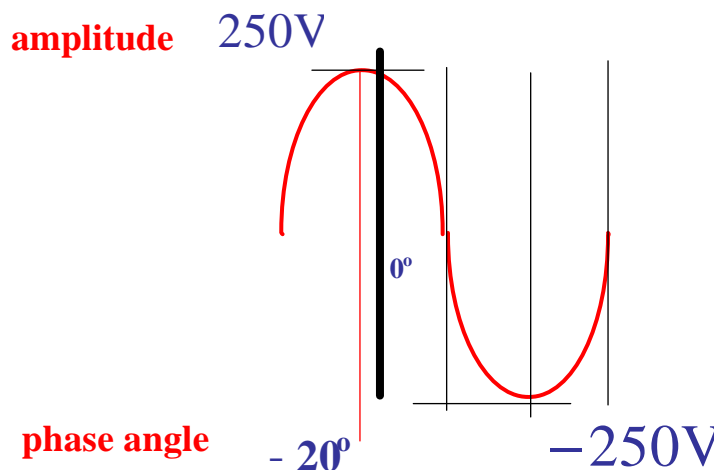
(a) Sketch $v(t)$ and $i(t)$ together.

Show clearly the phase angles and amplitudes.

$$v(t) = 250 \cos(100t + 20^\circ) \text{ V}$$


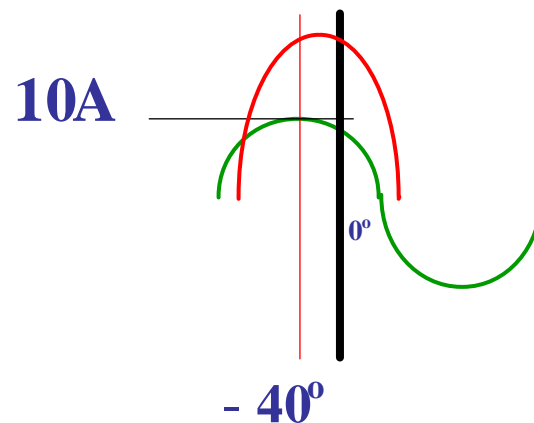
$$i(t) = 10 \cos(100t + 40^\circ) \text{ A}$$



$i(t)$ leads $v(t)$ by 20°

As $i(t)$ peak (10A) is at **left** side of $v(t)$ peak (250V)

(if at right side, then i lags v)

(b) If Z is two elements in series,
find the two elements and the values.

Find Z first, use complex method

Transform $v(t)$ into V phasor

$$v(t) = 250 \cos(100t + 20^\circ) \text{ V}$$

$$\Rightarrow V = 250 \angle 20^\circ \text{ V}$$

Frequency NOT included in phasor since
All current and voltage will have SAME frequency

$$\begin{aligned} \therefore Z &= \frac{V}{I} = \frac{250 \angle 20^\circ \text{ V}}{10 \angle 40^\circ \text{ A}} \\ &= \frac{250 \text{ V}}{10 \text{ A}} \angle (20^\circ - 40^\circ) \\ &= 25 \angle -20^\circ \text{ ohm} \end{aligned}$$

Using Euler equation

$$\begin{aligned} \therefore Z &= 25 [\cos(-20^\circ) + j\sin(-20^\circ)] \text{ ohm} \\ &= 23.5 - j8.55 \text{ ohm} \end{aligned}$$

Hence Z is C in series with R

$$\begin{aligned} \therefore Z &= R + \frac{1}{jC(2\pi f)} = R - \frac{j}{(2\pi f)C} \\ \frac{1}{j} &= -j \quad jj = -1 \end{aligned}$$

Equate real and j part

$$\therefore R = 23.5 \text{ ohm}$$

$$\therefore 8.55 = \frac{1}{(2\pi f)C}$$

$$\therefore C = \frac{1}{100(8.55)} = 1.17 \text{ mF}$$

Hence Z is 1.17mF in series with 23.5 ohm

(similarly if $Z = 25 \angle 20^\circ \text{ ohm}$

then Z is 23.5 ohm in series with 8.55 ohm L)


by complex method

Transform L into $j \omega L$

Transform C into $1 / j \omega C$


For example

If $L = 10\text{mH}$

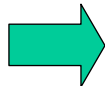

$$\begin{aligned}\text{Then } X_L &= j \omega L \\ &= j (100) 10\text{mH} \\ &= j \text{ ohm}\end{aligned}$$

$C = 1\text{mF}$

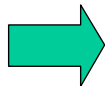


$$\begin{aligned}\text{Then } X_C &= 1 / j \omega C \\ &= 1 / j (100) 1\text{mF} \\ &= -j10 \text{ ohm}\end{aligned}$$

X_L : reactance of L


X_C : reactance of C

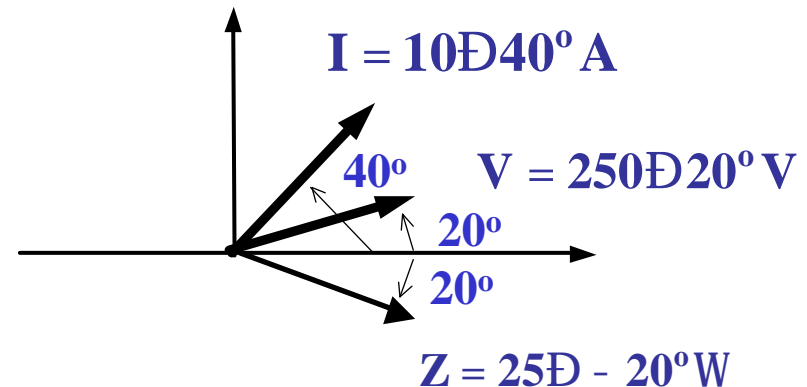Sketch impedance Z and phasors V , I in a **complex plane**
or **phasor diagram**



2

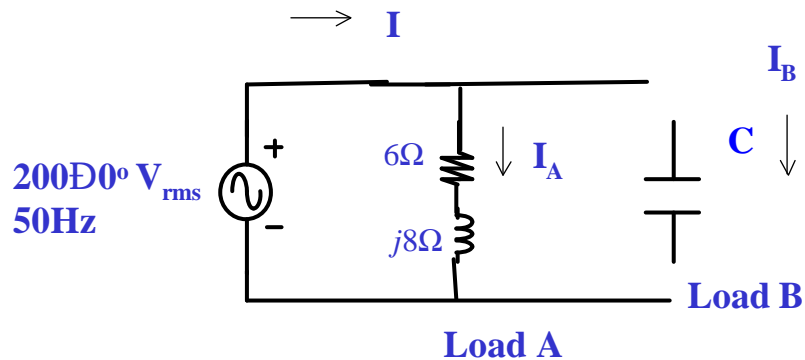2. An industrial load A is connected in parallel to a 200 V_{rms}, 50Hz power supply. Load A is composed of 6Ω in series with j8 Ω. (a) Find the complex current flowing in load A I_A . Find also the average power P, reactive power Q, apparent power S, and power factor PF supplied by the power supply. (b) If a load B is connected in parallel to load A to make the total power factor = 1, find the element and value of load B. (c) When PF = 1, find the current delivered by the 200V supply (I_S , in rms) and the current in load B (I_B , in rms). (d) Hence plot I_S , I_B , and I_A in a phasor diagram. [40]



Find the **complex current** flowing in load A I_A

For load A

$$\begin{aligned}
 \therefore I_A &= \frac{V}{Z} \\
 &= \frac{200\angle 0^\circ \text{ V}_{\text{rms}}}{6 + j8 \text{ ohm}} \\
 &= \frac{200\angle 0^\circ \text{ V}_{\text{rms}}}{\sqrt{6^2 + 8^2} \angle \tan^{-1} 8/6} \\
 &= \frac{200\angle 0^\circ \text{ V}_{\text{rms}}}{10\angle 53.1^\circ \text{ ohm}} \\
 &= 20\angle -53.1^\circ \text{ A}_{\text{rms}}
 \end{aligned}$$

Find also the average power P , reactive power Q , apparent power S , and power factor PF of load A supplied by the power supply.

Load A is R in series with L , same I , use $P = I^2 R$, I in rms

If parallel load, same V , use $P = V^2/R$, V in rms

$$\therefore P = I^2 R = 20^2 * 6 = 2400W$$


$$\therefore Q = I^2 \omega L = 20^2 * 8 = 3200VAR$$

$$\therefore S = \sqrt{P^2 + Q^2} = 4000VA$$


$$\therefore PF = \cos \theta_z = \cos 53.1^\circ = 0.6 \text{ lagging}$$

In L , I lags V

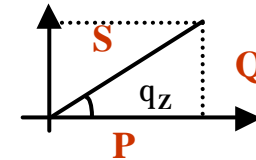Can remember equations using **power triangle**



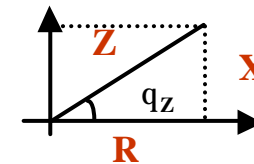power triangle is similar to **impedance triangle**



If a load B is connected in **parallel** to load A to make the **total power factor = 1**, find the element and value of load B.

Q is 3200 VAR, Q is QL

Hence QC of 3200 VAR is required to cancel the QL
(such that NET Q = 0)

$$\therefore Q_C = \frac{V^2}{1/C\omega}$$

$$\therefore C = \frac{Q_C}{V^2\omega} = \frac{3200}{200^2(2\pi 50)} = 0.255\text{mF}$$

Hence load B is a 0.255 mF capacitor

When PF = 1, find the current delivered by the 200V supply (I_S , in rms) and the current in load B (I_B , in rms).

$$\therefore I_B = \frac{V}{1/C\omega} = VC\omega = 200(2\pi 50 * 0.255\text{m}) = 16\text{A}_{\text{rms}}$$


Hence current in load B is 16 A rms

When $PF = 1$, net Q of load A and load $B = 0$

$S = P$ of combined load = $2400VA$


$$\therefore I_s = \frac{S}{V} = \frac{2400VA}{200V} = 12A_{rms}$$

Hence source current is $12A$ rms

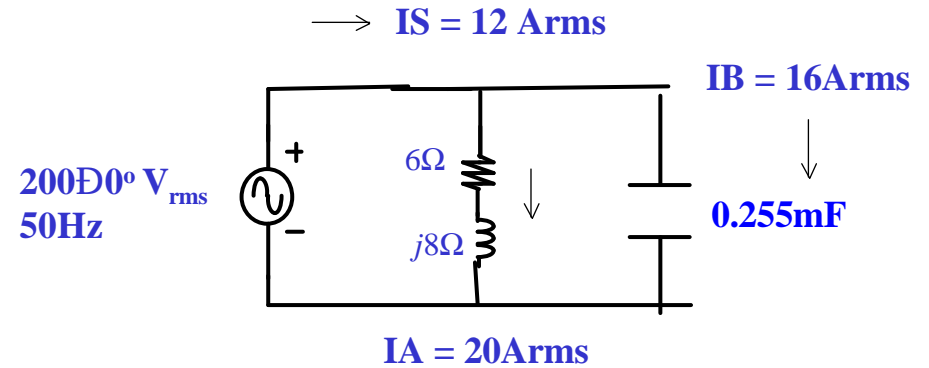

Hence plot I_s , I_B , and I_A in a phasor diagram


In C , I **leads** V by 90°

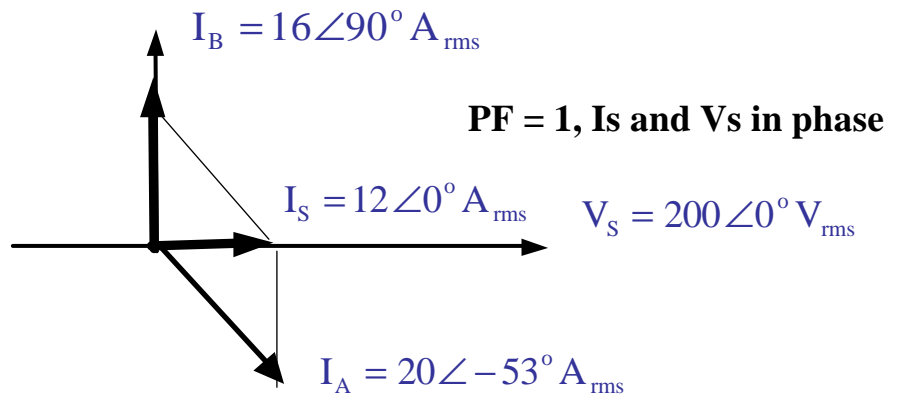

5. (a) Sketch the equivalent circuit of an ideal voltage amplifier. What are the values of the input and output resistances.

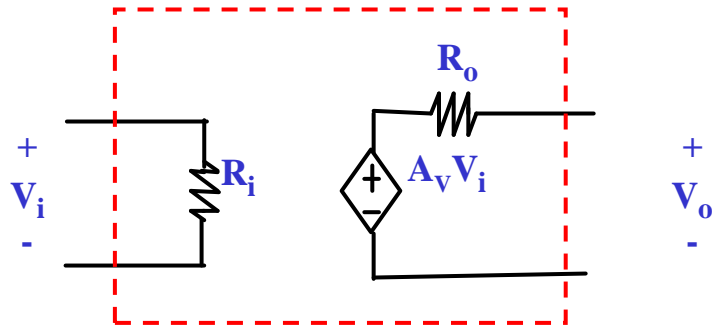(b) In the following ideal op amp circuit, find V_o when $V_i = 2V$. (26)

Sketch the equivalent circuit of an ideal voltage amplifier.



For ideal V amplifier,


input resistance :

$$R_i = \infty$$

output resistance :


$$R_o = 0$$

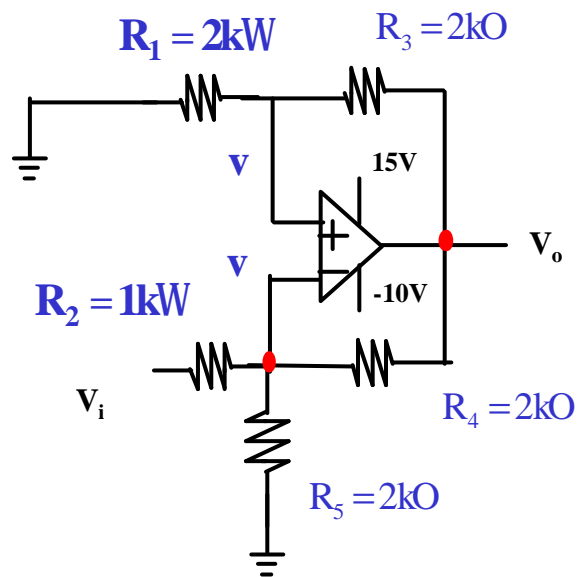In the following ideal op amp circuit, find V_o when $V_i = 2V$.



ideal op amp


$V_i = 0$ (virtual short)

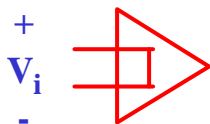

$$\therefore V_- = V_+ = v$$

$$\therefore V_+ = V_o \frac{2k}{2k + 2k} = \frac{V_o}{2} = v = V_-$$

$I_i = 0$ (virtual open)

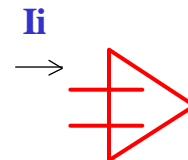

KCL

$$\therefore \frac{V_i - v}{1k} = \frac{v}{2k} + \frac{v - V_o}{2k}$$
$$\therefore 2V_i - 2v = v + v - V_o$$
$$\therefore 2V_i = 4v - V_o = V_o$$

$$\therefore v = \frac{V_o}{2}$$

$$\therefore A_v = \frac{V_o}{V_i} = \frac{2V_i}{V_i} = 2$$

If $V_i = 2V$, $V_o = 4V$

2

$$\therefore P = I^2 R \cong \left(\frac{10A}{\sqrt{2}}\right)^2 * 23.5\Omega = 1175W$$

$$\therefore Q = I^2 \frac{1}{\omega C} \cong \left(\frac{10A}{\sqrt{2}}\right)^2 * 8.55\Omega = 427.5VAR(C)$$

$$\therefore S = \sqrt{P^2 + Q^2} = \sqrt{1175^2 + 427.5^2} = 1250VA$$

$$\backslash PF = \cos(-20^\circ) = 0.94 \text{ leading}$$

P = real (or average) power dissipated by load Z

S = power supplied by source to load Z

Q = maximum reactive power stored in Z

Connect L in parallel to improve PF = 1

$$\backslash L = \frac{V^2}{\omega_o Q} = \frac{(250/\sqrt{2})^2}{100(427.53)} = 0.73H$$

**When L is connected (PF = 1),
S = P = 1174.62VA, hence**

$$\backslash I = \frac{S}{V} = \frac{1174.62}{250/\sqrt{2}} = 4.7\sqrt{2} \text{ Arms}$$

If V is 500V (2x of original V)

I is 2x of original I

but R and C are unchanged

hence P and Q ($\propto I^2$) are 4x of original P and Q

Hence new L $\propto V^2 / Q$ = original L = 0.73H

2. Using the same circuit in question (1),


(a) find the apparent power S, reactive power Q, average power P and power factor PF of load Z.

(b) What are the physical meanings of S, P, Q?

(c) A load B is now connected in parallel to Z to make the total power factor = 1. Find the load B and the value. Find also the current (in rms) supplied by v(t) when PF is 1.

(d) If v(t) is now changed to $500 \cos(100t + 20^\circ) V$, find the new load B required.

(31)

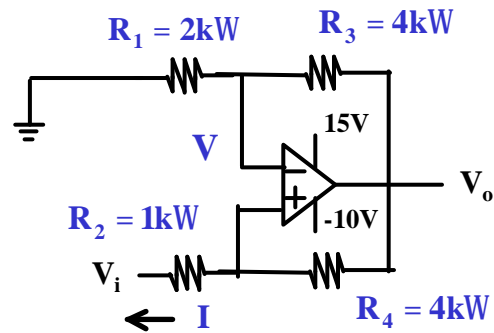

5. (d) In the following circuit, assume ideal op amp, (i) find V_o if $V_i = 3V$, (ii) find I if $V_i = -1V$. (40)

$$\because V_- = V_+ = V$$

$$\searrow V_- = V_o \frac{2k}{2k + 4k} = \frac{V_o}{3}$$

$$\searrow \frac{V_i - V}{1k} = \frac{V - V_o}{4k}$$

$$\searrow 4V_i - 4V = V - V_o \quad \searrow 4V_i = \frac{2}{3} V_o$$

$$\searrow A_v = \frac{V_o}{V_i} = 6$$

$$\text{If } V_i = 3V, \quad V_o = 15V$$

$$\text{If } V_i = -1V, \quad V_o = -6V$$

$$\searrow I = \frac{V_o - V_i}{5k} = \frac{-6 - (-1)}{5k} = -1mA$$