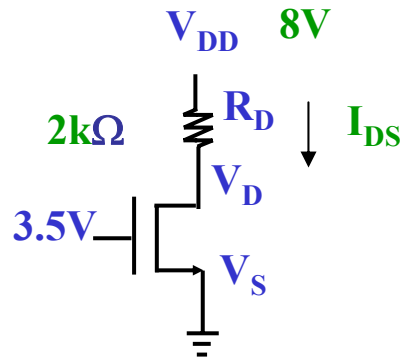


2

Given  $V_T = 1V$   
 $K = 0.25mA/V^2$



Find  $V_{DS}$  and  $I_{DS}$  for  $V_G = 3.5V$

If MOS is in **saturation mode**

$$\therefore I_{DS} = K (V_{GS} - V_T)^2 = 0.25m(3.5 - 1)^2 = 1.5625mA$$

$$\begin{aligned}\therefore V_{DS} &= V_{DD} - I_{DS} R_D \\ &= 8V - 1.5625mA * 2k\Omega \cong 4.875V\end{aligned}$$


**NMOS in saturation is confirmed since**

1.  $V_{GS} = 3.5V > V_T$
2.  $V_{DS} = 4.875V > V_{GS} - V_T$

4

(18)

Given  
 $V_T = 1V$   
 $K = 0.25mA/V^2$

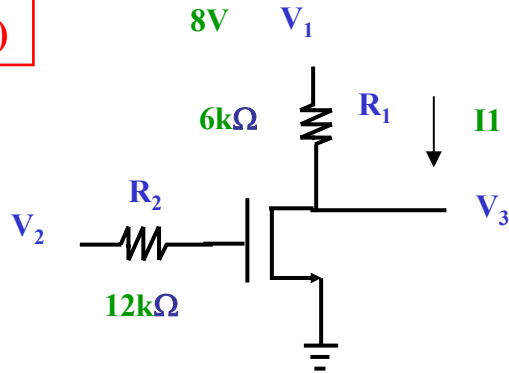

a

If  $V_2 = 0.5V$ 

$$V_{GS} < V_T \quad 0.5 < 1 \quad \text{NMOS cut off}$$

$$\therefore I_1 = 0 \quad \therefore V_3 = 8V$$

b

If  $V_2 = 3V$ 

Assume NMOS is in saturation

$$\therefore I_1 = K (V_{GS} - V_T)^2 = 0.25m(3-1)^2 = 1mA$$


$$\therefore V_3 = 8 - I_1 R_1 = 8 - 1m(6k) = 2V$$

NMOS in saturation is confirmed since

1.  $3 > 1$
2.  $2 = 3 - 1$

NMOS is saturated since

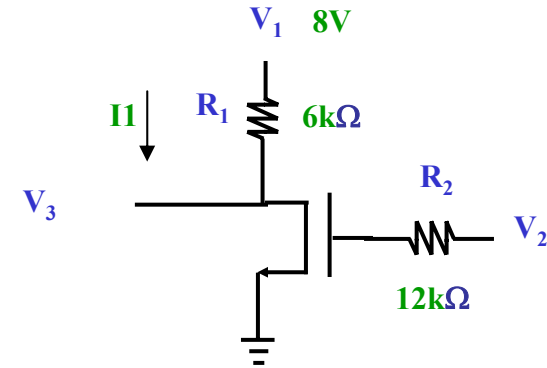1.  $V_{GS} > V_T$
2.  $V_{DS} = V_{GS} - V_T$



4. (a) If  $V_2 = 0.5V$ , find  $I_1$  and  $V_3$ . (b) If  $V_2 = 2V$ , find  $I_1$  and  $V_3$ . State clearly the reasons for your answer.

Given  $V_T = 1V$ ,  $K = 0.25mA/V^2$ .

Given that

at triode region,  $I_{DS} = 2K[(V_{GS} - V_T)V_{DS} - V_{DS}^2/2]$

at saturation region,  $I_{DS} = K[(V_{GS} - V_T)^2]$  (19).


5

(26)

Given

$$V_T = 1V$$

$$K = 0.5mA/V^2$$

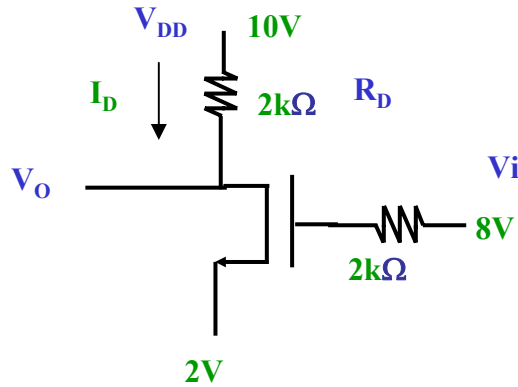

$$\begin{aligned}\therefore I_D &= \frac{V_{DD} - V_{DS}}{R_D} = \frac{10 - V_{DS}}{2k} \\ &= 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}] = 1m[(8 - 2 - 1)V_{DS} - \frac{V_{DS}^2}{2}] \\ \therefore \frac{10 - V_{DS}}{2k} &= 1m[5V_{DS} - \frac{V_{DS}^2}{2}] \\ \therefore 10 - V_{DS} &= 2[5V_{DS} - \frac{V_{DS}^2}{2}] \\ \therefore V_{DS}^2 - 11V_{DS} + 10 &= 0 \\ \therefore V_{DS} &= 10V \quad \text{or} \quad 1V\end{aligned}$$

$$\text{hence } V_O = 3 + 1 = 4V$$

$V_O = 13V = V_{DD}$  is impossible since MOS is not cut off ( $V_{DGS} > V_T$ )

NMOS is in triode since

$$1. V_{GS} > V_T$$

$$2. V_{DS} < V_{GS} - V_T$$

NMOS is triode since

$$1. 6 > 1$$

$$2. 1 < 6 - 1$$

$$\begin{aligned}\therefore I_D &= 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}] \\ &= 1m[(6 - 1)1 - \frac{1}{2}] = 4.5mA\end{aligned}$$

5. In the circuit, find  $V_O$ . State clearly the reasons for your answer.

Given  $V_T = 1V$ ,  $K = 0.5mA/V^2$ .

Given that

at triode region,  $I_{DS} = 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}]$



at saturation region,  $I_{DS} = K[(V_{GS} - V_T)^2]$  (26).

8

8. A BJT with the following  $I_C$ - $V_{CE}$  characteristics is used in the following circuit. (a) Sketch the load line  $V_{CE} = V_{CC} - I_C R_C$  and the Q point on the graph.


(b) If  $v_{in} = 0.1 \cos \omega t$  V, sketch the base current  $I_B$ , the collector current  $I_C$  and the output voltage  $V_{out}$ . Show clearly the DC value, the maximum and minimum value in your sketch. Estimate also the current gain  $dI_C / dI_B$  and voltage gain  $dV_{out} / dV_{in}$ .

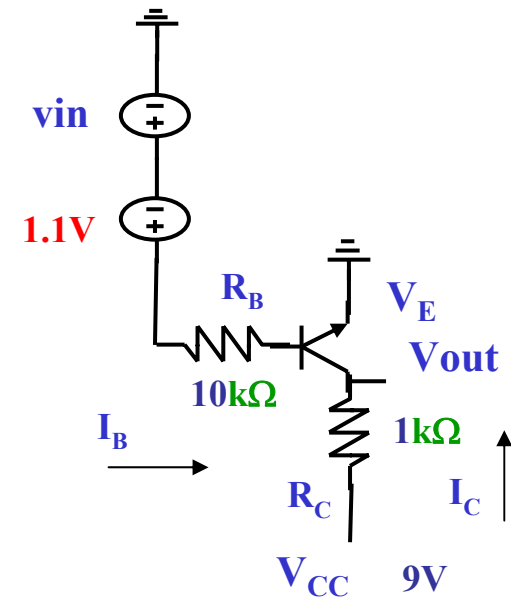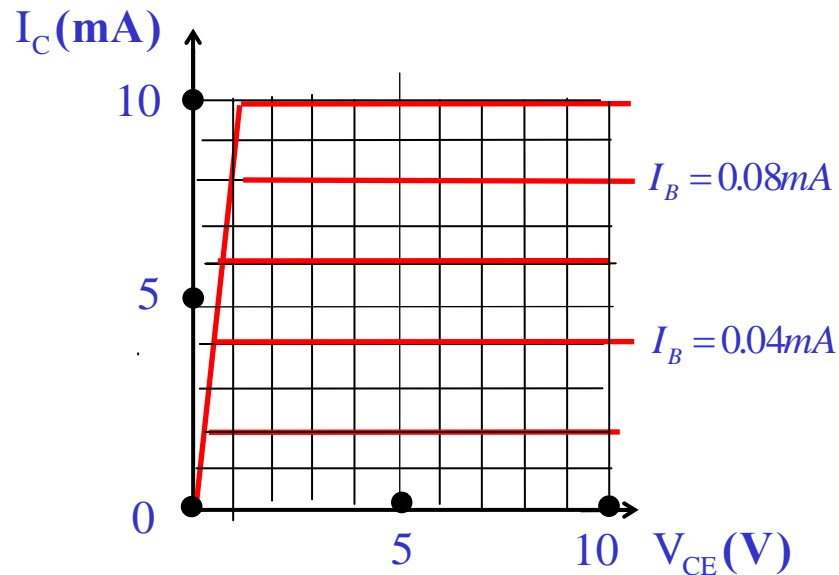(c) Sketch the small signal (AC) equivalent circuit of the amplifier and find the voltage gain  $A_v (= V_{out}/V_{in})$ . For the BJT, given  $r_{\pi} = 0\Omega$ ,  $V_{BE(ON)} = 0.7V$ . (49)




b

Find  $I_C$  from graph

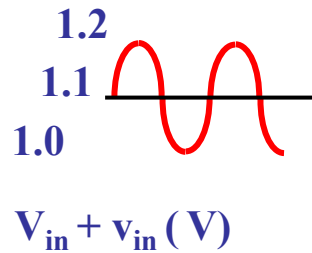


a

Find  $I_B$  from equation

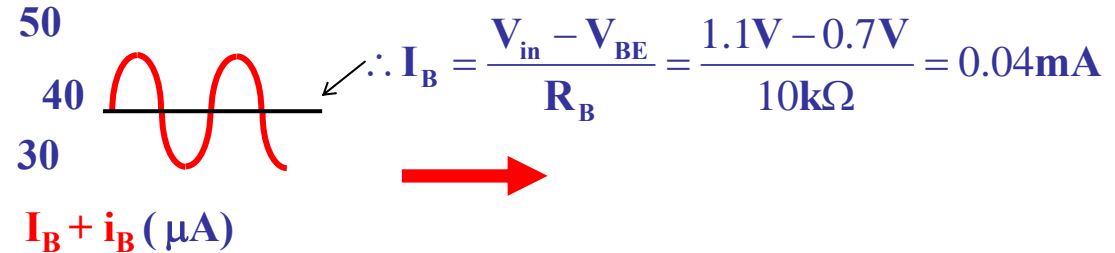


c

Find  $V_{CE}$  from graph

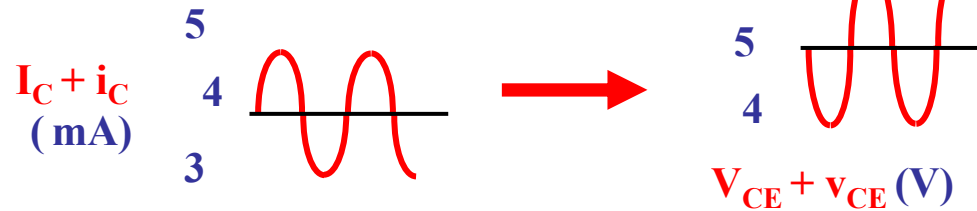

a

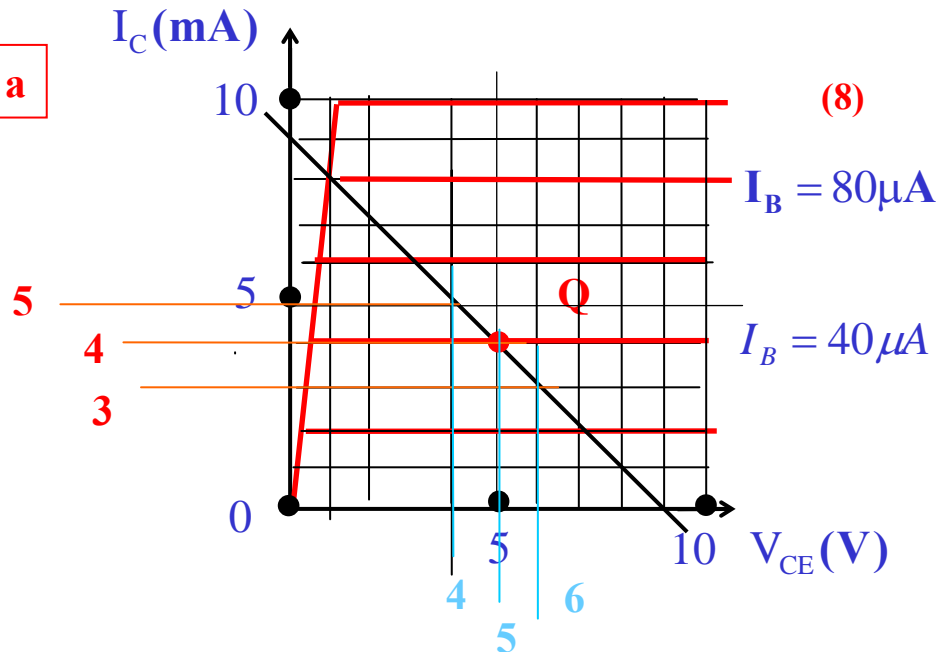


Estimate current and voltage gain

$$\therefore A_I = \beta_F = \frac{\Delta I_C}{\Delta I_B} \approx \frac{5m - 3m}{50\mu - 30\mu} = \frac{2mA}{20\mu A} = 100$$

$$\therefore A_V = \frac{\Delta V_{out}}{\Delta V_{in}} = \frac{6V - 4V}{1.0V - 1.2V} = \frac{2V}{-0.2V} = -10$$

c

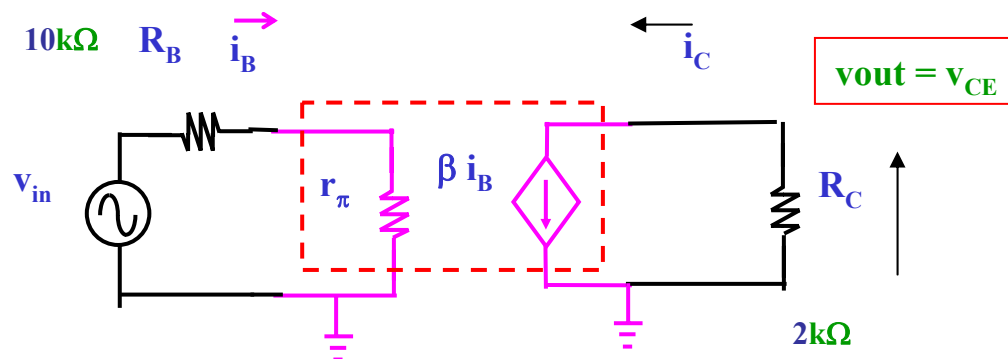

$$\therefore A_v = \frac{v_{out}}{v_{in}} = \frac{-\beta i_B R_C}{i_B (R_B + r_\pi)} = \frac{-\beta R_C}{R_B + r_\pi} = \frac{-(100)(1\text{k})}{10\text{k}} \cong -10$$


9

9. Given the BJT circuit.

Given that  $I_B$  is about 1.57mA. Show that the BJT is in saturation.

Hence show that the forced beta is about 2.7.

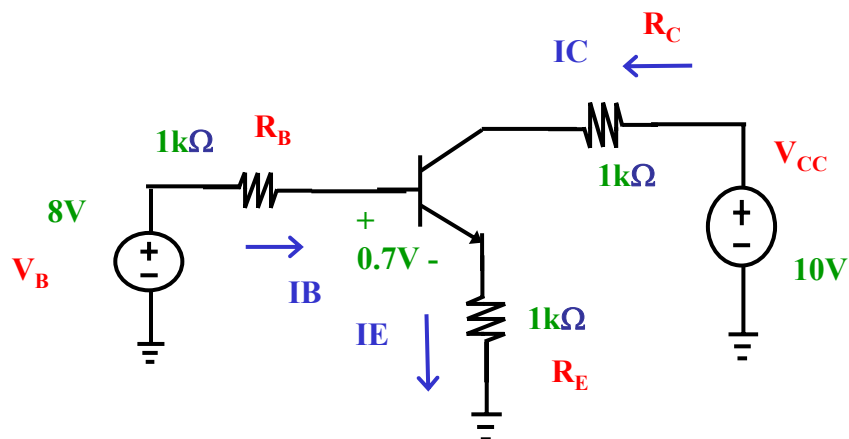For the BJT, given  $V_{BE} = 0.7V$ ,  $\beta = 100$ ,  $V_{CESAT} = 0.1V$ . (30)




$$\therefore I_C = \beta I_B = 100 * 1.57mA = 157mA$$

$$\gg I_C \text{ when } V_{CE} = 0V = \frac{10V}{2k\Omega} = 5mA$$

$\therefore$  BJT is in saturation

$$\therefore \frac{I_C}{I_B} = \beta^*$$

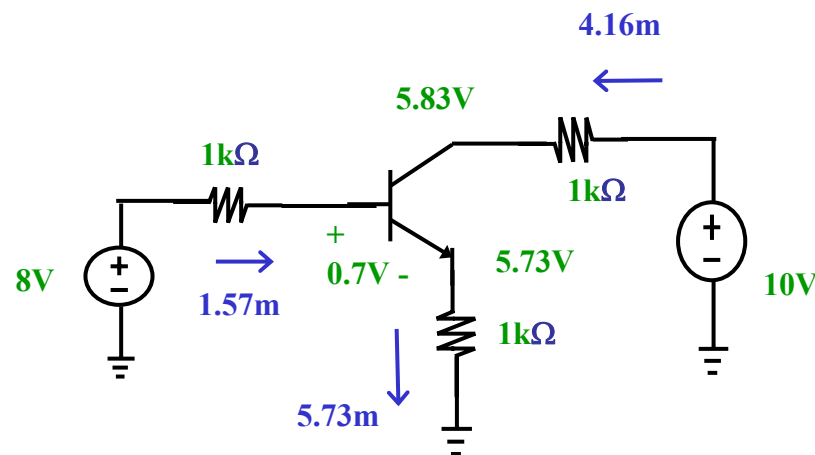

$$\therefore \frac{I_C}{I_B} = \beta^* = \frac{4.16m}{1.57m} \cong 2.65$$

or

$$\therefore I_B = \frac{V_B - V_{BE}}{R_B + (1 + \beta^*)R_E} = \frac{V_{CC} - V_{CESAT}}{\beta^* R_C + (1 + \beta^*)R_E}$$

$$\therefore I_B = \frac{8 - 0.7}{1k + (1 + \beta^*)1k} = \frac{10 - 0.1}{1k(1 + 2\beta^*)}$$



$$\therefore 7.3(1 + 2\beta^*) = 9.9(1 + \beta^*)$$

$$\therefore 14.6\beta^* + 7.3 = 9.9\beta^* + 9.9$$

$$\therefore \beta^* = \frac{9.9 - 7.3}{14.6 - 9.9} \cong 2.66$$


11

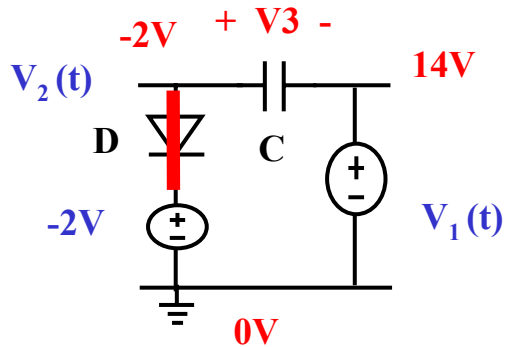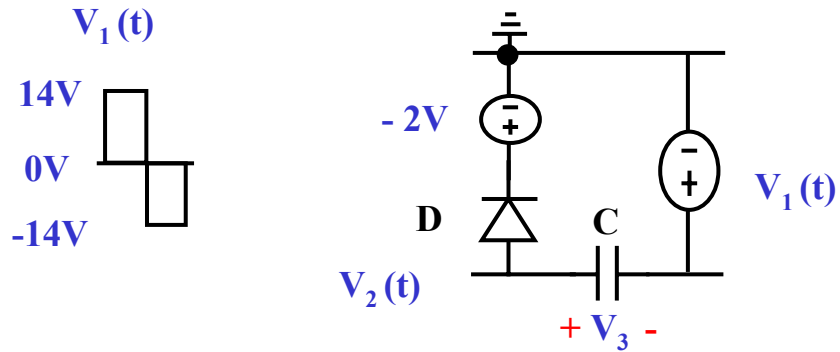11. (a) In the ideal diode circuit, find  $V_3$  and sketch  $V_2(t)$ . (15)



Hence  $V_3 = -16V$

Hence  $V_2 = V_1 + V_3 = V_1 - 16V$


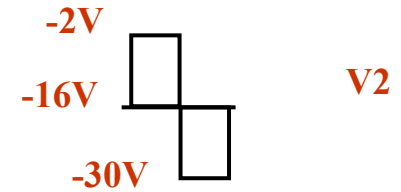




11

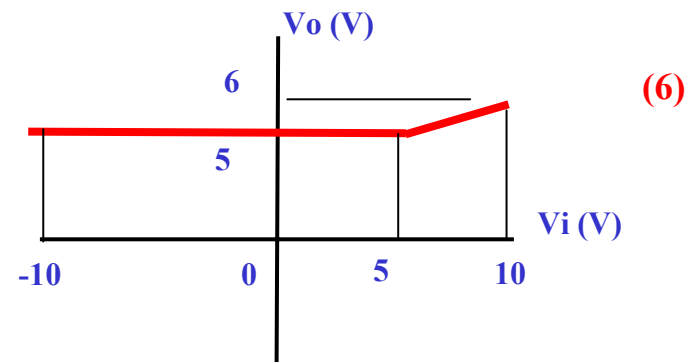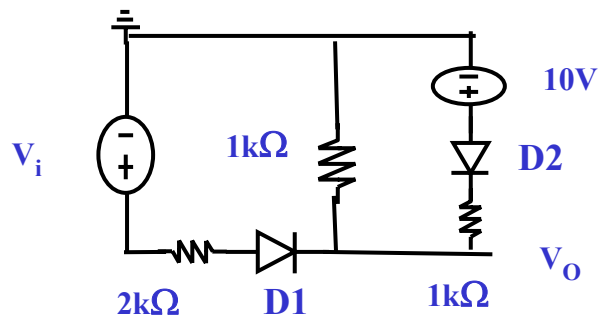(b) In the ideal diode circuit, plot  $V_o$  versus  $V_i$  for  $-10V \leq V_i \leq 10V$ .

Show clearly all voltages in your sketch. (20)



$V_i < 5V$ , D1 OFF and D2 ON

$\therefore V_o = 5V$

$V_i > 5V$ , D1 and D2 ON,

$$\therefore \frac{V_i - V_o}{2k} + \frac{10 - V_o}{1k} = \frac{V_o}{1k}$$


$$\therefore V_i - V_o + 20 - 2V_o = 2V_o$$

$$\therefore V_o = \frac{V_i + 20}{5}$$


12

12. In the diode circuit, the diode has the reverse characteristics as shown. The diode equation is  $I = I_o \exp [(V/25\text{mV}) - 1]$ .

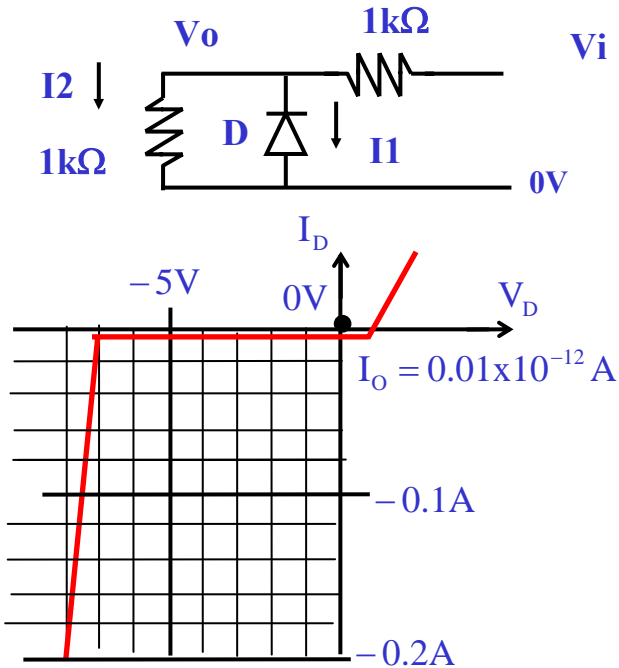- (a) Sketch the circuit model of the diode at breakdown.  
 (b) Find  $I_1$  if  $V_i = -1\text{V}$ .  
 (c) Find  $I_1$  if  $V_i = 2\text{V}$ .  
 (d) Find  $I_2$  if  $V_i = 16\text{V}$ . (35)



a

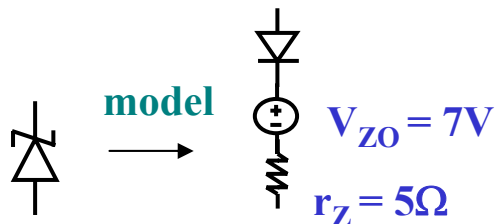

b

$$V_i = -1\text{V}, \therefore V_o = -0.5\text{V}$$

$$\therefore I_1 = -I_o \left( e^{\frac{0.5\text{V}}{25\text{mV}}} - 1 \right)$$

$$= -0.01 \times 10^{-12} \text{ A} \left( e^{\frac{500\text{m}}{25\text{m}}} - 1 \right) = -4.85 \times 10^{-6} \text{ A}$$

c

$$\therefore I_1 = I_o = 0.01 \times 10^{-12} \text{ A}$$

d

$$V_i = 16\text{V}, \therefore V_o = 8\text{V}, D \text{ breakdown}$$

$$\frac{16 - V_o}{1\text{k}} = \frac{V_o - 7}{5} + \frac{V_o}{1\text{k}}$$

$$16 - V_o = 200(V_o - 7) + V_o$$

$$V_o = \frac{1400 + 16}{202} \cong 7.01\text{V}$$

$$\therefore I_2 = \frac{V_o}{R_L} \cong \frac{7.01}{1\text{k}} = 7.01\text{mA}$$