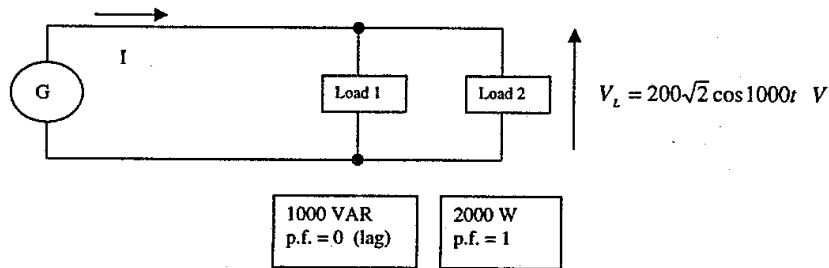


1. Referring to the following diagram :

- What are the elements of load 1 & load 2 ? (4 marks)
- Calculate their values. (9 marks)
- Calculate the total current I . (10 marks)
- Prove that the minimum size (in KVA) of the generator G is 2.24 KVA. (3 marks)
- Calculate the total power factor. (3 marks)
- The total power factor is improved to be unity when Load 3 is connected. Show the connection in the following figure. What is the reactive power of Load 3 ? (4 marks)
- After improving the power factor, an additional Load 4 is added. Show the connection in the following figure. What kind of this Load 4 is ? What is the max. power consumption of this Load 4 ? (5 marks)



$$\begin{aligned} \text{a) load 1 : } L & \quad 2 \\ \text{load 2 : } R & \quad 2 \end{aligned}$$

$$\text{b) } R = \frac{V^2}{P} = \frac{200^2}{2k} = 20 \Omega \quad 4$$

$$L = \frac{V^2}{Q_w} = \frac{200^2}{1k \cdot 1k} = 40 \text{ mH} \quad 5$$

$$\begin{aligned} \text{c) } I &= \frac{200}{40j} + \frac{200}{20} \quad 6 \\ &= 10 - 5j \\ &= \sqrt{125} \angle -0.5 \\ &= 11.2 \angle -26.6 \text{ A}_{\text{rms}} \quad 4 \end{aligned}$$


$$\text{d) } S = 200 (11.2) = 2240 \text{ VA} \quad 3$$

$$\text{e) } PF = \cos 26.6^\circ = 0.89 \quad 3$$

$$\text{f) } \begin{array}{c} \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \end{array} C \quad Q_C = -1k \text{ VAR} \quad 4$$

$$\begin{array}{c} \text{---} \\ | \\ \text{---} \\ | \\ \text{---} \end{array} R \quad \begin{aligned} P &= 2240 - 2k \\ &= 240 \text{ W} \end{aligned} \quad 5$$

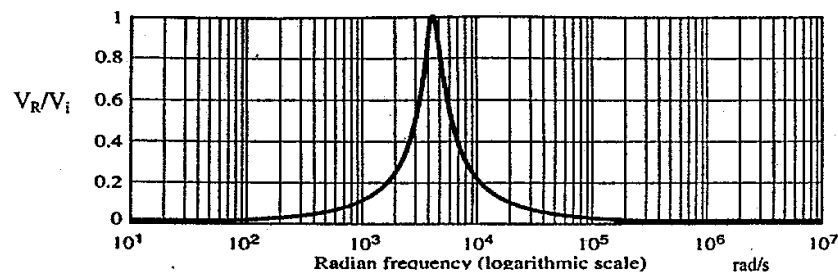2. A series RLC circuit has the following magnitude plot.



- Estimate the resonant frequency. (2 marks)
- Estimate the bandwidth. (2 marks)
- Estimate the lower cut-off and higher cut-off frequencies. (4 marks)
- Calculate the Q factor. (3 marks)
- Calculate the value of the inductor if the value of the resistor is $1 \text{ k}\Omega$. (4 marks)
- Calculate the value of the capacitor. (4 marks)
- Calculate the power consumption at resonance if the input voltage $V_i(t) = 10 \cos \omega t \text{ V}$. (5 marks)
- What is the ratio of V_c/V_i ? (2 marks)
- Calculate the resistance of another parallel RLC circuit that has the same magnitude plot. (6 marks)

a) $\omega_0 \sim 4.5 \text{ k rad/s}$ 2

b) $\text{BW} \sim 2 \text{ k rad/s}$ 2

c) $\omega_2 \sim 5.5 \text{ k rad/s}$ 2

$\omega_1 \sim 3.5 \text{ k rad/s}$ 2

d) $Q = \frac{\omega_0}{\text{BW}} = \frac{4.5 \text{ k}}{2 \text{ k}} = 2.25$ 3

e) $L = \frac{Q R}{\omega_0} = \frac{2.25 (1 \text{ k})}{4.5 \text{ k}} = 0.5 \text{ H}$ 4

f) $C = \frac{1}{\omega_0^2 L} = \frac{1}{(4.5 \text{ k})^2 (0.5)} = 0.1 \mu \text{ F}$ 4

g) $P = \frac{V^2}{R} = \left(\frac{10}{\sqrt{2}}\right)^2 \frac{1}{1 \text{ k}} = \frac{1}{20} \text{ W}$ 5


h) $\frac{V_c}{V_i} = Q = 2.25$ 2

i) $R = Q \omega_0 L = 2.25 (4.5 \text{ k}) 0.5 = 5.06 \text{ k}\Omega$ 6

or for $R/L = CR = Q\omega_0$

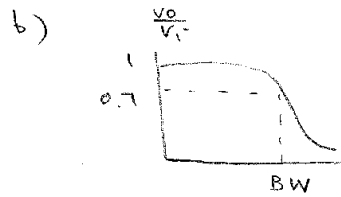4. Given a resistor (R), a capacitor (C) and an inductor (L).

- Show how to connect the resistor and the inductor to form a low-pass filter. Show the location of the output. (3 marks)
- Roughly sketch the frequency response of the low-pass filter (magnitude plot only). (2 marks)
- Show the relation between the half-power voltage gain and the bandwidth in your sketch. (2 marks)
- What is the relation between the resistance and the inductance to obtain the cut-off frequency to be 10kHz? (4 marks)
- How to add a capacitor to your circuit shown in (a) so that it can still be a low-pass filter. (3 marks)
- Derive the transfer function according to your circuit shown in (e). (5 marks)




c)

2

d)

$$\omega = R/L = 2\pi f$$
$$= 2\pi (10K)$$

4

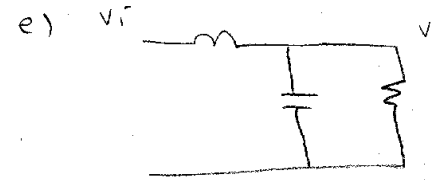

f)


$$\frac{V_o}{V_i} = \frac{R \parallel \frac{1}{j\omega C}}{j\omega L + R \parallel \frac{1}{j\omega C}}$$

$$= \frac{R}{1 + j\omega CR} \cdot \frac{1}{j\omega L + \frac{R}{1 + j\omega CR}}$$

$$= \frac{1}{1 + \frac{1 + j\omega CR}{R} j\omega L}$$


5

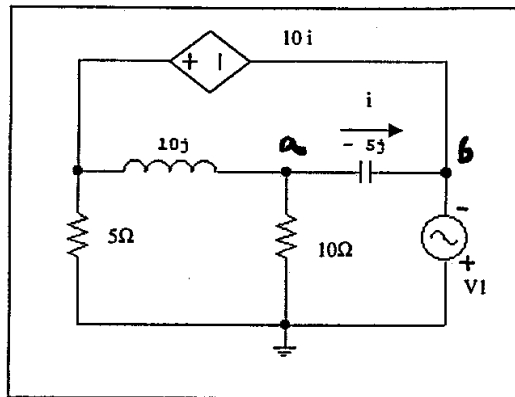5. Given : $V_1(t) = 10 \cos \omega t$ V.




at **ab**

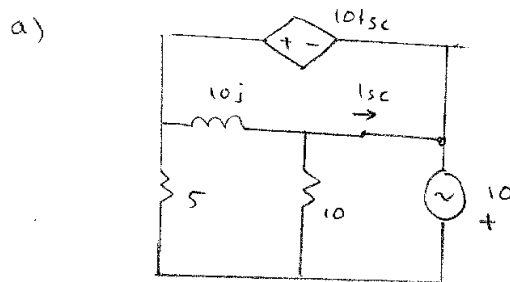- Calculate I_{sc} . (10 marks)
- Calculate V_{oc} . (9 marks)
- Prove the total impedance $Z_{th} = V_{oc} / I_{sc} = 10j \Omega$. (3 marks)
- Calculate $i(t)$. (8 marks)
- Does $i(t)$ lead $V_1(t)$? (2 marks)



$$I_{sc} = \frac{10 I_{sc}}{10j} + \frac{10}{10}$$

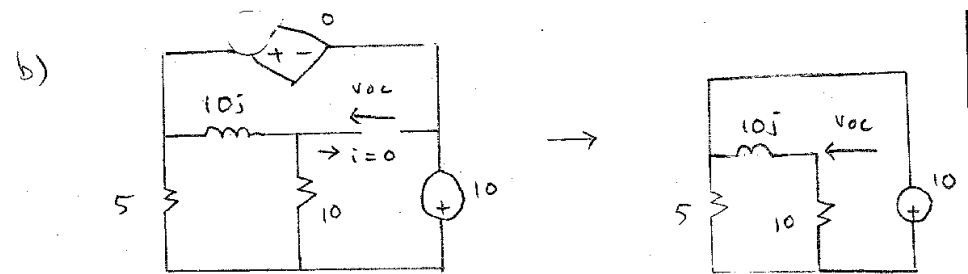
$$\therefore I_{sc} = \frac{1}{1 - \frac{1}{j}} = \frac{1}{1 + j}$$



$$\begin{aligned} \therefore V_{oc} &= \frac{10j}{10 + 10j} \cdot 10 \\ &= \frac{10j}{1 + j} \end{aligned}$$

9
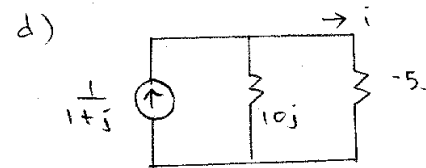
$$\therefore Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{10j}{1+j}}{\frac{1}{1+j}} = 10j \quad 3$$



$$\begin{aligned} \therefore i &= \frac{1}{1+j} \cdot \frac{10j}{10j - 5j} = \frac{2}{1+j} \\ &= \frac{2}{\sqrt{2} \angle 45^\circ} = \sqrt{2} \angle -45^\circ \quad 6 \end{aligned}$$

$$\therefore i(t) = \sqrt{2} \cos(\omega t - 45^\circ) \text{ A} \quad 2$$

$$e) \quad i(t) \text{ lags } v(t) \quad 2$$

END