

(5) $\therefore Y = \frac{1}{20} \angle -70^\circ \text{ S} = \frac{1}{R} + \frac{1}{j\omega L} \quad \text{--(2)}$

$\therefore Y = 0.05 (\cos -70^\circ + j \sin -70^\circ) \text{ S}$
 $= 0.0171 - j0.0470 \text{ S} \quad \text{--(3)}$

(5) $\therefore R = \frac{1}{0.0171} = 58.476 \Omega \quad \text{--(2)}$

$\therefore L = \frac{1}{0.047\omega} = \frac{1}{0.047(100)} = 0.213 \text{ H} \quad \text{--(3)}$

(3) $v(t) = 200 \cos(100t + 30^\circ) \text{ mV} \quad \text{--(1)}$

$i(t) = 10 \sin(100t + 50^\circ) = 10 \cos(100t - 40^\circ) \text{ A} \quad \text{--(1)}$

$v(t)$ leads $i(t)$ by $70^\circ \quad \text{--(1)}$


inductive element (L in parallel with R)

(5) $\therefore Z = \frac{V}{I} = \frac{200 \angle 30^\circ \text{ V}}{10 \angle -40^\circ \text{ A}} \quad \text{--(3)}$
 $= 20 \angle 70^\circ \Omega \quad \text{--(2)}$

1. In the following circuit, $v(t) = 200 \cos(100t + 30^\circ) \text{ V}$, $i(t) = 10 \sin(100t + 50^\circ) \text{ A}$.


(a) Sketch $v(t)$ and $i(t)$ together. Show clearly the phase angles and amplitudes. Find the phase angles between $v(t)$ and $i(t)$. Does $v(t)$ lead $i(t)$?

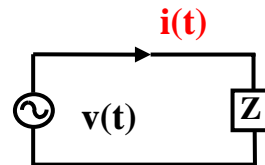(b) If Z is composed of two elements connected in parallel, determine their values. (23)



2

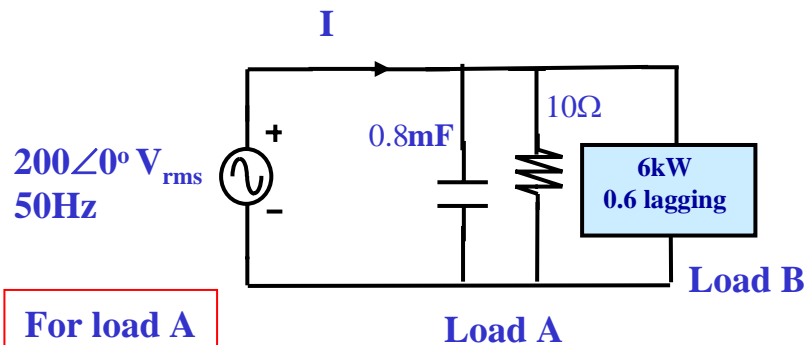2. Loads A and B are connected in parallel to a 200 Vrms, 50Hz power source. Load A is 0.8mF in parallel with 10 Ω. Load B is 6kW at 0.6 lagging power factor. (a) Find the average power P, reactive power Q, apparent power S and power factor PF supplied by the power source. (b) If a load D is connected in parallel to load A and B to make the total power factor = 0.99 leading, find the element and value of load D. (c) If total power factor of load A, B and D is 1, find the current in rms supplied by the power source. (33)



For load A

$$\begin{aligned} (3) \quad \therefore P &= \frac{V^2}{R} \quad --(2) \\ &= \frac{200^2}{10} = 4\text{kW} \quad --(1) \end{aligned}$$

$$\begin{aligned} (4) \quad \therefore Q &= V^2 \omega C \quad --(2) \\ &= 200^2 * 2\pi 50 * 0.8\text{m} = 10053\text{VAR(C)} \quad --(2) \end{aligned}$$

$$(2) \quad \text{For load B} \quad P = 6\text{kW} \quad --(2)$$

$$\begin{aligned} (3) \quad Q &= P \tan \theta \quad --(2) \\ &= 6\text{k} \tan(\cos^{-1} 0.6) = 8\text{kVAR(L)} \quad --(1) \end{aligned}$$

For load A and B

$$(2) \quad \text{total } P = 4\text{k} + 6\text{k} = 10\text{kW}$$

$$(2) \quad \text{total } Q = 8\text{k} - 10.0531\text{k} = 2.0531\text{ kVAR(C)}$$

$$\begin{aligned} (3) \quad \therefore \text{total } S &= \sqrt{P^2 + Q^2} \quad --(2) \\ &= \sqrt{10\text{k}^2 + 2.0531\text{k}^2} = 10.208\text{kVA} \quad --(1) \end{aligned}$$

$$\begin{aligned} (3) \quad \therefore \text{PF} &= \cos \tan^{-1} \frac{Q}{P} \quad --(1) \\ &= \cos \tan^{-1} \frac{2053}{10\text{k}} = 0.98 \text{ leading} \quad --(2) \end{aligned}$$

Add Load D to make PF = 0.99 leading (inductance L)

$$(3) \quad \therefore \text{new } Q = 10\text{k} \tan \cos^{-1} 0.99 = 1.425\text{kVAR(C)}$$


$$\begin{aligned} (4) \quad \therefore L &= \frac{V^2}{\omega Q_L} \quad --(2) \\ &= \frac{200^2}{2\pi 50 (2.0531\text{k} - 1.425\text{k})} = 0.2\text{mH} \quad --(2) \end{aligned}$$

When PF = 1, Load A , B and D is now like a pure resistance R with P = 10kW



I in rms

$$\begin{aligned} (4) \quad I &= \frac{S}{V} \quad --(2) \\ &= \frac{10\text{kVA}}{200\text{V}} = 50\text{Arms} \quad --(2) \end{aligned}$$

3

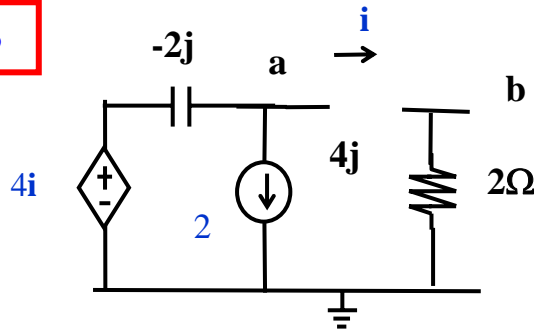

$$(5) \quad V_{oc} = -2(-2j) = 4jV$$

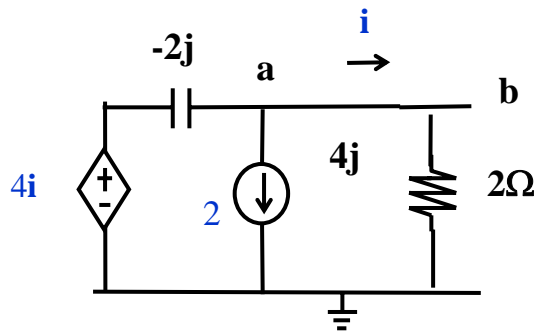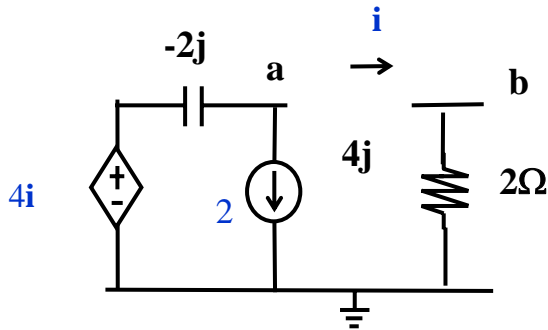

(8)

$$4i = (i + 2)(-2j) + 2i = -2ij - 4j + 2i \quad --(3)$$

$$2i + 2ij = -4j$$


$$I_{SC} = i = \frac{-4j}{2+2j} = \frac{-2j}{1+j} = \frac{2\angle-90^\circ}{\sqrt{2}\angle45^\circ} = \sqrt{2}\angle-135^\circ A \quad --(5)$$

(4)

$$\therefore Z_{th} = \frac{V_{oc}}{I_{sc}} \quad --(2)$$

$$= \frac{4j}{\frac{-2j}{1+j}} = -2(1+j) = 2\sqrt{2}\angle-135^\circ \Omega \quad --(2)$$

(2)

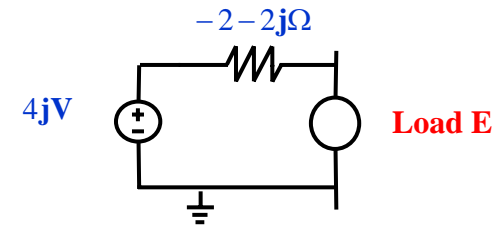

(5)

$$I = \frac{V_{oc}}{Z} \quad --(2)$$

$$= \frac{4j}{-2-2j+E}$$


$$\therefore \text{load } E = 4 + 2j \quad --(3)$$

3. In the following circuit,

(a) find the complex open circuit voltage and short circuit current at terminals ab. Hence sketch the Thevenin equivalent at ab.

(b) A load E is now connected across ab. Find load E if current in load E is $2\angle90^\circ A$. (24)

4

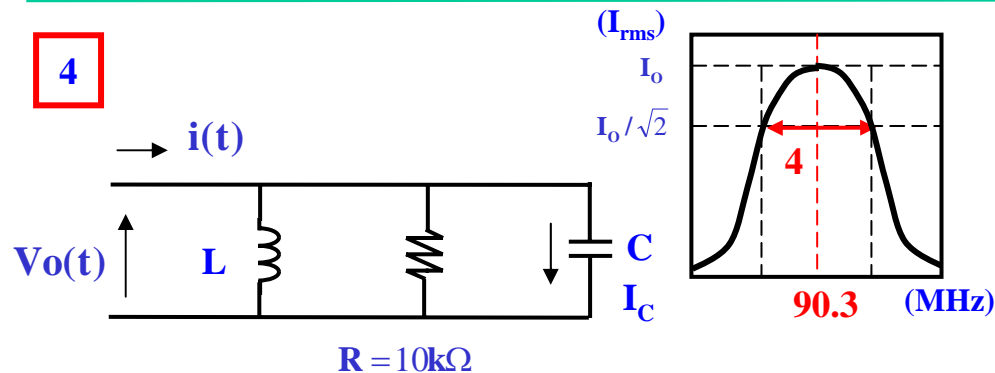

$$(2) f_o = 90.3\text{MHz}$$

$$\therefore \omega_o = 2\pi f_o = 567.372\text{Mrad/s}$$

$$(2) \therefore \text{BW} = 4\text{MHz or } 8\pi\text{Mrad/s}$$

$$(2) \therefore f_2 = f_o + \frac{\text{BW}}{2} = 90.3 + 2 = 92.3\text{MHz}$$

$$(2) \therefore f_1 = f_o - \frac{\text{BW}}{2} = 90.3 - 2 = 88.3\text{MHz}$$

$$(3) \therefore Q = \frac{f_o}{\text{BW}} \quad \text{--(2)}$$

$$= \frac{90.3}{4} = 22.575 \quad \text{--(1)}$$

If i received is 0.089mA rms

$$(4) \therefore \max i_C = Qi \quad \text{--(2)}$$

$$= 22.575(0.089) = 2.0\text{mA}_{\text{rms}} \quad \text{--(1)}$$

(27)

$$(3) \therefore R = \frac{0.89\text{V}}{0.089\text{mA}} = 10\text{k}\Omega$$

$$(3) \therefore L = \frac{R}{\omega_o Q} \quad \text{--(2)}$$


$$= \frac{10\text{k}}{567.372\text{M}(22.575)} = 0.781\mu\text{H} \quad \text{--(1)}$$

$$(3) \therefore C = \frac{Q}{\omega_o R} \quad \text{--(2)}$$

$$= \frac{22.575}{567.372\text{M}(10\text{k})} = 3.979\text{pF} \quad \text{--(1)}$$

$$(3) \therefore R = \frac{1}{\text{BW} * C} \quad \text{--(1)} \quad \text{Increase R to } 20\text{ k}\Omega \quad \text{--(2)}$$

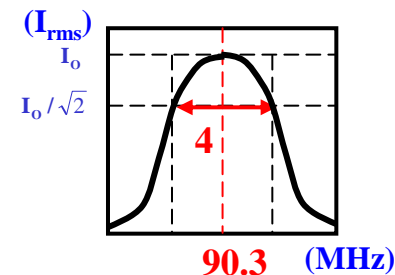
4. A parallel LCR radio tuner circuit is used to receive radio stations as shown in the tuner curve. (a) Find the resonant frequency, bandwidth, upper and lower frequencies (in Hz). (b) If the current signal received by the tuner is 0.089 mA rms and maximum output voltage of tuner is 0.89 V rms , find the maximum current (in rms) flowing in C. (c) Find also the values of L, C and R of the tuner circuit. (d) Suggest a method to improve the bandwidth to 2 MHz . (27)



5

In the filter circuit below,

- (a) Find the complex transfer function $G = V_o/V_i$ in terms of C , R and $j\omega$. (b) Show that at cut-off, the cutoff frequency = 500k rad/s . Find also the $|G|$ in dB. (c) Find $|G|$ when $\omega = 50\text{krad/s}$. What filter type is it? (d) Sketch $|G|$ versus angular frequency ω . Show clearly all intercepts in your sketch. (28)

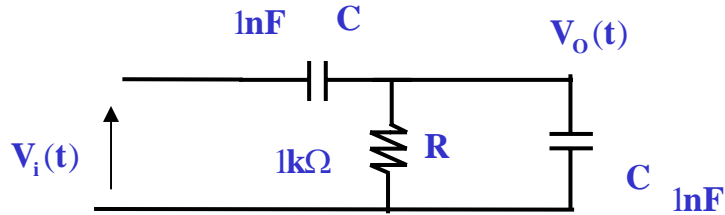

$$(7) \quad \therefore R // \frac{1}{j\omega C} = \frac{R \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega CR} \quad --(2)$$

$$\therefore G = \frac{V_o}{V_i} = \frac{\frac{R}{1 + j\omega CR}}{\frac{1}{j\omega C} + \frac{R}{1 + j\omega CR}} \quad --(2)$$

$$= \frac{1}{\left(\frac{1 + j\omega CR}{j\omega CR}\right) + 1} = \frac{1}{\left(\frac{1}{j\omega CR}\right) + 1 + 1} \quad --(3)$$

At cut-off

$$(2) \quad \therefore \frac{1}{\omega_0 CR} = 2$$

$$(3) \quad \therefore \omega_0 = \frac{1}{2CR} = \frac{1}{2 * 1n(1k)} = 0.5 \times 10^6 \text{ rad/s}$$

$$(3) \quad \therefore G = \frac{1}{2 - 2j} \quad \therefore |G| = \frac{1}{2\sqrt{2}}$$


$$(3) \quad \therefore 20 \log_{10} |G| = 20 \log_{10} \frac{1}{2\sqrt{2}} = -9 \text{ dB}$$


$$\text{at } \omega = \frac{\omega_0}{10} = 50 \text{ k rad/s}$$

$$(5) \quad \therefore G = \frac{1}{2 - 20j} \quad --(3)$$

$$\therefore |G| = \frac{1}{2\sqrt{101}} = 0.05 \quad --(2)$$

(2) A high pass filter

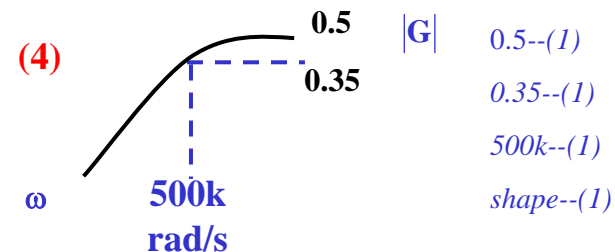

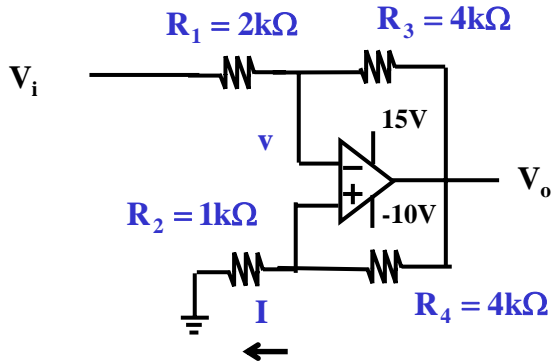6

(11) $\therefore V_- = V_+ = V \quad \text{---(3)}$

$\therefore V_+ = V_o \frac{1k}{1k + 4k} = \frac{V_o}{5} = v = V_- \quad \text{---(3)}$

$\therefore \frac{V_i - v}{2k} = \frac{v - V_o}{4k} \quad \text{---(3)}$

$\therefore 2V_i - 2v = v - V_o \quad \therefore 2V_i = 3v - V_o = -\frac{2}{5} V_o$

$\therefore A_v = \frac{V_o}{V_i} = -5 \quad \text{---(2)}$

(2) If $V_i = -1V$, $V_o = 5V$



(4) If $V_i = 4V$, $V_o = -15V \quad \text{---(2)}$

$\therefore I = \frac{-15V}{5k} = -3mA \quad \text{---(2)}$

(27)

6. (a) In the following ideal op amp circuit, (i) find V_o when $V_i = -1V$, (ii) find I when $V_i = 4V$. (17)

(b) Design an ideal op amp circuit (with very high input resistance) to generate an output current of $0.1V_i$ (mA) and output voltage of $5V_i$ (V) when input voltage is V_i (V). (10)

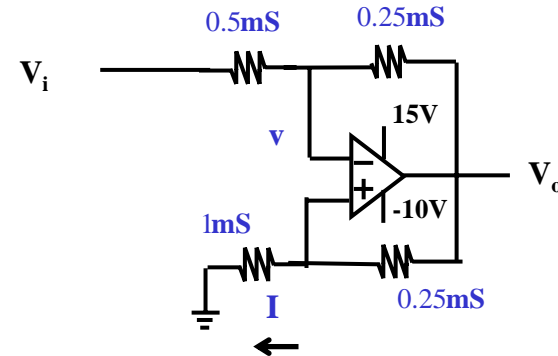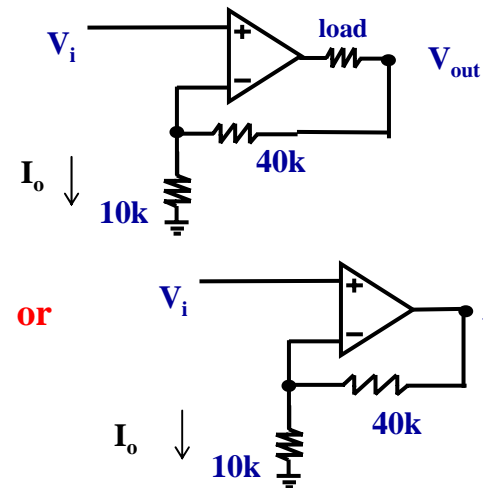**(10)**

Show Gain=5---(4)

Shpw $I = 0.1mV_i$ ---(4)

all correct ---(2)

or