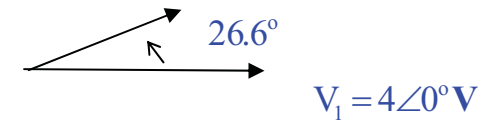


$$\therefore \mathbf{V}_{\text{OC}} = \mathbf{V}_3 = 4\angle 0^\circ + 2\angle 0^\circ * 1\Omega = 6\angle 0^\circ \text{ V} \quad (4.5)$$

$$\therefore \mathbf{V}_2 = \frac{1}{1+1-\mathbf{j}\Omega} * 6\angle 0^\circ \mathbf{V} \quad (5)$$

$$\begin{aligned} &= \frac{6\angle 0^\circ}{\sqrt{5}\angle -26.6^\circ} \\ &\cong 2.68\angle 26.6^\circ \text{ V} \end{aligned} \quad (5)$$


$$V_2 \cong 2.68 \angle 26.6^\circ \text{ V}$$




(5)

4

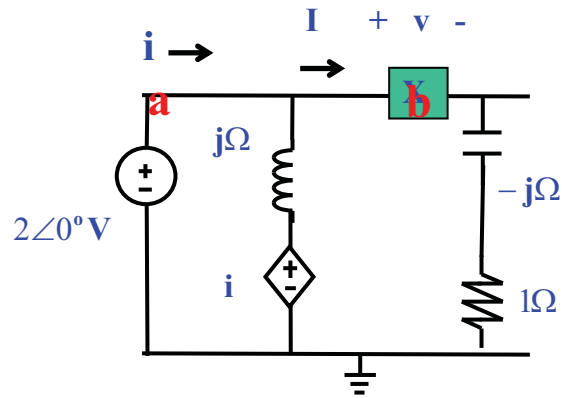- (a) If X is open, find v. (b) If  $X = 0 \Omega$ , find I.  
 (c) Find the Thevenin equivalent at terminals ab. (d) If  $I = 2\angle 0^\circ \text{ A}$ , find X.  
 (24)




(a) If X is open

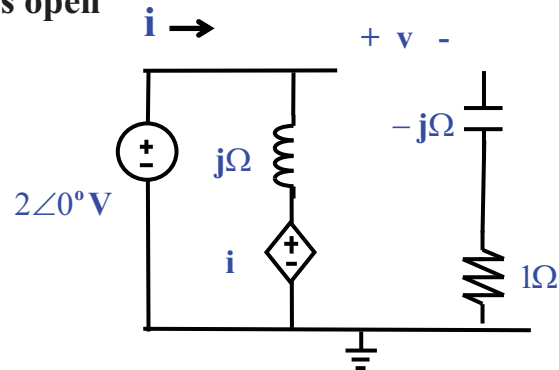

$$\therefore v = 2\angle 0^\circ \text{ V} \quad (6)$$

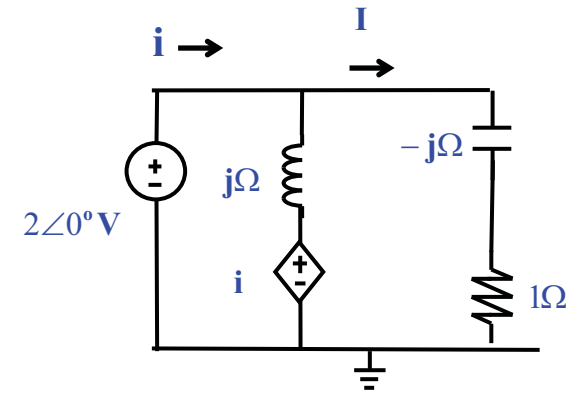
(b) If  $X = 0 \Omega$

$$\therefore I = \frac{2\text{ V}}{1\Omega - j\Omega} \quad (6)$$




(c) 
$$\therefore Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{v}{I} = \frac{2\angle 0^\circ}{2\angle 0^\circ / 1-j} = 1\Omega - j\Omega$$

Thevenin equivalent at terminals ab

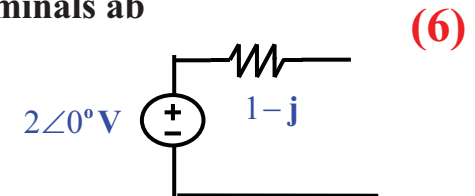

(d) If  $I = 2\angle 0^\circ \text{ A} = \frac{2\angle 0^\circ \text{ V}}{1\Omega}$


$$\therefore X = j\Omega \quad (6)$$

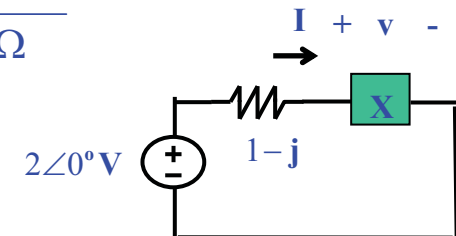

1

The circuit is at steady state for  $t < 0$ . At  $t = 0$ , the switch is switched from A to B (i.e. BC is shorted). (a) Find  $i(t)$  for  $t \geq 0$ . (b) Find the maximum energy stored in L. (c) Plot  $V(t)$  for  $t < 0$  and  $t \geq 0$ . Label clearly the voltage and time. (33)

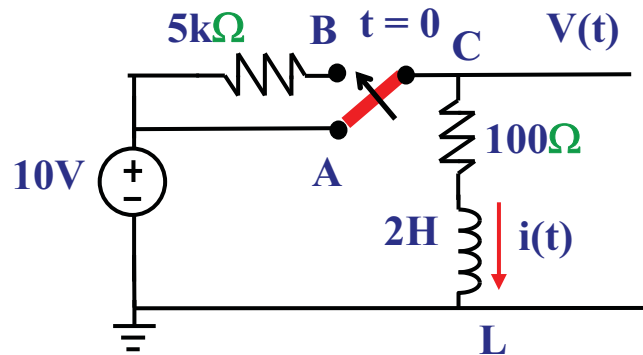Given that  $i(t) = i(\infty) + [i(0) - i(\infty)] * e^{-t/\tau}$  and  $\tau = L/R$



$$(a) \quad \therefore i(t = 0) = i(t < 0) = 0.1A \quad (4)$$

$$\therefore i(\infty) = \frac{10V}{5100\Omega} \cong 2mA \quad (4)$$



$$\therefore \tau = \frac{L}{R} = \frac{2H}{5100\Omega} \cong 0.4ms \quad (4)$$

$$\begin{aligned} \therefore i(t) &= i(\infty) + [i(0) - i(\infty)] * e^{-t/\tau} \\ &\cong 2mA + [100mA - 2mA] * e^{-t/0.4ms} \end{aligned} \quad (3)$$

(b)


$$\therefore E_L = \frac{1}{2} Li^2 = \frac{1}{2} (2H)(0.1A)^2 = 10mJ \quad (5)$$

(c)

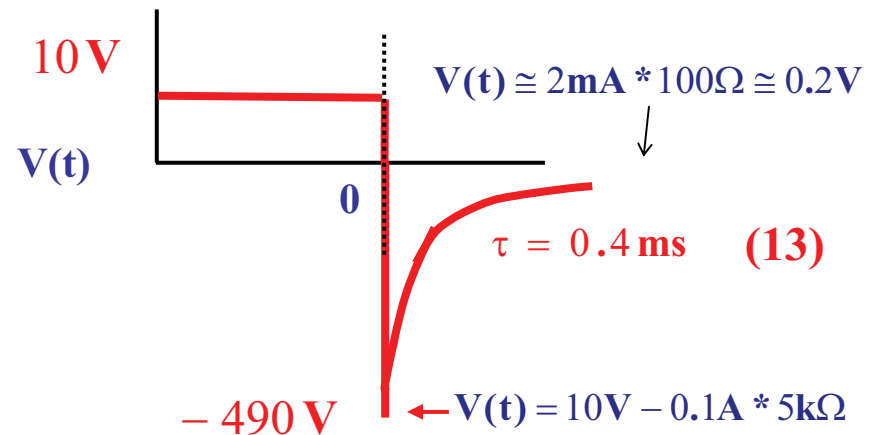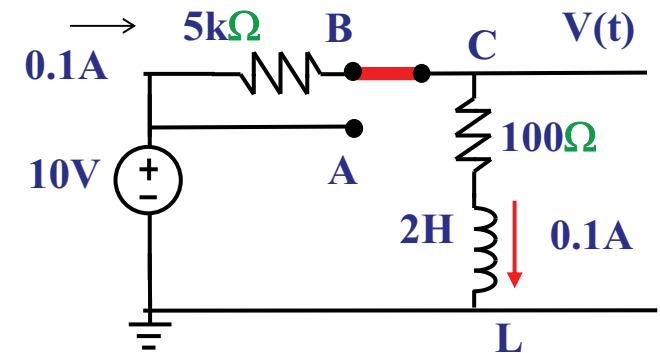

2

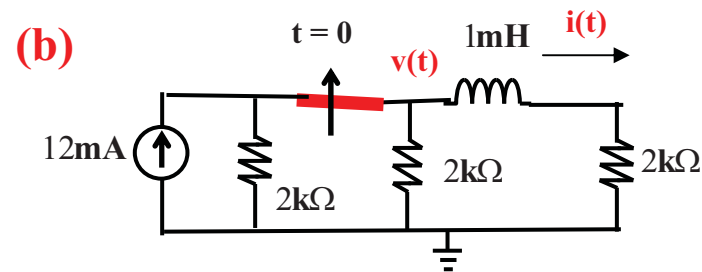- (a) Explain briefly why the current in an inductor is continuous with switching.
- (b) Circuit is at steady state for  $t < 0$ . At  $t = 0$ , the switch is opened. Find  $v(<0)$ ,  $v(0)$ ,  $v(10\tau)$  and sketch  $v(t)$ . (26)



(a) 
$$E_L = \frac{Li_L(t)^2}{2} \quad (8)$$


$E_L$  (hence  $i_L$ ) must be continuous with time

$$i(0) = i(<0) = 12\text{mA} * \frac{2\text{k}\Omega}{2\text{k}\Omega // 2\text{k}\Omega + 2\text{k}\Omega} * \frac{1}{2} = 4\text{mA} \quad (4)$$

$$v(<0) = 4\text{mA} * 2\text{k}\Omega = 8\text{V} \quad (3)$$

$$\begin{aligned} v(0) &= -i(0) * 2\text{k}\Omega \\ &= -4\text{mA} * 2\text{k}\Omega = -8\text{V} \end{aligned} \quad (4)$$





$$v(10\tau) \cong 0\text{V} \quad (3)$$

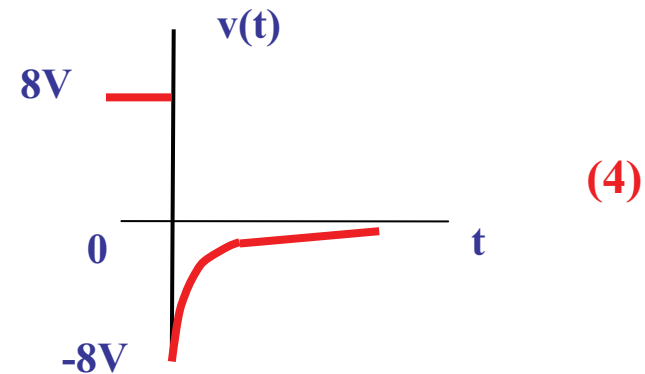

3

In the ideal diode circuit, plot  $V_3$  versus  $V_2$  for  $18V \geq V_2 \geq 0V$ . (24)






(b)

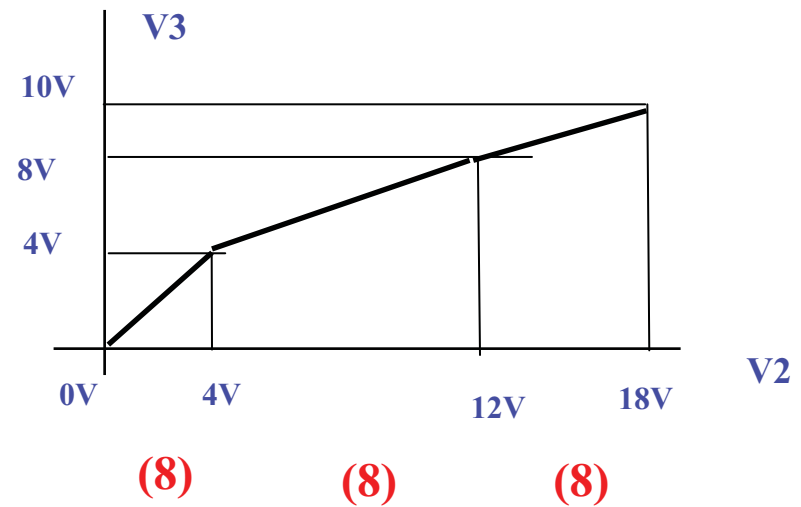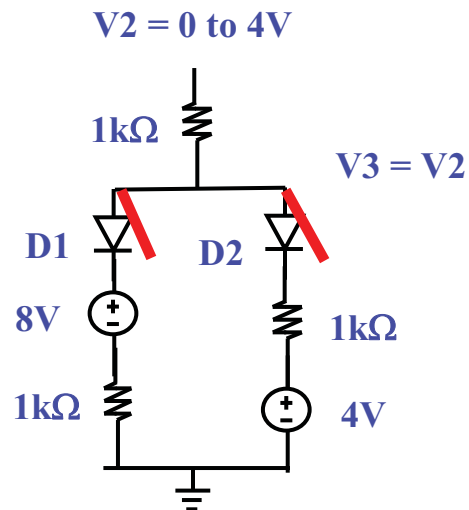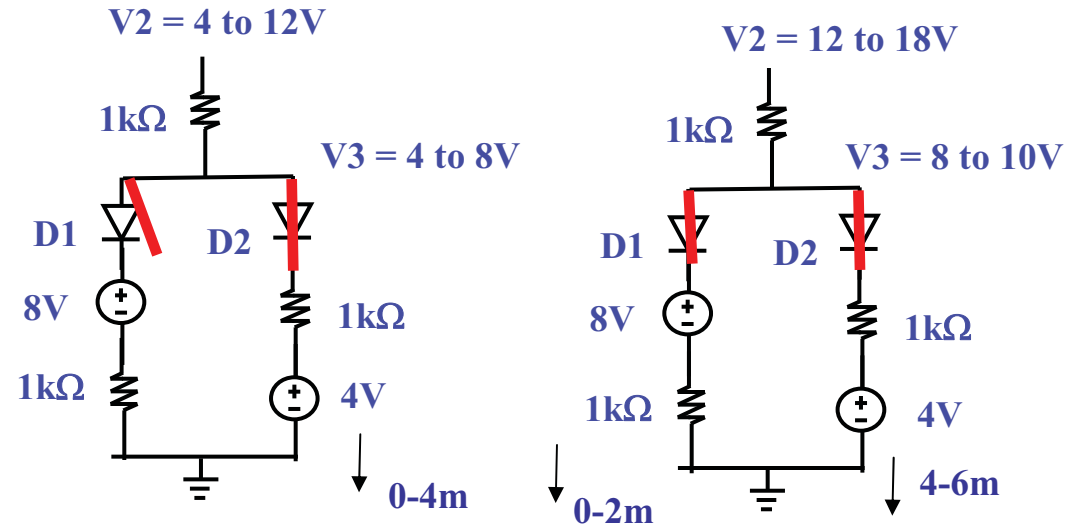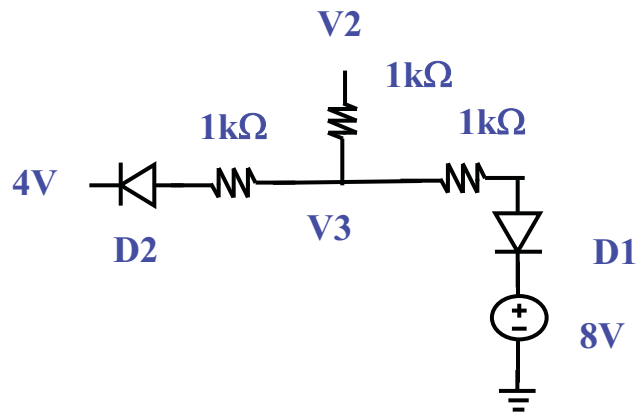

11

In the ideal diode circuit, plot  $V_2$  versus  $V_1$  for  $20V \geq V_1 \geq 0V$ . (22)

(c)

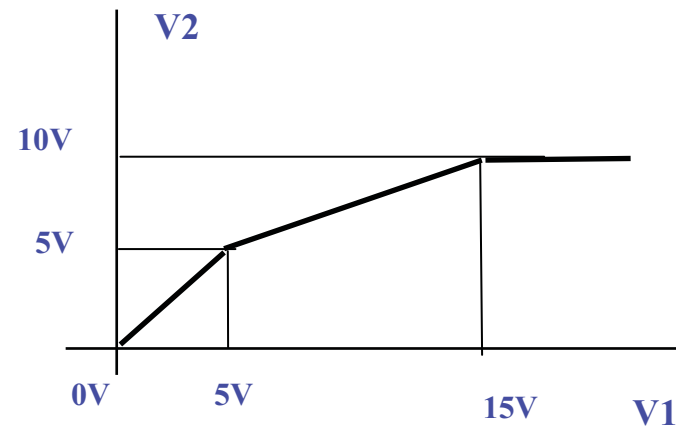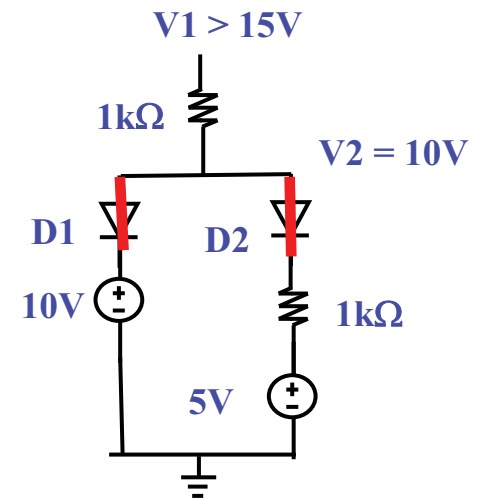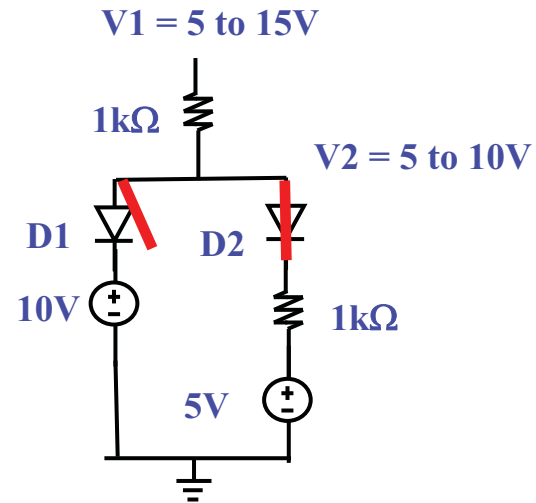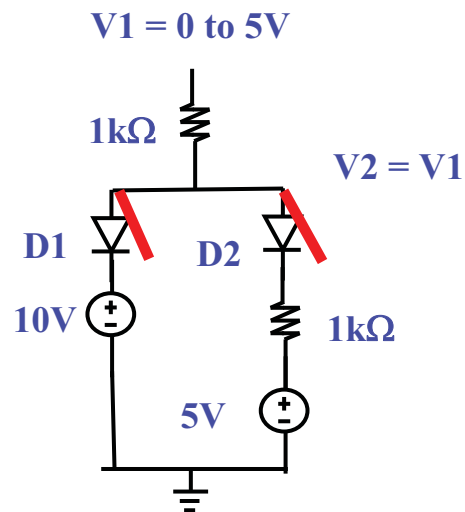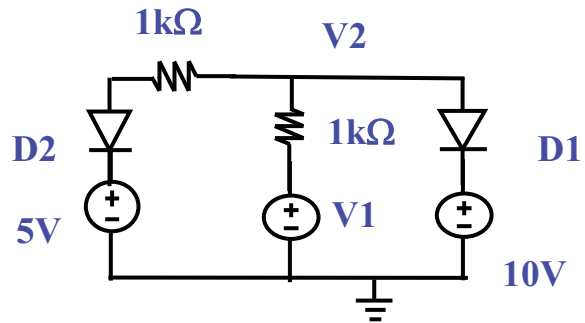



(7)

(8)

(7)

6

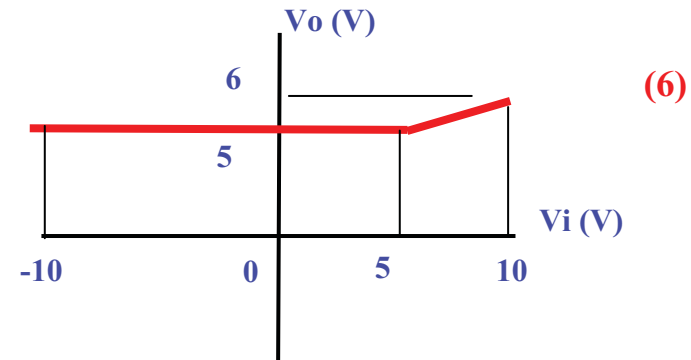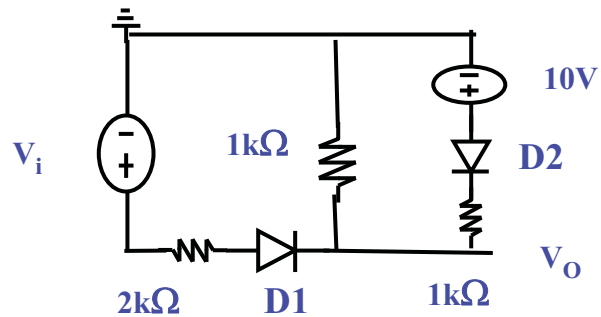(b) In the ideal diode circuit, plot  $V_o$  versus  $V_i$  for  $-10V \leq V_i \leq 10V$ .  
Show clearly all voltages in your sketch. (20)



$V_i < 5V$ , D1 OFF and D2 ON  $\therefore V_o = 5V$

$V_i > 5V$ , D1 and D2 ON,

$$\begin{aligned} \therefore \frac{V_i - V_o}{2k} + \frac{10 - V_o}{1k} &= \frac{V_o}{1k} \\ \therefore V_i - V_o + 20 - 2V_o &= 2V_o \\ \therefore V_o &= \frac{V_i + 20}{5} \end{aligned}$$