

(7)

1

(a)

(a) Explain very briefly why voltage in a capacitor and current in an inductor is continuous with time. (7)

1

Energy must be continuous with time.

Hence E_C and E_L must be continuous with time
(unchanged after switching)

$$\begin{array}{c}
 + \\
 V_C \quad \downarrow i_C \\
 - \quad \text{---} \\
 \end{array}
 \quad E_C = \frac{CV_C(t)^2}{2}$$

$$\begin{array}{c}
 i_L \downarrow \quad + \\
 \downarrow \quad \text{---} \quad V_L \\
 \quad \quad -
 \end{array}
 \quad E_L = \frac{Li_L(t)^2}{2} \quad (7)$$

Hence V_C and i_L must be continuous with time.

2

Another short proof

$$i_C = C \frac{dV_C(t)}{dt} \quad V_L = L \frac{di_L(t)}{dt}$$





If dt is 0, infinite i_C or V_L is required, which is not possible. Hence dV_C/dt and di_L/dt must be finite, or V_C and i_L must be continuous with time .

(19)

1

(b) The switch has been closed for a long time. At $t = 0$ second, the switch is opened. (i) If $X = 1\text{mH}$, find $i(0)$, $i(\infty)$, time constant $\tau (= L/R)$, $i(t)$ and $v(t)$ for $t \geq 0$. Given that $i(t) = i(\infty) + [i(0) - i(\infty)] \exp(-t/\tau)$. $v(t) = v(\infty) + [v(0) - v(\infty)] \exp(-t/\tau)$. (19)

(b)

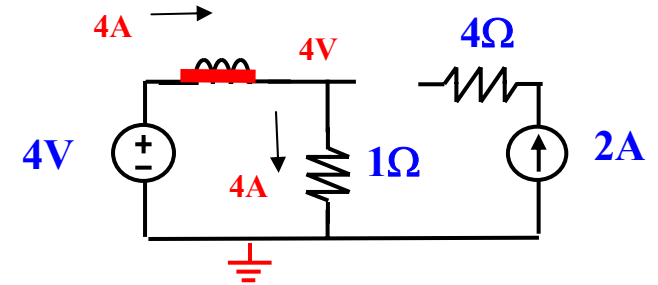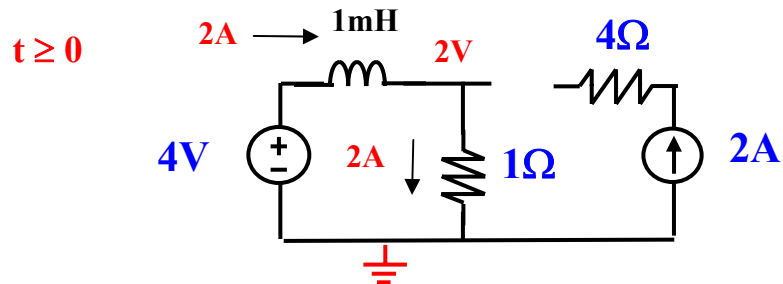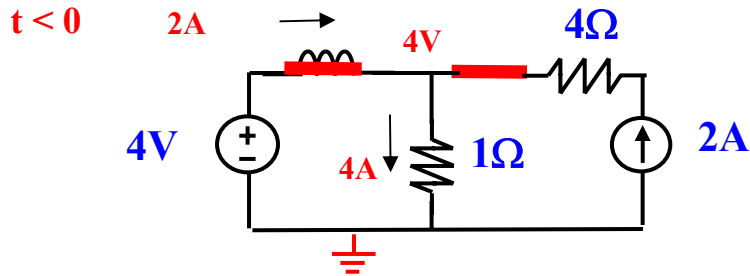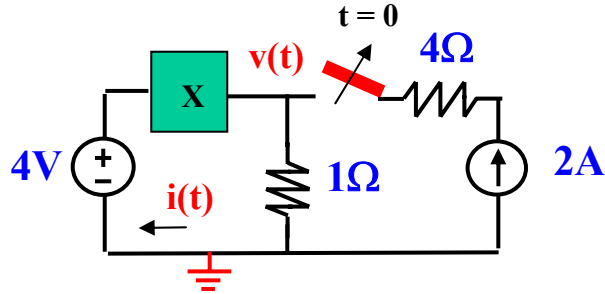

$$\therefore i(0) = 2\text{ A} \quad (5)$$

$$i(\infty) = 4\text{ A} \quad (4)$$


$$\tau = \frac{L}{R} = \frac{1\text{mH}}{1\Omega} = 1\text{ms} \quad (3)$$

$$\begin{aligned} \therefore i(t) &= i(\infty) + [i(0) - i(\infty)] * e^{-\frac{t}{\tau}} \\ &= 4\text{ A} + [2\text{ A} - 4\text{ A}] * e^{-t/1\text{ms}} \\ &= 4\text{ A} - 2\text{ A}e^{-t/1\text{ms}} \end{aligned} \quad (3)$$

$$v(t) = i(t) * 1\Omega = 4\text{ V} - 2\text{ V}e^{-t/1\text{ms}} \quad (4)$$

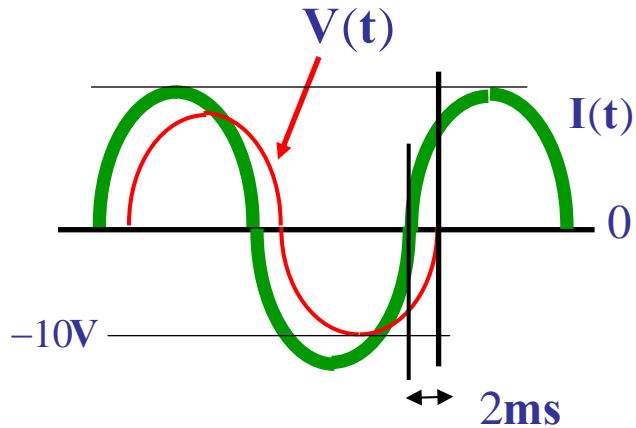(15)

2 If $I(t) = 2 \sin(\pi 100 * t + 5^\circ) \text{ A}$, find $V(t)$.
Does $I(t)$ lead $V(t)$ (15)



$$\therefore T = \frac{2\pi}{\omega} = \frac{2\pi}{100\pi} = 20\text{ms} \quad (4)$$

$$\theta = \frac{t}{T} * 360^\circ = \frac{2\text{ms}}{20\text{ms}} * 360^\circ = 36^\circ \quad (4)$$

$$\begin{aligned} \therefore V(t) &= 10V \sin(\omega t + \theta) \\ &= 10V \sin(100\pi t + 5^\circ - 36^\circ) \\ &= 10V \sin(100\pi t - 31^\circ) \end{aligned} \quad (5)$$


$I(t)$ leads $V(t)$ (2)

(10)

3

(28)

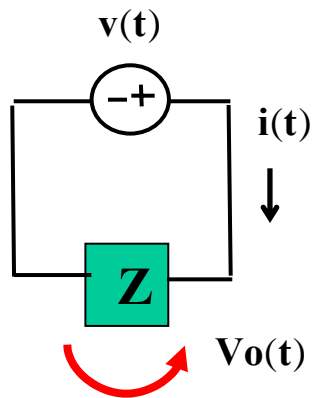(a) If $i(t) = 8\sin(2kt + 30^\circ)\text{mA}$, $Z = 2 \times 10^{-6}\text{F}$, find Z in Ω and find $V_o(t)$.



$$(a) \quad Z = \frac{1}{j\omega C} = \frac{1}{j * 2\text{krad/s} * 2\mu\text{F}} = -j250\Omega \quad (3)$$

$$V_o(t) = 8\text{mA} * 250\Omega \sin(2kt + 30^\circ - 90^\circ) \quad (7) \\ = 2\text{V} \sin(2kt - 60^\circ)$$

(18)

(b) If $i(t) = 2\cos(2kt - 30^\circ)\text{A}$, $v(t) = 10\cos(2kt + 30^\circ)\text{V}$, and Z is R in parallel with X . Find $Y (= 1/Z)$ in Ω^{-1} . Find also the element and value of X . Draw also the phasor diagram of $v(t)$ and $i(t)$.


(b)

$$\begin{aligned}\therefore \mathbf{Y} &= \frac{\mathbf{I}}{\mathbf{V}} = \frac{2\angle -30^\circ \text{A}}{10\angle +30^\circ \text{V}} = 0.2\angle -60^\circ \Omega^{-1} \\ &= 0.2\cos(-60^\circ) + 0.2j\sin(-60^\circ) \\ &= 0.1\text{S} - j0.1732\text{S} \\ &= \frac{1}{\mathbf{R}} + \frac{1}{j\mathbf{X}}\end{aligned}$$

(10)

$$\therefore \mathbf{X} = \omega\mathbf{L} \Rightarrow \mathbf{L} = \frac{\mathbf{X}}{\omega} = \frac{1}{0.1732 * 2k} \cong 2.89\text{mH}$$

(4)

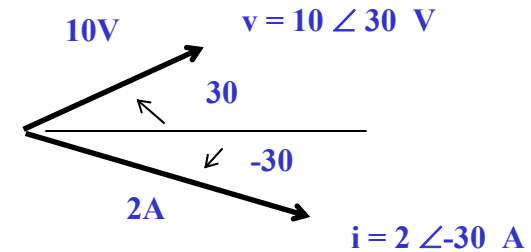


(4)

(10)


4

If $X = 2j\Omega$, find i using superposition.

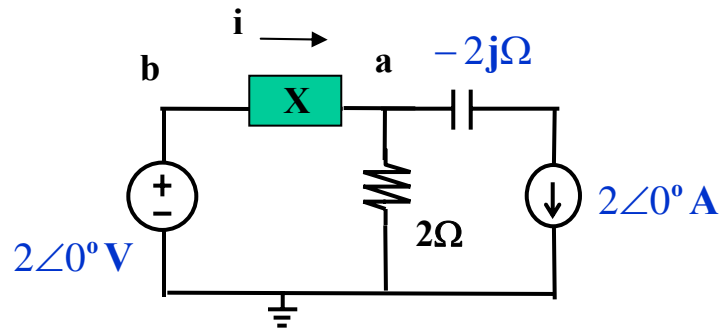
Find also the **Thevenin impedance** at terminals ab and hence find the **Thevenin voltage** at ab. (24)



(a)

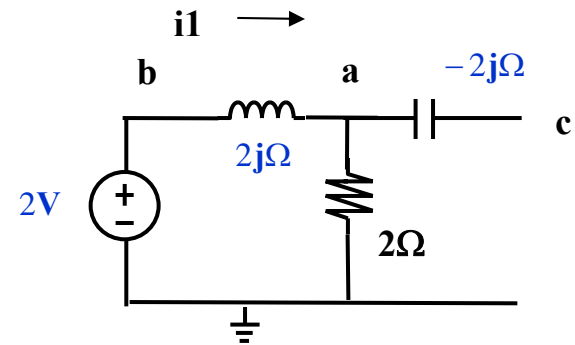
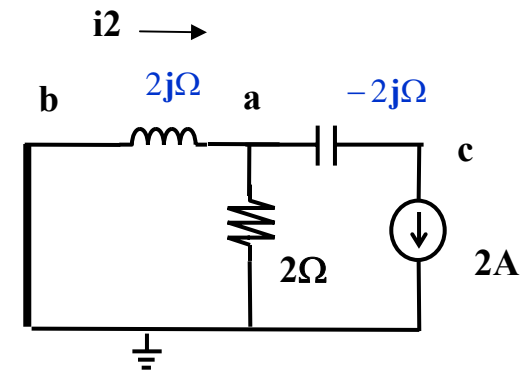
$$i_1 = \frac{2V}{2\Omega + 2j\Omega} = \frac{1A}{1+j} \quad (5)$$




$$i_2 = 2A * \frac{2\Omega}{2\Omega + 2j\Omega} = \frac{2A}{1+j} \quad (5)$$


(14)

$$\therefore \mathbf{i} = \mathbf{i}_1 + \mathbf{i}_2 = \frac{3\mathbf{A}}{1 + \mathbf{j}} \quad (2)$$


(b)

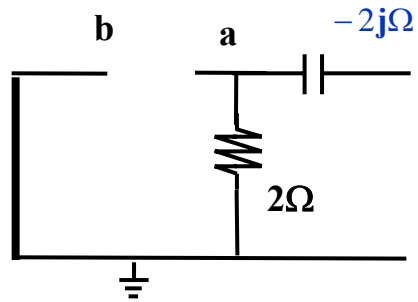

$$\mathbf{Z}_{th} = 2\Omega \quad (4)$$

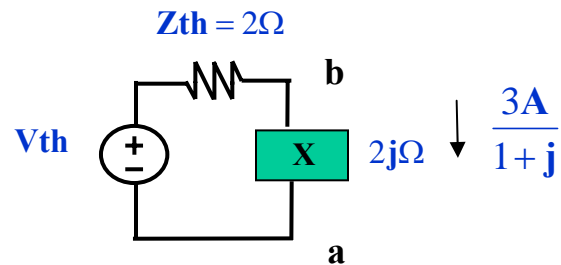

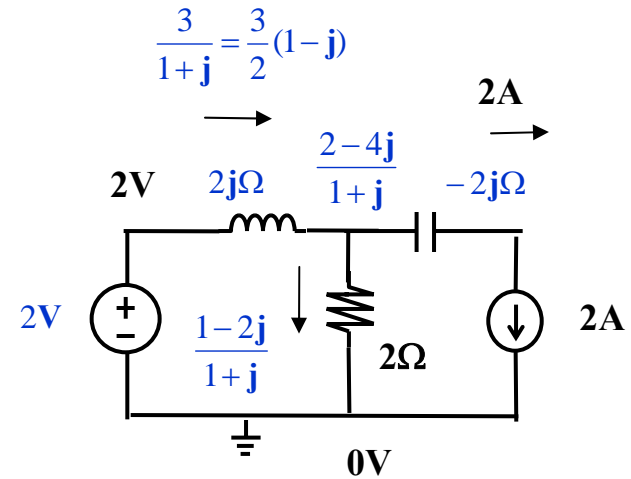
$$\therefore \mathbf{V}_{th} = \frac{3\mathbf{A}}{1 + \mathbf{j}} * (2 + 2\mathbf{j})\Omega = 6\mathbf{V} \quad (8)$$



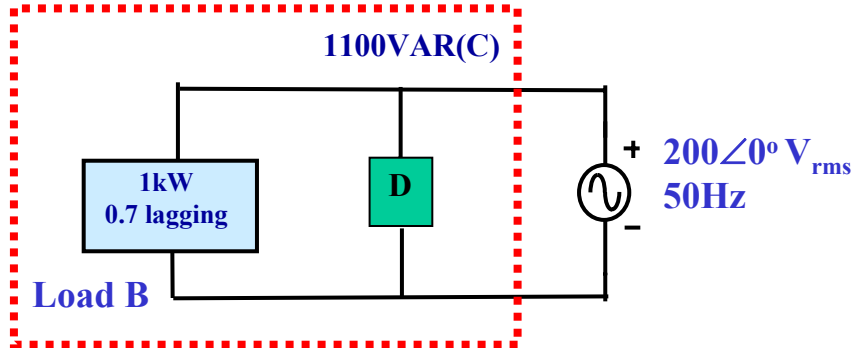
(19)

5

A load D with 1100VAR (C) is connected in parallel to load B. Find the power factor of the combined load. Find also the element and value of load D. (19)



Power triangle

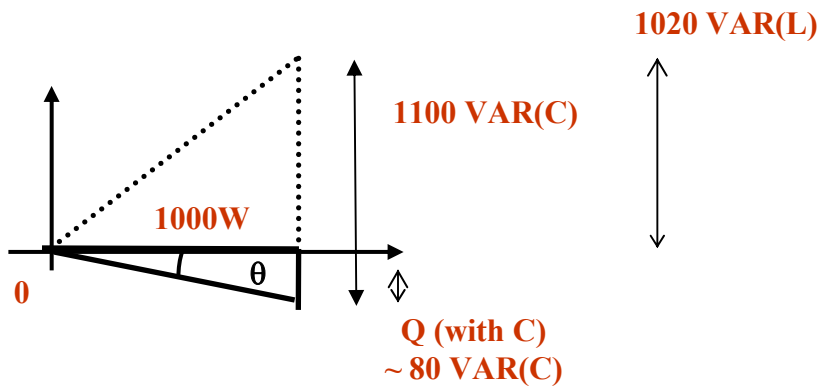

$$\therefore \text{New } Q = 1\text{kW} \tan(\cos^{-1} 0.7) - 1100$$

$$\cong 1020.2 - 1100 = 79.8\text{VAR(C)}$$

(7)

Power factor of combined load

$$= \cos(\tan^{-1} \frac{79.8}{1000}) \cong \cos(4.56^\circ) \cong 0.997 \text{ leading}$$

(6)

$$\therefore C = \frac{|Q_c|}{V^2 \omega} \cong \frac{1100\text{VAR(C)}}{(200^2)2\pi 50} \cong 87.5\mu\text{F}$$


(6)

(29)

6

(29) (a) Will electricity fee be reduced if the power factor of a load is improved to 1? Why?

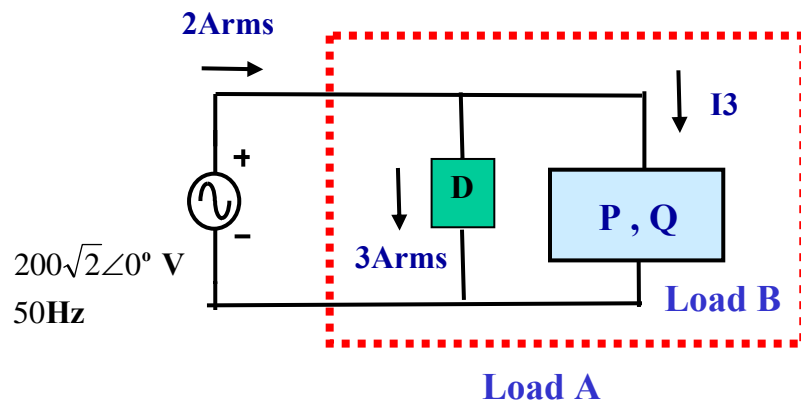(b) Power factor of Load A is 1. D is a capacitor. Find the average power P, reactive power Q, and I₃ in phasor form.



(a) Electric fees is related to P only
P is unchanged hence fees
will not be reduced (5)

$$(b) \quad P = VI = 200V_{\text{rms}} * 2A_{\text{rms}} = 400W \quad (6)$$

$$Q = VI = 200V_{\text{rms}} * 3A_{\text{rms}} = 600\text{VAR(L)} \quad (6)$$

$$I_3 = \frac{S}{V} = \frac{\sqrt{400^2 + 600^2}}{200} \cong 3.6A_{\text{rms}} \quad (6)$$

$$\therefore I_3 \cong 3.6 \angle -\tan^{-1} \frac{Q}{P}$$


$$= 3.6 \angle -\tan^{-1} \frac{600}{400} \cong 3.6 \angle -56.3^\circ A_{\text{rms}} \quad (6)$$

(17)


7

(a)

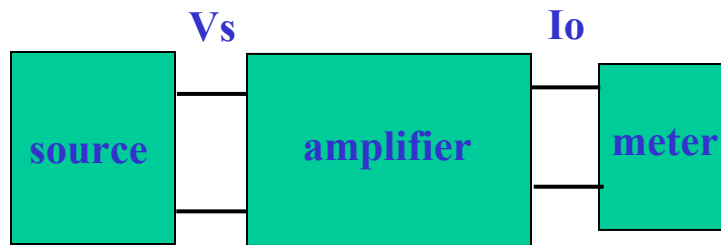An amplifier is used to amplify the voltage V_s of a source and display the current I_o with a meter. Draw the circuit model of the amplifier. What is the ideal value of the output resistance of the amplifier. (8)




(a)

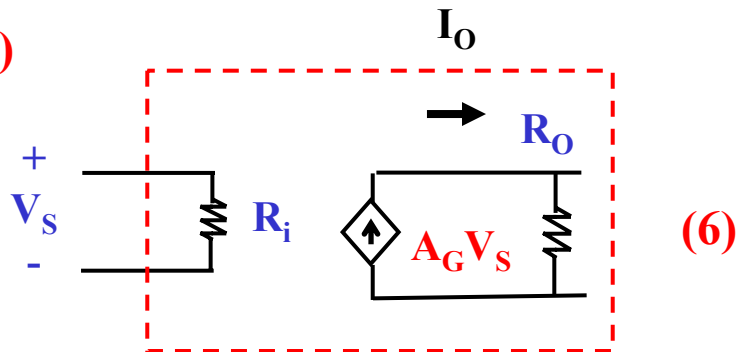

$$R_o = \infty \Omega \quad (2)$$

(b)

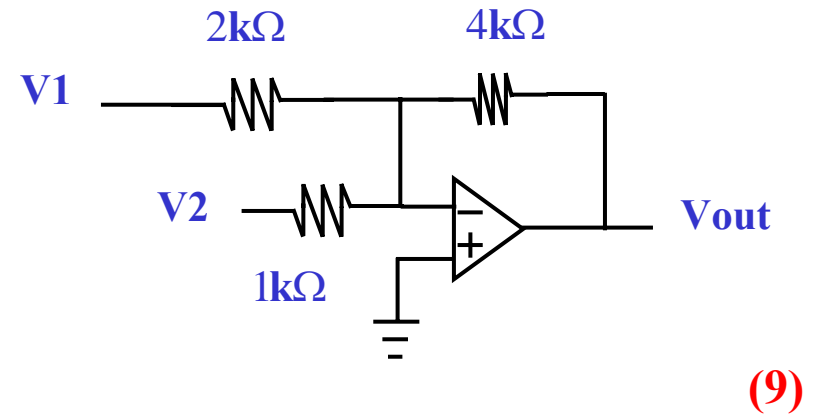
Design the ideal op amp circuit below if $V_{out} = -2V_1 - 4V_2$. Use $1k - 10k\Omega$ resistors in your design. (9)



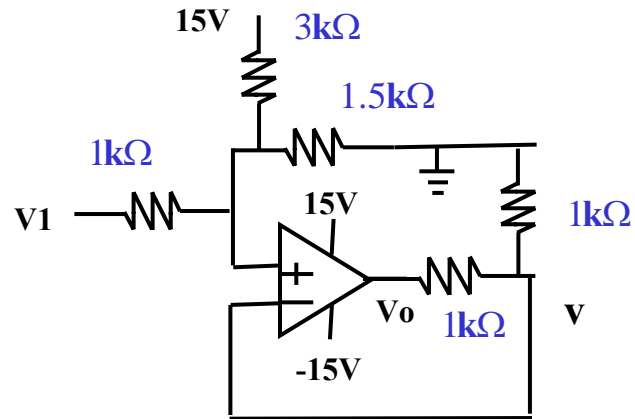(15)

8

If $v = 3V$, find V_o and V_1 . Assume the op amp is ideal. (15)




$$4\text{mA} = \frac{15V - 3V}{3k\Omega}$$

$$2\text{mA} = \frac{3V - 0V}{1.5k\Omega}$$

$$2\text{mA} = 4\text{mA} - 2\text{mA}$$

$$\text{Hence } V_1 = 3V - 2\text{mA} * 1k\Omega = 1V \quad (10)$$

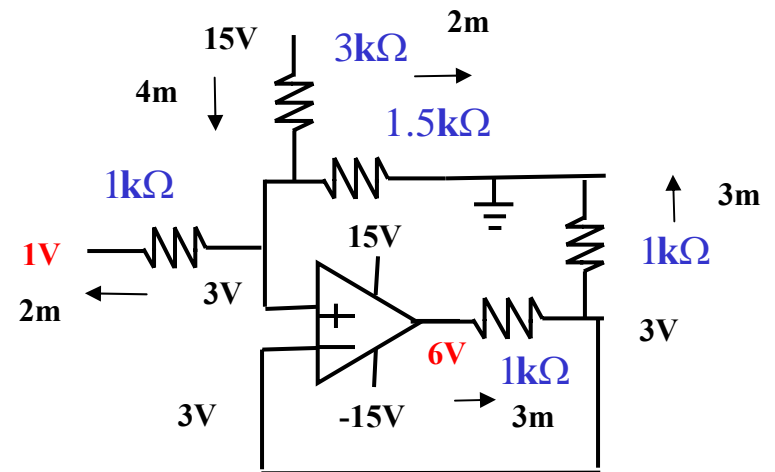
$$V_o = 3V + \frac{3V - 0V}{1k\Omega} * 1k\Omega = 6V \quad (5)$$



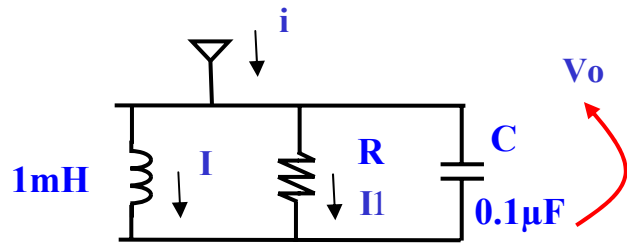(14)

9

In the parallel LCR circuit, $V_o(t) = 2\sqrt{2} \cos(100kt)V$
 $R = 10k\Omega$. Show that $I = I_1$ and hence find $i(t)$.
 (14)



$$\omega L = 100k\text{rad/s} * 1mH = \frac{1}{100k\text{rad/s} * 0.1\mu F} = \frac{1}{\omega C} = 100\Omega \quad (5)$$

$$\omega L // \frac{1}{\omega C} = \infty \quad \text{Hence LCR is equivalent to } R \quad (3)$$


$$\therefore i(t) = I_1(t) = \frac{V_o(t)}{10k\Omega} = \frac{2\sqrt{2} \cos 1ktV}{10k\Omega} = 200\sqrt{2} \cos 1kt \mu A \quad (6)$$

(26)

10

A series LCR circuit has a resonant frequency of 100MHz . $R = 5\Omega$.

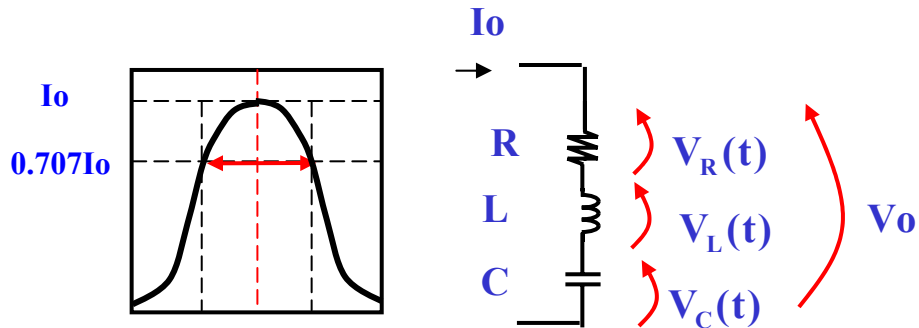- (a) If the quality factor (QF) is 100 , find the bandwidth .
 (b) Find C and L .
 (c) If at resonance, $I_o = 2\cos(\omega t)$ mA , find $V_o(t)$.
 (d) Find the new bandwidth and QF if R is changed to 2.5Ω .
 Given that $QF = f_o/BW = X/R$. (26)



(a)

$$BW = \frac{f_o}{QF} = \frac{100M}{100} = 1MHz \quad (3)$$

$$(b) \quad \therefore QF = \frac{\omega_o L}{R}$$

$$\therefore L = \frac{QF * R}{\omega_o} = \frac{100 * 5}{2\pi * 100M} \cong 0.8\mu H \quad (5)$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$

$$\therefore C = \frac{1}{\omega_o^2 L} \cong \frac{1}{(2\pi 100MHz)^2 0.8\mu H} \cong 3.17 \times 10^{-12} F \quad (5)$$

$$(c) \quad \therefore V_o(t) = I_o(t) * R = 2mA * 5\Omega \cos(2\pi 100Mt)$$

$$\cong 10mV \cos 2\pi 100Mt \quad (7)$$

$$(d) \quad QF = X/R = 200$$


$$BW = f_o/QF = 500kHz \quad (6)$$

(14)

11

In the circuit, the dependent source ($v = 2v_o$) is a voltage controlled voltage source and unit is volt. Find i in phasor form.

(14)

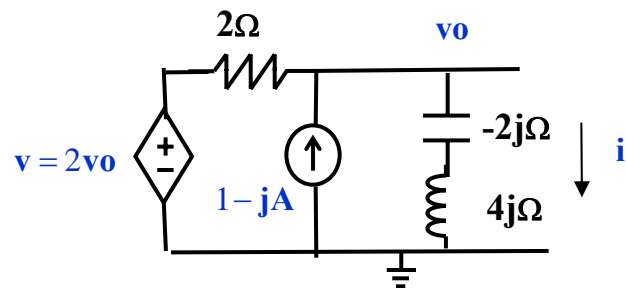

$$\frac{2v_o - v_o}{2\Omega} + 1 - j = \frac{v_o}{2j\Omega} \quad (7)$$

$$jv_o + 2j(1 - j) = v_o$$

$$\therefore v_o = \frac{2j(1 - j)}{1 - j} = 2jV \quad (5)$$

$$i = \frac{v_o}{2j\Omega} = 1A \quad (2)$$

