


1

(26)

(a) If $v(t) = 10 \cos(1kt + 30^\circ) \text{V}$, $Z = 2\Omega$, find $i(t)$.
Find also the power factor of Z , and power stored in Z .

(b) If $i(t) = 5 \cos(1kt + 30^\circ) \text{A}$, $Z = 2\text{mF}$,
find Z in Ω and find $v(t)$.

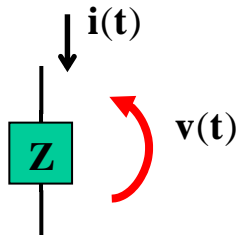(c) If $i(t) = 5 \cos(1kt - 30^\circ) \text{A}$, $v(t) = 10 \cos(1kt + 30^\circ) \text{V}$,
 Z is R in series with X . Find Z in Ω and find R .
Find also the apparent power S of Z .



(a) $i(t) = 5 \cos(1kt + 30^\circ) \text{A}$ (3)

$$\text{PF} = 1 \quad (2)$$

$$Q_R = 0 \quad (2)$$

(b) $Z = \frac{1}{j\omega C} = \frac{1}{j(1k)2\text{mF}} = -0.5j\Omega \quad (2)$

$$v(t) = 2.5 \cos(1kt - 60^\circ) \text{V} \quad (5)$$

(12)

(c)


$$\therefore \mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{10\angle 30^\circ \text{V}}{5\angle -30^\circ \text{A}} = 2\angle 60^\circ \Omega$$

$$\text{or } = 2\cos 60^\circ + 2j\sin 60^\circ = 1\Omega + j1.732\Omega$$

$$\therefore \mathbf{R} = 1\Omega \quad (2)$$


$$\therefore \mathbf{S} = \mathbf{V} * \mathbf{I} = \frac{10\text{V}}{\sqrt{2}} * \frac{5\text{A}}{\sqrt{2}} = 25\text{VA} \quad (5)$$

(5)

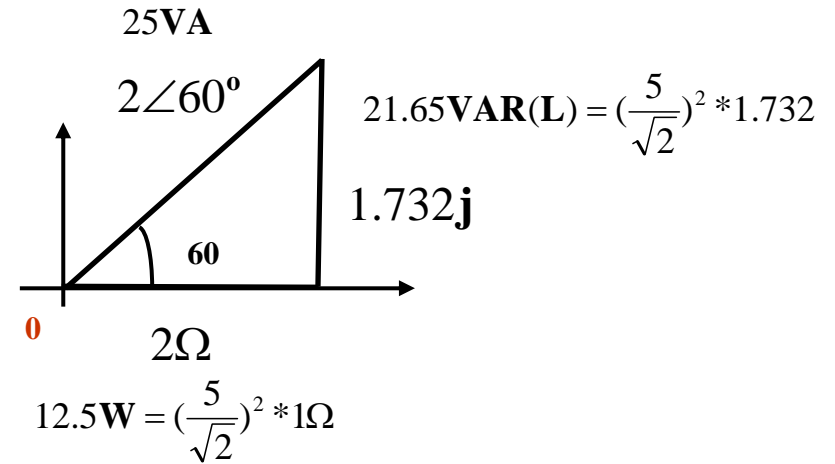

2

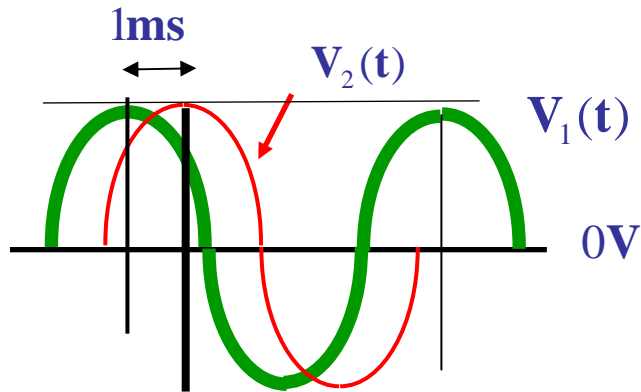(13) If $V_2(t) = 5 \cos 400\pi t$ V, find $V_1(t)$.



$$\therefore V_1(t) = 5 \cos(\omega t + \theta) \text{ V} = 5 \cos(400\pi t + 72^\circ) \text{ V} \quad (3)$$

$$V_2(t) = 5 \cos 2\pi f * t \text{ V} = 5 \cos 2 * \pi * 200t \text{ V}$$

$$\therefore T = \frac{1}{f} = \frac{1}{200} = 5\text{ms} \quad (6)$$



$$\theta = \frac{t}{T} * 360^\circ = \frac{1\text{ms}}{5\text{ms}} * 360^\circ = 72^\circ \quad (4)$$

(13)

3


(a) Draw V_1 and I_1 in a phasor diagram.

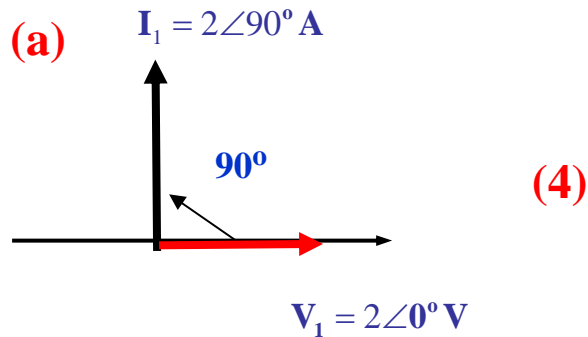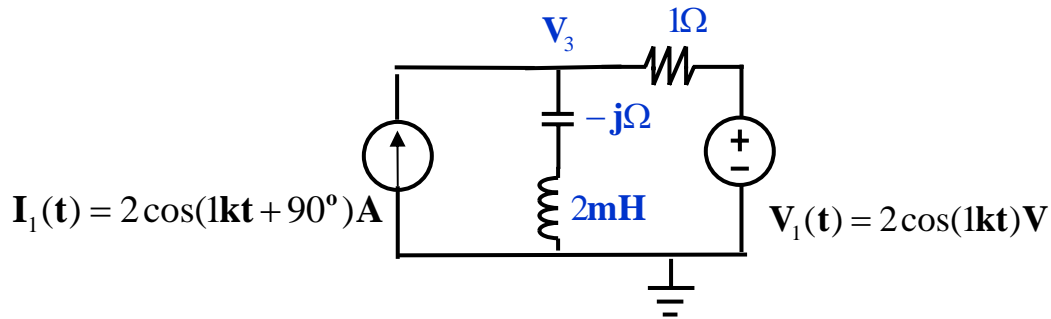(b) Use superposition to find the phasor V_3 . (25)




(b) $j\omega L = j(1k)2mH = 2j\Omega$ (2)

Use superposition

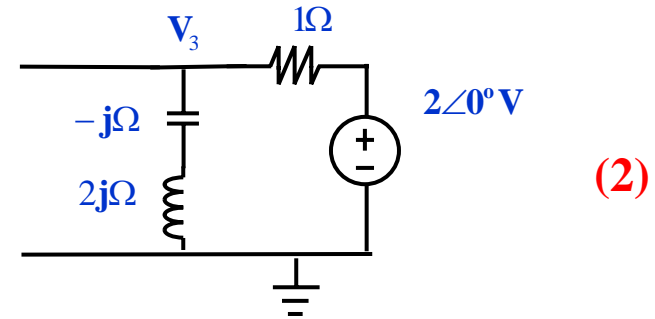

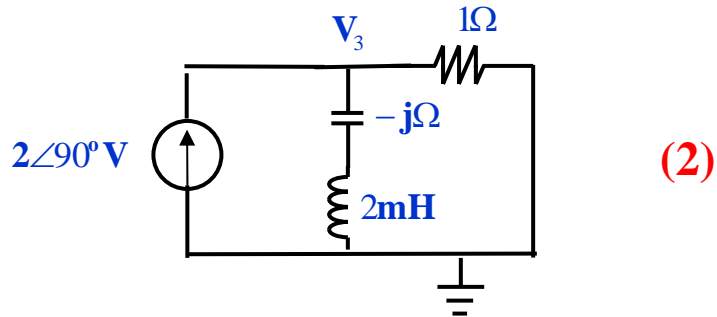
$$\therefore V_{3,2V} = 2\angle 0^\circ \text{ V} * \frac{j\Omega}{1\Omega + j\Omega} = \frac{2j}{1+j} \text{ V} \quad (5)$$



$$\therefore V_{3,2A} = 2\angle 90^\circ \text{ A} * \frac{1\Omega * j\Omega}{1 + j\Omega} = \frac{2j * j}{1 + j} \text{ V} \quad (5)$$
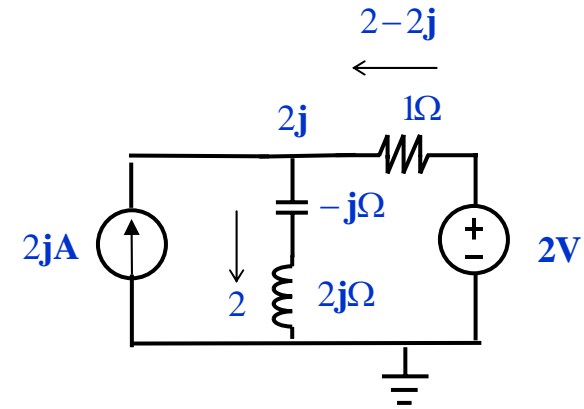
$$\therefore V_3 = \frac{2j}{1 + j} + \frac{2j * j}{1 + j} = \frac{2j(1 + j)}{1 + j} = 2j = 2\angle 90^\circ \text{ V} \quad (5)$$



$$\frac{2 - V_2}{1\Omega} + 2j = \frac{V_2}{j}$$


$$\therefore j(2 - V_2) - 2 = V_2$$

$$\therefore V_2 = \frac{2 - 2j}{-j - 1} = 2j$$


$$\therefore V_3(t) = 2\cos(1kt + 90^\circ) \text{ V}$$

4

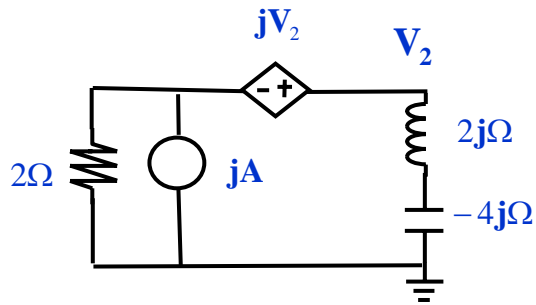Find V_2 . The voltage dependent voltage source is in volt and equal to jV_2 . (14)




Use KCL

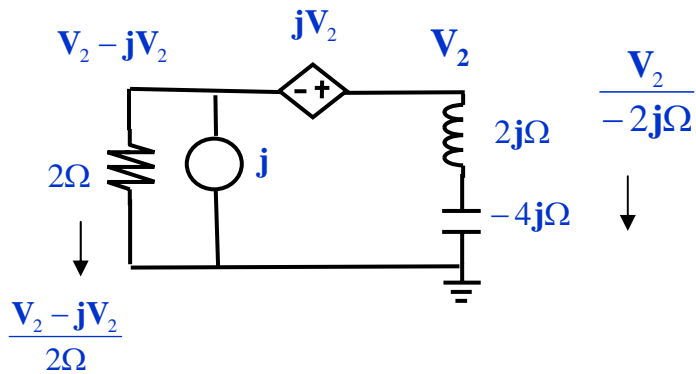

$$j = \frac{V_2}{-2j\Omega} + \frac{V_2 - jV_2}{2\Omega} \quad (7)$$

$$j = \frac{V_2}{-2j} + \frac{V_2}{2} - \frac{jV_2}{2} = \frac{V_2}{2}$$


$$\therefore V_2 = 2jV \quad (7)$$

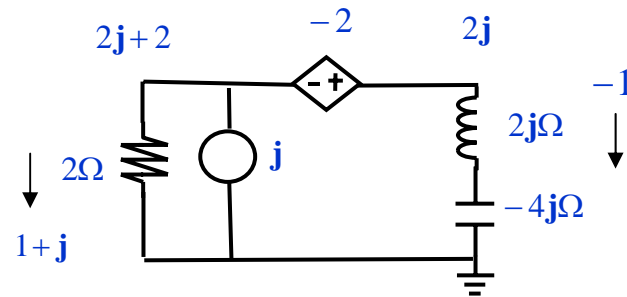

5

Reactive power Q of the 1kW electric heater is 750VAR(L). (a) Find the power factor PF of the heater. (b) If load B is connected in parallel to the heater such that the power factor of the combined load is 0.95 lagging, find the element and value of load B.

(21)

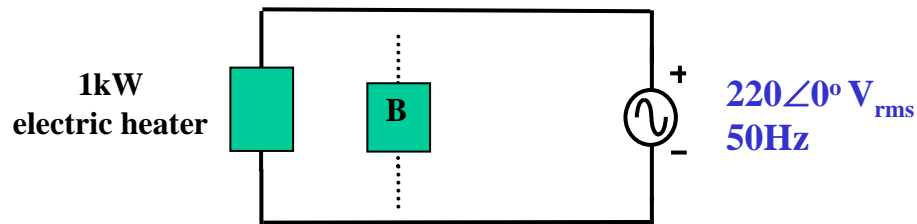

(a)


$$\tan \theta = \frac{Q}{P} = \frac{750 \text{ VAR(L)}}{1 \text{ kW}} = 0.75$$

$$\therefore \text{PF} = \cos \theta = \cos(\tan^{-1} 0.75) = 0.8 \text{ lagging} \quad (7)$$

(b)


$$\therefore Q_C \text{ required} = 750 - 1000 \tan(\cos^{-1} 0.95) \cong 421.316 \text{ VAR(C)} \quad (8)$$

$$\therefore C = \frac{|Q_C|}{V^2 \omega} \cong \frac{421.316}{(220^2) 2\pi 50} \cong 27.71 \mu\text{F} \quad (6)$$

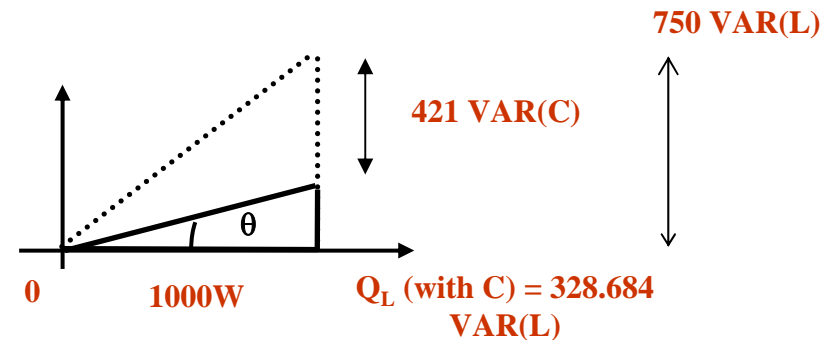

6

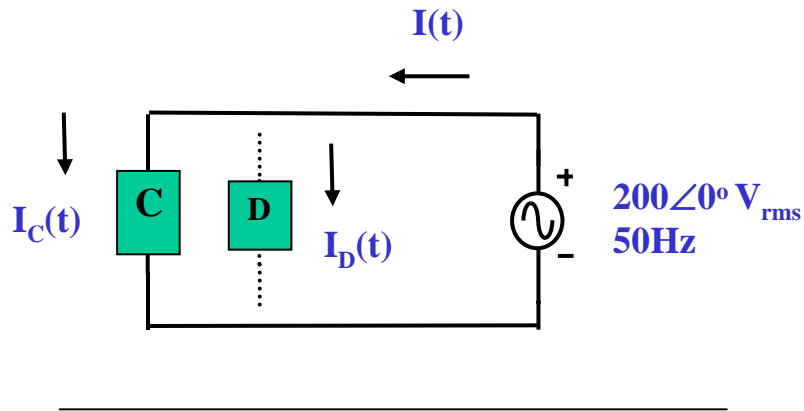Load C has 12kW and 5kVAR(L). (a) Find the apparent power S of load C. Find also I_C in Arms.
(b) If load D is connected in parallel to load C such that the power factor of the combined load is 1, find I_D in Arms. Find also $I(t)$. (22)



(a)

$$S = \sqrt{P^2 + Q^2} = \sqrt{12k^2 + 5k^2} = 13kVA$$

(5)

(b)

$$I_D = \frac{Q}{V} = \frac{5kVAR(L)}{200V_{rms}} = 25A_{rms} \quad (5)$$

$$I = \frac{P}{V} = \frac{12k}{200} = 60A_{rms}$$


$$I(t) = 60\sqrt{2} \cos(2\pi 50t)A \quad (8)$$

PF = 1, hence $I(t)$ and source are in phase

$$I = 60\angle 0^\circ$$

7

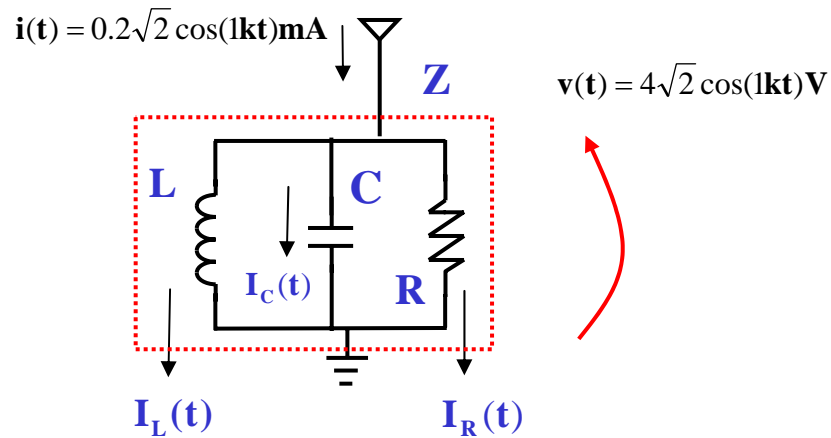In the circuit, $L = 0.5\text{H}$, $C = 2\mu\text{F}$. (a) Find the resonant frequency of Z . Show that $I_R(t) = i(t)$. (b) Find also R , power consumed by Z , quality factor QF , and power stored in C . Given that $QF = R/X$. (26)



(a)

$$\therefore \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.5\text{H} * 2\mu\text{F}}} = \frac{1}{\sqrt{1 * 10^{-6}}} = 1\text{krad/s} \quad (4)$$

$\omega(=1k) = \omega_0 (=1k)$, Z is in resonance, $Z = R$

$$\therefore I_R(t) = i(t) = 0.2\sqrt{2} \cos(1kt)\text{mA} \quad (4)$$

(b)

$$\therefore R = \frac{v}{I_R} = \frac{4V_{\text{rms}}}{0.2\text{mA}_{\text{rms}}} = 20\text{k}\Omega \quad (4)$$


$$\therefore P = I^2 R = (0.2\text{mA}_{\text{rms}})^2 * 20\text{k}\Omega = 0.8\text{mW} \quad (4)$$

$$\text{or } P = VI = 4V_{\text{rms}} * 0.2\text{mA}_{\text{rms}} = 0.8\text{mW}$$

$$QF = \frac{R}{\omega_o L} = \frac{20k\Omega}{1k * 0.5H} = 40 = \frac{Q_c}{P} \quad (4)$$

$$\therefore Q_c = P * QF = 0.8mW * 40 = 32mVAR(C) \quad (6)$$
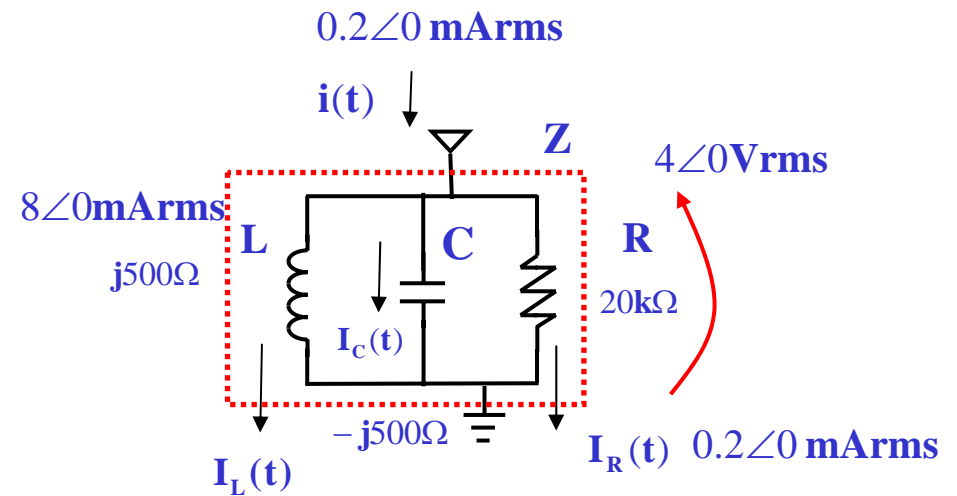
$$\begin{aligned} \therefore Q_c &= VI = 4V_{rms} * 0.2mA_{rms} * 40 \\ &= 32mVAR(C) \end{aligned}$$





$$\therefore I_C(t) = 0.2 * 40\sqrt{2} \cos(1kt + 90^\circ) mA$$

8

A series LCR tuner circuit is used to receive radio stations as shown in the resonance curve. (a) Find in Hz the resonant frequency f_o and bandwidth BW. Find also the quality factor QF of the tuner. (b) Find the value of L and find V_c in Vrms. (c) If R is changed from 10Ω to 5Ω (with L, C and $v(t)$ unchanged), find the new BW and new maximum I_o in mA rms. Given that $QF = X/R = f_o/BW$. (30)

(I_o in mA rms)

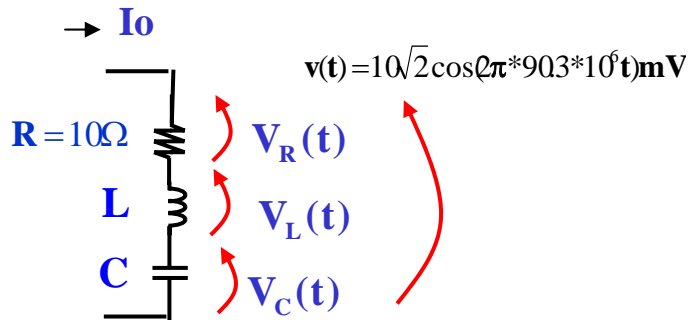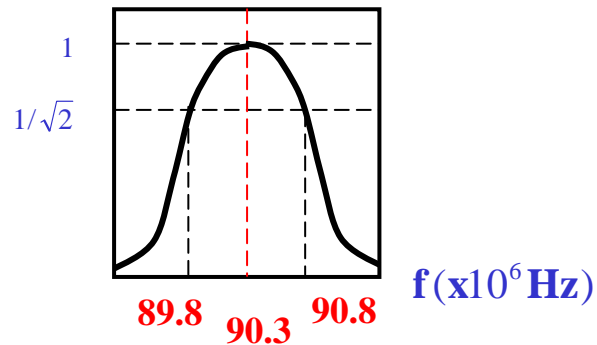

$$(a) \quad f_o = 90.3 \text{ MHz} \quad (2)$$

$$BW = 1 \text{ MHz} \quad (3)$$


$$QF = \frac{f_o}{BW} = \frac{90.3 \text{ MHz}}{1 \text{ MHz}} = 90.3 \quad (3)$$

$$(b) \quad L = \frac{QF * R}{\omega_o} = \frac{90.3 * 10\Omega}{2\pi * 90.3 \text{ MHz}} \cong 1.59 \mu\text{H} \quad (5)$$

$$V_c = I_o * X_C = I_o * QF * R \\ = 1 \text{ mA} * 90.3 * 10\Omega = 903 \text{ mV}_{\text{rms}} \quad (7)$$

$$(c) \quad QF = X/R = 180.6 = f_o/BW \\ \therefore BW = 0.5 \text{ MHz} \quad (5)$$
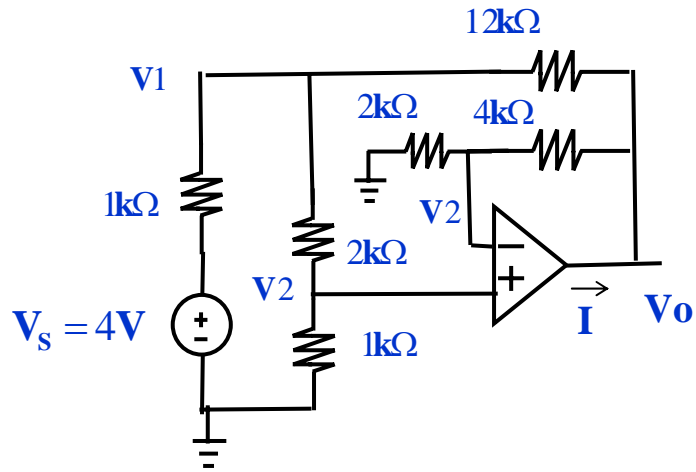
$$\max I_o = \frac{10 V_{\text{rms}}}{5\Omega} = 2 \text{ mA}_{\text{rms}} \quad (5)$$



$$\therefore V_2 = \frac{V_o}{2k\Omega + 4k\Omega} * 2k\Omega = \frac{V_o}{3} \quad (4)$$

$$\therefore V_1 = \frac{V_2}{1k\Omega} * 3k\Omega = 3V_2 = V_o \quad (4)$$


$$\therefore \frac{V_s - V_1}{1k\Omega} = \frac{V_1 - V_2}{2k\Omega} \quad (4)$$

$$\frac{4V - 3V_2}{1k\Omega} = \frac{2V_2}{2k\Omega}$$

$$\therefore V_2 = 1V$$


$$\therefore V_o = 3V \quad (5)$$

$$I = 0.5mA \quad (3)$$

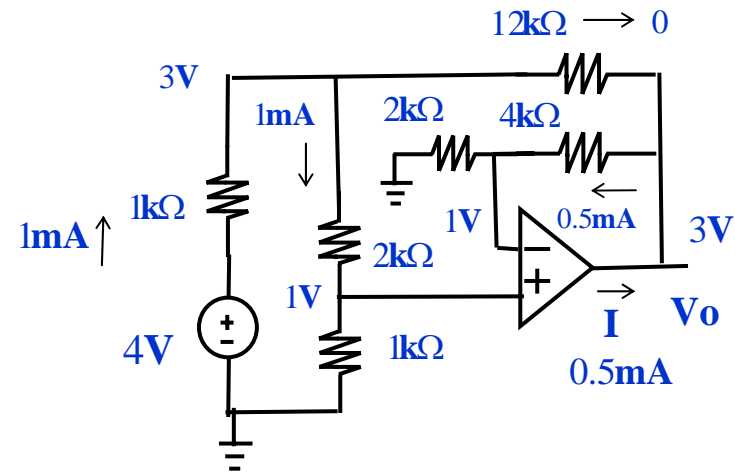


9

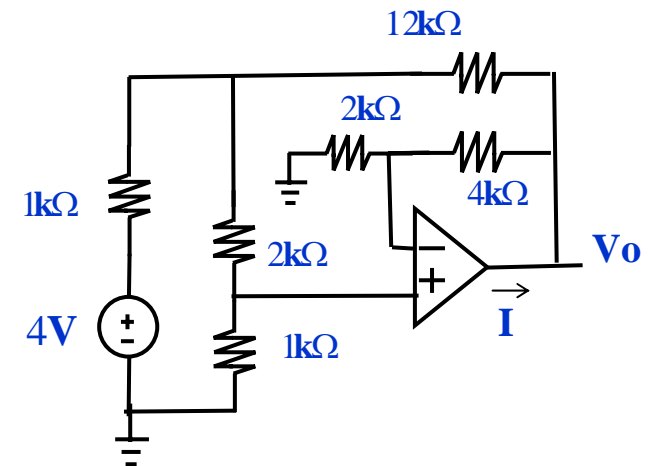Find V_o and I . Assume the op amp is ideal. (20)



10

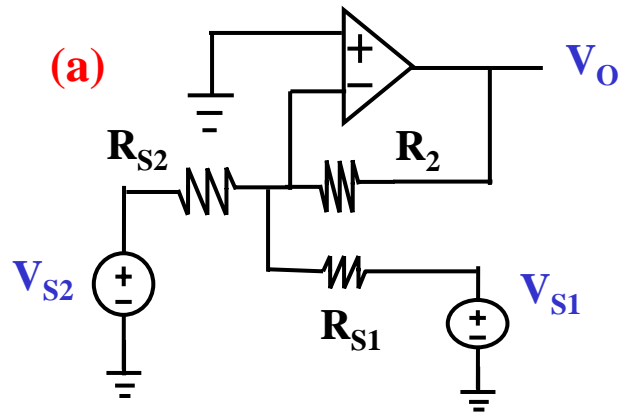
(a) Find the equation relating V_o , V_{S1} , V_{S2} , R_{S1} , R_{S2} , and R_2 . Assume the op amp is ideal. (9)



(a)
$$\therefore \text{KCL} \Rightarrow \frac{V_{S1} - 0}{R_{S1}} + \frac{V_{S2} - 0}{R_{S2}} = \frac{0 - V_o}{R_2} \quad (7)$$

$$V_o \cong -\frac{R_2}{R_{S1}} V_{S1} - \frac{R_2}{R_{S2}} V_{S2} \quad (2)$$

(b)

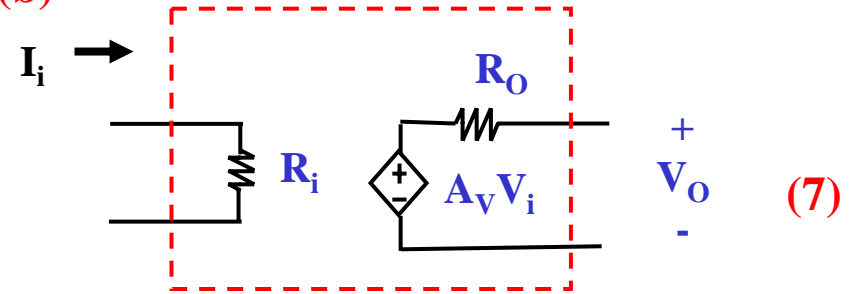

ideal I to V amplifier, $R_i = 0$ (2)

(b)

Draw the circuit model for a **resistance (I to V) amplifier**.
What is the ideal value of the input resistance of the amplifier? (9)