
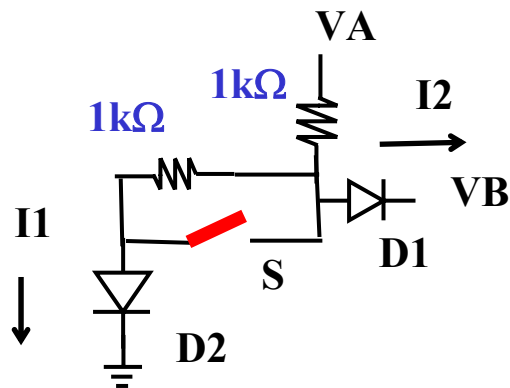


3

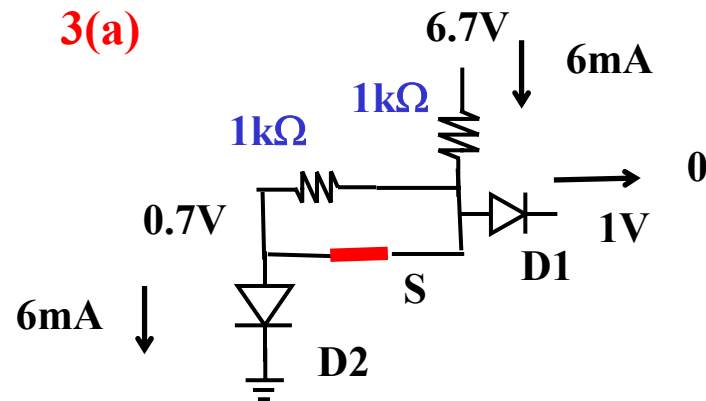(a) Given  $V_A = 6.7\text{V}$ ,  $V_B = 1\text{V}$ . If  $S$  is closed, find  $I_1$  and  $I_2$ . Assume  $D_1$  and  $D_2$  are offset diodes with  $V_F = 0.7\text{V}$ . (12)



3(a)



$$I_1 = 6\text{mA}$$

$$I_2 = 0\text{mA}$$

(12)


(12)

3

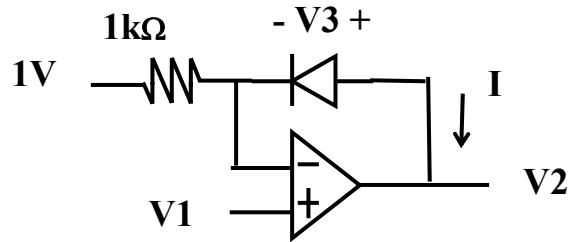3. (b) In the ideal op amp circuit, the diode equation is

$$I_D = 10^{-13} \text{ A} * [e^{\frac{V_D}{25\text{mV}}} - 1]$$

Find  $I$  if  $V_2 = V_1 + 0.6\text{V}$ . (12)




3(b)

$$\therefore V_3 = 0.6\text{V}$$

$$\therefore I = -I_0 (e^{\frac{0.6\text{V}}{25\text{mV}}} - 1)$$

$$= -10^{-13} \text{ A} * (e^{\frac{600\text{m}}{25\text{m}}} - 1) \cong -2.65\text{mA}$$

(12)

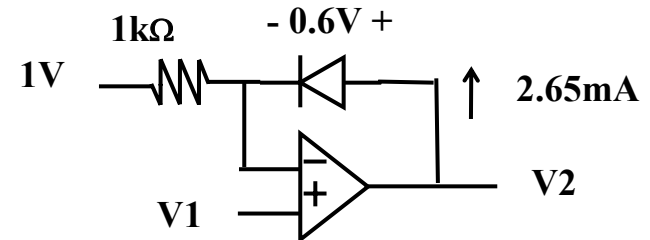


(19)

4



In the ideal diode circuit, sketch  $V_o(t)$ .

(a) If  $X = C$ .


(b) If  $X = R$ . (19)

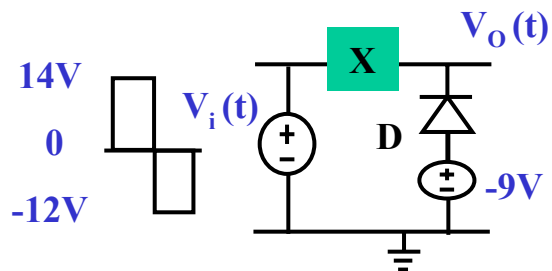

(a)

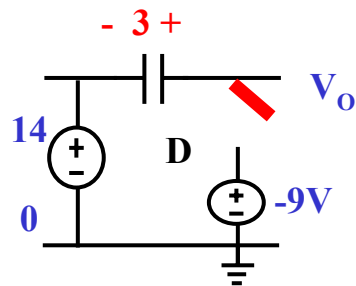
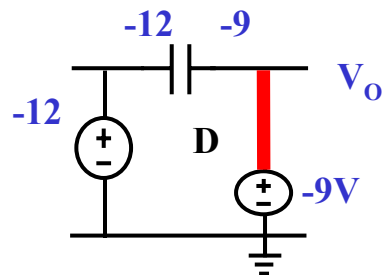


$$V_o = V_i + V_c = V_i + 3V$$

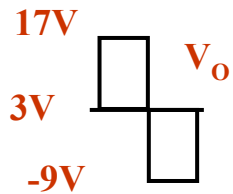

(11)

(b)

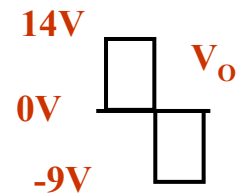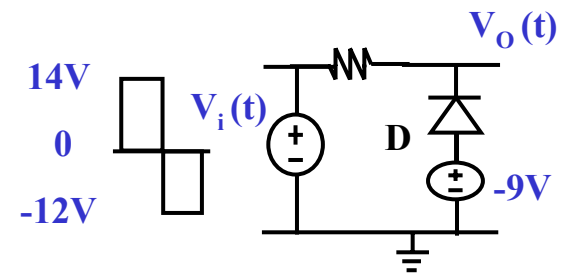

(8)

5



In the ideal op amp circuit, the diode has the reverse characteristics as shown.

(a) Find the model of the diode at breakdown.

(b) If  $V_1 = 10\text{V}$ , find  $V_3$  and  $I_2$ .


(c) If  $V_1 = 25\text{V}$ , find  $V_3$ .

(31)

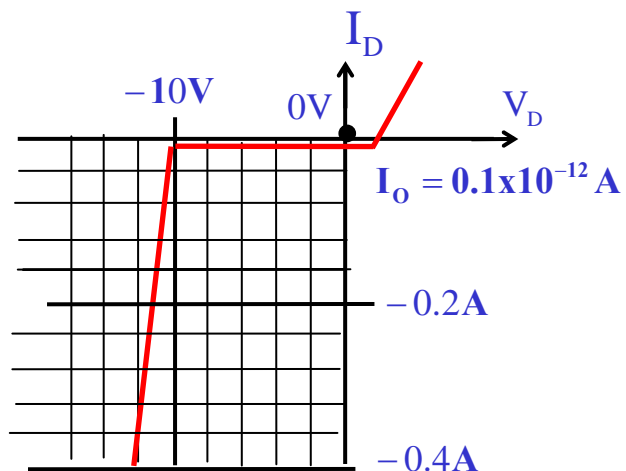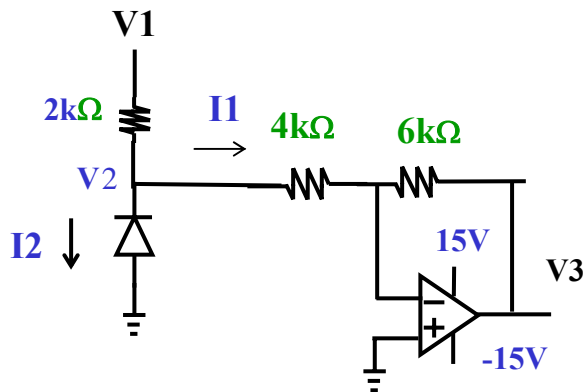

(a)

Model at breakdown

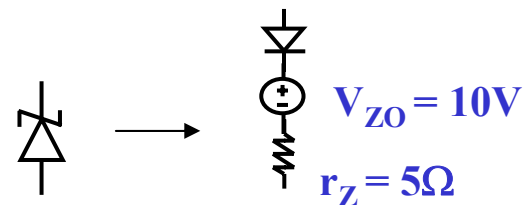

(7)

(b)


$V_1 = 10\text{V}$  diode is not breakdown and is an off diode (open)

$$\therefore V_3 = -\frac{6\text{k}\Omega}{4\text{k}\Omega + 2\text{k}\Omega} 10\text{V} = -10\text{V}$$

(6)

$$\therefore I_2 = 0.1 \times 10^{-12} \text{ A}$$

(4)

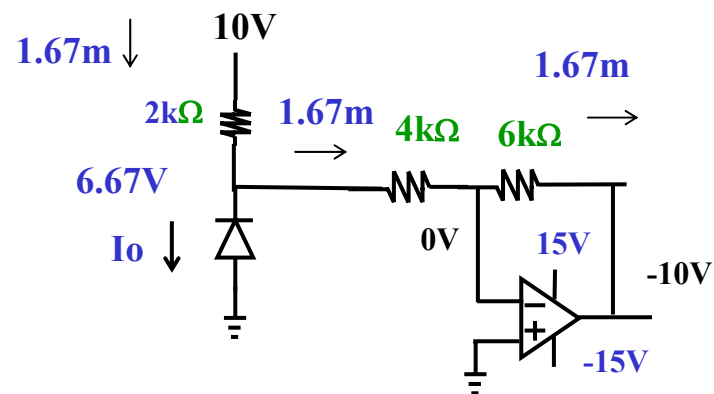


**V1= 25V    Zener is breakdown**

$$\therefore \frac{25 - V_2}{2\text{k}\Omega} \cong \frac{V_2 - 10}{5\Omega} + \frac{V_2}{4\text{k}\Omega}$$

$$2(25 - V_2) \cong 800(V_2 - 10) + V_2$$

$$\therefore V_2 \cong \frac{8000 + 50}{803} \cong 10.02\text{V} \quad (10)$$

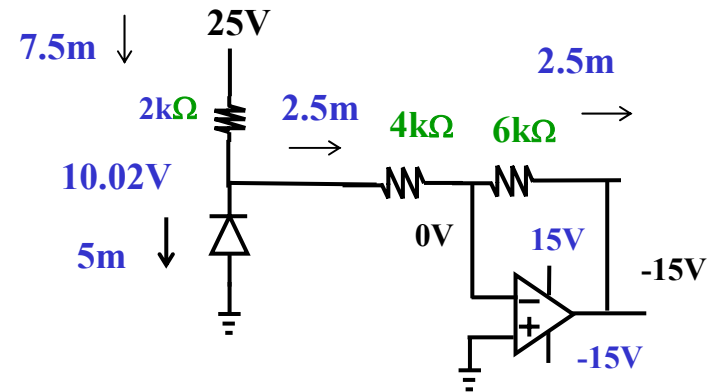
$$\therefore V_3 = -\frac{6\text{k}}{4\text{k}} * 10.02 = -15\text{V} \quad (4)$$



6

Draw the cross sectional structure of a NPN BJT transistor operated in the amplifier mode, describe the movement of electrons, and explain briefly the equation  $I_C / \alpha \cong I_E$ .  
If  $I_C \cong \beta I_B$ , find  $\beta$  in terms of  $\alpha$ . (16)

(a)

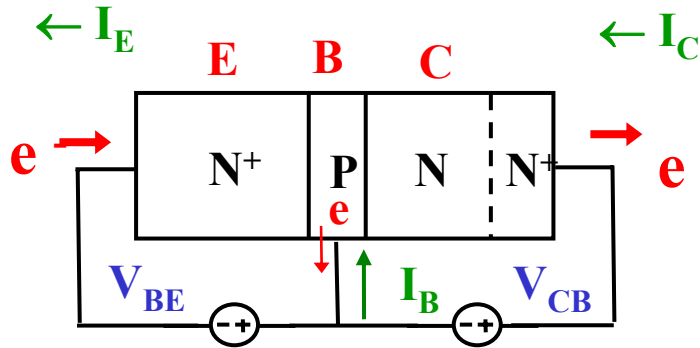

1. EB Junction is a forward bias (on) diode and BC is reverse bias (off) diode

2. E is very heavily doped ( $N^+$  for NPN). E has many electrons,

3. B is very thin. So most electrons injected from E (to B) are attracted to C and

$$I_C \cong \alpha I_E \quad (10)$$

$$I_E \cong \frac{I_C}{\alpha} = I_B + I_C = \frac{I_C}{\beta} + I_C$$




$$\text{hence } \frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{\alpha}{1 - \alpha} \quad (6)$$

7

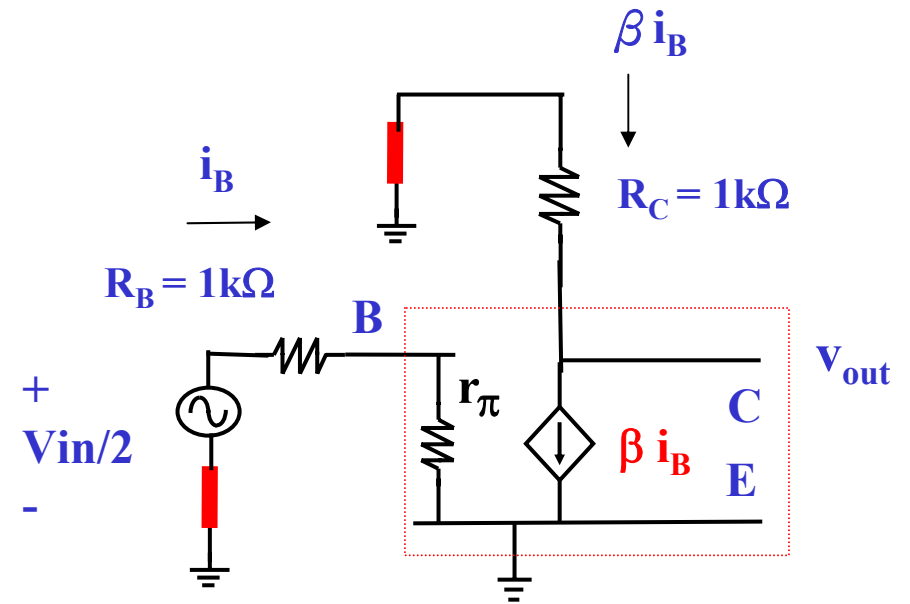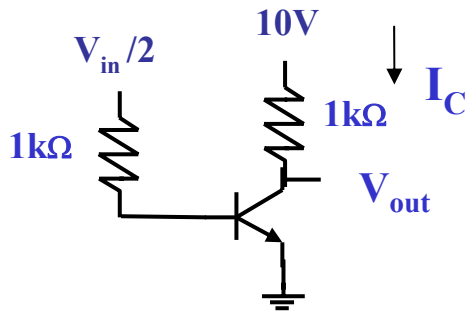
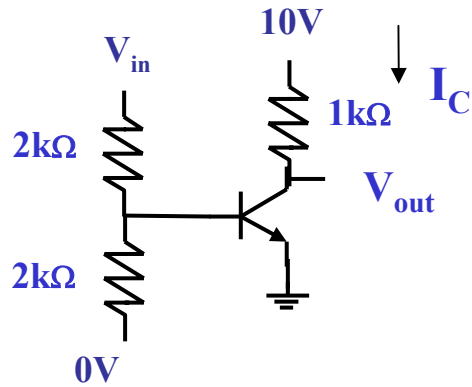
Sketch the small signal (AC) equivalent circuit of the BJT amplifier and find the voltage gain  $A_v (= V_{out} / V_{in})$ .  
 Given  $r_{\pi} = 0\Omega$ ,  $\beta = 100$ , and  $V_{CESAT} = 0.2V$ ,  $V_{BE(ON)} = 0.7V$ . (16)



(8)

$$\begin{aligned} \therefore A_v &= \frac{V_{OUT}}{V_{in}} = \frac{-\beta i_B R_C}{2i_B (R_B + r_{\pi})} \\ &= \frac{-\beta R_C}{2R_B + 2r_{\pi}} = \frac{-(100)(1k\Omega)}{2k\Omega} \cong -50 \end{aligned} \quad (8)$$

8

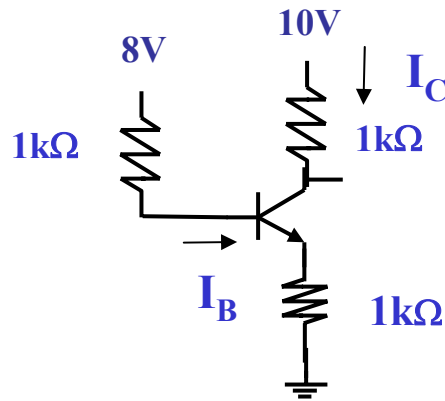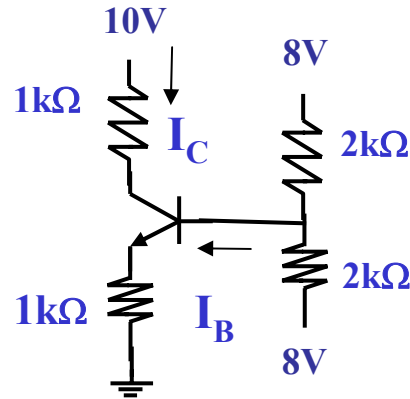Find  $I_C / I_B$ . Show clearly your reasons.For the BJT, given  $V_{BE(ON)} = 0.7V$ ,  $\beta = 100$ ,  $V_{CESAT} = 0.2V$ . (24)

$$I_B \cong \frac{10V - 0.2V}{1k\Omega + 1k\Omega} * \frac{1}{\beta} = 0.049mA \quad \text{when } V_{CE} = 0.2V$$

$$\text{But } I_B \cong \frac{8V - 0.7V}{\beta * 1k\Omega + 1k\Omega} \cong 0.072mA$$

 $\therefore$  BJT is in saturation

$$\therefore I_B = \frac{V_B - V_{BE}}{R_B + (1 + \beta^*)R_E} = \frac{V_{CC} - V_{CESAT}}{\beta^*R_C + (1 + \beta^*)R_E}$$


$$\therefore I_B = \frac{8V - 0.7V}{1k\Omega + (1 + \beta^*)1k\Omega} = \frac{10V - 0.2V}{1k\Omega(1 + 2\beta^*)}$$

$$\therefore 7.3V(1 + 2\beta^*) = 9.8V(2 + \beta^*)$$

$$\therefore 7.3V + 14.6\beta^* = 19.6V + 9.8\beta^*$$

$$\therefore \beta^* = \frac{19.6V - 7.3V}{14.6 - 9.8} = 2.5625$$

(24)

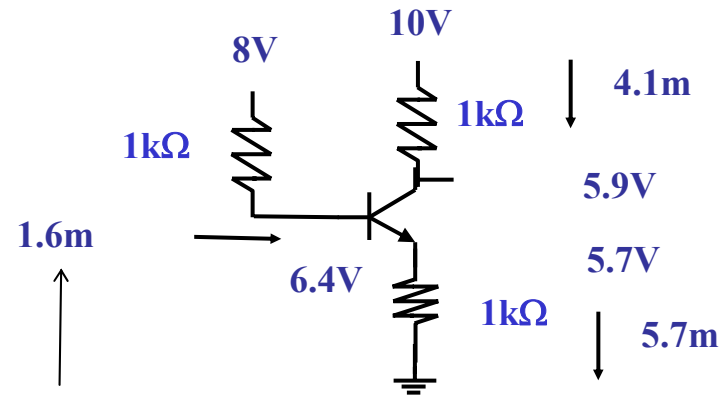

$$I_B = \frac{8V - 0.7V}{(2.5625 + 1) * 1k\Omega + 1k\Omega} = 1.6mA$$





9

Given the BJT circuit below and the  $I_C$ - $V_{CE}$  curve of the BJT.  $V_{CEQ} = 5V$ . (a) Draw the load line  $V_{CE} = V_1 - I_C R_1$ , and locate the Q point on the load line. Find also  $R_1$

(b) Estimate the voltage gain  $\Delta V_O / \Delta V_i$  from the  $I_C$ - $V_{CE}$  curves and sketch  $V_O(t)$ .

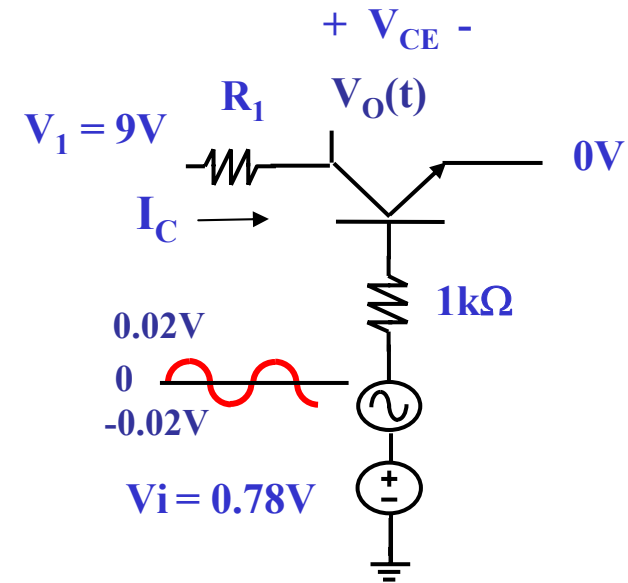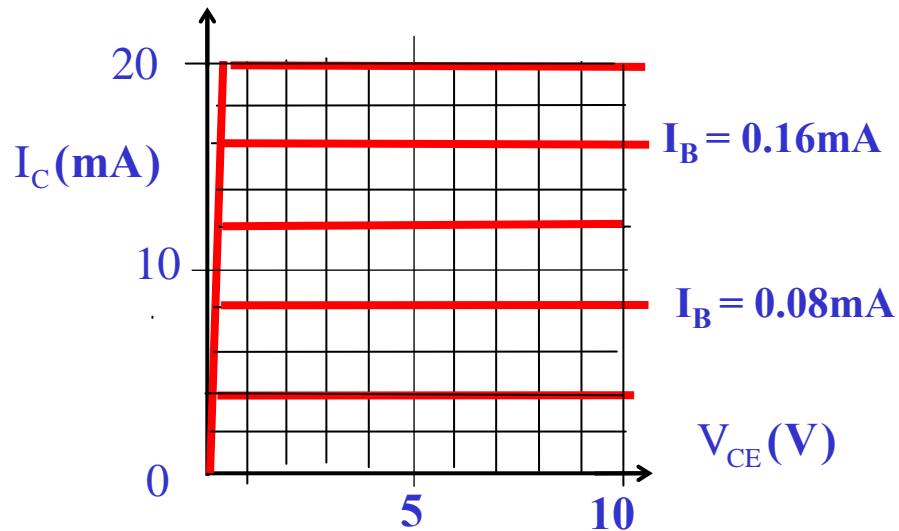(30)


For the BJT, given  $V_{BE(ON)} = 0.7V$ ,  $V_{CESAT} = 0.2V$ .



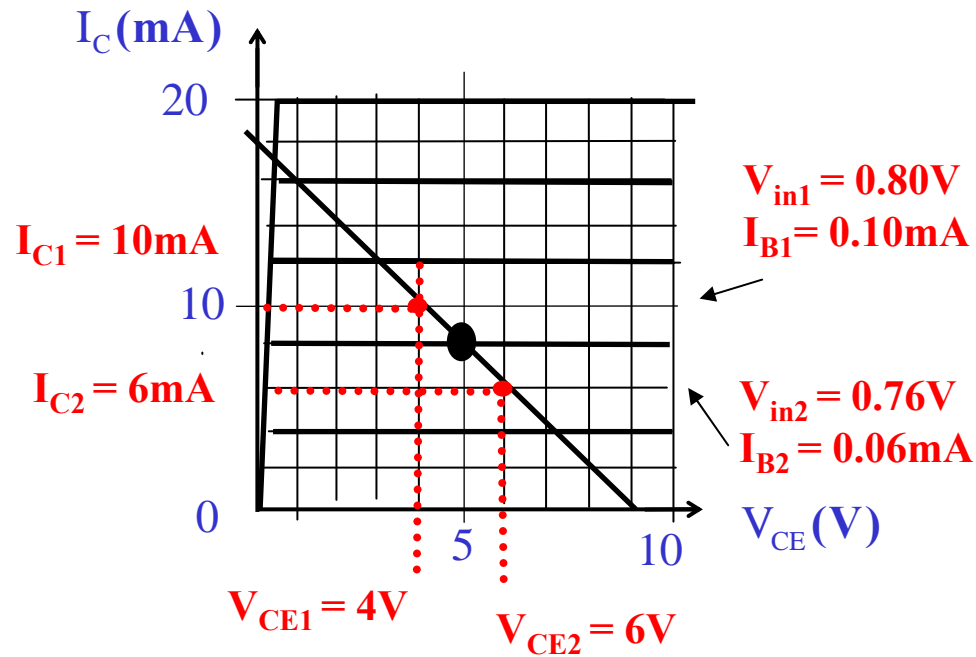(a) Draw load line,

$$\therefore I_B = \frac{0.78V - 0.7V}{1k\Omega} = 0.08mA \quad (5)$$


$$\therefore R_1 = \frac{V_{CC}}{I_C} = \frac{9V}{18mA} = 500\Omega \quad (5)$$



$$\begin{aligned} \text{voltage gain } A_v &= \frac{dV_{CE}}{dV_{in}} = \frac{V_{CE2} - V_{CE1}}{V_{in2} - V_{in1}} \\ &\cong \frac{6V - 4V}{0.76V - 0.8V} = -50 \end{aligned} \quad (8)$$

(8)

$V_O(t)$  V

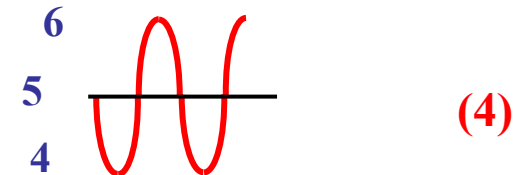

10

(a) Name two advantages of MOSFET. (b) Draw the cross sectional diagram for an enhancement NMOSFET and describe very briefly the structure.


(15)

(a)

small size (scaled down easily)  
and low power consumption.

(4)

(b)

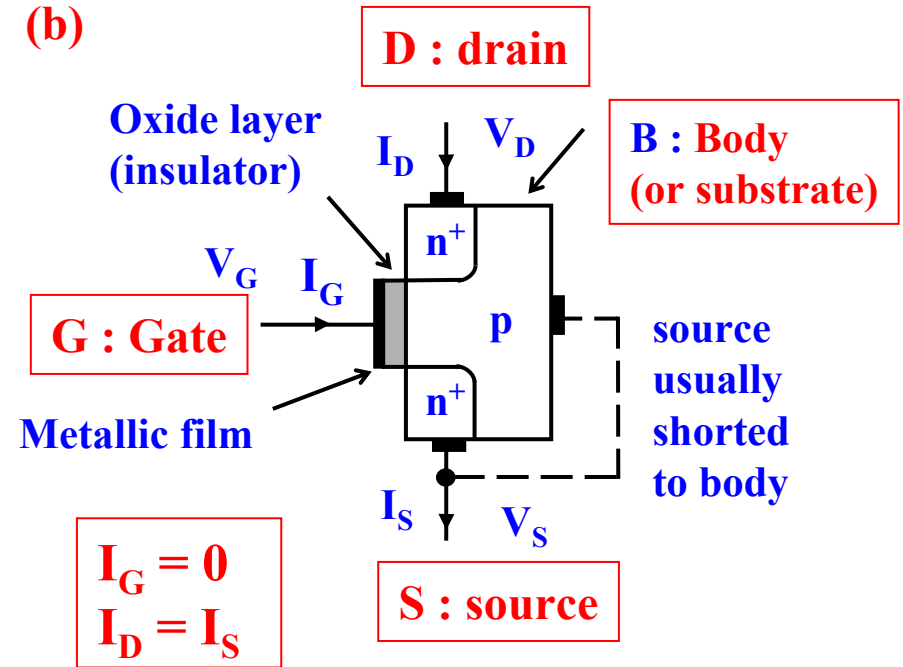


An NMOSFET consists of a **metal gate** insulated from a **p-type semiconductor** substrate (or body) by an insulating layer of **silicon dioxide**. On either side of the gate there are **n type** regions forming the **drain and source**.

(11)

11

Find  $V_o$ .

Given the NMOS are all identical,  $V_T = 2V$   
 $K = 1\text{mA/V}^2$ .

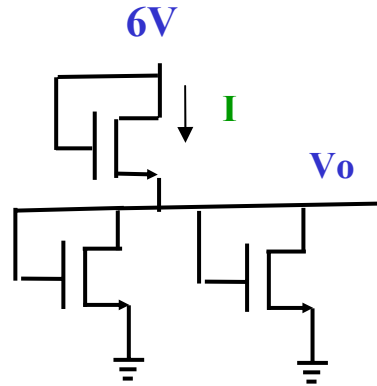Since  $V_{DS} = V_{GS}$ Since  $V_{GS} > V_T$ Hence  $V_{DS} > V_{GS} - V_T$ 

If  $V_{GS} < V_T$  for any 1 MOS (MOS off)  
 the other MOS will be saturated  
 Which is not possible

Hence only possibility is all 3 NMOS are **(6)**  
in saturation

$$\therefore I_D = K (V_{GS} - V_T)^2$$

$$I = 1(6 - V_o - 2)^2 = 1(V_o - 2)^2 + 1(V_o - 2)^2 \quad (7)$$

$$(4 - V_o)^2 = 2(V_o - 2)^2$$


$$16 - 8V_o + V_o^2 = 2V_o^2 - 8V_o + 8$$

$$V_o^2 - 8 = 0$$

$$V_o = \sqrt{8V} \cong 2.83V \quad (9)$$


$$I = 1(6 - V_o - 2)^2 = 1(6 - 2.83 - 2)^2 \cong 1.37\text{mA}$$

$$I = 1(V_o - 2)^2 = 1(2.83 - 2)^2 \cong 0.689\text{mA}$$

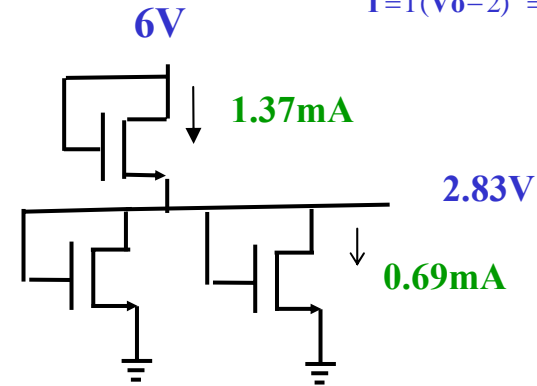11. Find  $V_o$ . Show clearly the reasons for your answers. (22)Given that the three NMOS are identical and  $V_T = 2V$ ,  $K = 1\text{mA/V}^2$ .At triode region,  $V_{GS} \geq V_T$ ,  $V_{DS} < V_{GS} - V_T$ ,  $I_D = 2K(V_{GS} - V_T)V_{DS} - KV_{DS}^2$ At saturation region,  $V_{GS} \geq V_T$ ,  $V_{DS} \geq V_{GS} - V_T$ ,  $I_D = K[(V_{GS} - V_T)^2]$

12

Find K and RD.

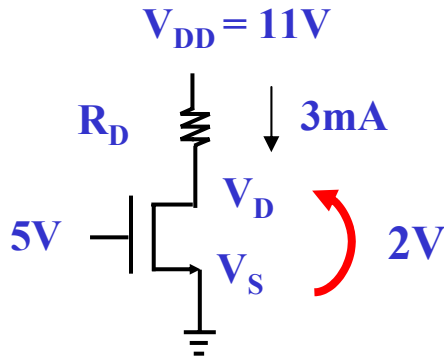Given  $V_T = 1V$ .

$$\therefore R_D = \frac{11V - 2V}{3mA} = 3k\Omega \quad (4)$$

 $V_{GS} = 5V$ ,  $V_{DS} = 2V$ , MOS is Triode.

$$\text{Since } V_{DS} < V_{GS} - V_T \quad V_{GS} > V_T \quad (3)$$

$$\therefore I_D = 2K[(V_{GS} - V_T)V_D - \frac{V_D^2}{2}]$$

$$3mA = 2K[(5V - 1V)2V - \frac{4V^2}{2}] = 2K[6V^2]$$

$$\therefore K = 0.25mA / V^2 \quad (8)$$

$$3mA = 2 * 0.25[(5V - 1V)2V - \frac{4V^2}{2}] = 2 * 0.25[6V^2]$$

Find K and RD . Show clearly the reasons for your answers. (15)

Given that  $V_T = 1V$ .

At triode region,  $V_{GS} \geq V_T$ ,  $V_{DS} < V_{GS} - V_T$ ,  $I_D = 2K(V_{GS} - V_T)V_{DS} - KV_{DS}^2$   
 At saturation region,  $V_{GS} \geq V_T$ ,  $V_{DS} \geq V_{GS} - V_T$ ,  $I_D = K[(V_{GS} - V_T)^2]$

13

(a) Explain very briefly the meaning of gain bandwidth product of a real op amp.

---

(a)

**Gain Bandwidth Product (GBP)**


Gain of op amp circuit x bandwidth  
of op amp circuit = constant

(5)

13

(b)

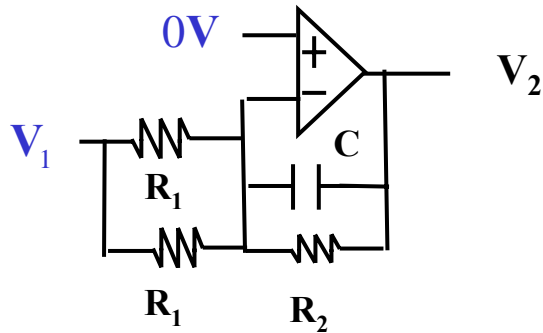Find the voltage gain  $V_2 / V_1$  in terms of  $R_1$ ,  $R_2$ ,  $C$  and  $j\omega$ .  
 If  $\omega_0$  is 1krad/s, find  $C$ . Estimate  $V_2(t)$  if  $V_1(t) = 2\cos 5tV$ .  
 Given that  $R_2 = 10k\Omega$ ,  $R_1 = 5k\Omega$ , and  $\omega_0 = 1/CR_2$ . Is the op amp circuit a low pass filter? Assume the op amp is ideal.  
 (22)



- (b) In the ideal op amp circuit, find the voltage gain  $V_2 / V_1$  in terms of  $R_1$ ,  $R_2$ ,  $C$  and  $j\omega$ .  
 If  $\omega_0 = 1\text{krad/s}$ , find  $C$ . Estimate also  $V_2(t)$  if  $V_1(t) = 2\cos 5tV$ .  
 Given that  $R_2 = 10k\Omega$ ,  $R_1 = 5k\Omega$ , and  $\omega_0 = 1/C \cdot R_2$ . Is the op amp circuit a low pass filter? (27)

(22)

$$\therefore Z_2 = \frac{R_2 \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{j\omega CR_2 + 1}$$

$$G = \frac{V_2}{V_1} = -\frac{Z_2}{Z_1} = -\frac{\frac{R_2}{j\omega CR_2 + 1}}{R_1 / 2} = -\frac{2R_2}{R_1} \frac{1}{1 + j\omega CR_2} \quad (10)$$

$$\therefore C = \frac{1}{\omega_0 R_2} = \frac{1}{1\text{krad/s} \cdot 10k\Omega} = 0.1\mu F \quad (3)$$

When frequency = 5rad/s,

$$V_2 \cong \frac{-2 \cdot 10k}{5k} \frac{1}{1 + j5/1k} \cdot V_1$$

$$V_2(t) \cong -8 \cos(5t)V \quad (6)$$

Circuit is a low pass filter (3)

14

In an ideal op amp filter circuit, the complex transfer function  $G (= V_O / V_S)$  is given as.  $\frac{-20}{1+2j\omega CR}$

Given that  $1/CR = 200\text{krad/s}$

(a) Plot the magnitude of  $G$  ( $|G|$ ) versus  $\omega$ . Show clearly the value of  $|G|$  when  $\omega = 0$ , cut-off frequency, and  $\infty$  in your plot.

(b) If  $V_S(t) = 2 \cos 200kt \text{ V}$ , find  $V_O(t)$ .  
(24)

(b)

$$G = \frac{-20}{1+2j*200k*CR} = \frac{-20}{1+j2}$$

$$\therefore V_O = 2\angle 0^\circ * \frac{-20}{1+2j} = \frac{-40}{\sqrt{5}\angle 63.4^\circ}$$

$$V_O(t) = -\frac{40}{\sqrt{5}} \cos(200kt - 63.4^\circ) \text{ V} \quad (12)$$

(a)

