

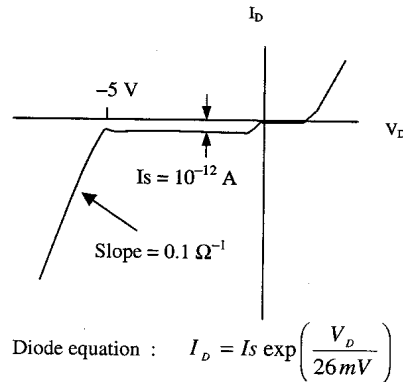
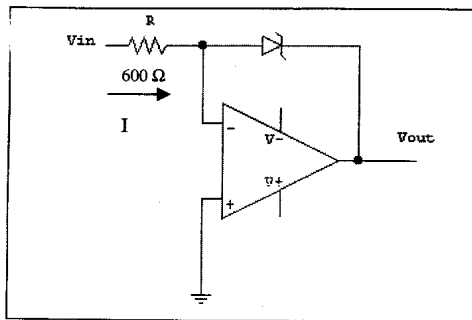
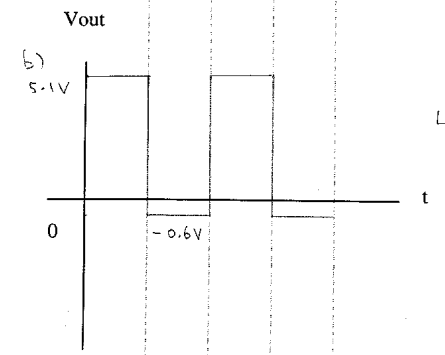


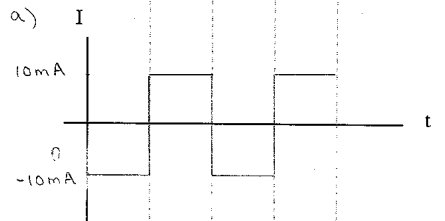7. Given the following circuit diagram, the input voltage  $V_{in}$  and the I-V characteristics of the zener diode.



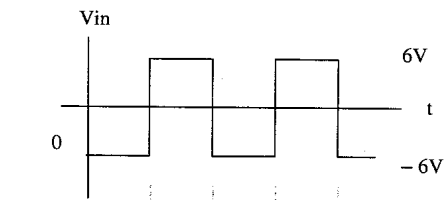- a) Sketch the current  $I$ . Show your calculations clearly. (6 marks)  
b) Sketch the output voltage  $V_{out}$ . Show your calculations clearly. (20 marks)



$$\begin{aligned} a) \quad I &= \frac{V_{in}}{R} \\ &= \frac{6 \text{ V}}{600} \\ &= 10 \text{ mA} \end{aligned}$$

$$b) \quad I = 10 \text{ mA}$$

diode is forward biased

$$I = 10 \text{ mA} = I_s e^{\frac{-V_D}{26 \text{ mV}}}$$


$$\therefore V_D = -0.6 \text{ V}$$

$$I = -10 \text{ mA}$$


diode is breakdown

$$\begin{aligned} V_D &= 5 + \frac{10 \text{ mA}}{0.1} \\ &= 5.1 \text{ V} \end{aligned}$$

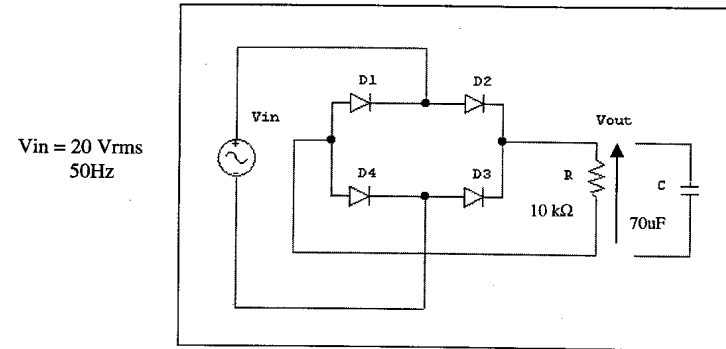8. Given the following ideal diode circuit diagram.



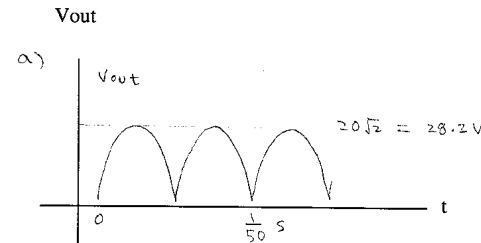- a) Sketch the output voltage  $V_{out}$ . Show clearly the voltage and time intercepts. (5 marks)  
b) Calculate the DC voltage  $V_{DC}$  across  $R$  ( $V_{DC} = 2V_m / \pi$ ). (3 marks)  
c) Find the peak inverse voltage (PIV) of the diode. (4 marks)  
d) Show that the ripple voltage  $V_r = 0.4 \text{ V}$  after a capacitor of  $70 \mu\text{F}$  is connected across  $R$ . (6 marks) Justify the assumption that you used. (3 marks)  
e) Estimate the DC voltage across  $R$  after the capacitor is added. (4 marks)



$$b) \quad V_{DC} = \frac{2V_m}{\pi} = \frac{2(28.2)}{\pi} = 18 \text{ V}$$

$$c) \quad \text{PIV} = V_m = 28.2 \text{ V}$$

$$d) \quad V_r = \frac{V_m}{2fRC} = \frac{28.2}{2(50)(10 \text{ k})(70 \mu\text{F})} = 0.4 \text{ V}$$

$$RC = 0.7 \text{ s} \gg \frac{1}{50} \text{ s} = T$$



$$\begin{aligned} e) \quad V_{DC} &\approx V_m - \frac{V_r}{2} = 28.2 - 0.2 \\ &= 28 \text{ V} \end{aligned}$$

9. In the ideal diode circuit,  $V_i$  is a 1 kHz triangular wave with 20V peak to peak (0V average).

(a) Sketch  $V_o(t)$ . (6)

(b) Show that the ripple voltage is roughly 0.5V. (8)

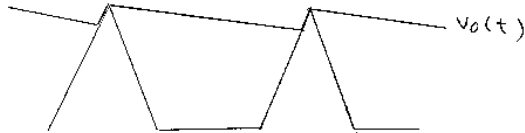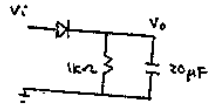(c) Show also that the peak inverse voltage (PIV) of the diode is 20V. (4)



6

$$CR = 20\mu \cdot 1k = 20ms$$

$$\gg T = 1ms$$

$$\therefore V_r = \frac{V_m T}{CR} = \frac{10V (1ms)}{20ms}$$



$$= 0.5V$$

8

$$PIV = 2V_m = 20V$$


4

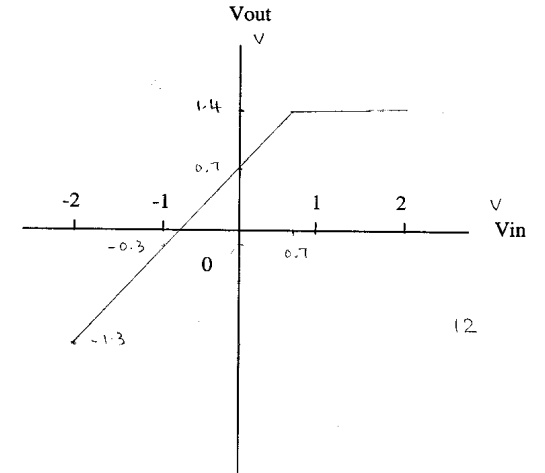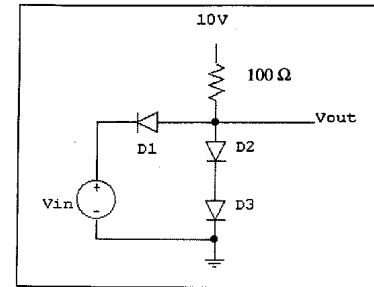9. a) Plot the transfer curve  $V_{out}$  versus  $V_{in}$  for the following circuit ( $-2V \leq V_{in} \leq 2V$ ). Assume  $V_D = 0.7V$  when the diode is on. Show clearly the voltages. (12 marks)





12

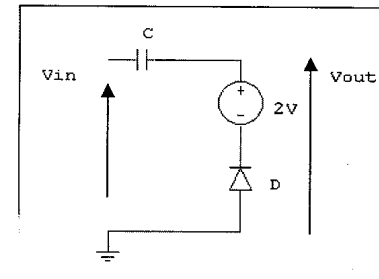b) Sketch  $V_{in}$  and  $V_{out}$  for the following circuit. Assume the diode is ideal. Show clearly the voltage and time intercepts. (12 marks)



$$V_{in} = 5 \sin 100\pi t \text{ V}$$

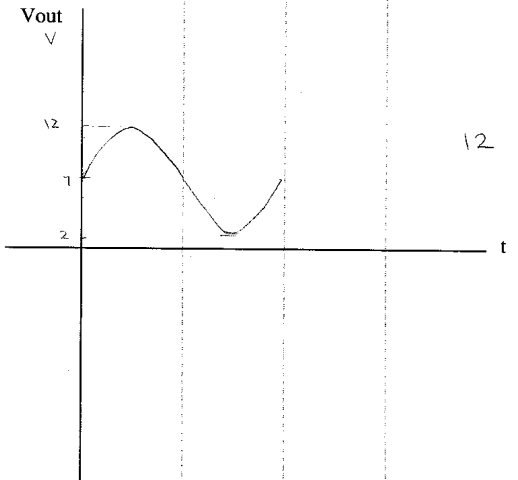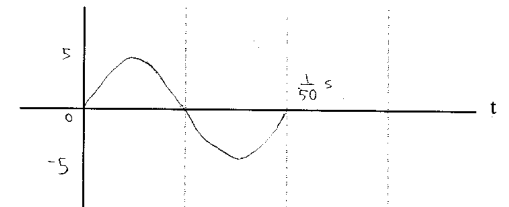

12

$$\omega = 2\pi f$$

$$= 100\pi$$



$$\therefore f = 50 \text{ Hz}$$

$$T = \frac{1}{50} \text{ s}$$

10. In the following diode circuit, the diode has the reverse characteristics as shown.

(a) Find  $V_o$  and  $I$  if  $V_i = 4V$ . (9)

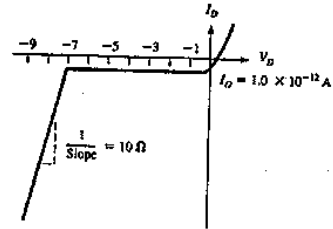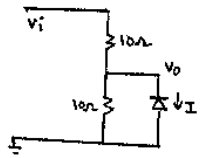(b) Show that  $I = 0.2A$  if  $V_i = 20V$ . (17)



$$V_i = 4V$$


$$V_o = 2V$$

$$I = I_o = 1pA$$

5

4

$$V_i = 20V$$

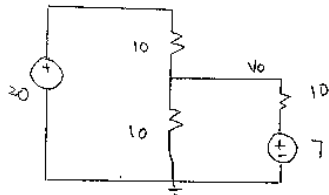

$$\therefore \frac{20 - V_o}{10} = \frac{V_o - 7}{10} + \frac{V_o}{10}$$

$$\therefore V_o = 9V$$

$$\therefore I = \frac{9 - 7}{10} = 0.2A$$



6

8


3

MC Poon 05/24/99

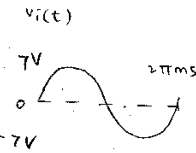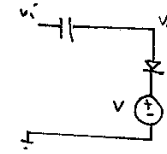6. (a) If  $V_i(t) = 7 \sin 1000t$  V and  $V = -2V$ , sketch  $V_i(t)$  and  $V_o(t)$  for the following ideal diode circuit. Show clearly the voltages and time in your sketch. (12)





$$V_o(t)$$

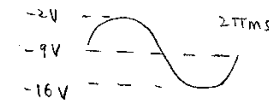

12

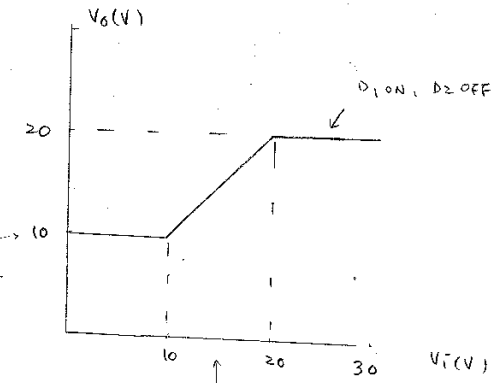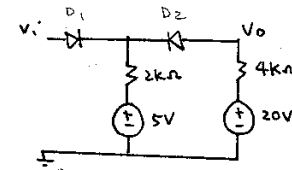(b) Plot  $V_o$  versus  $V_i$  for  $0V \leq V_i \leq 30V$  for the following ideal diode circuit. Show clearly all the voltages in your sketch. (13)



13