
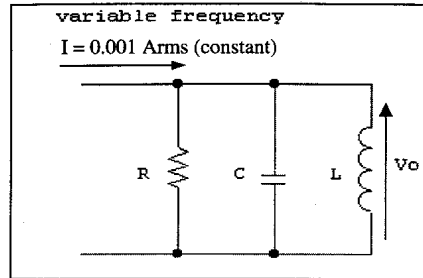


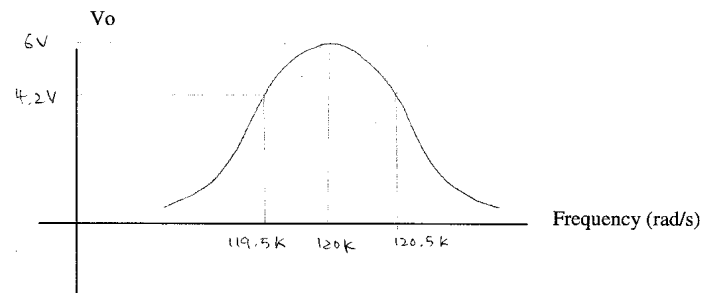1. The parallel RLC circuit shown below has a resonant frequency (ω_0) of 120k rad/s, a Q factor of 120 and a maximum V_o of 6 Vrms.



- a) Find the bandwidth. (4 marks)
 b) Sketch V_o versus frequency. Show the voltage at ω_0 and at the bandwidth in your sketch. (6 marks)
 c) Find the values of R, L and C. (14 marks)



$$a) BW = \frac{\omega_0}{Q} = \frac{120k}{120} = 1k \text{ rad/s} \quad 4$$


$$c) R = \frac{6V}{1mA} = 6k\Omega \quad 4$$

$$L = \frac{R}{\omega_0 Q} = \frac{6k}{120k(120)} = 0.42mH \quad 5$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(120k)^2 \cdot 0.42m} = 167nF \quad 5$$

5. Given the following circuit diagram. Each load contains only one element.

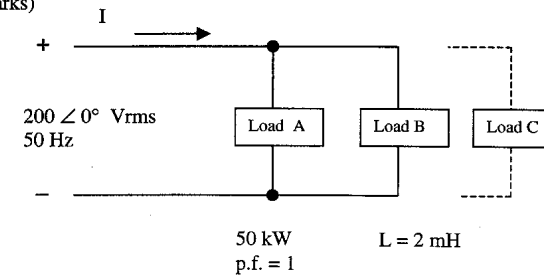- a) Determine the element and value of Load A. (5 marks)
 b) Calculate the reactive power of Load B. (5 marks)
 c) Calculate the total current I. (8 marks)
 d) Calculate the power factor. Show lagging or leading. (5 marks)
 e) If Load C is connected to improve the power factor to 1, calculate the reactive power of Load C. (5 marks)



$$a) A \text{ is } R$$

$$R = \frac{V^2}{P} = \frac{200^2}{50k} = 0.8\Omega \quad 5$$

$$b) Q_B = \frac{V^2}{2\pi f L} = \frac{200^2}{2\pi(50)(2m)} = 63.7 \text{ kvar} \quad 5$$

$$c) I = \frac{200}{0.8} + \frac{200}{j(2\pi \cdot 50)(2m)}$$


$$= 250 - 318j \text{ Arms} \quad 8$$

$$d) PF = \cos \theta = \cos \tan^{-1} \frac{63.7k}{50k}$$


$$= 0.62 \text{ lagging} \quad 5$$

$$e) Q_c = -63.7 \text{ kvar} \quad 5$$

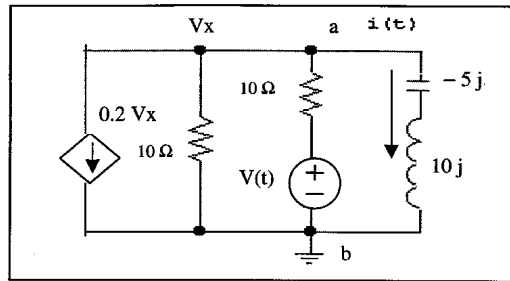6. Given : $V(t) = 20 \cos \omega t$ V. Use Norton's Theorem to find the current $i(t)$.



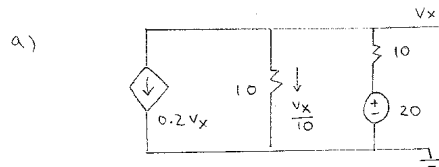- Find the open circuit voltage V_{oc} at terminals ab. (10 marks)
- Find the short circuit current I_{sc} at terminals ab. (7 marks)
- Show that the equivalent impedance $Z_{th} = 2.5\Omega$. ($Z_{th} = V_{oc} / I_{sc}$). (2 marks)
- Draw the Norton equivalent circuit of the whole circuit. (3 marks)
- Hence, find the current $i(t)$. (9 marks)
- Does $i(t)$ lag $V(t)$? (2 marks)




$$KCL = \frac{20 - V_x}{10} = \frac{V_x}{10} + 0.2 V_x$$

$$20 - V_x = V_x + 2 V_x$$

$$\therefore V_x = 5V = V_{oc}$$

10

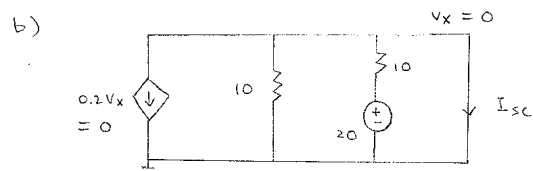


$$\therefore I_{sc} = \frac{20}{10} = 2A$$

7

$$c) \quad Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{5V}{2A} = 2.5 \Omega$$

2

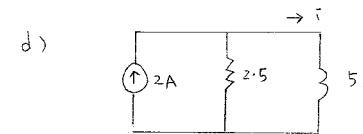

3

$$e) \quad \vec{i} = 2 \frac{2.5}{2.5 + 5j} = \frac{1}{0.5 + j} = \frac{1}{\sqrt{1.25} \angle 63^\circ}$$

6


$$\therefore i(t) = 0.89 \cos(\omega t - 63^\circ) A$$

3

$$f) \quad i(t) \text{ lags } v(t)$$

2

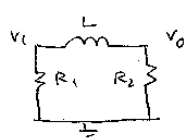3. In the following circuit, (a) find the complex transfer function $H (= V_o/V_i)$ if $R_1 = R_2 = 1\Omega$ and $L = 1H$. (b) Find the pole and zero of H . Find the frequency of V_i when (c) magnitude of V_o is one half the magnitude of V_i , and (d) phase of V_o is 30° lagging V_i . (e) What type of filter is the circuit? (f) Find the cut-off frequency if L is changed to $2mH$. (29)



$$(a) \quad \frac{V_o}{V_i} = \frac{R_2}{R_2 + j\omega L} = \frac{1}{1 + j\omega}$$

$$= \frac{1}{\sqrt{1+\omega^2}} \angle -\tan^{-1}\omega$$

9

$$(c) \quad \frac{V_o}{V_i} = \frac{1}{2} = \frac{1}{\sqrt{1+\omega^2}}$$

6

$$\therefore \omega = \sqrt{3} \text{ rad/s}$$

$$(d) \quad \theta = \tan^{-1}\omega = 30^\circ$$

6

$$\omega = \tan 30 = 0.577 \text{ rad/s}$$


(e) low pass filter

3

$$(f) \quad \omega_c = \frac{R}{L} = \frac{1}{2m} = 500 \text{ rad/s}$$

5

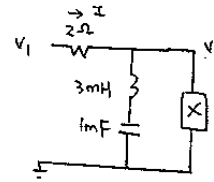5. In the following circuit, $V_1(t) = 2 \cos(1000t - \pi/2) \text{ V}$. (a) If X is an open circuit, find $V_2(t)$. Find the element and value of X (b) if $I = 0$, (c) if V_1 and I are in phase, and (d) if I leads V_1 by 45° . (35)



$$= -2j$$

$$j\omega L = j(1k)3m = 3j$$

$$\frac{1}{j\omega C} = \frac{1}{j(1k)1m} = -j$$

$$(a) \quad \therefore V_2 = -2j \frac{2j}{2+2j} = \frac{2}{1+j}$$

$$= \sqrt{2} \angle -45^\circ$$

$$\therefore V_2(t) = \sqrt{2} \cos(1kt - \frac{\pi}{4}), \text{ V}$$

12

$$(b) \quad I = 0 \text{ if } X \parallel 2j = \infty = \frac{X(2j)}{X+2j}$$

8

$$\therefore X = -2j = \frac{-j}{\omega C}$$

$$\therefore C = \frac{1}{2\omega} = \frac{1}{2k} = 0.5mF$$

$$(c) \quad V_1 \text{ and } I \text{ in phase if } X = 0$$

4

$$(d) \quad \frac{X(2j)}{X+2j} = -2j$$

11

$$\therefore X = -j$$

$$\therefore C = 1mF$$