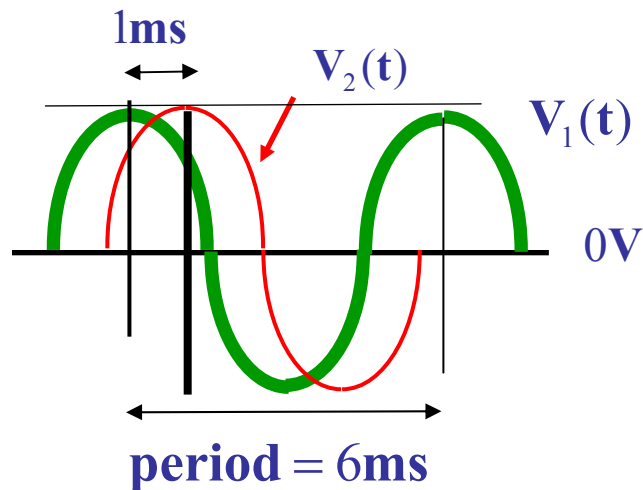


(16)

1

If  $V_2(t) = 5 \cos \omega t$  V, find  $V_1(t)$ .  
Draw also  $V_1$  and  $V_2$  in a phasor diagram. (16)




If  $V_2(t) = 5 \cos(\omega t)$  V

then  $\theta = \frac{t}{T} * 360^\circ = \frac{1\text{ms}}{6\text{ms}} * 360^\circ = 60^\circ$  (4)

then

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{6\text{ms}} \quad (4)$$
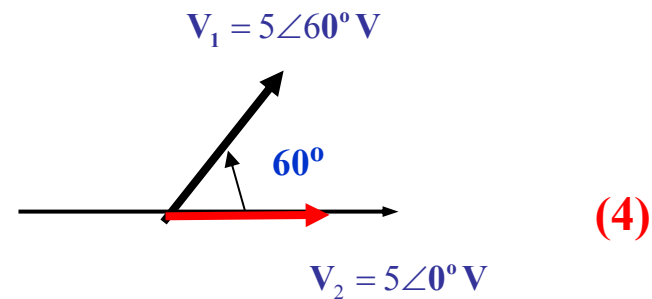
$$V_1(t) = 5 \cos(\omega t + \theta) \text{ V} = 5 \cos(\pi t / 3 + 60^\circ) \text{ V} \quad (4)$$



(12)


2

(12)

(a) If  $v(t) = 5 \cos(\omega t + 30^\circ) \text{V}$ ,  $i(t) = 2.5 \cos(\omega t + 30^\circ) \text{mA}$ , find  $X$ .

Find also the power factor of  $X$  and power stored in  $X$ .

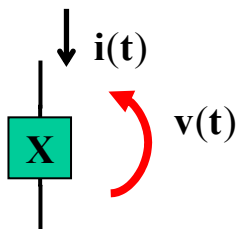(a) If  $v(t) = 10 \cos(\omega t + 30^\circ) \text{V}$ ,  $i(t) = 5 \cos(\omega t - 30^\circ) \text{mA}$ , find  $X$  in  $\Omega$  and power factor of  $X$ .



(a)

$$X = 2 \text{k}\Omega$$

(3)

$$\text{PF} = 1$$

(2)

$$Q_R = 0$$

(2)

(b)


$$X = j\omega L = j(1 \text{k})2 \text{m} = j2 \Omega \quad (3)$$

$$\text{PF} = 0$$

(2)

3

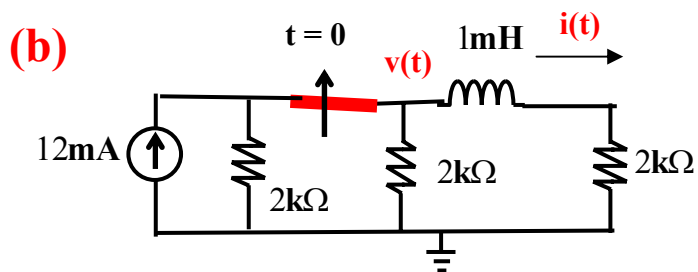- (a) Explain briefly why the current in an inductor is continuous with switching.
- (b) Circuit is at steady state for  $t < 0$ . At  $t = 0$ , the switch is opened. Find  $v(<0)$ ,  $v(0)$ ,  $v(10\tau)$  and sketch  $v(t)$ . (26)



$$(a) \quad E_L = \frac{L i_L(t)^2}{2} \quad (8)$$


$E_L$  (hence  $i_L$ ) must be continuous with time

$$i(0) = i(<0) = 12\text{mA} * \frac{2\text{k}\Omega}{2\text{k}\Omega // 2\text{k}\Omega + 2\text{k}\Omega} * \frac{1}{2} = 4\text{mA} \quad (4)$$


$$v(<0) = 4\text{mA} * 2\text{k}\Omega = 8\text{V} \quad (3)$$

$$v(0) = -i(0) * 2\text{k}\Omega \\ = -4\text{mA} * 2\text{k}\Omega = -8\text{V} \quad (4)$$

$$v(10\tau) \cong 0\text{V} \quad (3)$$

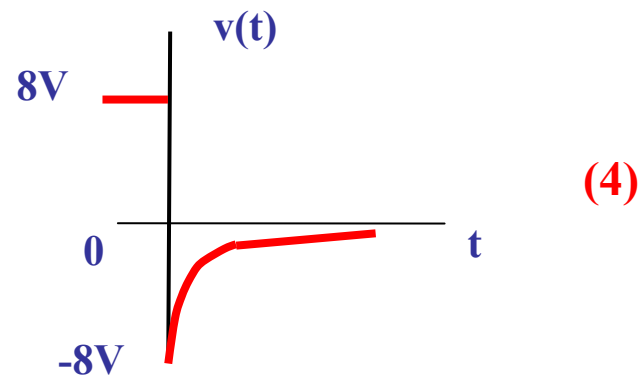

4

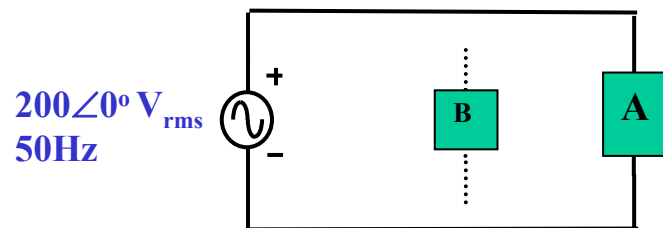

(a)

$$Q = P \tan \theta = 6\text{k} \tan(\cos^{-1} 0.6) = 8\text{kVAR(L)} \quad (6)$$

$$S = P / \cos \theta = 6\text{k} / 0.6 = 10\text{kVA} \quad (5)$$

(b)


$$\therefore Q_c \text{ required} = 8\text{k} - 6\text{k} \tan(\cos^{-1} 0.9) \cong 5.1\text{kVAR(C)} \quad (8)$$

$$\therefore C = \frac{|Q_c|}{V^2 \omega} \cong \frac{5.1\text{k}}{(200^2) 2\pi 50} \cong 0.41\text{mF} \quad (6)$$

For load A, power factor is 0.6 lagging and power consumed is 6kW. (a) Find the reactive power Q and apparent power S of load A.

(b) If load B is connected in parallel to load A such that the power factor of the combined load is 0.9 lagging, find the element and value of load B. (25)

5

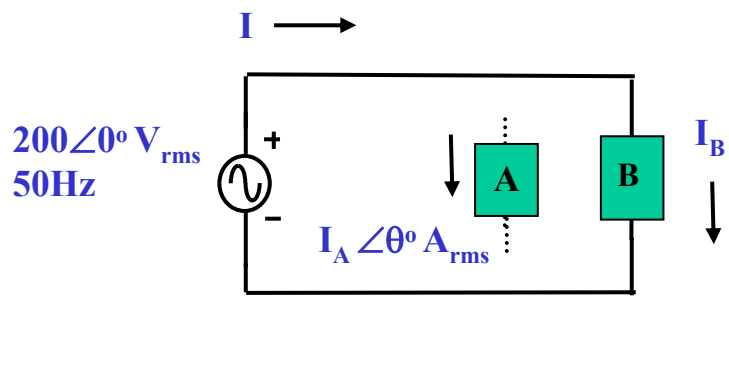

$$I_B = \frac{S}{V} = \frac{50\text{kVA}}{200\text{V}} = 250\text{A}_{\text{rms}} \quad (6)$$

$$I_A = \frac{Q}{V} = \frac{\sqrt{S^2 - P^2}}{200} = \frac{40\text{k}}{200} = 200\text{A}_{\text{rms}} \quad (6)$$

$$I = \frac{S}{V} = \frac{30\text{k}}{200} = 150\text{A}_{\text{rms}} \quad (6)$$

Power consumed by load B is 30kW. (a) If power supplied by source is 50kVA. Find  $I_B$  in Arms.  
 (b) If load A is connected in parallel to load B such that the power factor of the combined load is 1, find  $I$  and  $I_A$  in Arms.  
 (18)


6

In the circuit,  $v(t) = 2\sqrt{2} \cos(1kt) \text{ V}$

$$I(t) = 40\sqrt{2} \cos(1kt) \text{ mA}$$

Find power consumed by Z, power stored by L, and  $V_C(t)$ .

Does  $V_C(t)$  lag  $V(t)$ ? (22)

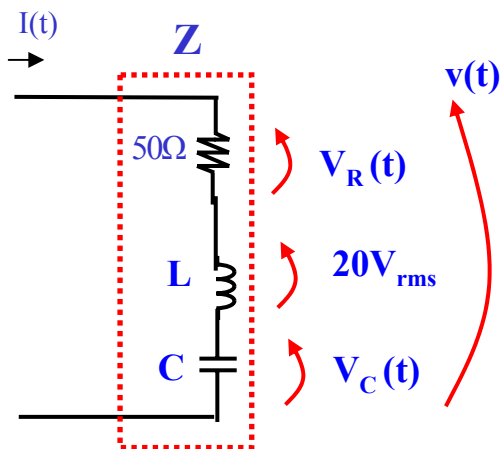


$$\therefore P = I^2 R = (40 \text{ mA}_{\text{rms}})^2 * 50 \Omega = 80 \text{ mW} \quad (6)$$

$$\therefore Q_L = VI = 20 \text{ V}_{\text{rms}} * 40 \text{ mA}_{\text{rms}} = 800 \text{ mVAR(L)} \quad (6)$$

Since  $V_R = v$ , hence  $V_C = -20 \text{ V rms}$



$$V_C(t) = 20\sqrt{2} \cos(1kt - 90^\circ) \text{ V} \quad (7)$$
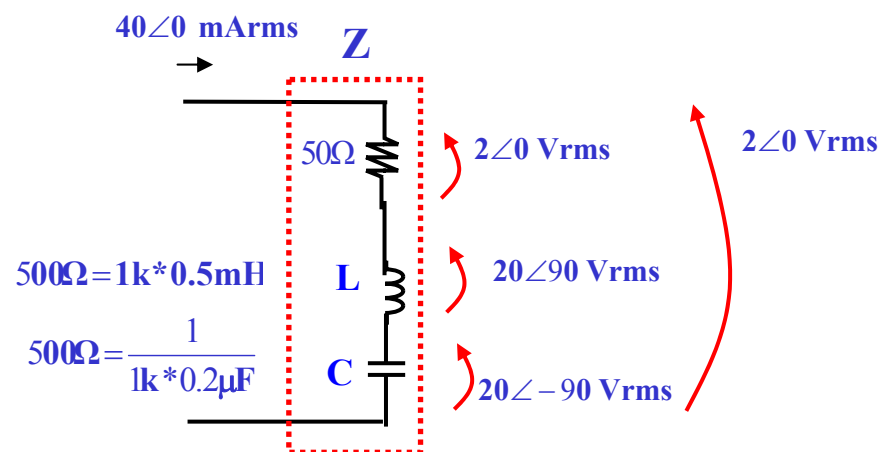
$$V_C(t) \text{ lags } V(t) \text{ by } 90^\circ \quad (3)$$



7

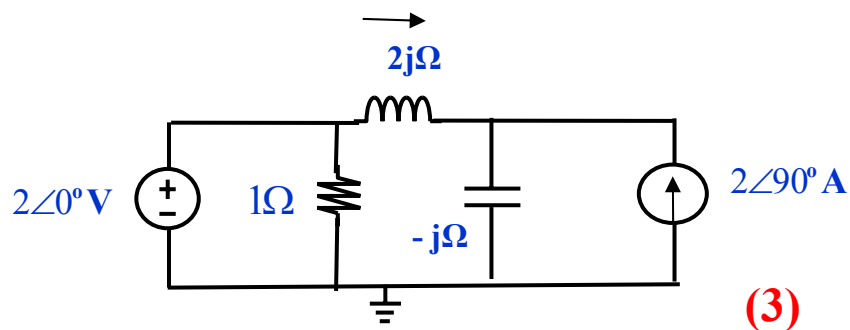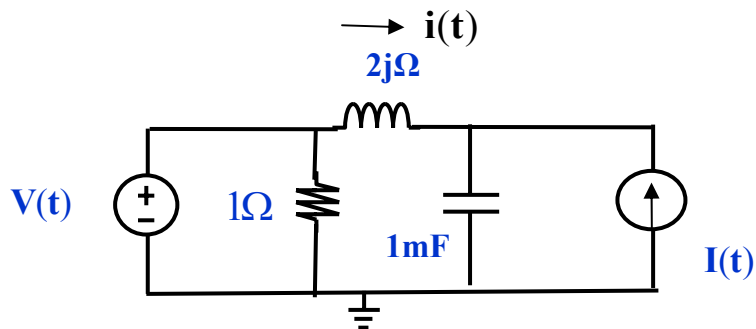In the circuit,  $V(t) = 2 \cos(1kt)V$  find  $i(t)$ . (20)  
 $I(t) = 2 \cos(1kt + 90^\circ)A$




$$\frac{1}{j\omega C} = \frac{1}{j(1k)1mF} = -j\Omega \quad (2)$$

Use superposition

$$\therefore i_{2V} = \frac{2\angle 0^\circ V}{j\Omega} \quad (5)$$

$$\therefore i_{2jA} = -2j * \frac{-j}{2j - j} = 2jA \quad (6)$$


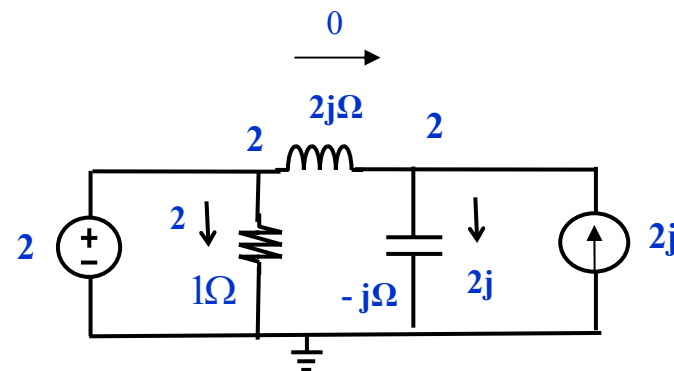
$$\therefore i = i_{2V} + i_{2jA} = \frac{2\angle 0^\circ V}{j\Omega} + 2jA = 0 \quad (4)$$



(24)


8

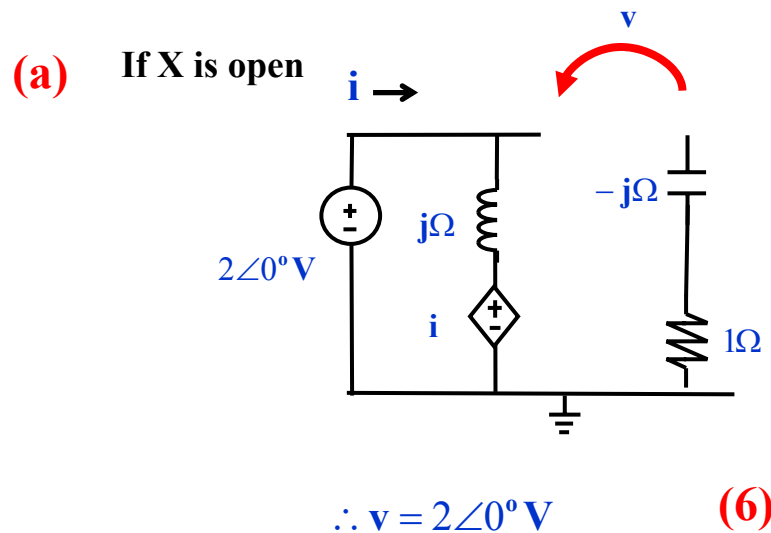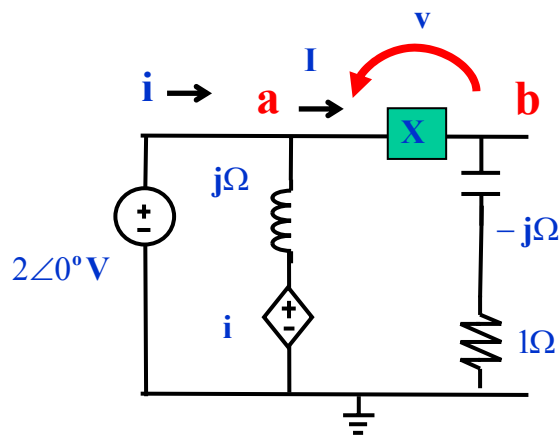- (a) If X is open, find  $v$ . (b) If  $X = 0 \Omega$ , find  $I$ .  
 (c) Find the Thevenin equivalent at terminals ab. (d) If  $I = 2\angle 0^\circ \text{ A}$ , find X.  
 (24)



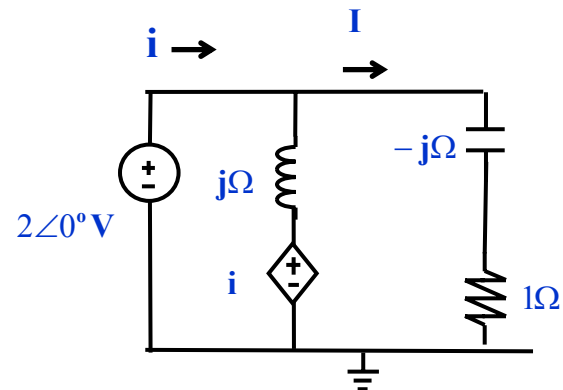
- (b) If  $X = 0 \Omega$

$$\therefore I = \frac{2\text{V}}{1\Omega - j\Omega} \quad (6)$$




(c)  $\therefore Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{v}{I} = \frac{2\angle 0^\circ}{2\angle 0^\circ / 1-j} = 1\Omega - j\Omega$

Thevenin equivalent at terminals ab

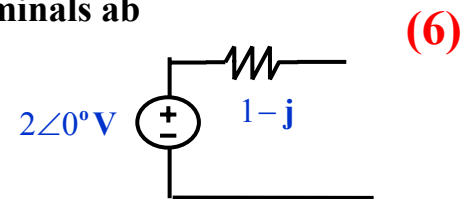

(d) If  $I = 2\angle 0^\circ \text{ A} = \frac{2\angle 0^\circ \text{ V}}{1\Omega}$

$\therefore X = j\Omega$  (6)

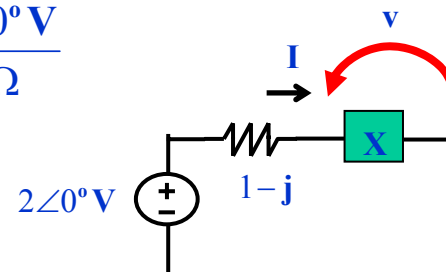



(9)


9

(a)

Draw the circuit model for a **conductance amplifier**.  
What are the ideal value of the output and input resistance?

(9)


(a)

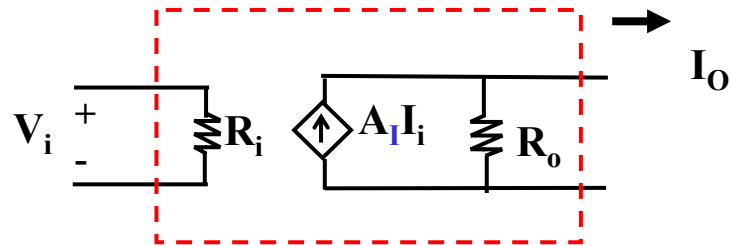

ideal V to I amplifier,  $R_i = \infty$  .  $R_o = \infty$  (9)

9 Find the elements A and B. Given that one element is  $1\text{k}\Omega$ . (18)

(b)

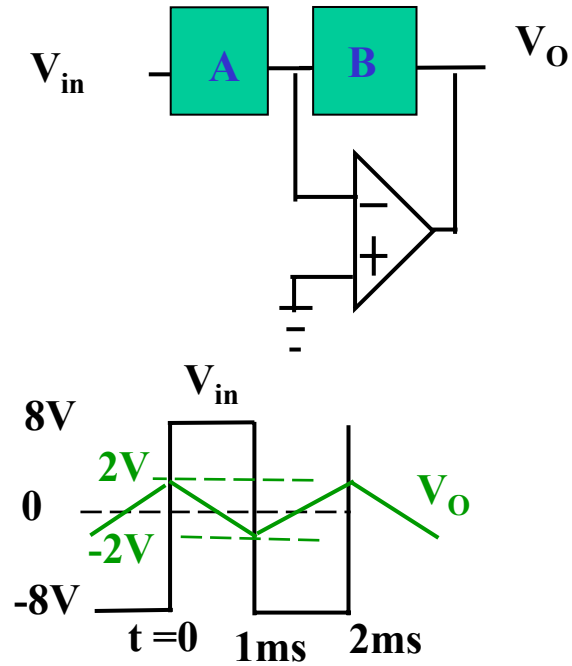

Circuit is an integrator

$$\therefore \frac{V_{in} - 0}{R} = -C \frac{dV_o}{dt}$$

$$\therefore \frac{dV_o}{dt} = -\frac{V_{in}}{RC} \quad (8)$$


$$\therefore \frac{2\text{V} - (-2\text{V})}{1\text{ms}} = -\frac{8\text{V}}{RC}$$

$$\therefore RC = 2\text{ms} \quad (8)$$

$$\therefore A = R = 1\text{k}\Omega$$

$$\therefore B = C = 2\mu\text{F} \quad (2)$$

10

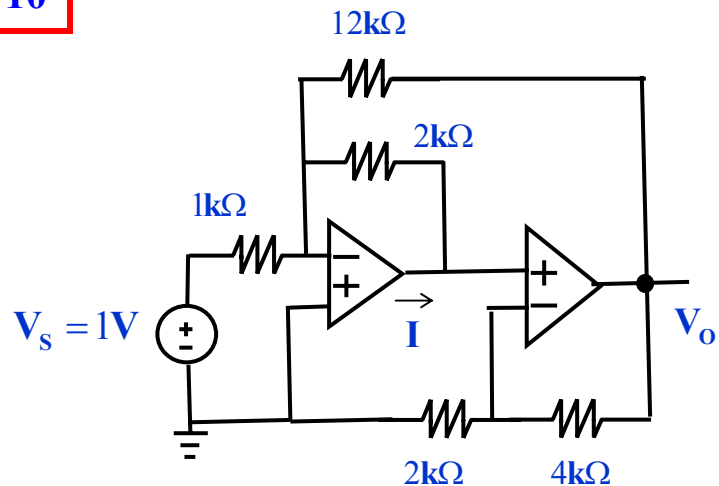

In the amplifier,  
find  $V_o$  and  $I$ . Assume the op amps are ideal. (21)

$$\therefore \frac{V_s - 0}{1\text{k}\Omega} = \frac{0 - V_o}{12\text{k}\Omega} + \frac{0 - V}{2\text{k}\Omega}$$

$$\therefore V = V_o * \frac{2\text{k}\Omega}{4\text{k}\Omega + 2\text{k}\Omega} = \frac{V_o}{3} \quad (8)$$

$$\therefore 12V_s = -V_o - 6V = -3V_o$$

$$\therefore \frac{V_o}{V_s} = -4$$

(21)

$$\therefore V_o = -4V \quad (5)$$

$$\therefore I = -\frac{2}{3}\text{mA} \quad (8)$$

