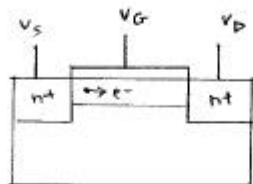


10. (a) What do the letters NMOSFET stand for? Sketch the cross section of an enhancement NMOSFET, describe the movement of electrons, the threshold voltage, and explain very briefly the operation of the NMOSFET. (12)

N-channel Metal Oxide Semiconductor
Field Effect Transistor



$$V_g > V_T$$

channel forms (e^- attracted)


I flow

I control by V_g

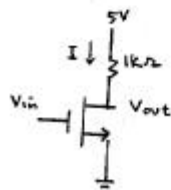(b) In the NMOSFET circuit, $V_T = 1V$, $K = 1mA/V^2$. Find the current I and the voltage V_{out} when (i) $V_{in} = 0.5V$, (ii) $V_{in} = 2V$, and (iii) $V_{in} = 4V$. Show the reasons for your methods. Estimate also the value of r_{on} at $V_{GS} = 3.5V$.

Given that $I_{DS} = 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}]$ at Triode region,

$I_{DS} = K(V_{GS} - V_T)^2$ at saturation region, and $\frac{1}{r_{on}} = \frac{\partial I_{DS}}{\partial V_{DS}}$ at $V_{DS} = 0$. (34)



(i) $V_{in} = 0.5V$

$$V_{GS} < V_T$$

$$\therefore I = 0$$

$$V_{out} = 5V$$

$$\begin{aligned} \therefore I &= K(V_{GS} - V_T)^2 \\ &= 1m(2 - 1)^2 \\ &= 1mA \end{aligned}$$

$$\therefore V_{out} = 5 - I(1K) = 4V$$

$$\begin{aligned} V_{DS} &> V_{GS} - V_T & \therefore \text{saturation} \\ 4 &> 2 - 1 & \text{confirmed} \end{aligned}$$

(iii) $V_{in} = 4V$ assume triode

$$\therefore I = 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}] = \frac{5 - V_{DS}}{1K}$$

$$\therefore 2(1m)[(4 - 1)V_D - \frac{V_D^2}{2}] = \frac{5 - V_D}{1K}$$

$$\therefore 2(3V_D - \frac{V_D^2}{2}) = 5 - V_D$$

$$\therefore V_D^2 - 7V_D + 5 = 0$$

$$V_D = \frac{7 \pm \sqrt{7^2 - 4(5)}}{2}$$


$$V_D = \frac{7 \pm 5.38}{2} = 6.19 \text{ or } 0.81V$$

$$\therefore V_{out} = 0.81V$$

$$\begin{aligned} V_{DS} &< V_{GS} - V_T & \therefore \text{triode} \\ 0.81 &< 4 - 1 & \text{confirmed} \end{aligned}$$

$$\begin{aligned} r_{on} &= \frac{\partial V_{DS}}{\partial I_{DS}} = \frac{1}{2K(V_{GS} - V_T)} \\ &= \frac{1}{2(1m)(3.5 - 1)} \\ &= 200\Omega \end{aligned}$$

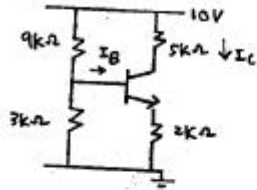11. (a) Explain briefly why the circuit can have stable I_C .
 (b) In the BJT circuit, find I_B .
 (c) Find the operating mode of BJT and show your reasons.
 For the BJT, given $V_{BE} = 0.7V$ and $\beta = 100$. (29)




$$(a) I_C \uparrow \quad V_E \uparrow \quad V_{BE} \downarrow$$

$$I_B \downarrow \quad I_C \downarrow$$

$$(b) V_B = 10 \frac{3k}{9k+3k} = 2.5V$$
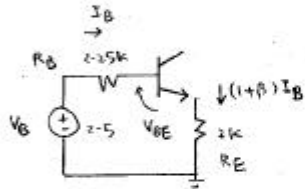
$$R_B = 3k \parallel 9k = \frac{27}{12} k = 2.25 k\Omega$$



$$I_B = \frac{V_B - V_{BE}}{R_B + (1+\beta)R_E}$$

$$= \frac{2.5 - 0.7}{2.25k + (1+100)2k}$$

$$= \frac{1.8}{204.25k} = 8.8 \mu A$$

$$(c) \text{ If active, } I_C = \beta I_B$$

$$= 100 (8.8 \mu A) = 0.88 mA$$

$$i. I_C 5k + I_E 2k$$



$$= 6.2V < 10V$$

\therefore BJT active

12. The BJT in the circuit has the output characteristic curves as shown.

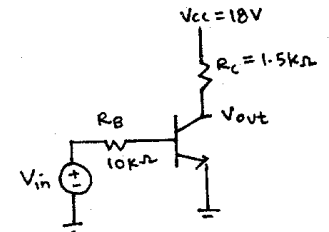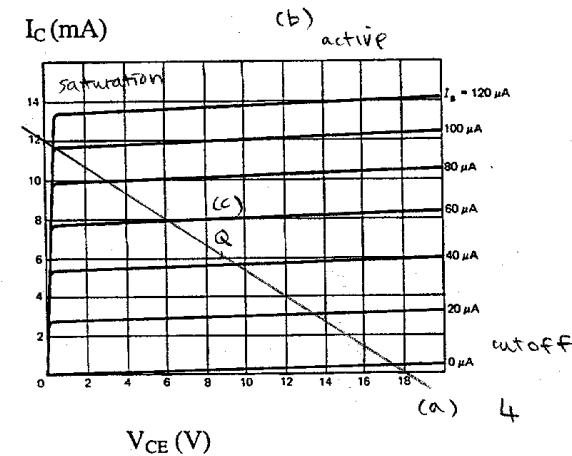- (a) Sketch the load line $V_{CC} = I_C R_C + V_{CE}$. (b) Show roughly on the output curves the three operating regions of the BJT. (c) Locate the Q-point on the loadline if $V_{in} = 1.15V$. (d) Estimate β and α for the BJT. (e) Sketch the AC equivalent circuit and find the voltage gain $A_V (= \Delta V_{out} / \Delta V_{in})$ of the circuit.

Given that for the BJT, $V_{BE} = 0.7V$, $r_{\pi} = 1 k\Omega$, $r_o = \infty$. (30)



$$(c) V_{in} = 1.15V$$

$$I_B = \frac{1.15 - 0.7}{10k} = 45 \mu A$$

$$(d) \beta \sim \frac{I_C}{I_B} \sim \frac{14mA}{120\mu A} \sim 120 \quad 3$$

$$\alpha = \frac{\beta}{1+\beta} \sim \frac{120}{121} \quad 3$$