

1. In the following circuit,  $V_1(t) = 4 \cos(1000t) \text{ V}$ .



(a) If element A =  $1 \text{ mH}$ , element B =  $0.5 \text{ mF}$ ,  $R = 2 \Omega$ ,

show that  $V(t) = 4\sqrt{5} \cos(1000t - 26.6^\circ) \text{ V}$ .

(b) Does  $V(t)$  lead  $V_1(t)$ ?

(c) If  $R = 2 \Omega$ ,  $V(t) = 1 \cos(1000t) \text{ V}$ , suggest the elements and values of A and B.

(29 marks)

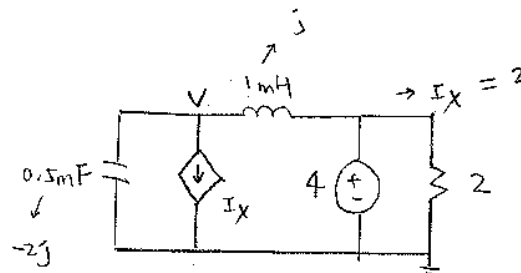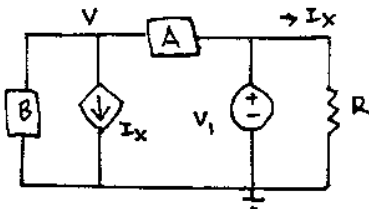

(a)

$$j\omega L = j(1k)(1m) = j$$

$$\frac{1}{j\omega C} = \frac{1}{j(1k)(0.5m)} = -2j$$

$$4 \cos 1kt \rightarrow 4 \angle 0 \rightarrow 4 \text{ V}$$

$$I_X = 2 \angle 0 = 2 \text{ A}$$

Using KCL =

(node V)

$$\frac{4 - V}{j} = I_X + \frac{V}{-2j}$$

$$\therefore 8 - 2V = 2(2j) - V$$

$$V = 8 - 4j = 4(2 - j)$$


$$= 4\sqrt{5} \angle -26.6^\circ$$

$$\therefore V(t) = 4\sqrt{5} \cos(1000t - 26.6^\circ) \text{ V}$$

(b)

$V(t)$  lags  $V_1(t)$

(c)

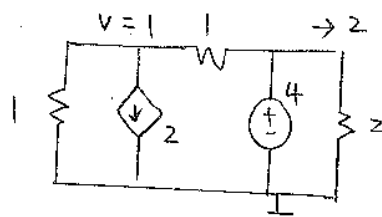


$$\therefore A = 1 \Omega$$

$$B = 1 \Omega$$

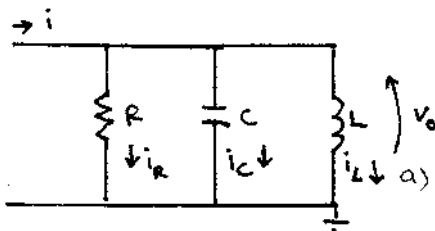2. In the following parallel LCR circuit,  $i(t) = \sqrt{2} \cos \omega t$  mA,  $L = 50$  mH,  $C = 10$   $\mu$ F,  $R = 10$  k $\Omega$ .

- Find the resonant frequency in rad/s.
- Find the Q factor.
- Show that the bandwidth is  $\frac{10}{2\pi}$  Hz.
- Find the upper and lower cut-off frequencies.
- Find the maximum  $V_o(t)$ .
- Sketch  $V_o$  (in Vrms) versus  $\omega$ . Label clearly all intercepts
- Find the maximum  $i_c$  (in mA rms).
- Explain briefly two advantages if  $R$  is changed to 20k $\Omega$ .



(33 marks)

$$a) \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{50 \text{ m} \cdot 10 \mu}} = 1414 \text{ rad/s} \quad 4$$


$$b) \quad Q = \frac{R}{\omega_0 L} = \frac{10 \text{ k}}{1414 (50 \text{ m})} = 141.4 \quad 4$$

$$c) \quad BW = \frac{\omega_0}{Q} = \frac{1414}{141.4} = 10 = \frac{10}{2\pi} \text{ Hz} \quad 3$$

$$d) \quad \omega_2 = \omega_0 + \frac{BW}{2} = 1414 + 5 \text{ rad/s} \quad 4$$

$$\omega_1 = \omega_0 - \frac{BW}{2} = 1414 - 5 \text{ rad/s}$$
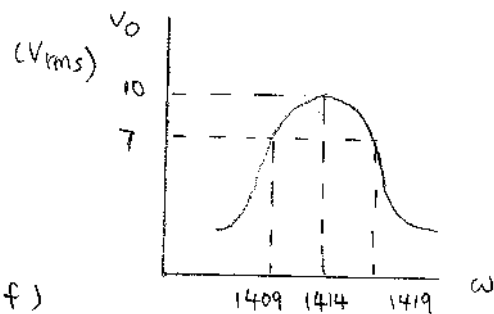
$$e) \quad \max V_o(t) = iR = 10\sqrt{2} \cos 1414 t \text{ V} \quad 5$$



$$g) \quad \max i_c = Q i = 141.4 \text{ mA rms} \quad 4$$

f)

5

$$h) \quad R = 20 \text{ k}$$

Q increases

BW decreases


4

3. (a) Load A is connected in parallel to a  $200 \angle 0^\circ$  Vrms 50Hz power supply. If load A is a  $10 \Omega$  resistor in parallel with a  $31.8$  mH inductor, find the apparent power  $S$ , reactive power  $Q$ , average power  $P$  and power factor  $PF$  of load A.

(b) A load B of  $2\text{kW}$  and  $PF = 1$  is connected in parallel with load A, find the total  $Q$  of the combined load.

(c) A load C is now connected in parallel to the combined load in (b) to make the total power factor  $= 1$ , show that load C is a  $0.318$  mF capacitor. Find also the apparent power and current (in Arms) supplied by the power supply.


(35 marks)

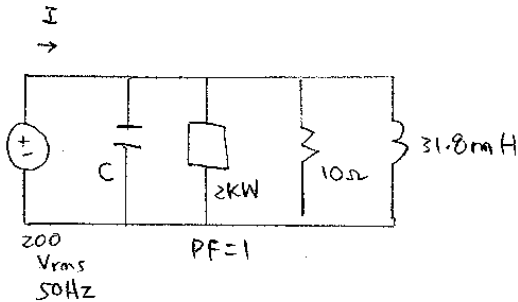

(a)

$$P = \frac{V^2}{R} = \frac{200^2}{10} = 4\text{kW} \quad 4$$
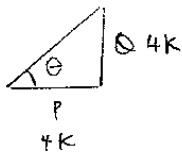
$$Q = \frac{V^2}{\omega L} = \frac{200^2}{2\pi 50 (31.8\text{m})} = 4\text{kVAR} \quad 4$$



$$S = \sqrt{P^2 + Q^2} = 4\sqrt{2} \text{ kVA} \quad 4$$

$$PF = \cos \theta = \cos 45^\circ = 0.707 \quad 4$$

lagging

(b) total  $Q = 4\text{kVAR} \quad 4$

(c)  $Q = \frac{V^2}{\frac{1}{\omega C}} = V^2 \omega C$

$$\therefore C = \frac{Q}{V^2 \omega} = \frac{4\text{k}}{200^2 2\pi 50} = 0.318 \text{ mF} \quad 6$$

$$S = 2\text{k} + 4\text{k} = 6\text{kVA} \quad 5$$

$$I = \frac{S}{V} = \frac{6\text{k}}{200} = 30 \text{ A}_{\text{rms}} \quad 4$$

(4) In the following circuit,  $R_1 = R_2 = R$ .

(a) Find the complex transfer function  $G (= V_o/V_i)$  as a function of  $j\omega$ ,  $C$  and  $R$ .


(b) Find the pole and zero of  $G$ .

(c) If  $C = 2\text{mF}$  and  $R = 1\text{k}\Omega$ , find the cut-off frequency.

(d) Sketch the magnitude of  $G$  versus angular frequency  $\omega$ . Label clearly the intercepts.

(e) Find the magnitude of  $G$  in dB at the half-power frequency.

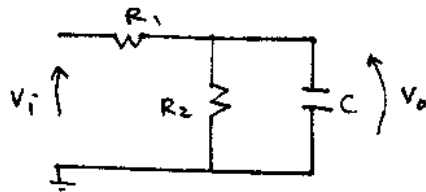(f) What is the type and order of the filter?



(31 marks)

$$R \parallel C = \frac{R \left( \frac{1}{j\omega C} \right)}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega CR}$$

$$\begin{aligned} \text{a) } \therefore G = \frac{V_o}{V_i} &= \frac{\frac{R}{1 + j\omega CR}}{R + \frac{R}{1 + j\omega CR}} = \frac{1}{1 + 1 + j\omega CR} \\ &= \frac{1}{2 + j\omega CR} \end{aligned}$$

8

b) No Zero

$$\begin{aligned} \text{pole : } 2 + j\omega CR &= 0 \\ j\omega &= \frac{-2}{CR} \end{aligned}$$


5

$$\text{c) cut off : } 2 + j\omega CR = 2 + 2j$$

$$\omega CR = 2$$

5
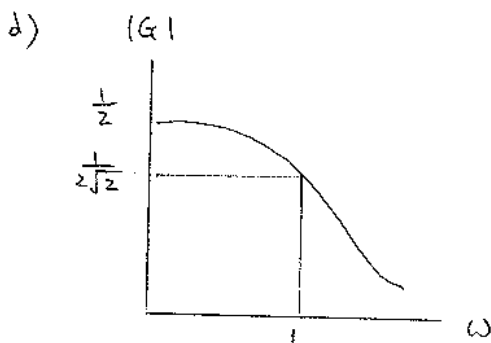
$$\therefore \omega_{co} = \frac{2}{CR} = \frac{2}{2\text{m} \cdot 1\text{k}} = 1 \text{ rad/s}$$



$$|G| = \frac{1}{\sqrt{4 + (\omega CR)^2}}$$

5

$$\text{e) } 20 \log \frac{1}{2\sqrt{2}} = -9 \text{ dB}$$


4

f) 1st order low pass filter


4

5. (a) In the following circuit, assume op amp is ideal. (i) Show that  $i = -0.5\text{mA}$  if  $V_i = 4\text{V}$ . (ii) Find  $i$  if  $V_i = -8\text{V}$ .

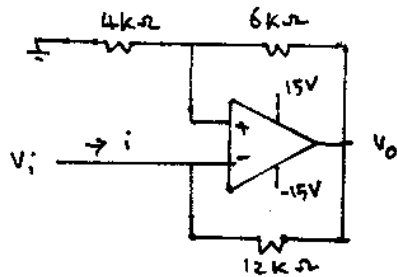(b) A voltage amplifier (with input resistance  $R_{in}$ , voltage gain  $A$  and output resistance  $R_{out}$ ) is connected between a source (with voltage  $V_s$  and source resistance  $R_s$ ) and a load ( $R_L$ ). Sketch the circuit model of the whole circuit and explain briefly why an ideal voltage amplifier should have infinite input resistance and zero output resistance.



(24 marks)

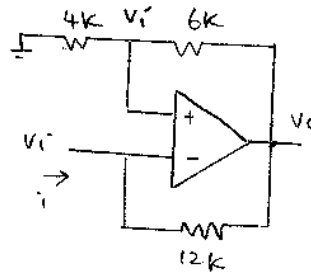

(a)

$$V_o = V_i + \frac{V_i}{4k} 6k$$

$$= 4 + 6 = 10\text{V}$$

$$\therefore i = \frac{V_i - V_o}{12k} = \frac{4 - 10}{12k} = -0.5\text{mA}$$

9


$$V_o = V_i + \frac{V_i}{4k} 6k$$

$$= -8 - 12 = -20\text{V} \quad \text{op amp saturates!}$$

$$\therefore V_o = -15\text{V}$$

$$\therefore i = \frac{V_i - V_o}{12k} = \frac{-8 + 15}{12k} = \frac{7}{12}\text{mA}$$

6

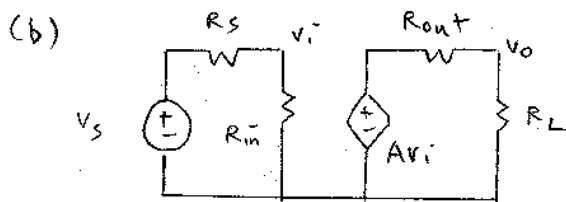

$$R_{in} \rightarrow \infty \quad v_i \rightarrow V_s$$

$$R_{out} \rightarrow 0 \quad v_o \rightarrow Av_i \rightarrow AV_s$$

9