

1

(a)

(a) Explain very briefly why current in an inductor and voltage in a capacitor is continuous with time. (7)

1

Energy must be continuous with time.

Hence E_C and E_L must be continuous with time
(unchanged after switching)

$$\begin{array}{cc} \begin{array}{c} + \\ V_C \\ - \end{array} \begin{array}{c} \downarrow i_C \\ \text{---} \\ \uparrow \end{array} & E_C = \frac{CV_C(t)^2}{2} \\ \begin{array}{c} i_L \\ \downarrow \end{array} \begin{array}{c} + \\ \text{---} \\ - \end{array} & E_L = \frac{Li_L(t)^2}{2} \end{array} \quad (7)$$

Hence V_C and i_L must be continuous with time.

2

Another short proof

$$i_C = C \frac{dV_C(t)}{dt} \quad V_L = L \frac{di_L(t)}{dt}$$




If dt is 0, infinite i_C or V_L is required, which is not possible. Hence dV_C/dt and di_L/dt must be finite, or V_C and i_L must be continuous with time.

1

The switch has been closed for a long time. At $t = 0$ second, the switch is opened. (i) If $X = 1\text{mH}$, find $i(0)$, $i(\infty)$, time constant $\tau (= L/R)$, $i(t)$ and $v(t)$ for $t \geq 0$. Given that $i(t) = i(\infty) + [i(0) - i(\infty)] \exp(-t/\tau)$. Given that $v(t) = v(\infty) + [v(0) - v(\infty)] \exp(-t/\tau)$. (17)

(b)

(i)

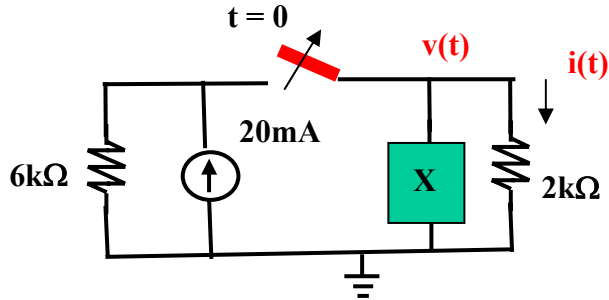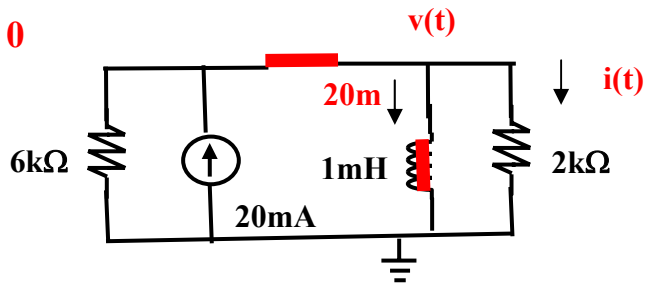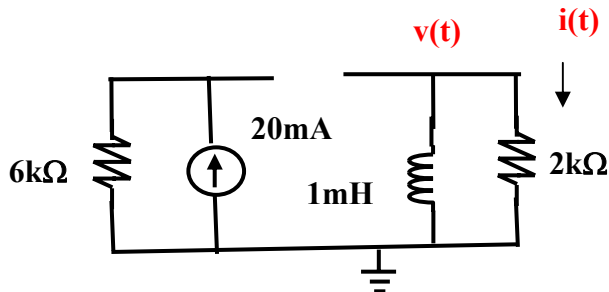 $t < 0$  $t \geq 0$ 

$$\therefore i(0) = -20 \text{ mA} \quad (4)$$

$$i(\infty) = 0 \text{ mA} \quad (3)$$

$$\tau = \frac{L}{R} = \frac{1\text{mH}}{2\text{k}\Omega} = 0.5 \mu\text{s} \quad (3)$$


$$\begin{aligned} \therefore i(t) &= i(\infty) + [i(0) - i(\infty)] * e^{-\frac{t}{\tau}} \\ &= 0 \text{ mA} + [-20 \text{ mA} - 0] * e^{-t/0.5 \mu\text{s}} \\ &= -20 \text{ mA} e^{-t/0.5 \mu\text{s}} \end{aligned} \quad (3)$$

$$v(t) = i(t) * 2\text{k}\Omega = -40 \text{ V} e^{-t/0.5 \mu\text{s}} \quad (4)$$

1

(ii) If $X = 1\text{mF}$, find $v(0)$, $i(0)$ for $t \geq 0$. Given that $i(t) = i(\infty) + [i(0) - i(\infty)] \exp(-t/\tau)$. (7)


(ii)

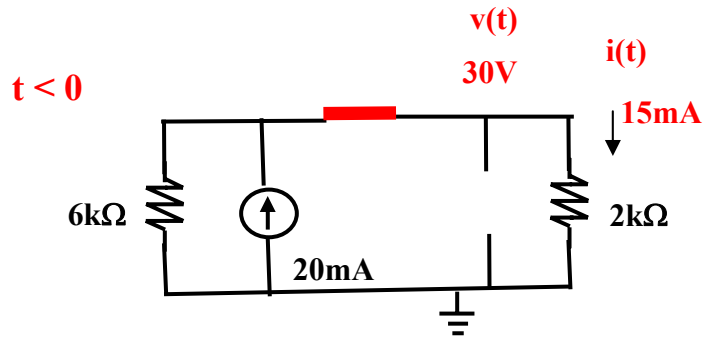

$$\therefore v(0) = 30\text{ V} \quad (4)$$

$$i(0) = 15\text{ mA} \quad (3)$$

$t \geq 0$

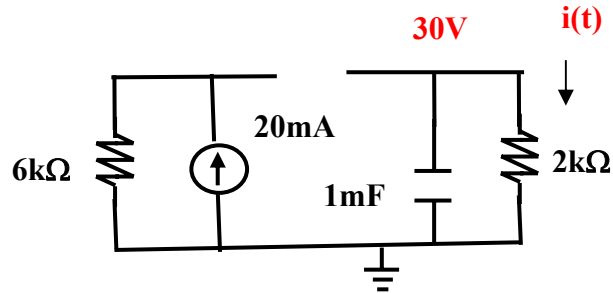


2

(24)

(a) If $i(t) = 10 \sin(100t + 30^\circ) \text{ A}$, $Z = 2\Omega$, find $v(t)$.

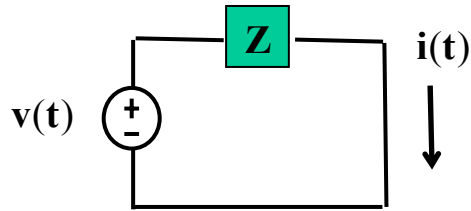(b) If $v(t) = 8 \sin(2kt + 30^\circ) \text{ V}$, $Z = 2\text{mH}$, find Z in Ω and find $i(t)$.



(a) $v(t) = 20 \sin(100t + 30^\circ) \text{ V}$ (3)

(b) $Z = j\omega L = j(2\text{krad/s})2\text{mH} = 4j\Omega$ (2)

$$\begin{aligned} i(t) &= \frac{8\text{V}}{4\Omega} \sin(2kt + 30^\circ - 90^\circ) \text{ A} \\ &= 2\text{A} \sin(2kt - 60^\circ) \end{aligned} \quad (6)$$

- (c) If $i(t) = 5\cos(1kt + 30^\circ)\text{A}$, $v(t) = 20\cos(1kt - 30^\circ)\text{V}$, and Z is R in series with X . Find Z in Ω . Find also the element and value of X . Does $i(t)$ lag $v(t)$?

$$\begin{aligned}\therefore Z &= \frac{V}{I} = \frac{20\angle -30^\circ\text{V}}{5\angle 30^\circ\text{A}} = 4\angle -60^\circ\Omega \\ &= 4\cos(-60^\circ) + 4j\sin(-60^\circ) \\ &= 2\Omega - j3.464\Omega \\ &= R - jX\end{aligned}\tag{7}$$


$$\therefore X = \frac{1}{\omega C} \Rightarrow C = \frac{1}{X\omega} = \frac{1}{3.464 * 1k} \cong 0.289\text{mF}\tag{4}$$

$$i(t) \text{ leads } v(t)\tag{2}$$

3

(a) If $V(t) = 200 \cos(200\pi t + 30^\circ) \text{ V}$, find $I(t)$.

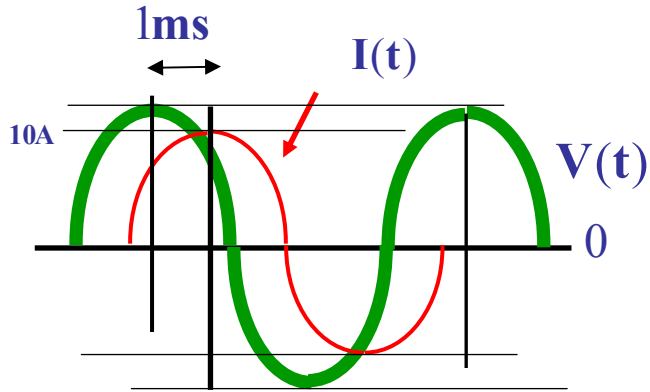
(a) Draw also the phasor diagram of $V(t)$ and $I(t)$. (17)



$$\therefore T = \frac{2\pi}{\omega} = \frac{2\pi}{200\pi} = 10\text{ms} \quad (4)$$

$$\theta = \frac{t}{T} * 360^\circ = \frac{1\text{ms}}{10\text{ms}} * 360^\circ = 36^\circ \quad (4)$$

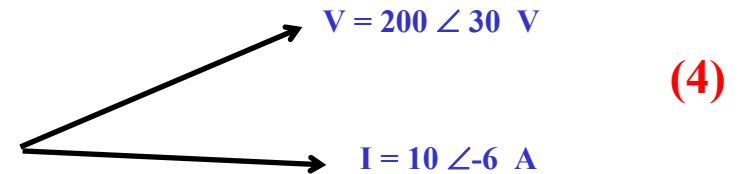
$$\begin{aligned} \therefore I(t) &= 10\text{A} \cos(\omega t + \theta) \\ &= 10\text{A} \cos(200\pi t + 30^\circ - 36^\circ) \\ &= 10\text{A} \cos(200\pi t - 6^\circ) \end{aligned} \quad (5)$$



3

(b)


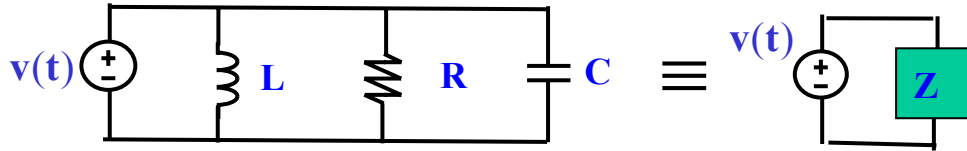
(b) If $v(t) = V_m \cos \omega t$, express the impedance Z in terms of R , L , C and ω . (6)



$$Z = \frac{1}{Y} = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}} \quad (6)$$

4

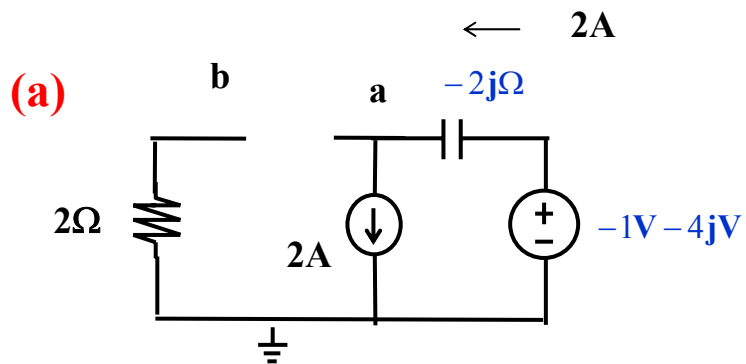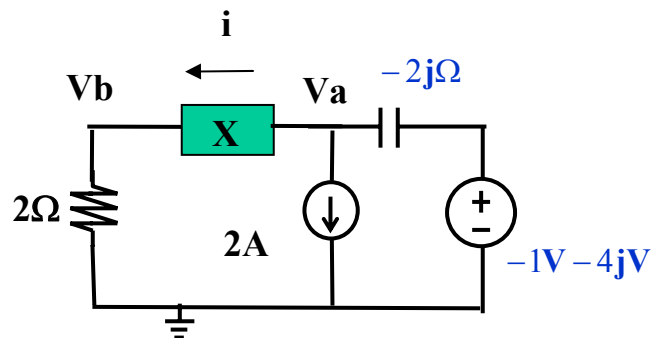- (a) If $X = \infty\Omega$, find $V_a - V_b$.
 (b) If $X = 0\Omega$, find i .
 (c) Find the Thevenin impedance and hence the Thevenin equivalent at terminals ab. (21)




$$V_{oc} = V_{ab} = (-1 - 4j) - (2A * -2j\Omega)$$

$$= -1 - 4j + 4j = -1V$$

(6)

(21)

(b)

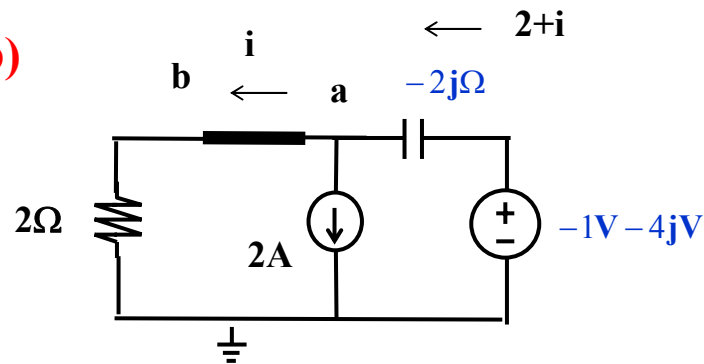


$$-1V - 4jV - (2 + i) * (-2j\Omega) - i * 2\Omega = 0$$

$$-1 - 4j + 4j + 2ij - 2i = 0$$


$$i = \frac{1}{2(j-1)} A \quad (8)$$

(c)

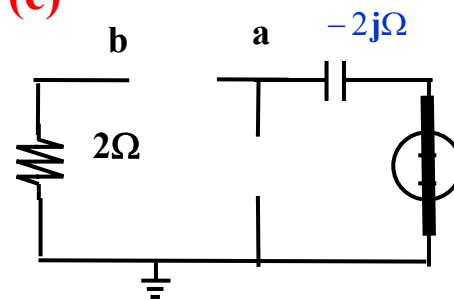

$$Z_{th} = 2\Omega - 2j\Omega \quad \text{or}$$
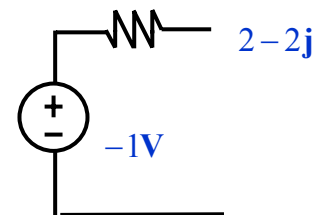
$$Z_{th} = \frac{V_{ab}}{i} = 2 - 2j \quad (4)$$




(3)

(15)

5

If a load D is connected in parallel to load B to make the total power factor = 0.9 lagging, find the element and value of load D. (15)

(a)

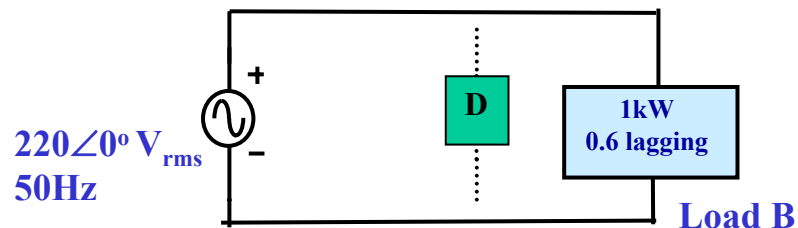

$\therefore Q_C$ required

$$= 1\text{kW} \tan(\cos^{-1} 0.6) - 1\text{kW} \tan(\cos^{-1} 0.9)$$


$$\cong 849\text{VAR}(\text{C})$$

(9)

Add load D to make PF = 0.9 lagging (capacitance C)

$$\therefore C = \frac{|Q_C|}{V^2 \omega} \cong \frac{849\text{VAR}(\text{C})}{(220^2) 2\pi 50} \cong 55.84\mu\text{F} \quad (6)$$

Power triangle

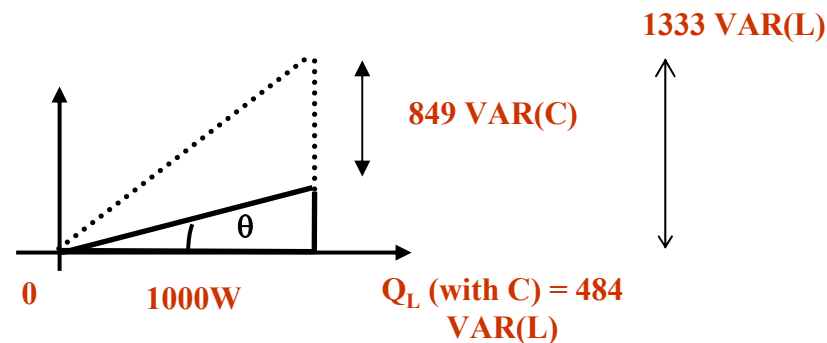


(13)

5

For load A, the apparent power S is 2200VA, and the reactive power Q is $2200 * \frac{\sqrt{3}}{2} \text{VAR(L)}$

(b)

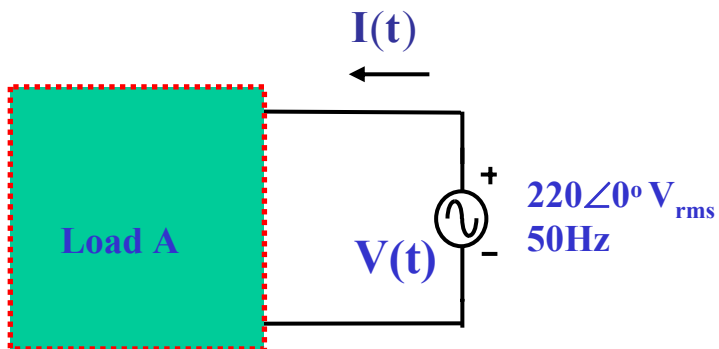Find the average power P , power factor PF of load A, and $I(t)$. (13)




$$\sin \theta = \frac{Q}{S} = \frac{2200\sqrt{3}/2}{2200} = \frac{\sqrt{3}}{2}$$

$$\therefore \text{PF} = \cos \theta = \cos(\sin^{-1} \frac{\sqrt{3}}{2})$$

$$= \cos 60^\circ = 0.5 \text{lagging} \quad (9)$$
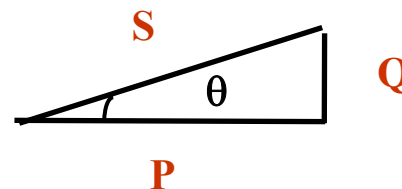
$$P = S \cos \theta = 2200\text{VA} * \cos(60^\circ) = 1100\text{W} \quad (4)$$




(21)

6

(a) Will electricity fee be reduced if the power factor is improved to 1? Why? (21)

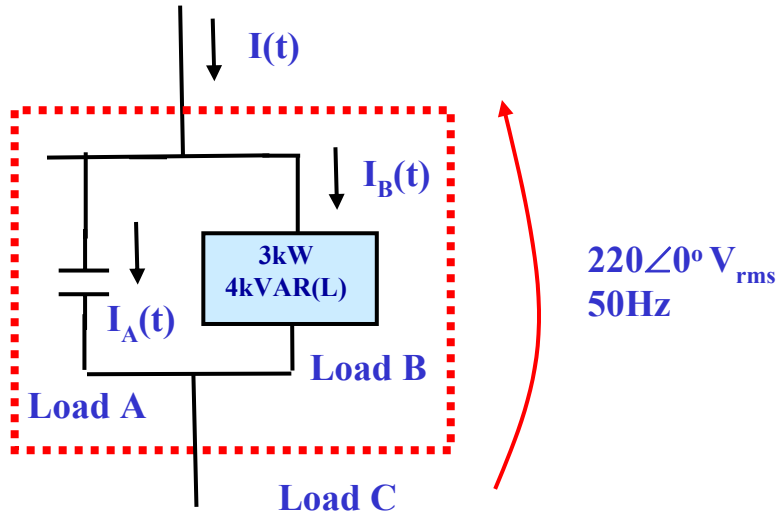(b) The power factor of Load C is 1, find I in Arms . If load B is R in series with X. Find R in Ω .



(a) Electric fees is related to P only
 P is unchanged hence fees will not be reduced (5)

(b)

$$I = \frac{P}{V} = \frac{3\text{kW}}{220\text{V}_{\text{rms}}} \cong 13.64\text{A}_{\text{rms}} \quad (6)$$
$$I_B = \frac{S}{V} = \frac{\sqrt{3\text{k}^2 + 4\text{k}^2}}{V} = \frac{5\text{kVA}}{220\text{V}_{\text{rms}}} \cong 22.73\text{A}_{\text{rms}} \quad (6)$$

$$R = \frac{P}{I_B^2} \cong \frac{3\text{kW}}{(22.73\text{A}_{\text{rms}})^2} \cong 5.8\Omega \quad (4)$$


7

(a) If $V_a = 1V$, find V_b , V_c and I_a .

(b) If $V_a = 10V$, find V_c .

Given $X = 8k\Omega$, $R_1 = 1k\Omega$, $R = 2k\Omega$.

Assume the op amps are ideal. (23)

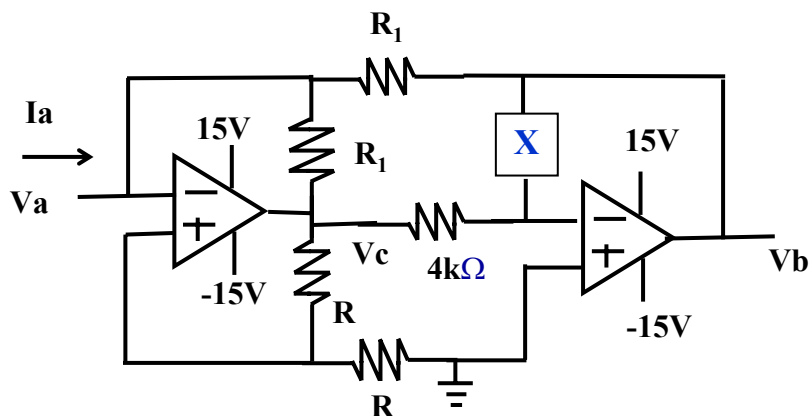

(a)

$$V_c = 2V_a = 2V \quad (5)$$

$$\therefore V_b = -\frac{X}{4k} V_c = -\frac{8k}{4k} V_c$$

$$= -2V_c = -4V_a = -4V \quad (6)$$

$$\therefore I_a = \frac{V_a - V_b}{R_1} + \frac{V_a - V_c}{R_1}$$


$$= \frac{1}{R_1} [5V_a - V_a]$$

$$= \frac{4V_a}{R_1} = \frac{4V}{1k} = 4mA \quad (7)$$

(b)



If V_a is changed to 10V,
 $V_c = 15V$ (op amp saturated)

(5)

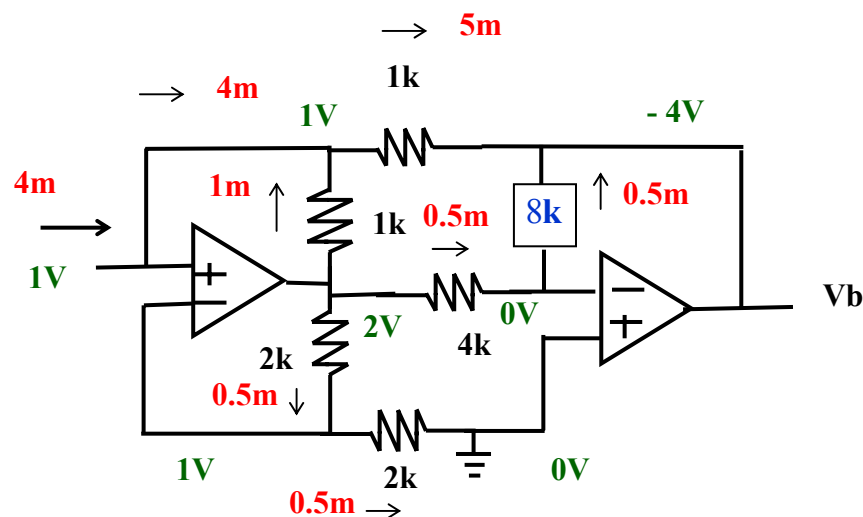

8

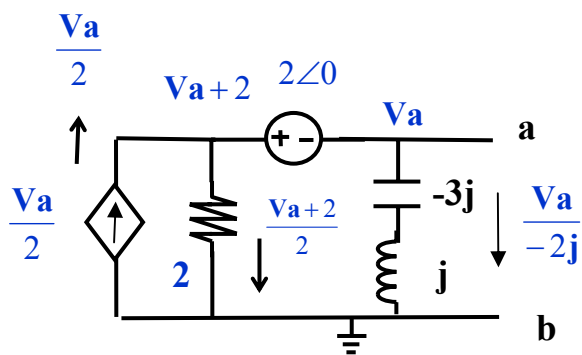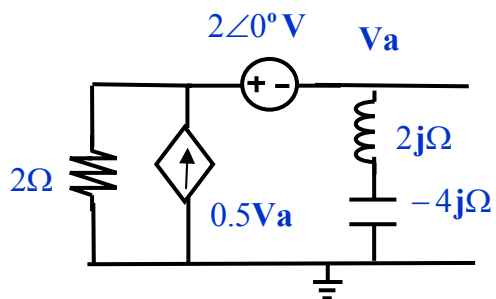
Find V_a . The voltage dependent current source is in ampere and equal to $0.5V_a$. (14)



$$\frac{V_a}{2\Omega} = \frac{V_a + 2V}{2\Omega} + \frac{V_a}{-2j\Omega} \quad (8)$$

$$0 = 1 - \frac{V_a}{2j\Omega}$$

$$\therefore V_a = 2jV \quad (6)$$

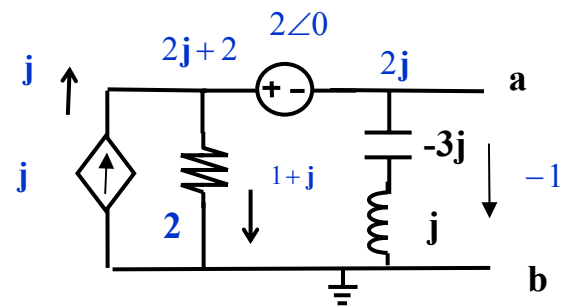


9

A parallel LCR radio tuner circuit is used to receive HK Radio Station 5 as shown in the resonance curve .

- (a) Show that the quality factor (QF) is 50 .
 (b) If $L = 1\mu\text{H}$, find C and R .
 (c) If at resonance, $i = 1\angle 0^\circ \text{ mArms}$, find $V_o(t)$ at resonance .
 (d) Suggest a method to improve the bandwidth to 1 MHz .

Given that $QF = f_o/BW = R/X$. (25)

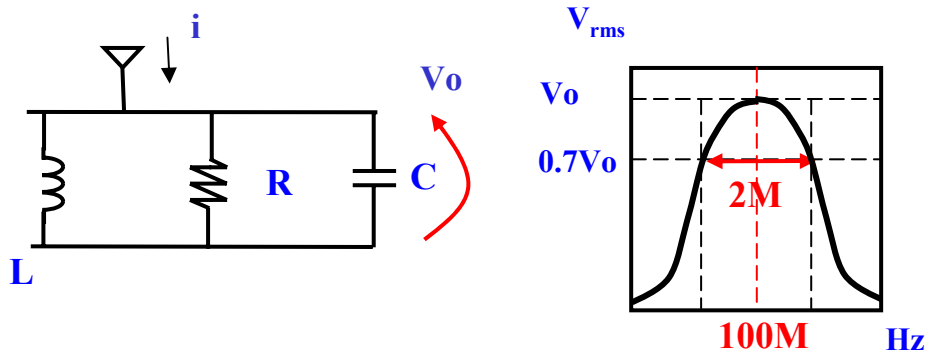

(a)

$$QF = \frac{f_o}{BW} = \frac{100\text{M}}{2\text{M}} = 50 \quad (3)$$

(b)

$$\omega_o = \frac{1}{\sqrt{LC}}$$

$$\therefore C = \frac{1}{\omega_o^2 L} = \frac{1}{(2\pi 100\text{MHz})^2 1\mu\text{H}} \cong 2.53 \times 10^{-12} \text{F} \quad (5)$$

$$\therefore QF = \frac{R}{\omega_o L}$$

$$\therefore R = \omega_o L * QF = 2\pi * 100\text{MHz} * 1\mu\text{H} * 50 \cong 31416\Omega \quad (5)$$

(c)

$$\therefore V_o(t) = i(t) * R \cong (1\text{mA}\sqrt{2} \cos 2\pi 100\text{Mt}) * 31416\Omega$$

$$\cong 31.4\sqrt{2}\text{V} \cos 2\pi 100\text{Mt} \quad (7)$$

(d)

Change R to 2R

(5)


10

The series LCR circuit is in resonance. R is 0.05Ω and

$$V_R(t) = 0.2\sqrt{2} \cos(500t) \text{ V}$$

Find Z, resonant frequency f_o in Hz, and $v(t)$. (13)

$$i(t) = I_m \cos(\omega t + \theta_i)$$

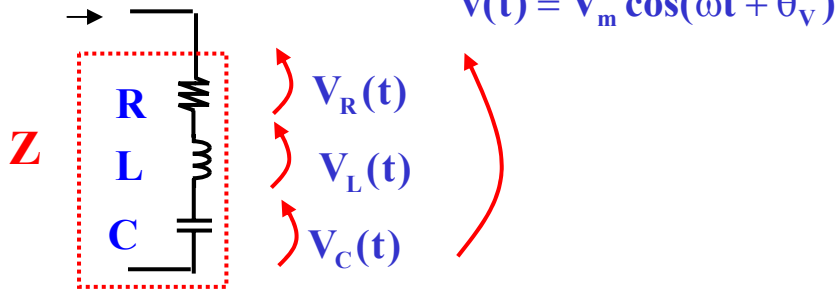


$$Z = R = 0.05\Omega \quad (4)$$

$$\therefore f_o = \frac{\omega_o}{2\pi} = \frac{500}{2\pi} \text{ Hz} \quad (4)$$

$$\therefore v(t) = 0.2\sqrt{2} \cos(500t) \text{ V} \quad (5)$$

8

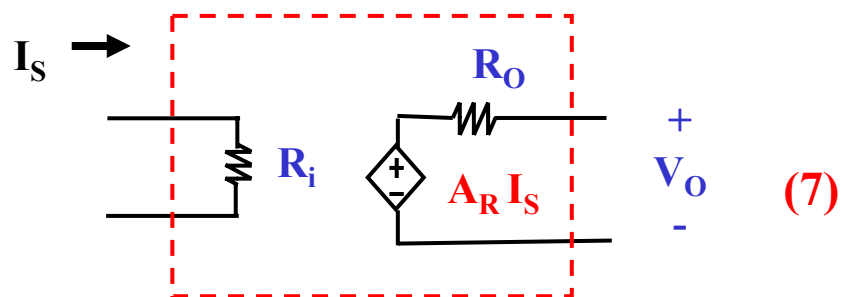(a)
Draw the circuit model for a current to voltage (resistance) amplifier. What is the ideal value of the input resistance. (8)



$$R_i = 0\Omega \quad (2)$$

(b)

Design the ideal op amp circuit below if $V_{out} = 11 V_{in}$. Use $1k - 10k\Omega$ resistors in your design. (8)



(a)

