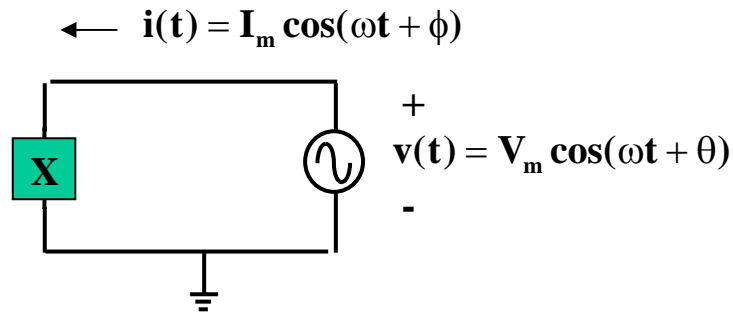


1

In the circuit, X is an unknown element. . (23)

(a) If  $V_m = 10\text{V}$ ,  $I_m = 5\text{A}$ ,  $\theta = \phi = 60^\circ$ , find  $X$  in  $\Omega$ , power factor of  $X$ , and power dissipated by  $X$ .

(b) If  $V_m = 8\text{V}$ ,  $I_m = 4\text{A}$ ,  $\theta = 0^\circ$ ,  $\phi = 90^\circ$ , find  $X$  in  $\Omega$ , and power stored by  $X$ .



$$(a) \quad X = R = \frac{V_m}{I_m} = \frac{10\text{V}}{5\text{A}} = 2\Omega$$

$$\text{PF} = 1$$

$$P_R = I^2 * R = \left(\frac{5\text{A}}{\sqrt{2}}\right)^2 * 2\Omega = 25\text{W}$$

$$(b) \quad X = C = -j2\Omega$$


$$Q_C = I^2 * \frac{1}{\omega C} = \left(\frac{4\text{A}}{\sqrt{2}}\right)^2 * 2\Omega = 16\text{VAR(C)}$$

2

The circuit is at steady state for  $t < 0$ . At  $t = 0$ , the switch is closed.

If  $X = 0.2\text{mF}$ , find  $V_o(0)$ ,  $V_o(\infty)$  and time constant  $\tau$  for  $t > 0$ . Find also  $I_o(t)$  when  $t = 0$  and  $10\tau$ .  
(21)

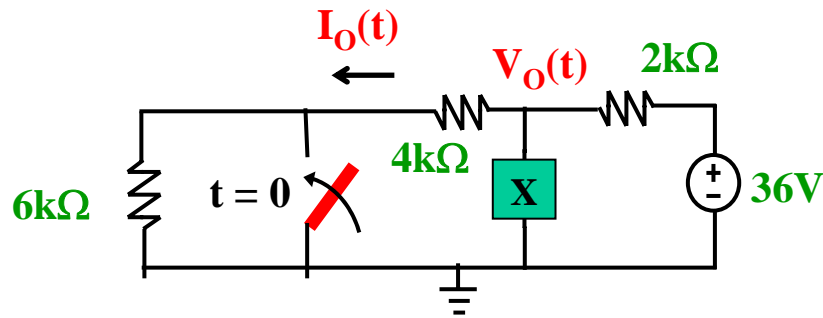Given that  $V_c(t) = V_c(\infty) + [V_c(0) - V_c(\infty)] * e^{-t/\tau}$  and  $\tau = CR$



(a)

$$\therefore V_o(0) = V_o(0^-) = 36\text{V} \left( \frac{10\text{k}\Omega}{12\text{k}\Omega} \right) = 30\text{V}$$


$$\therefore \tau = CR = 200\mu\text{F} * (2\text{k}\Omega // 4\text{k}\Omega) = 0.267\text{s}$$

$$\therefore V_o(\infty) = 36\text{V} * \frac{4\text{k}\Omega}{6\text{k}\Omega} = 24\text{V}$$

$$I_o(0) = \frac{30\text{V}}{4\text{k}\Omega} = 7.5\text{mA}$$

$$I_o(10\tau) \cong \frac{24\text{V}}{4\text{k}\Omega} = 6\text{mA}$$

3

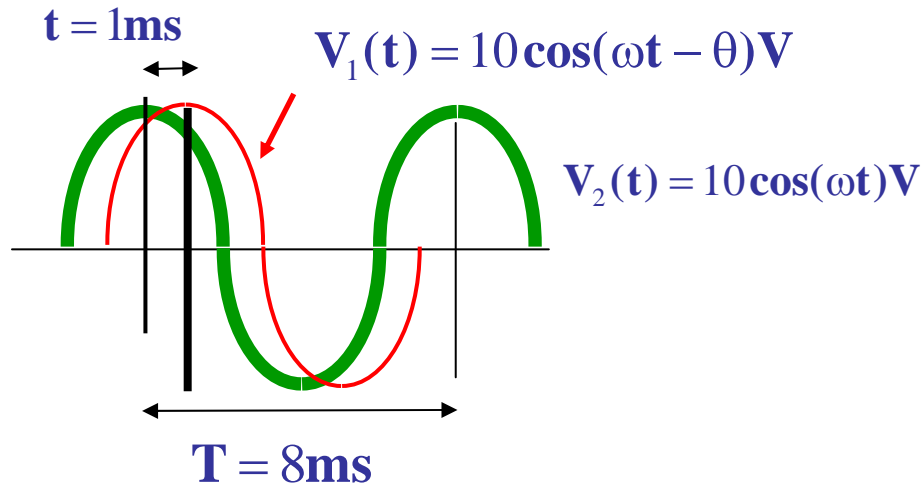Find  $\omega$ ,  $\theta$  and  $V_1(0)$ Does  $V_2(t)$  lag  $V_1(t)$ ?Given  $2\pi$  radian =  $360^\circ$ , period of  $V_2(t)$  is 8 ms, and difference between the peaks of  $V_1(t)$  and  $V_2(t)$  is 1 ms. (14)

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{8\text{ms}}$$

$$\theta = \frac{t}{T} * 360^\circ = \frac{1\text{ms}}{8\text{ms}} * 360^\circ = 45^\circ$$


$$\therefore V_1(t) = 10\cos\left(\frac{2\pi}{8\text{ms}}t - 45^\circ\right)V$$

$$\therefore V_1(0) = 10\cos(0 - 45^\circ)V = \frac{10}{\sqrt{2}}V$$

 **$V_2(t)$  leads  $V_1(t)$**


4

(a)

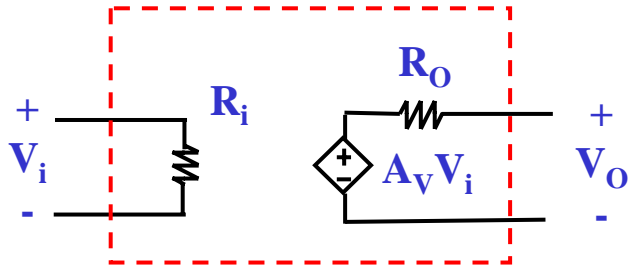

$$R_{in} = \infty, R_o = 0$$

(b)

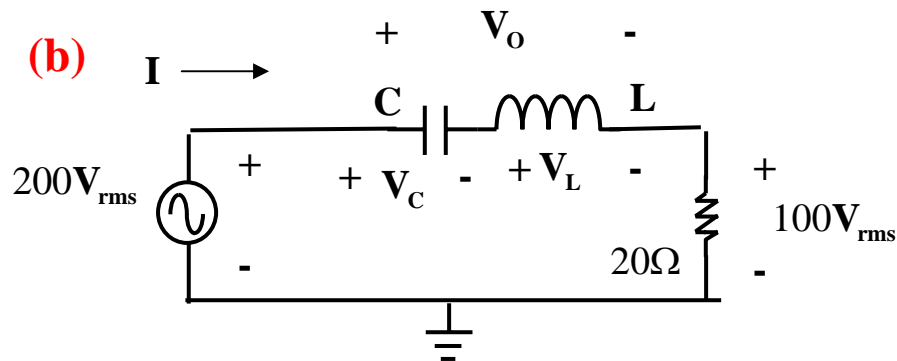

$$I = \frac{100V_{rms}}{20\Omega} = 5A_{rms}$$

$$\therefore V_o = \sqrt{200^2 - 100^2} \cong 173V_{rms}$$

(a) Draw the circuit model for a **voltage amplifier**.  
What are the ideal values of the input resistance and output resistance of the voltage amplifier?

(b) In the circuit, find  $I$  in Arms and find  $V_o$  in Vrms .  
(19)

**5**

A load consumes 6kW at power factor (PF) of 0.6 lagging from a  $200\angle 0^\circ$  Vrms 50 Hz line.

(a) Find the real power (dissipated power) P and apparent power (supply power) S of the load. Show that the reactive power (stored power) Q is 8kVAR. ,

(b) Show that the current I in the load is 50Arms.

Find also the current I in phasor form.

If the load is a resistance R in series with an inductance L, find L.

(c) An element X is connected in parallel to the load to improve the power factor to 1. Find the element and value of X.

(32)

**(a)**  $P = 6\text{kW}$

$$Q = P \tan \theta = 6\text{kW} \tan(\cos^{-1} 0.6) = 8\text{kVAR(L)}$$

$$\therefore S = \sqrt{P^2 + Q^2} = \sqrt{6\text{k}^2 + 8\text{k}^2} = 10\text{kVA}$$

**(b)**  $I = \frac{S}{V} = \frac{10\text{k}}{200} = 50\text{A}_{\text{rms}}$

**phasor I**  $= 50\text{A}_{\text{rms}} \angle -\cos^{-1} 0.6 = 50\text{A}_{\text{rms}} \angle -53^\circ$


$$L = \frac{Q}{\omega I^2} = \frac{8\text{k}}{2\pi 50(50^2)} = 10.2\text{mH}$$

**(c)** Connect a C parallel to the load


$$\therefore C = \frac{|Q_c|}{V^2 \omega} = \frac{8\text{kVAR}}{(200\text{V}_{\text{rms}})^2 * 2\pi 50\text{rad/s}} = 0.64\text{mF}$$

6

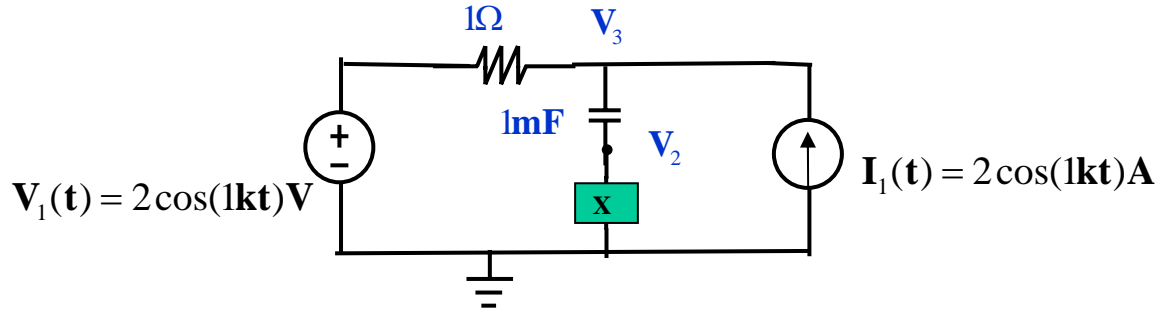- (a) If  $X$  is an open circuit, find  $V_3$  in phasor form.  
 (b) If  $X = 1\text{mH}$ , find  $V_3(t)$ .  
 (c) If  $X = 1\Omega$ , find  $V_2$  in phasor form.  
 Draw also  $V_1$  and  $V_2$  in a **phasor diagram**. (30)



(a)

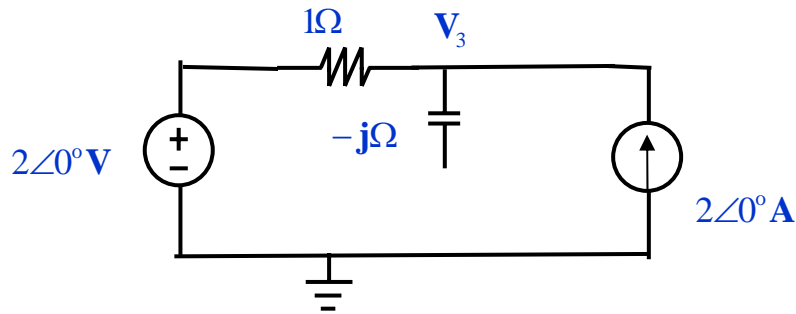

$$\therefore V_3 = 4 \angle 0^\circ \text{ V}$$

$$(b) \quad \frac{1}{j\omega C} = \frac{1}{j(1k)1mF} = -j\Omega$$

$$j\omega L = j(1k)1mH = j\Omega$$

$$\therefore V_3 = 0 \text{ V}$$


(c) using Thevenin's Theorem,  $Z = 1 - j$

$$\therefore V_2 = \frac{1}{1 + 1 - j\Omega} * 4 \angle 0^\circ \text{ V}$$

$$= \frac{4 \angle 0^\circ}{\sqrt{5} \angle -26.6^\circ}$$


$$\cong 1.79 \angle 26.6^\circ \text{ V}$$
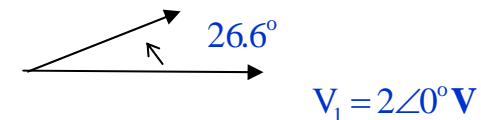
$$V_2 \cong 1.79 \angle 26.6^\circ \text{ V}$$




7 The circuit is at steady state for  $t < 0$ . At  $t = 0$ , the switch is opened. If  $X = 0.4\text{H}$ , find  $I_O(0)$ ,  $I_O(\infty)$ , and time constant  $\tau$ . Plot also  $V_O(t)$  versus  $t$  for  $\infty \geq t \geq 0$  and label clearly the intercepts. (22)

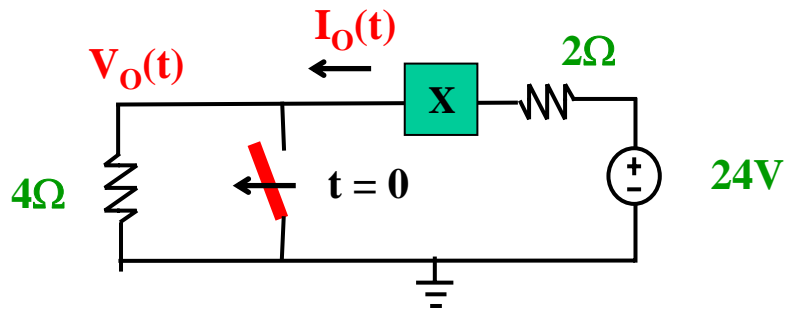Given that  $I_L(t) = I_L(\infty) + [I_L(0) - I_L(\infty)] * e^{-t/\tau}$  and  $\tau = L/R$



(b)

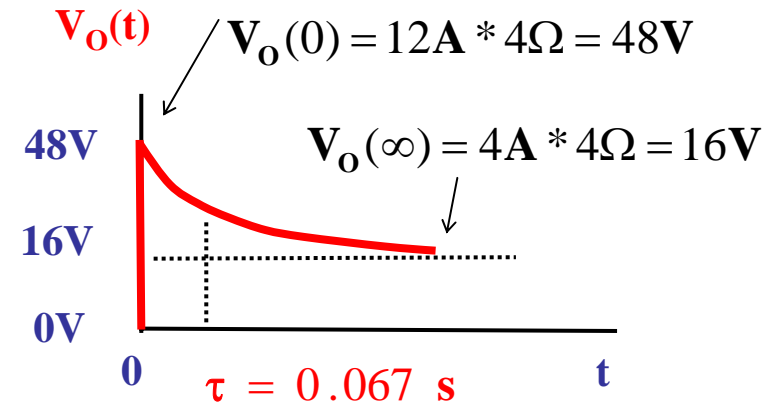


$$\therefore I_O(0) = I_O(0-) = \frac{24\text{V}}{2\Omega} = 12\text{A}$$

$$\therefore \tau = \frac{L}{R} = \frac{0.4\text{H}}{6\Omega} \cong 66.7\text{ms}$$


$$\therefore I_O(\infty) = \frac{24\text{V}}{6\Omega} = 4\text{A}$$

8

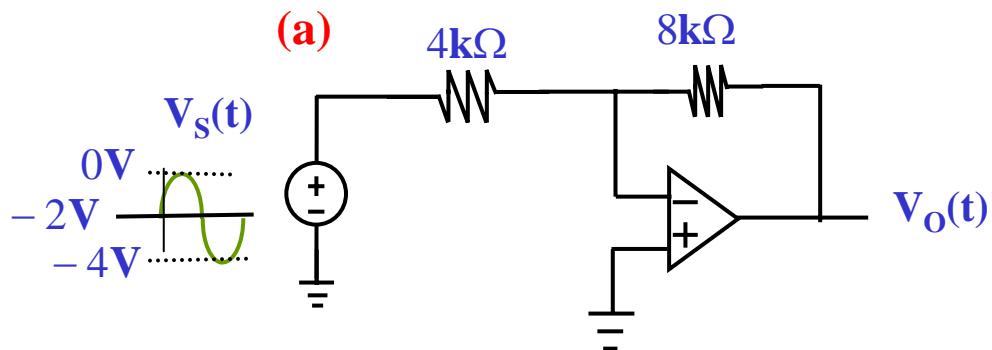
(a) Find the voltage gain  $A (=V_o/V_s)$  and draw the  $V_o(t)$  waveform. Assume an ideal op amp. (9)



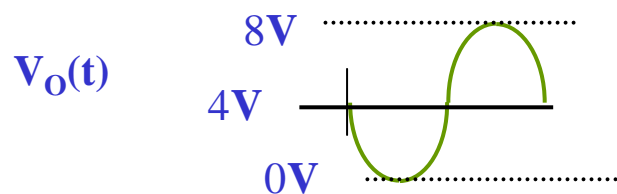(a) 
$$A = -\frac{8\text{k}\Omega}{4\text{k}\Omega} = -2$$



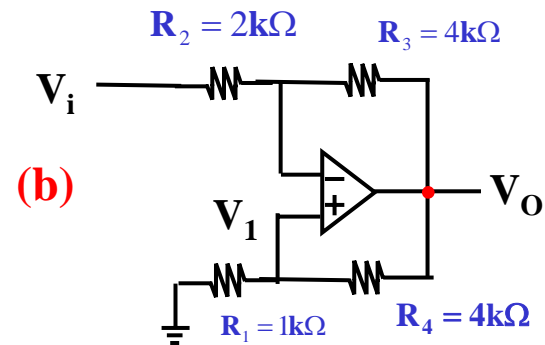(b) Show that  $V_1 = V_o/5$ . Hence find the voltage gain  $A (=V_o/V_i)$ . Assume an ideal op amp. (17)



(b)

$$\therefore V_- = V_+ = V_1$$

$$\therefore \frac{V_1}{1\text{k}} = \frac{V_o - V_1}{4\text{k}}$$

$$\therefore V_1 = \frac{V_o}{5}$$

$$\therefore \frac{V_i - V_1}{2\text{k}} = \frac{V_1 - V_o}{4\text{k}}$$

$$\therefore 2V_i - 2V_1 = V_1 - V_o$$

$$\therefore 2V_i = 3\frac{V_o}{5} - V_o$$

$$\therefore 2V_i = -\frac{2}{5}V_o$$




$$\therefore A_v = \frac{V_o}{V_i} = -5$$



9

In the circuit, the dependent source is a **voltage controlled current source** and is in A.

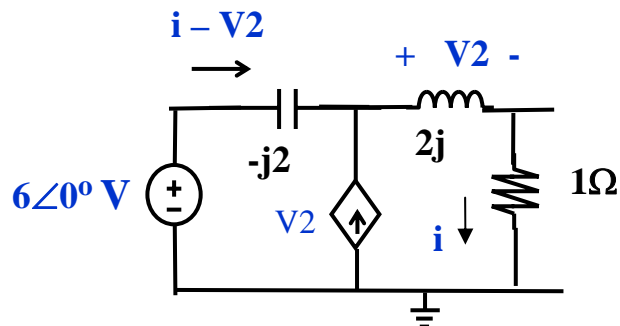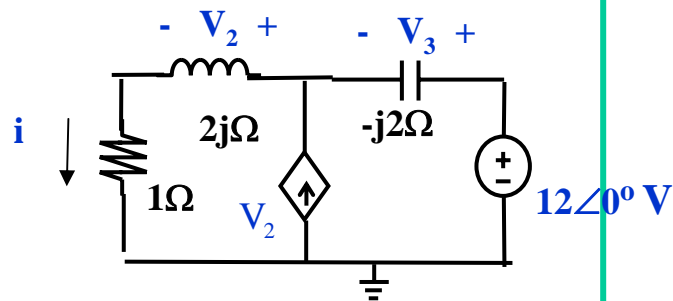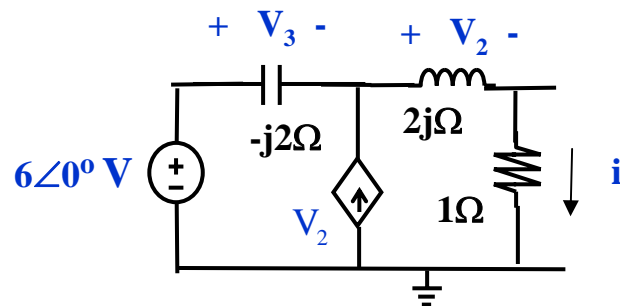Find  $i$ ,  $V_2$  and  $V_3$  in phasor form.  
(20)



$$\therefore i \cdot 1\Omega + V_2 + (i - V_2)(-2j\Omega) = 6V$$

$$\therefore V_2 = i \cdot 2j\Omega = 2ijV$$

$$\therefore i \cdot 1\Omega + 2ijV + (i - 2ij)(-2j\Omega) = 6V$$

$$i \cdot 1\Omega + 2ijV - 2ijV - 4iV = 6V$$

$$-3iV = 6V$$

$$\therefore i = -2A$$

$$\therefore V_2 = 2jiV = -4jV$$

$$\therefore V_3 = (i - V_2) \cdot -2j = (-2 + 4j) \cdot -2j = 4j + 8V$$

