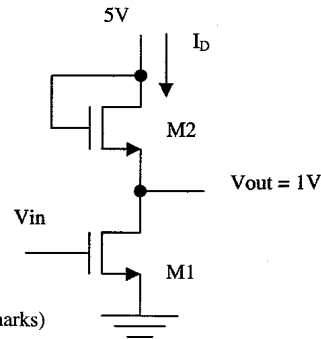


2. The MOS transistors M1 and M2 are identical.
Given : $K = 10 \text{ mA/V}^2$ and $V_T = 1 \text{ V}$.

$$I_D = K(V_{GS} - V_T)^2 \quad \text{Saturation}$$

$$I_D = 2K \left[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right] \quad \text{Ohmic}$$



- a) Find and prove the operation mode of M2. (6 marks)
b) Calculate the current I_D . (4 marks)
c) Find V_{in} if M1 is in ohmic. (7 marks)
d) Estimate the ON resistance r_{on} of M1 ($r_{on} = \partial V_{DS} / \partial I_D$). (5 marks)

$$\begin{aligned} a) \quad & V_{GS} > V_T & V_{DS} > V_{GS} - V_T \\ & 5 - 1 > 1 & 4 > 4 - 1 \end{aligned}$$

\therefore M2 is saturate

$$b) \quad I_D = K(V_{GS} - V_T)^2 = 10 \text{ m} (4 - 1)^2 = 90 \text{ mA} \quad 4$$


$$\begin{aligned} c) \quad I_D &= 2K \left[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2} \right] \\ 90 \text{ m} &= 2(10 \text{ m}) \left[(V_{in} - 1)1 - \frac{1}{2} \right] \end{aligned}$$

$$4.5 = V_{in} - 1.5$$


$$\therefore V_{in} = 6 \text{ V} \quad 7$$

$$\begin{aligned} d) \quad r_{on} &= \frac{1}{2K(V_{GS} - V_T)} = \frac{1}{2(10 \text{ m})(6 - 1)} \\ &= 10 \Omega \quad 5 \end{aligned}$$

3. Given the following circuit diagram.

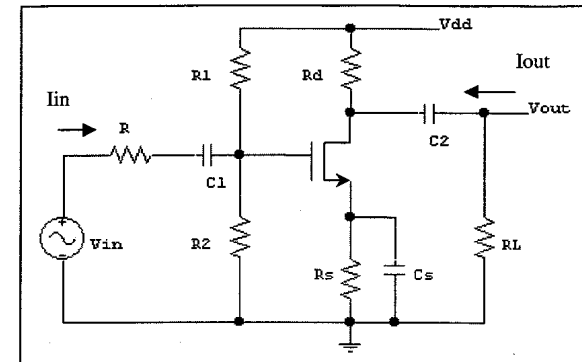

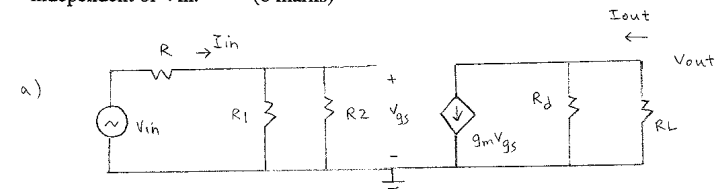- a) Draw the ac equivalent circuit for the whole circuit. Assume C_1 , C_2 and C_s are large, and r_o of NMOS model is infinity. (7 marks)
b) Find the total input resistance R_{in} ($R_{in} = V_{in} / I_{in}$). (3 marks)
c) Find the total output resistance R_{out} ($R_{out} = V_{out} / I_{out}$). (3 marks)
d) Find the ac voltage gain of the amplifier ($A_v = V_{out} / V_{in}$). The expression is required to be independent of V_{in} . (6 marks)




$$b) \quad R_{in} = \frac{V_{in}}{I_{in}} = R + R_1 \parallel R_2 \quad 3$$

$$c) \quad R_{out} = R_L \quad 3$$

$$\begin{aligned} d) \quad A_v &= \frac{V_{out}}{V_{in}} = \frac{-g_m V_{gs} (R_d \parallel R_L)}{\frac{V_{gs}}{R_1 \parallel R_2} (R + R_1 \parallel R_2)} \\ &= \frac{-g_m (R_d \parallel R_L)}{R + R_1 \parallel R_2} \quad 6 \end{aligned}$$

12. Given the following circuit diagram.

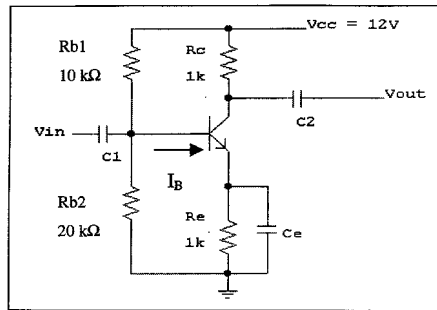


$$\beta = 50$$

$$V_{CE(sat)} = 0.2 \text{ V}$$

$$V_{BE} = 0.7 \text{ V}$$

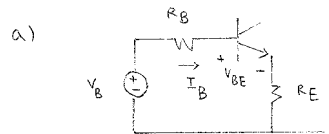- Show that the base current I_B is 0.127 mA. (Hint: Use Thevenin's Theorem) (13 marks)
- Show that the Q-point is in the saturation region. (8 marks)
- Show that the forced β is 29.7 (18 marks)
- Suggest a method to move the Q-point to the active region. (4 marks)
- Give two advantages of this circuit connection. (4 marks)
- Briefly explain the function of C1, C2 & Ce. (5 marks)



$$V_B = V_{CC} \frac{R_{b2}}{R_{b1} + R_{b2}} = 12 \frac{20k}{10k + 20k} = 8 \text{ V} \quad 3$$

$$R_B = R_{b1} \parallel R_{b2} = 10k \parallel 20k = \frac{20k \cdot 10k}{30k} = \frac{20k}{3} \quad 3$$

$$I_B = \frac{V_B - V_{BE}}{R_B + (1 + \beta) R_E} = \frac{8 - 0.7}{\frac{20k}{3} + (1 + 50) 1k} = 0.127 \text{ mA} \quad 7$$

- b) If BJT active, $I_C = \beta I_B = 50 (0.127 \text{ mA}) = 6.33 \text{ mA} \approx I_E$
- but $I_C R_C + I_E R_E \approx 6.33 \text{ mA} (2k) > 12 \text{ V}$

\therefore BJT saturates

c) BJT saturates

$$V_{CC} = I_C R_C + V_{CE(sat)} + I_E R_E$$

$$12 = \beta I_B 1k + 0.2 + (1 + \beta) I_B 1k$$

$$\therefore I_B = \frac{11.8}{1k(2\beta + 1)}$$

$$\text{But } I_B \text{ also} = \frac{V_B - V_{BE}}{R_B + (1 + \beta_f) R_E} = \frac{8 - 0.7}{\frac{20k}{3} + (1 + \beta_f) 1k}$$

$$\therefore 7.3k(1 + 2\beta_f) = 11.8k \left(\frac{20}{3} + 1 + \beta_f \right)$$

$$\therefore \beta_f = 29.7 \quad 18$$

- d) BJT active, $I_B \downarrow$
or $R_B + (1 + \beta) R_E \uparrow \quad 4$


- e) single supply (V_{CC})
stable Q point 4

- f) C_1, C_2 : block DC and pass AC current 5

C_e : short R_E at AC
increase A_v

11

(30)

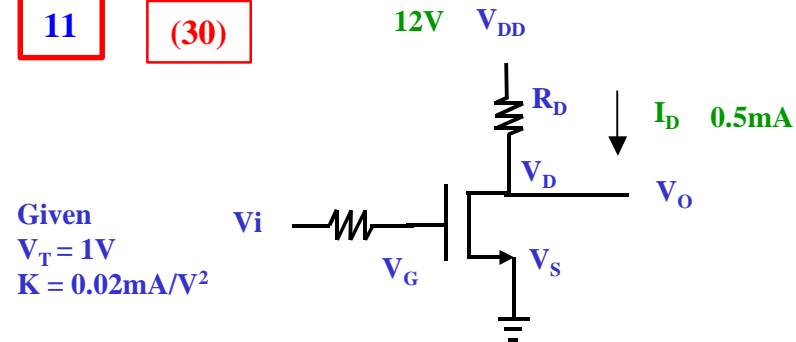

Find R_D such that $V_i = V_O$,
 i.e. $V_{GS} = V_{DS}$ and NMOS saturates

$$\therefore I_{DS} = K (V_{GS} - V_T)^2 = 0.02m(V_{GS} - 1)^2 = 0.5mA$$

$$\therefore V_{GS} = \sqrt{\frac{0.5m}{0.02m}} + 1 = 6V$$

$$\therefore V_{DD} = I_{DS}R_D + V_{DS}$$

$$\therefore R_D = \frac{V_{DD} - V_{DS}}{I_{DS}} = \frac{12 - 6}{0.5m} = 12kW$$

Find V_O such that $V_i = V_{DD}$
 i.e. $V_{GS} = 12V$, hence $V_{GS} - V_T > V_{DS}$ and NMOS in triode

$$\begin{aligned} I_{DS} &= 2K[(V_{GS} - V_T)V_{DS} - \frac{V_{DS}^2}{2}] \\ &= 2(0.02m)[(12 - 1)V_{DS} - \frac{V_{DS}^2}{2}] \end{aligned}$$

$$I_{DS} = \frac{V_{DD} - V_{DS}}{R_D} = \frac{12 - V_{DS}}{12.5k} = 0.04m(11V_{DS} - \frac{V_{DS}^2}{2})$$

$$12 - V_{DS} = 0.5[11V_{DS} - \frac{V_{DS}^2}{2}]$$


$$12 - 6.5V_{DS} + 0.25V_{DS}^2 = 0$$

$$V_{DS}^2 - 26V_{DS} + 48 = 0$$

$$V_{DS} = 24V \quad \text{or} \quad 2V$$

hence $V_O = V_{DS} = 2V$ ($24V > V_{DS}$ is impossible)

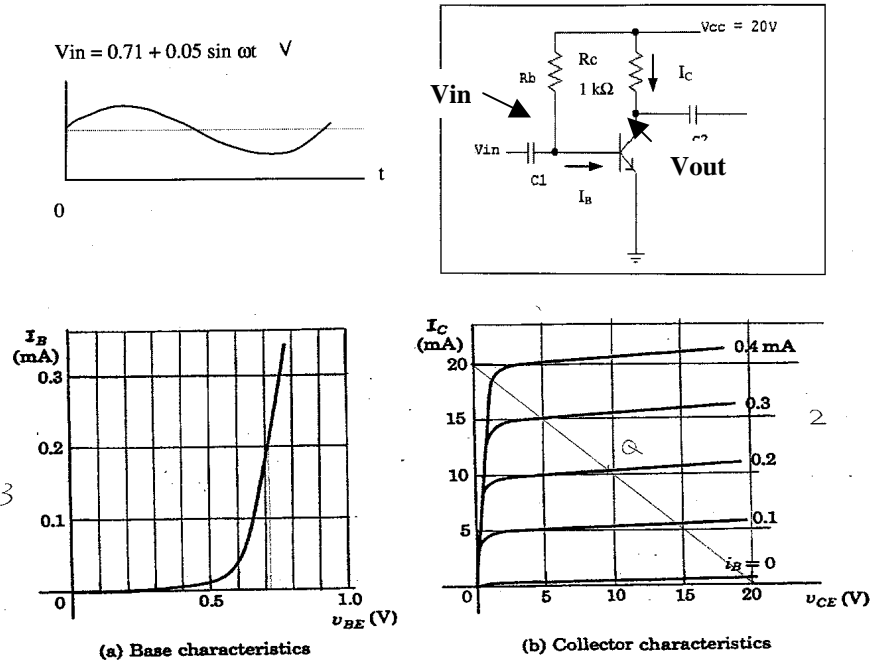13. Given the following circuit diagram. The input (base) and output (collector) characteristics of the BJT are given.



- Plot the dc load line in the output characteristics. Show clearly your calculations. (4 marks)
- Show that the base current I_B is 0.2 mA. (3 marks)
- Calculate R_b . (3 marks)
- Show the location of the Q-point in the output characteristics. (2 marks)
- Find I_C and V_{CE} at the Q-point. (4 marks)
- Sketch the base current I_B , the collector current I_C and the output voltage V_{out} . Show clearly the dc level, the maximum and the minimum values in your sketch. (15 marks)
- Calculate the ac voltage gain ($A_v = \Delta V_{out} / \Delta V_{in}$). (3 marks)
- Calculate the ac current gain ($A_i = \Delta I_C / \Delta I_B$). (3 marks)

$$a) \quad V_{CC} = I_C R_C + V_{CE}$$


$$I_C = 0 \quad V_{CE} = V_{CC} = 20 \text{ V}$$

$$V_{CE} = 0 \quad I_C = \frac{V_{CC}}{R_C} = \frac{20 \text{ V}}{1 \text{ k}\Omega} = 20 \text{ mA}$$



$$b) \quad V_{BE} \approx 0.7 \text{ V}$$

$$I_B = 0.2 \text{ mA}$$

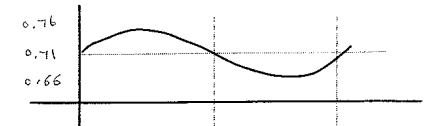
$$V_{in} = 0.71 + 0.05 \sin \omega t \text{ V}$$



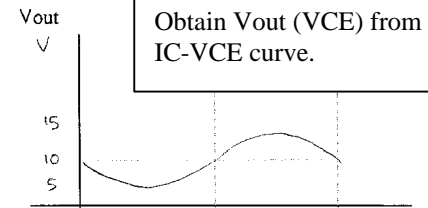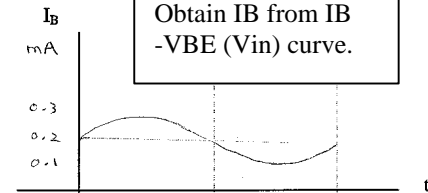Obtain I_B from I_B - V_{BE} (V_{in}) curve.



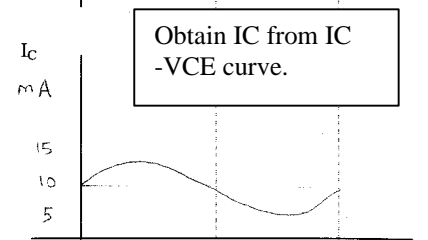Obtain V_{out} (V_{CE}) from I_C - V_{CE} curve.



Obtain I_C from I_C - V_{CE} curve.

$$c) \quad R_b = \frac{V_{CC} - V_{BE}}{I_B}$$

$$= \frac{20 - 0.7}{0.2 \text{ mA}}$$

$$= 96.5 \text{ k}\Omega \quad 3$$

d) Q point

$$e) \quad I_C \approx 10 \text{ mA}$$

$$V_{CE} \approx 10 \text{ V} \quad 4$$

f) 15

$$g) \quad A_v = \frac{\Delta V_{out}}{\Delta V_{in}}$$

$$\approx \frac{5 - 15}{0.76 - 0.66}$$

$$= -100 \quad 3$$

$$A_i = \frac{\Delta I_C}{\Delta I_B}$$

$$\approx \frac{15 - 5}{0.3 - 0.1}$$

$$= 50 \quad 3$$

END

12. The BJT in the circuit has the output characteristic curves as shown.



(a) Sketch the load line $V_{CC} = I_C R_C + V_{CE}$. (6)

(b) Locate the Q-point on the loadline and find the operating modes of the BJT (i) if $V_i = 0.8V$, and (ii) if the circuit is to give maximum symmetric V_{CE} output. (14)

(c) Show that the voltage gain $A_v (= \Delta V_o / \Delta V_i)$ of the circuit is -90 . (11)

Given that for the BJT, $V_{BE} = 0.7V$, $\beta = 120$, $r_\pi = 1\text{ k}\Omega$, $r_o = \infty$.

I_C (mA)

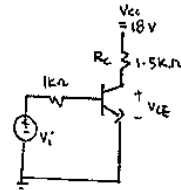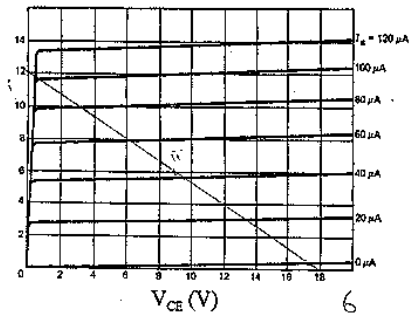

(i) $V_i = 0.8V$

$$I_B = \frac{0.8 - 0.7}{1K} = 0.1\text{mA} \quad 4$$

BJT ON. 3



(ii) middle of loadline 4

BJT active 3

11. In the circuit, (a) show that $I_B \sim 25\text{ }\mu\text{A}$. (19)

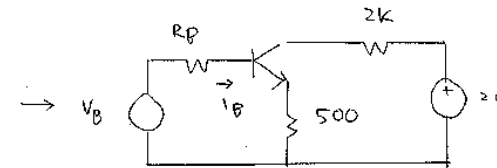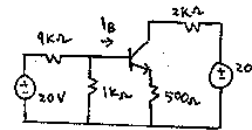(b) Explain briefly why the circuit can have stable I_C . (7)

For the BJT, given $V_{BE} = 0.7V$ and $\beta = 100$.



$$V_B = 20 \frac{1K}{10K} = 2V \quad 5$$

$$R_B = 1K \parallel 9K = 900\Omega \quad 4$$

$$\begin{aligned} \therefore 2 &= I_B R_B + V_{BE} + I_E 500 \\ &= I_B 900 + 0.7 + (101) I_B 500 \end{aligned}$$

$$\therefore I_B = \frac{2 - 0.7}{900 + 101(500)} \approx 25\text{ }\mu\text{A} \quad 10$$

$$I_C \uparrow \quad V_E \uparrow \quad V_{BE} \downarrow \quad I_B \downarrow \quad I_C \downarrow \quad 7$$