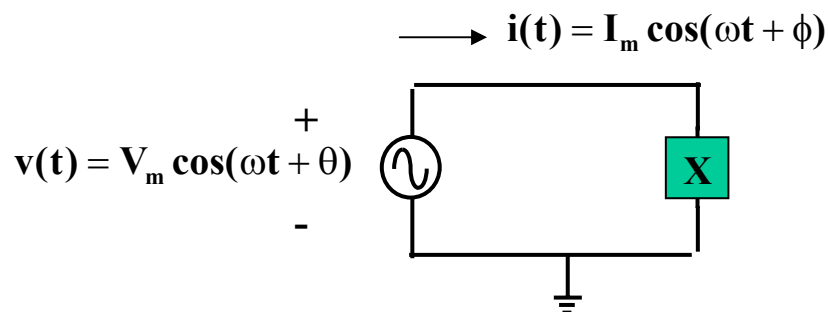


1

In the circuit, X is an unknown element. (32)

(a) If  $V_m = 10V$ ,  $I_m = 5A$ ,  $\theta = \phi = 60^\circ$ , find X in  $\Omega$ , power factor of X, power stored in X, and power absorbed by X.

(b) If  $V_m = 8V$ ,  $I_m = 2A$ ,  $i(t)$  leads  $v(t)$  by  $90^\circ$ , find X in  $\Omega$ , power factor of X, power stored in X, and power absorbed by X.



(a) V and I in phase

$$\therefore X = R = \frac{V_m}{I_m} = \frac{10V}{5A} = 2\Omega \quad (4)$$

$$PF = 1 \quad (3)$$

$$P_R = I^2 * R = \left(\frac{5A}{\sqrt{2}}\right)^2 * 2\Omega = 25W \quad (5)$$

$$Q_R = 0 \quad (3)$$

(b) I leads V

$$\therefore X = C = -j4\Omega \quad (6)$$

$$PF = 0 \quad (3)$$


$$Q_C = I^2 * X = \left(\frac{2A}{\sqrt{2}}\right)^2 * 4\Omega = 8VAR(C) \quad (5)$$

$$P_C = 0W \quad (3)$$

2

The circuit is at steady state for  $t < 0$ . At  $t = 0$ , the switch is switched from A to B (i.e. BC is shorted). (a) Find  $i(t)$  for  $t \geq 0$ . (b) Find the maximum energy stored in L. (c) Plot  $V(t)$  for  $t < 0$  and  $t \geq 0$ . Label clearly the voltage and time. (33)

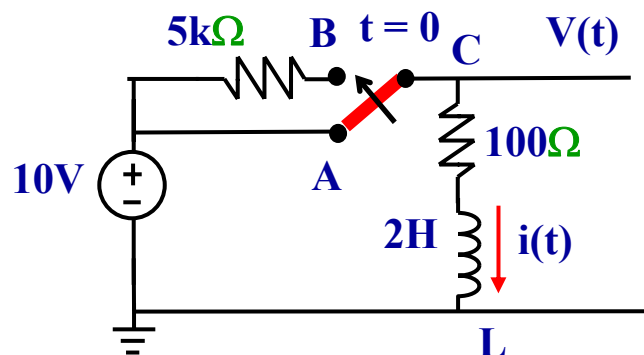Given that  $i(t) = i(\infty) + [i(0) - i(\infty)] * e^{-t/\tau}$  and  $\tau = L/R$



$$(a) \quad \therefore i(t = 0) = i(t < 0) = 0.1A \quad (4)$$

$$\therefore i(\infty) = \frac{10V}{5100\Omega} \cong 2mA \quad (4)$$



$$\therefore \tau = \frac{L}{R} = \frac{2H}{5100\Omega} \cong 0.4ms \quad (4)$$

$$\begin{aligned} \therefore i(t) &= i(\infty) + [i(0) - i(\infty)] * e^{-\frac{t}{\tau}} \\ &\cong 2mA + [100mA - 2mA] * e^{-t/0.4ms} \end{aligned} \quad (3)$$

(b)

$$\therefore E_L = \frac{1}{2} Li^2 = \frac{1}{2} (2H)(0.1A)^2 = 10mJ \quad (5)$$


(c)

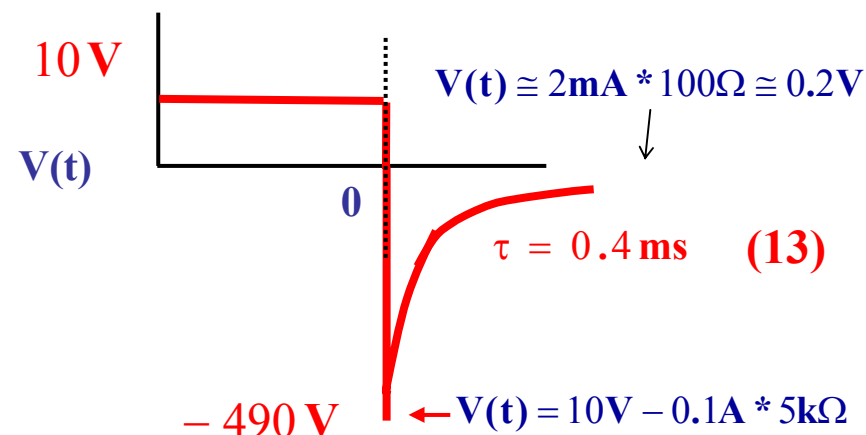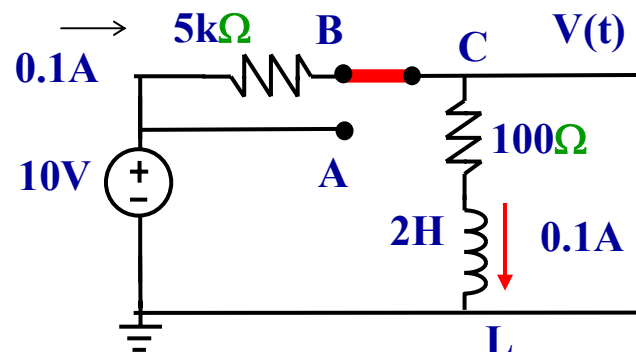

3

The circuit is at steady state for  $t < 0$ . At  $t = 0$ , the switch is closed. (a) Find  $V(0)$ ,  $V(\infty)$  and time constant  $\tau$  for  $t > 0$ . (b) Plot  $I_O(t)$  for  $t < 0$  and  $t \geq 0$ . (25)

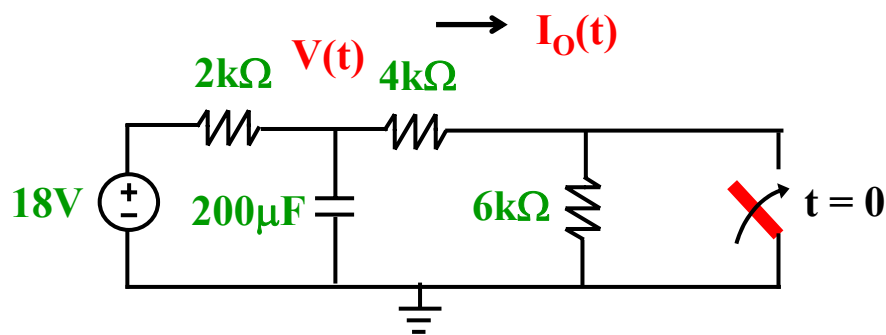Given that  $V(t) = V(\infty) + [V(0) - V(\infty)] * e^{-t/\tau}$   
and  $\tau = CR$





(a)

$$\therefore V(0) = V(0-) = 18V \left( \frac{10k\Omega}{12k\Omega} \right) = 15V \quad (4)$$

$$\therefore \tau = CR = 200\mu F * (2k\Omega // 4k\Omega) = 0.267s \quad (4)$$

$$\therefore V(\infty) = 18V * \frac{4k\Omega}{6k\Omega} = 12V \quad (4)$$



(b)

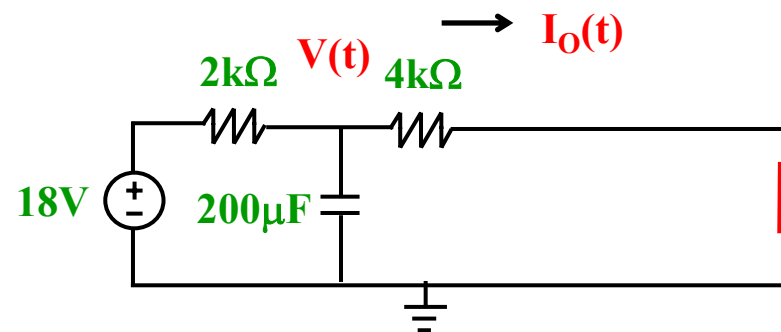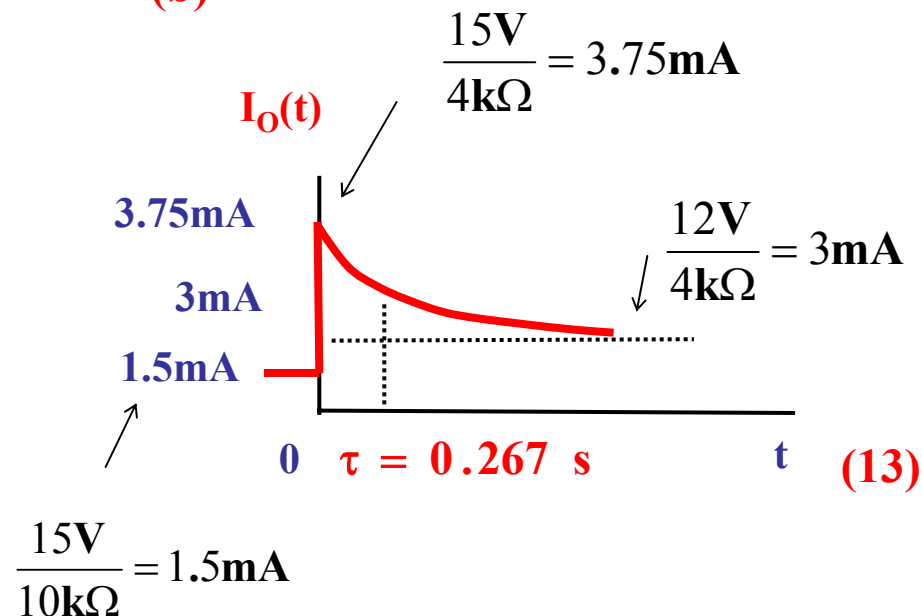

4

In the circuit,  $V_1$  versus log-frequency  $f$  is given as shown.  
Find roughly the magnitude of  $V_S$  in V, bandwidth of DMM in Hz, and  $V_1$  at bandwidth in Vrms.  
Assume  $R_{in} \gg R$ . (18)

$V_1 ( \times 1.4V_{rms} )$

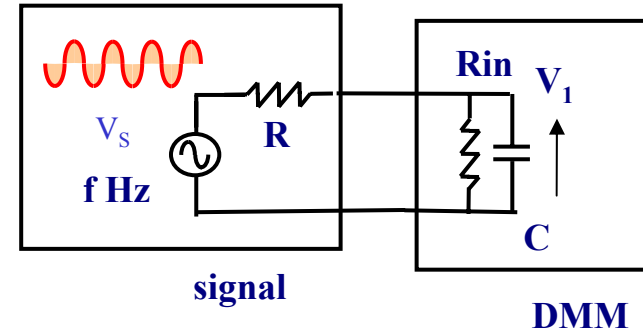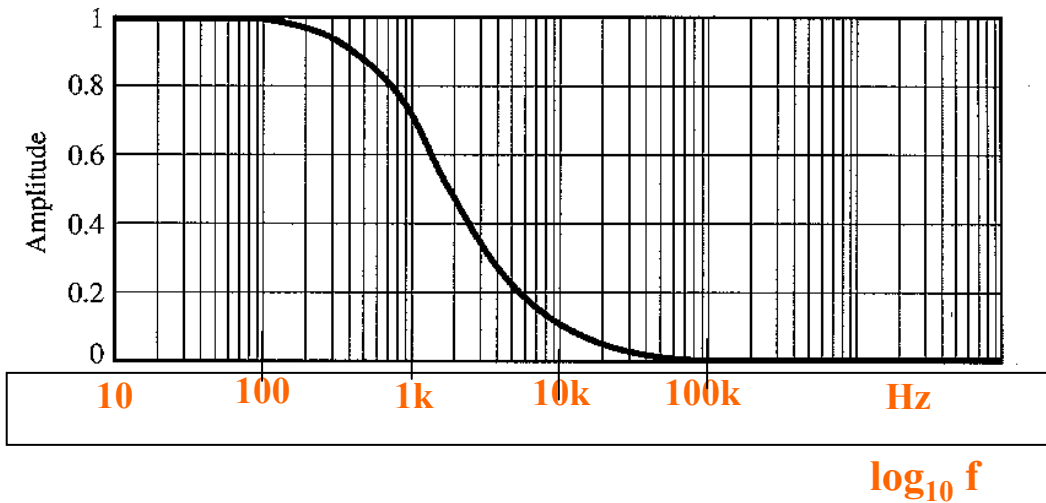

magnitude  $V_m \approx 2V$  (6)


bandwidth  $\approx 1\text{kHz}$  (6)

At bandwidth,  $V_1 \approx 0.7 \times 1.4 V_{rms}$  (6)

5

Find  $\omega$  and  $\theta$ . Show that  $V_2(t)$  is roughly  $-3.5V$  when  $t = 2ms$ .

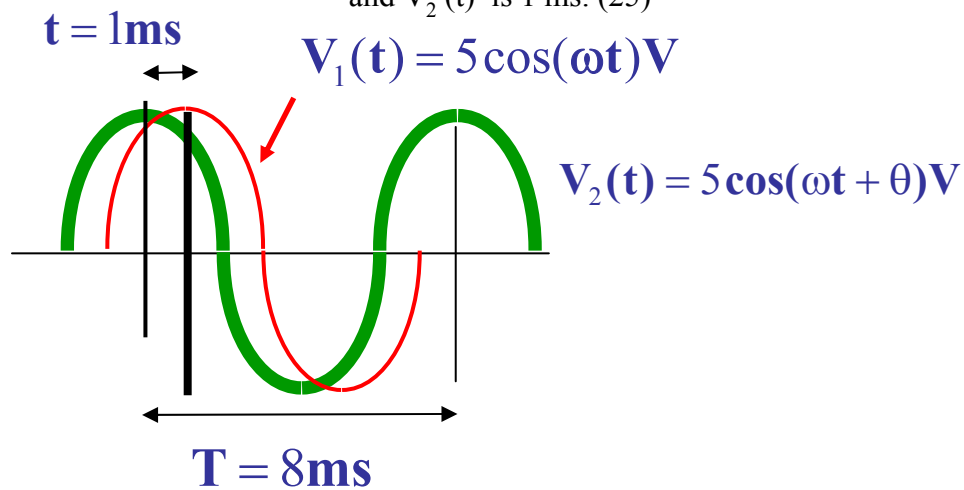Does  $V_2(t)$  lag  $V_1(t)$ ? Given  $2\pi$  radian =  $360^\circ$ , period of  $V_2(t)$  is  $8ms$ , and difference between the peaks of  $V_1(t)$  and  $V_2(t)$  is  $1ms$ . (25)



$$\omega = \frac{2\pi}{T} = \frac{2\pi}{8ms} \quad (5)$$


$$\theta = \frac{t}{T} * 360^\circ = \frac{1ms}{8ms} * 360^\circ = 45^\circ \quad (6)$$

$$\therefore V_2(t) = 5\cos\left(\frac{2\pi}{8ms}t + 45^\circ\right)V \quad (2)$$

$$\begin{aligned} \therefore V_2(t) &= 5\cos\left(\frac{2\pi}{8ms} * 2ms + 45^\circ\right)V \\ &= 5\cos\left(\frac{\pi}{2} + 45^\circ\right)V = 5\cos(90^\circ + 45^\circ)V \\ &\cong -3.54V \end{aligned} \quad (9)$$

$$V_2(t) \text{ leads } V_1(t) \quad (3)$$

6

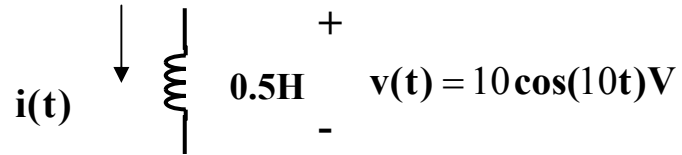(a). Find  $i(t)$ . (12)



$$\begin{aligned}
 i(t) &= \left( \frac{V_m}{\omega L} \right) \cos(10t - 90^\circ) \text{ A} \\
 &= \left( \frac{10 \text{ V}}{10 \text{ rad/s} * 0.5 \text{ H}} \right) \cos(10t - 90^\circ) \\
 &= 2 \text{ A} \cos(10t - 90^\circ)
 \end{aligned} \tag{12}$$

or 
$$\begin{aligned}
 \therefore I &= \frac{V}{Z} = \frac{10 \angle 0^\circ \text{ V}}{j\omega L} = \frac{10 \angle 0^\circ \text{ V}}{j * 10 \text{ rad/s} * 0.5 \text{ H}} \\
 &= \frac{10 \angle 0^\circ \text{ V}}{5j\Omega} = 2 \angle -90^\circ \text{ A}
 \end{aligned}$$

(b)

(b). Find  $V_L$  in  $V_{\text{rms}}$  and  $I$  in  $A_{\text{rms}}$ . (15)

(27)

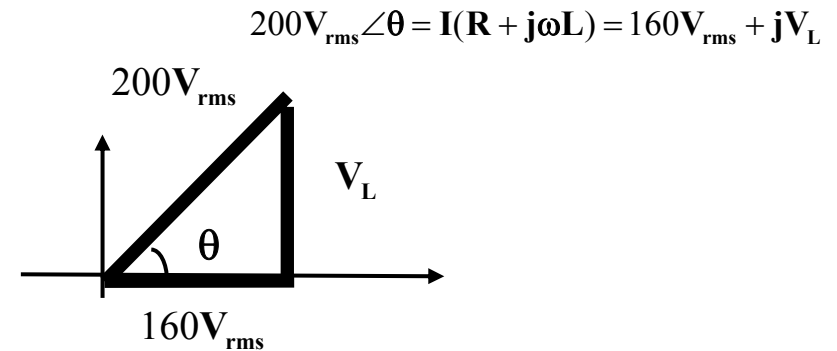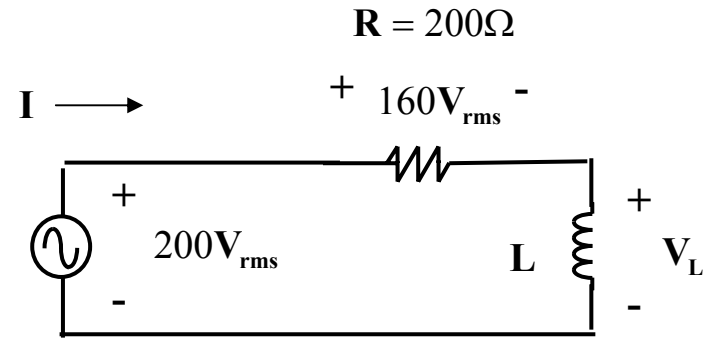


$$\begin{aligned}
 V_L &= \sqrt{200 V_{\text{rms}}^2 - 160 V_{\text{rms}}^2} \\
 &= 120 V_{\text{rms}}
 \end{aligned} \tag{10}$$


$$I = \frac{160 V_{\text{rms}}}{200 \Omega} = 0.8 A_{\text{rms}} \tag{5}$$

7

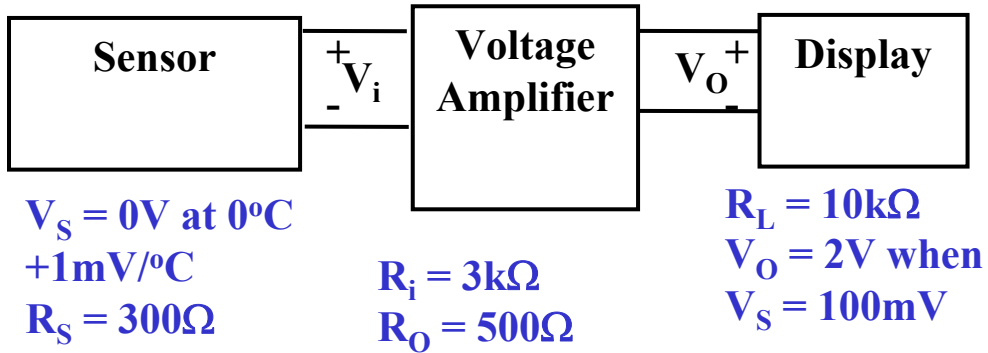7. A voltage amplifier is used to amplify the sensor signal (0 to 100mV) to drive the display (0 to 2V) as shown. Draw the **circuit model** and then find the voltage gain of the voltage amplifier. (22).



### Circuit Model

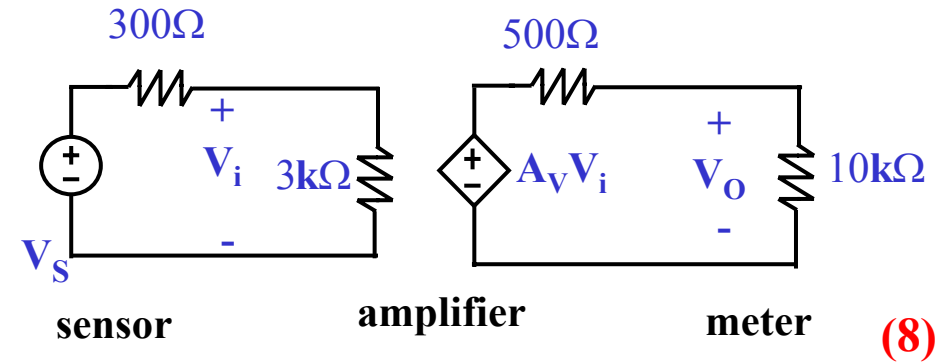


Use voltage divider

$$\begin{aligned}
 V_o &= A_v * V_i * \frac{10\text{k}\Omega}{10\text{k}\Omega + 500\Omega} \\
 &= A_v * V_s * \frac{3\text{k}\Omega}{3\text{k}\Omega + 300\Omega} * \frac{10\text{k}\Omega}{10\text{k}\Omega + 500\Omega}
 \end{aligned}
 \quad (8)$$

$$2V = A_v * 100\text{mV} * \frac{3\text{k}\Omega}{3.3\text{k}\Omega} * \frac{10\text{k}\Omega}{10.5\text{k}\Omega}$$

$$\therefore A_v = 23.1 \quad (6)$$

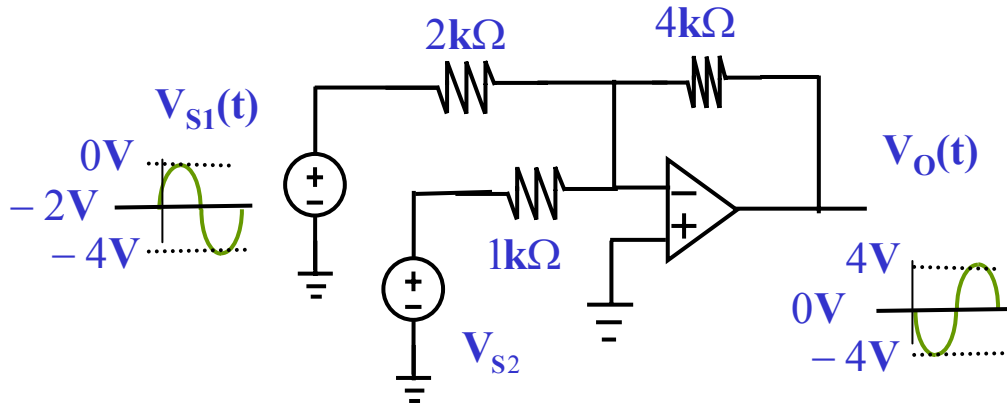**8**(a). Find the value of  $V_{s2}$ . Assume op amp is ideal. (18)

$$(a) \quad V_o(t) = -\frac{4k\Omega}{2k\Omega} V_{s1}(t) - \frac{4k\Omega}{1k\Omega} V_{s2} \quad (7)$$


$$= -2V_{s1}(t) - 4V_{s2} \quad (2)$$

$$4V = -2 * (-4V) - 4V_{s2}$$

$$\therefore V_{s2} = 1V \quad (9)$$


$$0V = -2 * (-2V) - 4V_{s2} \quad -4V = -2 * (0V) - 4V_{s2}$$

$$\therefore V_{s2} = 1V \quad \therefore V_{s2} = 1V$$

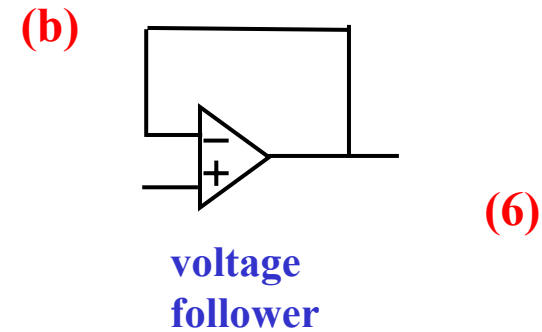(b) Draw the circuit of an op amp voltage follower and name two advantages of the circuit. (12)

1. Very high input resistance
  2. Very low output resistance
- (6)



or

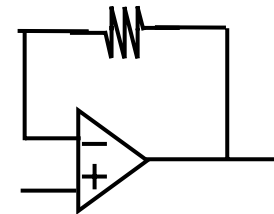



9

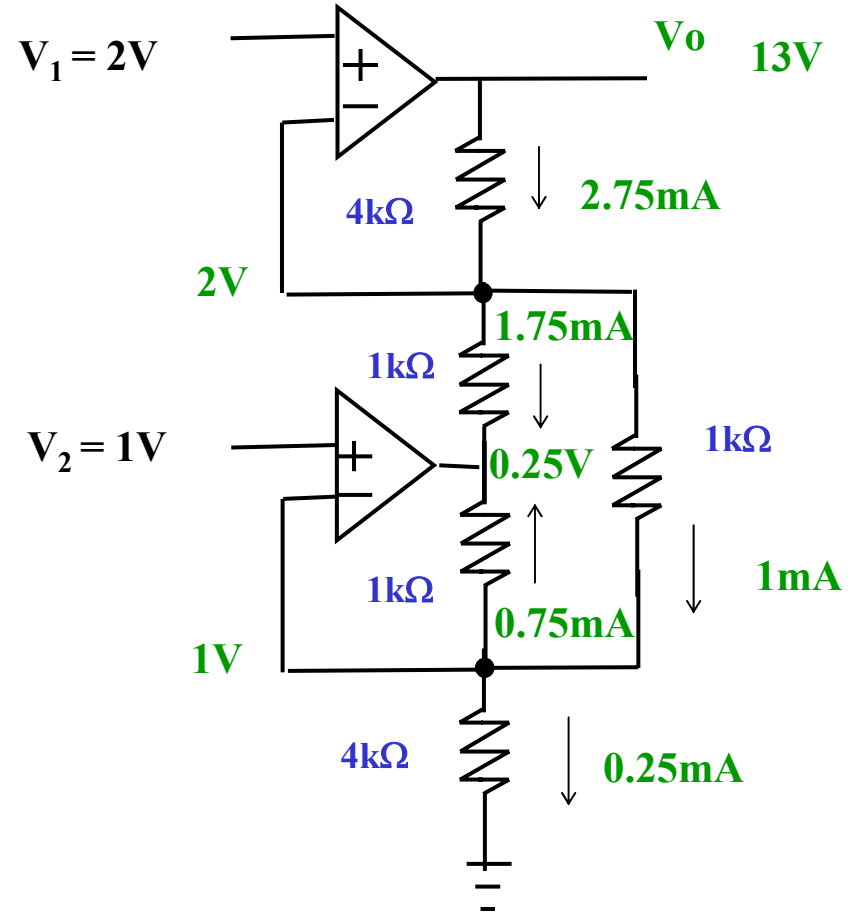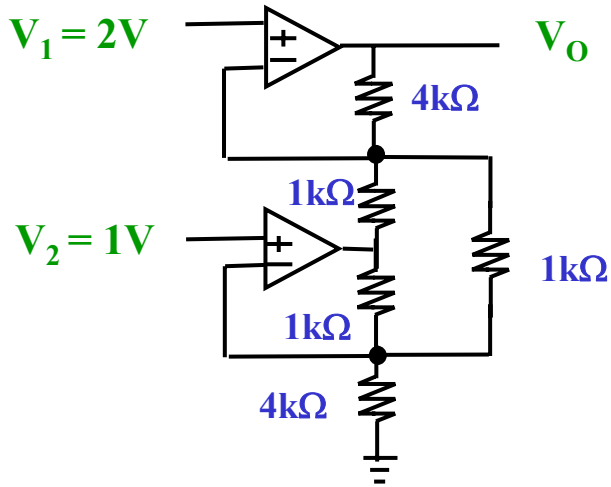Find  $V_O$ . Show clearly all your steps. Assume op amp is ideal.  
(30)




$$V_O = 13V \quad (30)$$

10

In the circuit,  $v(t) = 240\sqrt{2} \cos(2\pi 50t) \text{ V}$ .

Find the frequency and period of  $v(t)$ , and the V phasor of  $v(t)$ . Show that  $i(t) \cong 60 \cos(2\pi 50t - 45^\circ) \text{ A}$ .

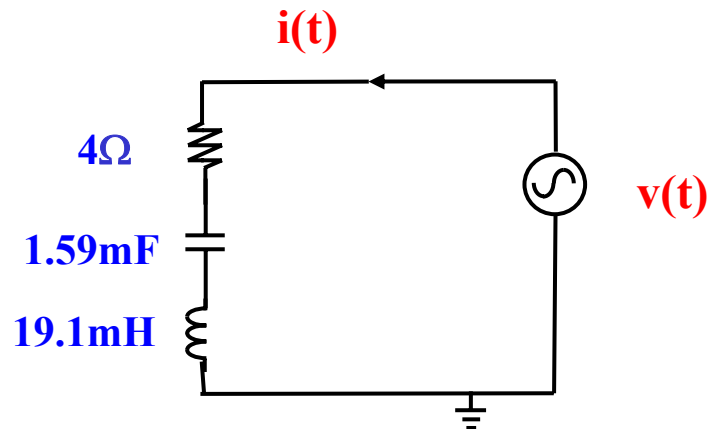Plot also phasor V and I in a phasor diagram. (33)



Find frequency  $f$  of  $v(t)$

$$f = 50 \text{ Hz} \quad (2)$$

Find period of  $v(t)$

$$T = \frac{1}{f} = \frac{1}{50 \text{ Hz}} = 20 \text{ ms} \quad (3)$$

Find V phasor

$$V = 240\sqrt{2} \angle 0^\circ \text{ V} \quad (2)$$

## Find impedance $Z$

$$\frac{1}{j\omega C} = \frac{1}{j(2\pi 50)(1.59 \text{ mF})} \cong -2j\Omega \quad (3)$$


$$j\omega L = j * 2\pi 50 * 19.1 \text{ mH} \cong 6j\Omega \quad (3)$$

$$\begin{aligned} Z &= R + j\omega L + \frac{1}{j\omega C} = 4 + j6 - j2\Omega \\ &= 4 + j4\Omega \\ &= 4\sqrt{2}\angle 45^\circ\Omega \end{aligned} \quad (6)$$
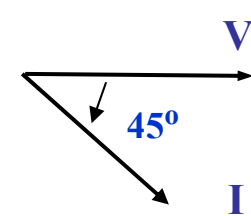
## Find $I$


$$\begin{aligned} \therefore I &= \frac{V}{Z} = \frac{240\sqrt{2}\angle 0^\circ \text{ V}}{4\sqrt{2}\angle 45^\circ\Omega} \\ &= 60\angle -45^\circ \text{ A} \end{aligned} \quad (4)$$

$$\therefore i(t) = 60\cos(2\pi 50t - 45^\circ) \text{ A} \quad (4)$$



$$V = 240\sqrt{2}\angle 0^\circ \text{ V} \quad (6)$$



$$I = 60\angle -45^\circ \text{ A}$$

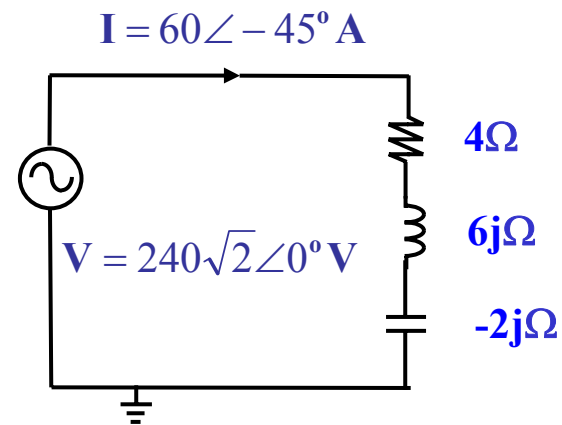

11

A parallel LCR tuner circuit is used to receive radio stations as shown in the resonance curve.

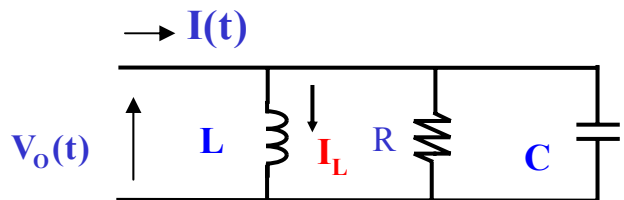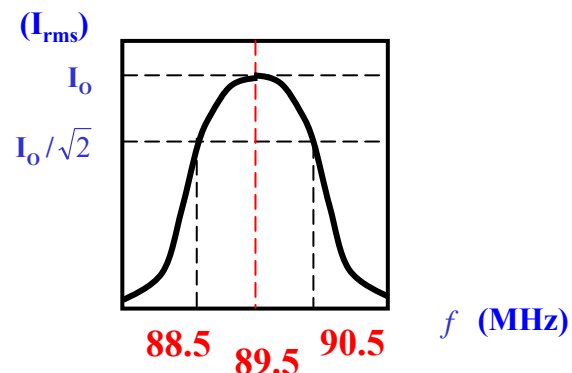(a) Find in Hz the resonant frequency ( $f_o$ ), bandwidth (BW), upper and lower frequencies of the tuner. Show also the quality factor (QF) is 44.75. (b) If maximum  $V_o$  of the tuner is  $1V_{rms}$  and maximum current in the inductor  $I_L$  is  $4.475mA_{rms}$ , show that  $R$  is  $10k\Omega$  and  $L$  is about  $0.4 \times 10^{-6}H$ . Find also the value of  $C$  of the tuner circuit. Given that  $QF = f_o/BW$  and  $QF = R/\omega_o L$ . (32)



$$(a) \quad f_o = 89.5 \text{ MHz} \quad (2)$$

$$BW = 2 \text{ MHz} \quad (2)$$

$$f_{\text{upper}} = 90.5 \text{ MHz} \quad (2)$$

$$f_{\text{lower}} = 88.5 \text{ MHz} \quad (2)$$

$$QF = \frac{f_o}{BW} = \frac{89.5 \text{ MHz}}{2 \text{ MHz}} = 44.75 \quad (4)$$

$$(b) \quad \therefore I = \frac{I_L}{QF} = \frac{4.475 \text{ mA}}{44.75} = 0.1 \text{ mA} \quad (5)$$

$$\therefore R = \frac{V_o}{I} = \frac{1V_{rms}}{0.1mA_{rms}} = 10k\Omega \quad (5)$$

$$\therefore L = \frac{R}{QF * \omega_o} = \frac{10k\Omega}{44.75 * 89.5 \text{ MHz} * 2\pi} \cong 0.397 \mu\text{H} \quad (5)$$

$$\therefore C = \frac{1}{\omega_o^2 L} \cong \frac{1}{(2\pi * 89.5 \text{ M})^2 * 0.397 \mu\text{H}} \cong 8 \text{ pF} \quad (5)$$


12

The series LCR circuit is in resonance. If  $V_R(t) \cong 0.28 \cos(500t) \text{ V}$

Show that the quality factor (QF) is 20. Show also


$$V(t) = 0.2\sqrt{2} \cos(500t) \text{ V}$$

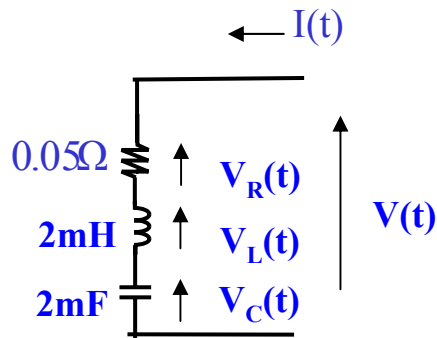Find also  $V_L$  in  $V_{\text{rms}}$  and  $I$  in  $A_{\text{rms}}$ . Given that  $QF = \omega_0 L / R$ . (27)



$$j\omega_0 L = j * 500 \text{ rad/s} * 2 \text{ mH} = j\Omega$$
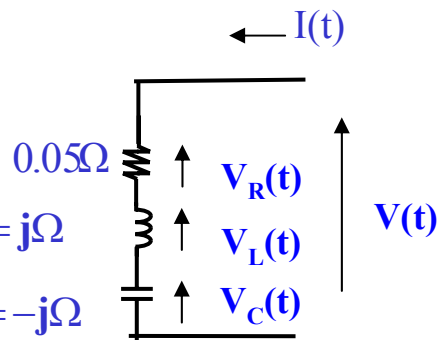
$$\frac{1}{j\omega_0 C} = \frac{1}{j * 500 \text{ rad/s} * 2 \text{ mF}} = -j\Omega$$



$$\therefore \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2 \text{ mH} * 2 \text{ mF}}} = 500 \text{ rad/s} \quad (5)$$

$$\therefore QF = \frac{\omega_0 L}{R} = \frac{500 \text{ rad/s} * 2 \text{ mH}}{0.05 \Omega} = 20 \quad (5)$$

Circuit is in resonance

$$\therefore V_R(t) = V(t)$$


$$\therefore V(t) = 0.2\sqrt{2} \cos(500t) \text{ V} \quad (5)$$

$$\therefore V_L = 20 * 0.2 V_{\text{rms}} \quad (6)$$

$$I = \frac{V}{R} = \frac{0.2 V_{\text{rms}}}{0.05 \Omega} = 4 A_{\text{rms}} \quad (6)$$

13


In the circuit, find  $V_2$ . (17)

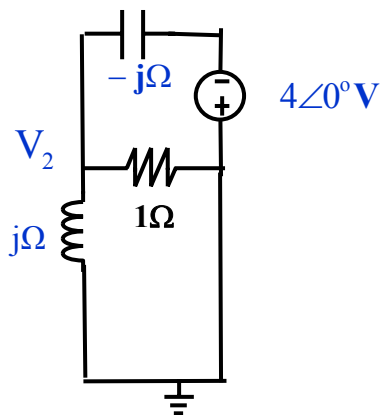

$$\frac{0 - V_2}{j\Omega} = \frac{V_2}{1\Omega} + \frac{V_2 + 4}{-j\Omega} \quad (9)$$

$$-V_2 = jV_2 - (V_2 + 4) \quad (8)$$

$$V_2 = -j4V$$

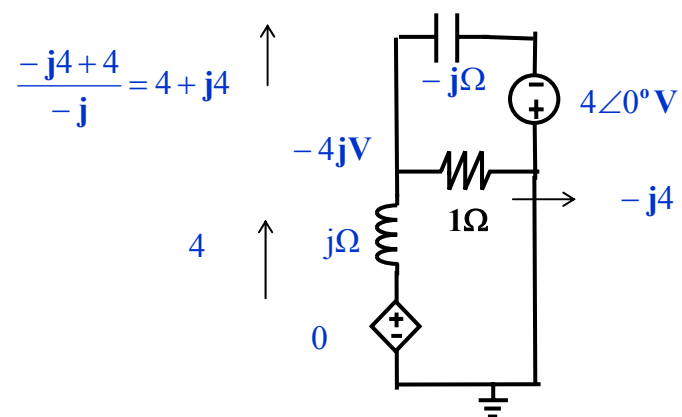

14

Load A is connected to  $V(t)$  as shown. Given  $V(t) = 200\sqrt{2} \cos(2\pi 50t) \text{ V}$


(a) Show that the power absorbed by load A is 800W. Find also the power stored by load A.

(b) Show that the power supplied (S) by  $V(t)$  is roughly 1504VA. Find also the power factor of load A. (25)

(c) Show that I is about 7.5Arms.

(d) If load B is connected in parallel to load A such that the power factor (PF) of the combined load is 1, find the element and value of load B. Show also the new I is about 4 Arms.

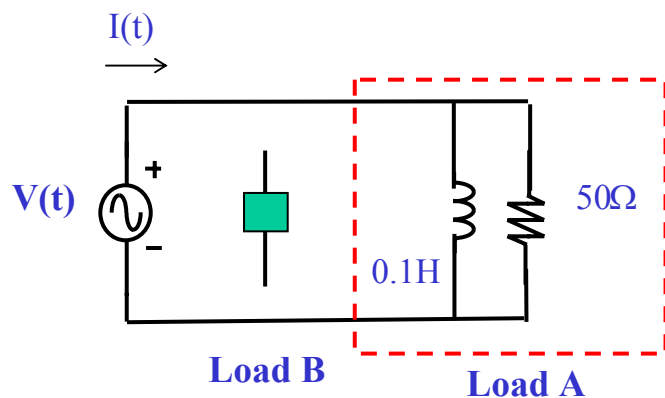(e) Will electric fees be reduced if the power factor is improved to 1? Why? Name also two advantages of improving the power factor. (33) Given that  $S = VI$  and  $P = S \cdot \text{PF}$



(a)

power absorbed by load A = P (2)

$$P = \frac{V^2}{R} = \frac{(200V_{\text{rms}})^2}{50\Omega} = 800\text{W} \quad (4)$$

power stored by load A = Q (2)

$$Q = \frac{V^2}{\omega L} = \frac{(200V_{\text{rms}})^2}{2\pi(50\text{Hz})0.1\text{H}} \cong 1273.2\text{VAR(L)} \quad (4)$$

(b)

power supplied by  $v(t) = S$  (2)

$$\therefore S = \sqrt{P^2 + Q^2} \cong \sqrt{800^2 + 1273.2^2} \cong 1503.7\text{VA} \quad (5)$$

power factor of load A = PF

$$\therefore \text{PF} = \frac{P}{S} = \frac{800}{1503.7} \cong 0.532 \text{ lagging} \quad (6)$$

(c)

$$\therefore \theta \cong \cos^{-1} 0.532 \cong 57.9^\circ$$

$$I = \frac{S}{V} = \frac{1503.7 \text{ VA}}{200 \text{ V}_{\text{rms}}} \cong 7.52 \text{ A}_{\text{rms}} \quad (6)$$

(d)

load B is capacitance (2)

$$Q = V^2 \omega C$$

$$\therefore C = \frac{Q}{V^2 \omega} = \frac{1273.2 \text{ VAR}}{200^2 (2\pi 50)} \cong 101.4 \mu\text{F} \quad (7)$$

$$I = \frac{V}{R} = \frac{200 \text{ V}_{\text{rms}}}{50 \Omega} = 4 \text{ A}_{\text{rms}} \quad (6)$$

(e)

Electric fees is related to P only (6)  
P is unchanged hence fees  
will not be reduced

Any two : Lower line current from source (6)  
Lower line loss  
Source can supply more load



(27)


15. (a) Show that the ideal op amp circuit acts as a differentiator, that is

15

$$V_o(t) = -CR \frac{dV_s(t)}{dt}$$

- (b) Plot the output voltage for the circuit,  $v_o(t)$ , as a function of time. Label clearly the voltage and time. Given  $R = 10\text{k}\Omega$ ,  $C = 0.1\mu\text{F}$ , and op amp is ideal. (27)

(a)

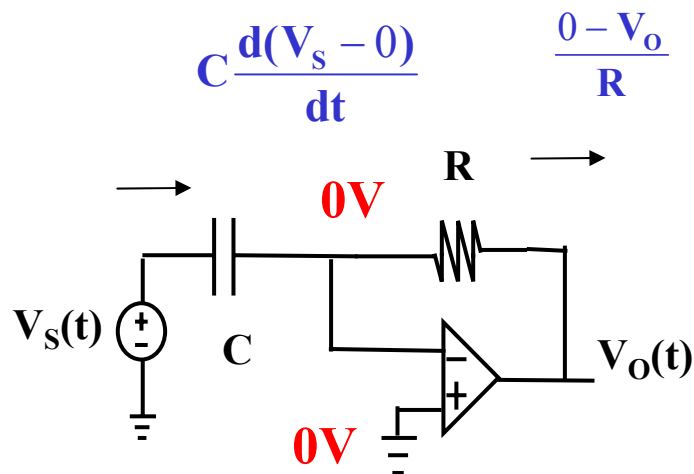




(9)

apply KCL  $\Rightarrow C \frac{dV_s}{dt} \cong \frac{-V_o}{R} \quad \therefore V_o \cong -CR \frac{dV_s}{dt}$

(b)

$$CR = 0.1\mu\text{F} * 10\text{k}\Omega = 1\text{ms}$$
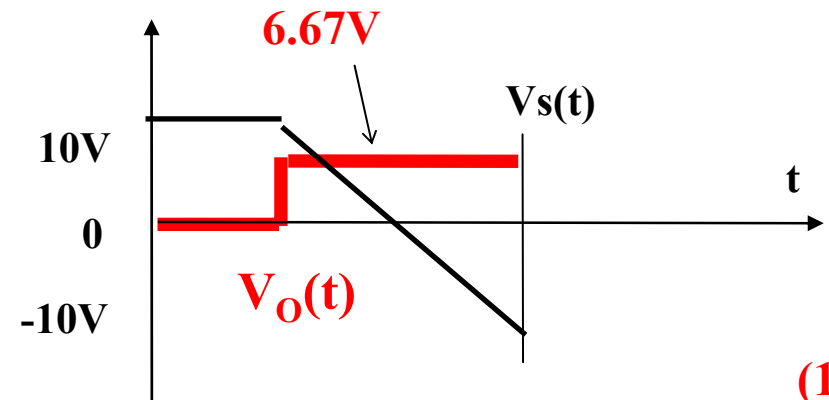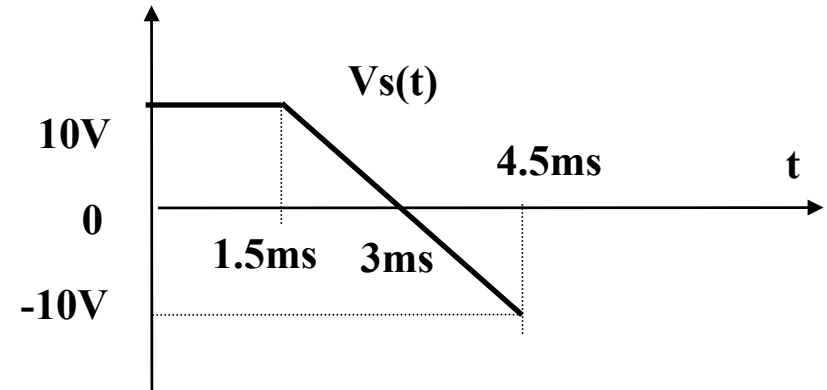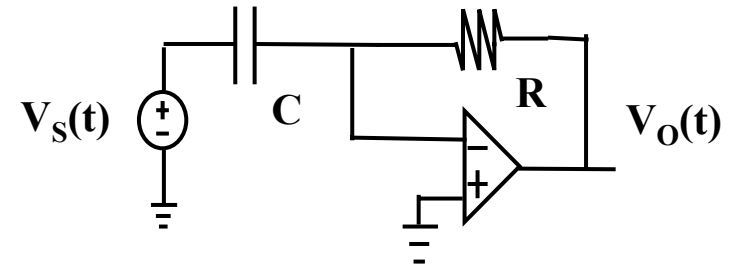
$$\therefore V_o \cong -CR \frac{dV_s}{dt} = -1\text{ms} * \frac{-10\text{V} - 10\text{V}}{3\text{ms}} \cong 6.67\text{V}$$



(18)